


## COE 405, Term 131

### Design & Modeling of Digital Systems

#### HW# 5

Due date: Sunday, Dec. 8

 **Q.1.** Consider the logic network below with inputs  $\{a, b, c, d, e, f, g, h\}$  and output  $\{X\}$ :



Assume that the delay of a gate is related to the number of its inputs i.e. the delay of a 2-input AND gate is 2. Also, assume that the input data-ready times are zero for all inputs.

- (i) Compute the data ready times and slacks for all vertices in the network.
  - (ii) Determine the topological critical path(s).
  - (iii) Suggest an implementation of the function  $X$  to reduce the delay of the circuit to the minimum possible and determine the maximum propagation delay in the optimized circuit. Has the area been affected?
- Q.2.** It is required to design a circuit to compute the equation  $Y=A+B+C+D+E+F$  using only two adders. Assume that the inputs will hold their values until the end of the operation. Also, assume that the inputs will be ready when a Start input is asserted and a Done signal will be set when the result is ready.
- (i) Show a schedule with minimum latency (i.e., clock cycles) satisfying the area constraints.
  - (ii) Show the DataPath design of your circuit.
  - (iii) Show the ASMD diagram of your control unit.
  - (iv) Model the DataPath and Control units in Verilog and verify the correctness of your model.