

Name:

Id#


COE 405, Term 181

Design & Modeling of Digital Systems

Quiz# 2 Solution

Date: Sunday, October 7, 2018

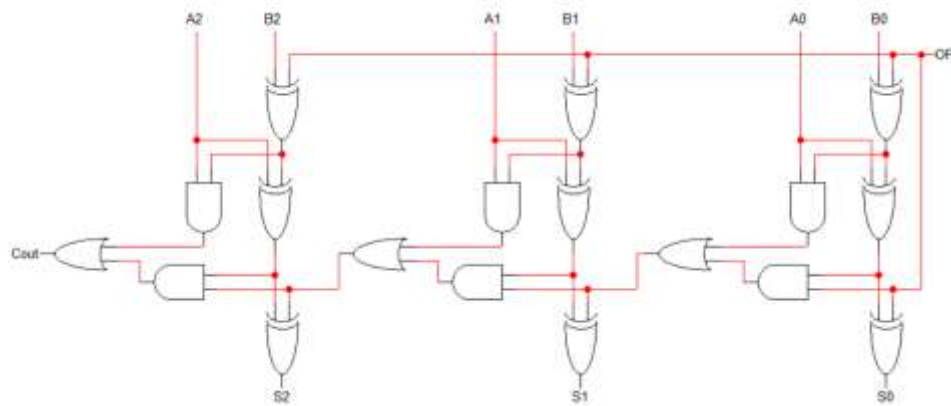Q.1. The circuit given below is a 3-bit adder/subtractor. The circuit performs addition when OP=0 and performs subtraction otherwise.



(i) Write a Verilog model to model a 1-bit cell design of the circuit using either primitive gates or assign statement.

```
module addsubcell (output cout, sum, input a, b, cin, op);
```

```
    assign op2 = b ^ op;  
    assign p = a ^ op2;  
    assign g = a & op2;  
    assign sum = p ^ cin;  
    assign cout = g | p & cin;
```

```
endmodule
```

(ii) Write a parametrizable Verilog model for modeling an n-bit adder/subtractor circuit using generate loop construct.

```
module addsub #( parameter n = 3)  
    (output cout, output [n-1:0] sum,  
    input [n-1:0] a, b, input op);
```

```

wire [n:0] carry;

assign carry[0] = op;
assign cout = carry[n];
genvar i;

for ( i = 0; i < n; i = i+1 ) begin : ripple
    addsubcell AS(carry[i+1], sum[i], a[i], b[i], carry[i], op);
end

endmodule

```

- (iii)** Write a test bench that instantiates and tests a 3-bit adder/subtractor circuit by applying the following input patterns to your circuit with a delay of 30 unit delays between successive input patterns: {(A=1, B=5, OP=0), (A=1, B=5, OP=1), (A=7, B=7, OP=0), (A=0, B=7, OP=1)}.

```

module t_addsub();
    wire    [2:0] sum;
    reg     [2:0] a, b;
    reg     op;

    addsub M1 (cout, sum, a, b, op);

    initial begin
        a=3'b001; b=3'b101; op=1'b0;
        #30      op=1;
        #30      a=3'b111; b=3'b111; op=1'b0;
        #30      a=3'b000; b=3'b111; op=1'b1;

    end
endmodule

```