

Name: KEY

Id#


COE 405, Term 131

Design & Modeling of Digital Systems


Quiz# 3

Date: Thursday, Nov. 28, 2013

 Q.1. It is required to model an n-bit iterative magnitude comparator. A 4-bit comparator is shown below:



 The model for a 1-bit comparator is as follows:



Write a parametrizable Verilog model for modeling an n-bit comparator with a default of n=4.

```
module comparator #(parameter n=4)(
output reg G, L,
input [n-1:0] a, b);
integer k;


always @ (a, b) begin: compare_loop

G = 0; L = 0;
for (k=n-1; k>=0; k=k-1) begin
    G = G | a[k] & ~b[k] & ~L;
    L = L | ~a[k] & b[k] & ~G;
end

end
endmodule
```

Q.2. The ASMD chart given below describes a state machine that counts 1's in a word and terminates activity as soon as possible. The machine remains in its reset state, S_idle , until an external agent asserts $start$. This action asserts the output, $load_temp$, which will cause $data$ to be loaded into register $temp$ when the state makes a transition to $S_counting$ at the next active edge of clk . The machine remains in $S_counting$ while $temp$ contains a 1. Two actions occur concurrently at each subsequent clock: (1) $temp$ is shifted towards its LSB and (2) $temp[0]$ is added to bit_count . When $temp$ finally has a 1 in only the LSB, the machine's state moves to $S_waiting$, where $done$ is asserted. The state remains in $S_waiting$ until $start$ is reasserted. Assume that when the synchronous $reset$ input is asserted the machine is reset to the state S_idle and bit_count and $temp$ are initialized to 0.

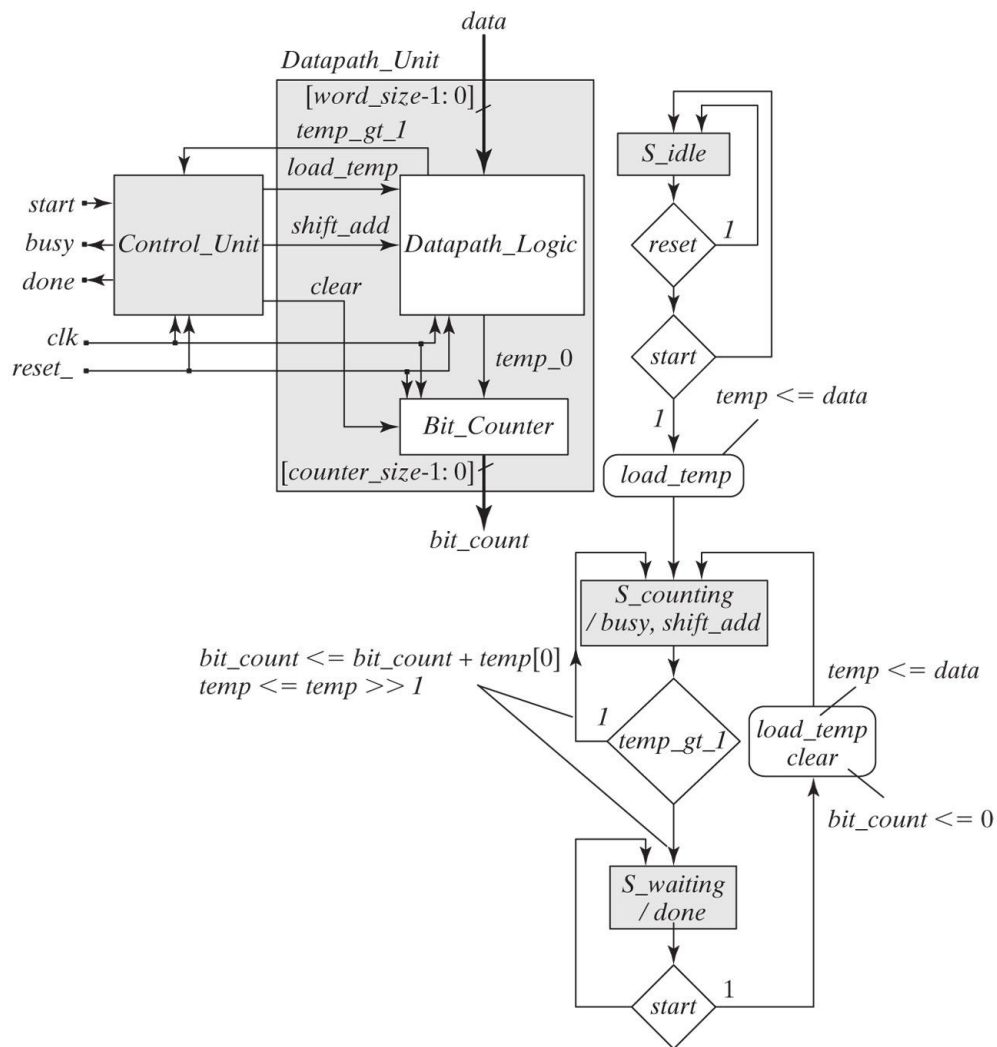- (i) Write a Verilog model for modeling the data-path unit.
- (ii) Write a Verilog model for modeling the control unit using the following state assignment: $S_idle=00$, $S_counting=01$, and $S_waiting=10$.



(i)

```
module OnesCount_DPU #(parameter word_size=4, counter_size=3)(
output reg [counter_size-1: 0] bit_count,
output temp_gt_1,
input [word_size-1:0] data,
input load_temp, shift_add, clear, clock, reset
);

reg [word_size-1:0] temp;

assign temp_gt_1 = | temp[word_size-1:1];

always @ (posedge clock)
if (load_temp) temp <= data;
else if (shift_add) temp <= temp >> 1;

always @ (posedge clock)
if (reset || clear) bit_count <= 0;
else if (shift_add) bit_count <= bit_count + temp[0];

endmodule
```

(ii)

```
module OnesCount_CU (output reg load_temp,
shift_add, clear, done, busy,
input start, temp_gt_1, clock, reset);

parameter S_idle = 2'b00, S_counting = 2'b01, S_waiting = 2'b10;

reg [1:0] state, next_state;

always @(posedge clock)
if (reset) state <= S_idle;
else state <= next_state;

always @(state, start, temp_gt_1) begin
load_temp=0; shift_add=0; clear=0; done=0; busy=0;

case (state)
S_idle:
if (start) begin
load_temp = 1;
next_state = S_counting;
end
else next_state = S_idle;
```

```
S_counting: begin
    shift_add = 1; busy = 1;
    if (temp_gt_1) next_state = S_counting;
    else next_state = S_waiting;
end
S_waiting: begin
    done = 1;
    if (start) begin
        load_temp = 1; clear = 1;
        next_state = S_counting;
    end
    else next_state = S_waiting;
end
default: begin
    next_state = 2'bxx;
    load_temp='bx; shift_add='bx; clear='bx; done='bx; busy='bx;
end
endcase
end
endmodule
```