

COE 405, Term 152

Design & Modeling of Digital Systems


Quiz# 3

Date: Sunday, April 3, 2016


**Q1.** Given below the design of an  $n$ -bit magnitude comparator. The circuit receives two  $n$ -bit unsigned numbers  $A$  and  $B$  and produces two outputs  $GT$  and  $EQ$  as given in the table to the right.

	GT	EQ
IF $A > B$	1	0
IF $A = B$	0	1
IF $A < B$	0	0

 The input operands are processed in a bitwise manner *starting with the most significant bit (MSB)*. The comparator circuit is constructed using  $n$  identical copies of the basic 1-bit cell shown to the right.



 The Figure below shows the  $n$ -bit comparator circuit implemented using  $n$  copies of the basic 1-bit cell.




Boolean expressions of the outputs of *cell i* and its gate-level implementation are given below:

$$GT_i = GT_{i+1} + A_i \bar{B}_i EQ_{i+1}$$

$$EQ_i = (A_i \odot B_i) \cdot EQ_{i+1}$$

 - (i) Write a Verilog model **Comp1Bit** to model the 1-bit comparator circuit using *either* a structural model of basic logic gates *or* a behavioral model using the **assign** statement.



The declaration of the Comp1Bit module is as follows:

```
module Comp1Bit (output GT_out, EQ_out , input GT_in , EQ_in, Ai, Bi);
```

```
module Comp1Bit (output GT_out, EQ_out, input GT_in, EQ_in, Ai, Bi);  
    assign GT_out = GT_in || Ai && !Bi && EQ_in;  
    assign EQ_out = (Ai ~^ Bi) && EQ_in;  
endmodule
```

OR

```
module Comp1Bit (output GT_out, EQ_out, input GT_in, EQ_in, Ai, Bi);  
    not (g1, Bi);  
    and (g2, g1, Ai);  
    xnor(g3, Ai, Bi);  
    and (g4, g2, EQ_in);  
    or (GT_out, GT_in, g4);  
    and (EQ_out, EQ_in, g3);  
endmodule
```

(ii) Complete the following Verilog model **Comp3Bit** that models a 3-bit comparator circuit.

```
module Comp3Bit (output Greater, Equal,  
                input [2:0] A , B) ;  
  
    wire [2:1] GT, EQ ; // internal wires connecting cells  
    /* First instance "M1" of the cell Comp1Bit with its inputs GT_in and EQ_in  
    connected to fixed values of 0 and 1 respectively */  
    //  
    Comp1Bit M1 (GT[2] , EQ [2], 1'b0, 1'b1, A[2], B[2]);  
    Comp1Bit M2 (GT[1], EQ[1], GT[2], EQ[2], A[1], B[1]);  
    Comp1Bit M3 (Greater, Equal, GT[1], EQ[1], A[0], B[0]);  
endmodule
```

(iii) Write a Verilog test bench to test the 3-bit comparator **Comp3Bit** by applying the following input patterns consecutively with a delay of 20ps:

1. {A=100, B=011},
2. {A=101, B=101},
3. {A=011, B=111}.

```
module t_Comp3Bit();  
    wire Greater, Equal;  
    reg [2:0] A, B;  
    Comp3Bit M1 (Greater, Equal, A, B) ;  
  
    initial begin  
        A=3'b100; B=3'b011;  
        #20 A=3'b101; B=3'b101;  
        #20 A=3'b011; B=3'b111;  
    end  
endmodule
```