

Name:

Id#

COE 405, Term 162

Design & Modeling of Digital Systems

Quiz# 4 Solution



Date: Tuesday, May 1, 2017

Q1. It is required to design an **n-bit signed multiplier** circuit. The architecture and the algorithm for performing signed multiplication are given below:

❖ ALU produces **32-bit result + Sign bit**

❖ **Sign bit** set as follows:

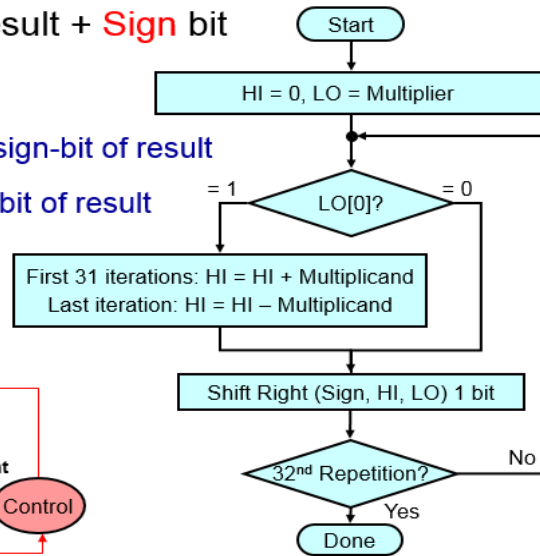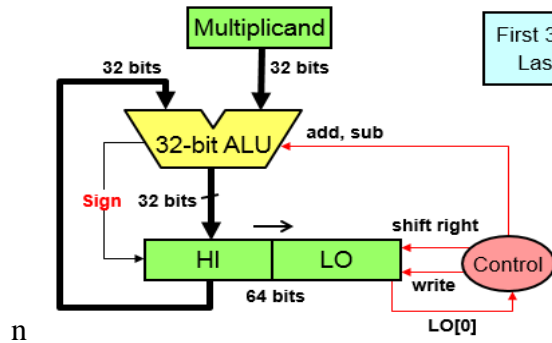- ❖ No overflow → Extend sign-bit of result
- ❖ Overflow → Invert sign-bit of result



Write a parametrizable Verilog module to model the signed multiplication circuit as a combinational circuit using for loop.

```

module MULC #(parameter N=4) (output reg [N-1:0] HI, LO, input [N-1:0] A, B);
integer i;
reg [N-1:0] C;
reg OVF, Sign;
always @(A, B) begin
    HI = 0; LO = B;
    for (i=0; i<N; i=i+1) begin
        if( LO[0] ) begin
            if ( i==N-1 ) begin
                C = HI - A;
                OVF = (HI[N-1] ^ A[N-1]) & (HI[N-1]^C[N-1]);
            end
            else begin
                C = HI + A;
                OVF = (HI[N-1] ~^ A[N-1]) & (HI[N-1]^C[N-1]);
            end
            Sign = OVF ^ C[N-1];
            HI = C;
        end
        else Sign = HI[N-1];
        {HI, LO} = {Sign, HI, LO[N-1:1]};
    end
end
endmodule

```