
COE 561
**Digital System Design &
Synthesis**
Sequential Logic Synthesis

Dr. Aiman H. El-Maleh
Computer Engineering Department
King Fahd University of Petroleum & Minerals

[Adapted from slides of Prof. G. De Micheli: Synthesis & Optimization of Digital Circuits]

Outline

- **Modeling synchronous circuits**
 - State-based models.
 - Structural models.
- **State-based optimization methods**
 - State minimization.
 - State encoding
 - State encoding for two-level logic
 - Input encoding
 - Output encoding
 - State encoding for multiple-level logic
- **Structural-based optimization methods**
 - Retiming


Synchronous Logic Circuits

■ Interconnection of

- Combinational logic gates.
- Synchronous delay elements
 - E-T or M-S registers.

■ Assumptions

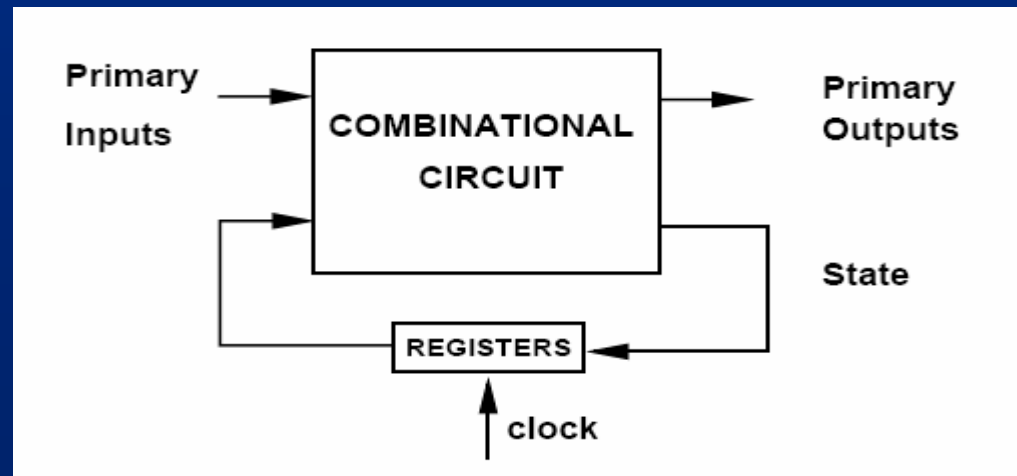- No direct combinational feedback.
- Single-phase clocking.



Modeling Synchronous Circuits


■ State-based model

- Model circuits as finite-state machines.
- Represented by state tables/diagrams.
- Lacks a direct relation between state manipulation and corresponding area and delay variations.
- Apply exact/heuristic algorithms for
 - State minimization.
 - State encoding.


■ Structural models

- Represent circuit by synchronous logic network.
- Apply
 - Retiming.
 - Logic transformations.


State-Based Optimization

 


FSM Specification

 

State Minimization

 


State Encoding

 

Combinational Optimization

Formal Finite-State Machine Model

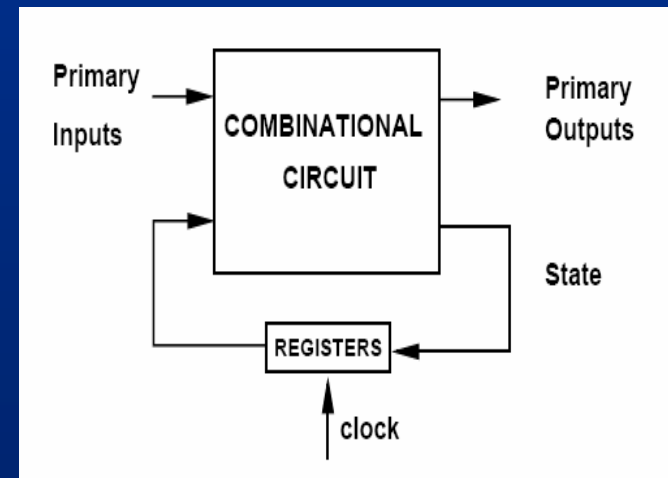- Defined by the quintuple $(X, Y, S, \delta, \lambda)$.
- A set of primary inputs patterns X .
- A set of primary outputs patterns Y .
- A set of states S .
- A state transition function
 - $\delta : X \times S \rightarrow S$.
- An output function
 - $\lambda : X \times S \rightarrow Y$ for Mealy models
 - $\lambda : S \rightarrow Y$ for Moore models.



State Minimization

- **Aims at reducing the number of machine states**
 - reduces the size of transition table.
- **State reduction may reduce**
 - the number of storage elements.
 - the combinational logic due to reduction in transitions
- **Completely specified finite-state machines**
 - No don't care conditions.
 - Easy to solve.
- **Incompletely specified finite-state machines**
 - Unspecified transitions and/or outputs.
 - Intractable problem.

State Minimization for Completely-Specified FSMs

■ Equivalent states

- Given any input sequence the corresponding output sequences match.

■ Theorem: Two states are equivalent iff

- they lead to identical outputs and
- their next-states are equivalent.

■ Equivalence is *transitive*

- Partition states into *equivalence classes*.
- Minimum finite-state machine is unique.


Algorithm

- **Stepwise partition refinement.**
- **Initially**
 - Π_1 = States belong to the same block when outputs are the same for any input.
- **Refine partition blocks: While further splitting is possible**
 - Π_{k+1} = States belong to the same block if they were previously in the same block and their next-states are in the same block of Π_k for any input.
- **At convergence**
 - Blocks identify equivalent states.

Example ...

- $\Pi_1 = \{(s1, s2), (s3, s4), (s5)\}$.
- $\Pi_2 = \{(s1, s2), (s3), (s4), (s5)\}$.
- $\Pi_2 =$ is a partition into equivalence classes
 - States (s1, s2) are equivalent.


| INPUT | STATE | N-STATE | OUTPUT |
|-------|-------|---------|--------|
| 0 | s1 | s3 | 1 |
| 1 | s1 | s5 | 1 |
| 0 | s2 | s3 | 1 |
| 1 | s2 | s5 | 1 |
| 0 | s3 | s2 | 0 |
| 1 | s3 | s1 | 1 |
| 0 | s4 | s4 | 0 |
| 1 | s4 | s5 | 1 |
| 0 | s5 | s4 | 1 |
| 1 | s5 | s1 | 0 |

 

... Example ...


Original FSM

| INPUT | STATE | N-STATE | OUTPUT |
|-------|-------|---------|--------|
| 0 | s1 | s3 | 1 |
| 1 | s1 | s5 | 1 |
| 0 | s2 | s3 | 1 |
| 1 | s2 | s5 | 1 |
| 0 | s3 | s2 | 0 |
| 1 | s3 | s1 | 1 |
| 0 | s4 | s4 | 0 |
| 1 | s4 | s5 | 1 |
| 0 | s5 | s4 | 1 |
| 1 | s5 | s1 | 0 |

 

Minimal FSM

| INPUT | STATE | N-STATE | OUTPUT |
|-------|-------|---------|--------|
| 0 | s12 | s3 | 1 |
| 1 | s12 | s5 | 1 |
| 0 | s3 | s12 | 0 |
| 1 | s3 | s12 | 1 |
| 0 | s4 | s4 | 0 |
| 1 | s4 | s5 | 1 |
| 0 | s5 | s4 | 1 |
| 1 | s5 | s12 | 0 |

 

... Example

Original FSM

```
{OUT_0} = IN_0 LatchOut_v1' + IN_0 LatchOut_v3' + IN_0' LatchOut_v2'  
v4.0 = IN_0 LatchOut_v1' + LatchOut_v1' LatchOut_v2'  
v4.1 = IN_0' LatchOut_v2 LatchOut_v3 + IN_0' LatchOut_v2'  
v4.2 = IN_0 LatchOut_v1' + IN_0' LatchOut_v1 + IN_0' LatchOut_v2 LatchOut_v3  
sis> print_stats  
pi= 1 po= 1 nodes= 4 latches= 3  
lits(sop)= 22 #states(STG)= 5
```

Minimal FSM

```
{OUT_0} = IN_0 LatchOut_v1' + IN_0 LatchOut_v2 + IN_0' LatchOut_v2'  
v3.0 = IN_0 LatchOut_v1' + LatchOut_v1' LatchOut_v2'  
v3.1 = IN_0' LatchOut_v1' + IN_0' LatchOut_v2'  
sis> print_stats  
pi= 1 po= 1 nodes= 3 latches= 2  
lits(sop)= 14 #states(STG)= 4
```

Computational Complexity

- **Polynomially-bound algorithm.**
- **There can be at most $|S|$ partition refinements.**
- **Each refinement requires considering each state**
 - Complexity $O(|S|^2)$.
- **Actual time may depend upon**
 - Data-structures.
 - Implementation details.

State Minimization for Incompletely-Specified FSMs ...

- **Applicable input sequences**
 - All transitions are specified.
 - Does not lead to any unspecified transition.
- **Compatible states**
 - Given any applicable input sequence the corresponding output sequences match.
- **Theorem: Two states are compatible iff**
 - they lead to identical outputs (when both are specified),
 - their next-states are compatible (when both are specified).
- Compatibility is not an equivalency relation (**not transitive**).

An Interesting Example

- Moore machine with 3-states.
- Replace don't care output of s1 by 0 → Can't be minimized.
- Replace don't care output of s1 by 1 → Can't be minimized.
- Replacing don't cares with all possible assignments does not guarantee a minimum solution.
- Maximal compatible classes
 - $(s1, s2) \Leftarrow (s1, s3)$
 - $(s1, s3) \Leftarrow (s1, s2)$
- Machine can be reduced to two states.

| Input | State | N-State | Out |
|-------|-------|---------|-----|
| 0 | s1 | s2 | - |
| 1 | s1 | s3 | - |
| 0 | s2 | - | 0 |
| 1 | s2 | s1 | 0 |
| 0 | s3 | s1 | 1 |
| 1 | s3 | - | 1 |

| Input | State | N-State | Out |
|-------|-------|---------|-----|
| 0 | A | A | 0 |
| 1 | A | B | 0 |
| 0 | B | A | 1 |
| 1 | B | B | 1 |

... State Minimization for Incompletely Specified FSMs

- **Minimum** finite-state machine is **not unique**.
- Implication relations make problem intractable.

■ Example

- Replace * by 1.
 - $\{(s1, s2), (s3), (s4), (s5)\}$.
- Replace * by 0.
 - $\{(s1, s5), (s2, s3, s4)\}$.
- Compatible states $(s1, s2)$.
- Incompatible states $(s1, s3)$,
 $(s1, s4)$, $(s2, s5)$, $(s3, s5)$,
 $(s4, s5)$.
- If $(s3, s4)$ are compatible
 - then $(s1, s5)$ are compatible.

| INPUT | STATE | N-STATE | OUTPUT |
|-------|-------|---------|--------|
| 0 | s_1 | s_3 | 1 |
| 1 | s_1 | s_5 | * |
| 0 | s_2 | s_3 | * |
| 1 | s_2 | s_5 | 1 |
| 0 | s_3 | s_2 | 0 |
| 1 | s_3 | s_1 | 1 |
| 0 | s_4 | s_4 | 0 |
| 1 | s_4 | s_5 | 1 |
| 0 | s_5 | s_4 | 1 |
| 1 | s_5 | s_1 | 0 |

Compatibility and Implications ...

■ Compatible pairs

- (s1, s2)
- (s1, s5) \Leftarrow (s3, s4)
- (s2, s4) \Leftarrow (s3, s4)
- (s2, s3) \Leftarrow (s1, s5)
- (s3, s4) \Leftarrow (s2, s4) and (s1, s5)

■ Incompatible pairs

- (s2, s5), (s3, s5)
- (s1, s4), (s4, s5)
- (s1, s3)

| INPUT | STATE | N-STATE | OUTPUT |
|-------|-------|---------|--------|
| 0 | s1 | s3 | 1 |
| 1 | s1 | s5 | * |
| 0 | s2 | s3 | * |
| 1 | s2 | s5 | 1 |
| 0 | s3 | s2 | 0 |
| 1 | s3 | s1 | 1 |
| 0 | s4 | s4 | 0 |
| 1 | s4 | s5 | 1 |
| 0 | s5 | s4 | 1 |
| 1 | s5 | s1 | 0 |

... Compatibility and Implications

- **A class of compatible states is such that all state pairs are compatible.**
- **A class is maximal**
 - If not subset of another class.
- **Closure property**
 - A set of classes such that all compatibility implications are satisfied.
- **The set of maximal compatibility classes**
 - Satisfies always the closure property.
 - May not provide a minimum solution.
- **Minimum covers may involve compatibility classes that are not necessarily maximal.**

Maximal Compatible Classes

- $(s1, s2)$
- $(s1, s5) \Leftarrow (s3, s4)$
- $(s2, s3, s4) \Leftarrow (s1, s5)$
- Cover with MCC has cardinality 3.
- Minimum cover: $\{(s1, s5), (s2, s3, s4)\}$.
- Minimum cover has cardinality 2.

| INPUT | STATE | N-STATE | OUTPUT |
|-------|-------|---------|--------|
| 0 | s1 | s3 | 1 |
| 1 | s1 | s5 | * |
| 0 | s2 | s3 | * |
| 1 | s2 | s5 | 1 |
| 0 | s3 | s2 | 0 |
| 1 | s3 | s1 | 1 |
| 0 | s4 | s4 | 0 |
| 1 | s4 | s5 | 1 |
| 0 | s5 | s4 | 1 |
| 1 | s5 | s1 | 0 |

Reduced Table

| Input | State | N-State | Output |
|-------|-------|---------|--------|
| 0 | A | B | 1 |
| 1 | A | A | 0 |
| 0 | B | B | 0 |
| 1 | B | A | 1 |

Finding Maximal Compatible Classes ...

- Knowing that s_i and s_j are two incompatible states implies that no maximal compatible class will contain both s_i and s_j .
- Every set of states that does not contain any incompatible pair is a compatible set.
- Associate a variable x_i to state s_i such that $x_i = 1$ implies that s_i is an element of the set.
- Write a conjunction of two-literal clauses.
- Each clause corresponds to an incompatible pair.
- Convert the expression into a prime and irredundant sum-of-product form.
- Every term corresponds to a maximal compatible set and represents the sets that do not appear in the prime implicant.

... Finding Maximal Compatible Classes

■ Example

- Incompatible pairs
 - (s2, s5), (s3, s5)
 - (s1, s4), (s4, s5)
 - (s1, s3)
- Two-literal Clauses
 - $(x_2' + x_5') (x_3' + x_5') (x_4' + x_5') (x_1' + x_4') (x_1' + x_3')$
- Prime and Irredundant sum-of-product
 - $= (x_2' x_3' x_4' + x_5') (x_1' + x_3' x_4')$
 - $= x_1' x_2' x_3' x_4' + x_1' x_5' + x_2' x_3' x_4' + x_3' x_4' x_5'$
 - $= x_1' x_5' + x_2' x_3' x_4' + x_3' x_4' x_5'$
- Maximal Compatible Classes
 - $x_1' x_5' \rightarrow (S_2, S_3, S_4)$
 - $x_2' x_3' x_4' \rightarrow (S_1, S_5)$
 - $x_3' x_4' x_5' \rightarrow (S_1, S_2)$

Formulation of the State Minimization Problem

- A class is **prime**, if not subset of another class implying the same set or a subset of classes.
- Compute the prime compatibility classes.
- Select a minimum number of PCC such that
 - all states are covered.
 - all implications are satisfied.
- **Binate covering problem.**
- **Upper bound on optimum solution given by**
 - Cardinality of set of maximal compatible classes and
 - Original state set cardinality.
- **Lower bound on optimum solution given by**
 - A unate cover solution that disregards implications.

Setting Up Covering Problem ...

- All states must be contained in at least one compatible class (covering).
- All compatible classes implied by any compatible class must be contained in a compatible class in the solution (closure).
- Associate a variable c_i to the i -th compatible class such that $c_i = 1$ implies that class i is part of the solution.
- We write a Boolean formula (product of sum form) to express the conditions for a set of compatible classes to represent a closed cover.
 - Terms representing covering constraints
 - Terms representing closure constraints.

... Setting Up Covering Problem ...

■ Maximal compatibles classes

- $c_1: (s1, s2)$
- $c_2: (s1, s5) \Leftarrow (s3, s4)$
- $c_3: (s2, s3, s4) \Leftarrow (s1, s5)$

■ Covering constraints

- $s1: (c_1 + c_2)$
- $s2: (c_1 + c_3)$
- $s3: (c_3)$
- $s4: (c_3)$
- $s5: (c_2)$

■ Closure constraints

- $c_2 \rightarrow c_3 : (c_2' + c_3)$
- $c_3 \rightarrow c_2 : (c_3' + c_2)$

... Setting Up Covering Problem

■ Binate covering problem

- $(c_1 + c_2) (c_1 + c_3) (c_2) (c_3) (c_2' + c_3) (c_3' + c_2)$
- $= (c_1 + c_2 c_3) (c_2) (c_3) (c_2' + c_3) (c_3' + c_2)$
- $= (c_2 c_3) (c_2' + c_3) (c_3' + c_2)$
- $= (c_2 c_3)$

■ Minimum cover: $\{c_2 c_3\}$.

■ Minimum cover: $\{(s1, s5) , (s2, s3, s4)\}$.

Finding Prime Compatible Classes ...

- All maximal compatible classes are prime.
- Let C_1 and C_2 be two compatible classes such that $C_1 \supset C_2$.
 - One tempted to favor C_1 over C_2 as it covers more states.
 - It might be better to choose C_2 in case that C_1 implies the selection of other compatible classes that would not be required if C_2 is selected.
- The set of compatible classes implied by a compatible class is denoted as its *class set (CS)*.
- For each maximal compatible class p of size k with a *non-empty* class set, consider all its subsets S_p of compatible classes of size $k-1$.
- For each $s \in S_p$, and if there is a prime q of size $> k-1$, such that $s \subset q$ and $CS_s \supseteq CS_q$ then s is **not prime**. Otherwise, it is prime.

... Finding Prime Compatible Classes

■ Maximal compatibles classes

- (s1, s2)
- (s1, s5) \Leftarrow (s3, s4)
- (s2, s3, s4) \Leftarrow (s1, s5)

■ Prime compatibles classes

- (s2, s3, s4)
 - (s2, s3) \Leftarrow (s1, s5) Not prime
 - (s2, s4) \Leftarrow (s3, s4) **Prime**
 - (s3, s4) \Leftarrow (s2, s4) and (s1, s5) Not prime
- (s1, s5)
 - (s1) Not prime
 - (s5) **Prime**
- (s2, s4)
 - (s2) Not prime
 - (s4) **Prime**

■ Set of prime compatible classes

- (s1, s2), (s1, s5), (s2, s3, s4), (s2, s4), (s5), (s4)

Additional State Minimization Example

Flow Table

| | x_1 | x_2 | x_3 | x_4 | x_5 | x_6 | x_7 |
|---|-------|-------|-------|-------|-------|-------|-------|
| a | a,0 | – | d,0 | e,1 | b,0 | a,– | – |
| b | b,0 | d,1 | a,– | – | a,– | a,1 | – |
| c | b,0 | d,1 | a,1 | – | – | – | g,0 |
| d | – | e,– | – | b,– | b,0 | – | a,– |
| e | b,– | e,– | a,– | – | b,– | e,– | a,1 |
| f | b,0 | c,– | –,1 | h,1 | f,1 | g,0 | – |
| g | – | c,1 | – | e,1 | – | g,0 | f,0 |
| h | a,1 | e,0 | d,1 | b,0 | b,– | e,– | a,1 |

Compatibility Table

| | | | | | | | |
|---|---------|-------------|---------|---|---------|-----|---|
| b | a,d | | | | | | |
| c | × | ~ | | | | | |
| d | b,e | a,b d,e | d,e a,g | | | | |
| e | a,b a,d | d,e a,b a,e | × | ~ | | | |
| f | × | × | c,d | × | × | | |
| g | ~ | × | c,d f,g | × | × | e,h | |
| h | × | × | × | ~ | a,b a,d | × | × |
| | a | b | c | d | e | f | g |

Maximal Compatibility Classes Computation

$$= (a' + c')(a' + f')(a' + h')(b' + f')(b' + g')(b' + h')(c' + e') \\ (c' + h')(d' + f')(d' + g')(e' + f')(e' + g')(f' + h')(g' + h').$$

$$= (f' + a'b'd'e'h')(h' + a'b'c'g')(g' + b'd'e')(c' + a'e').$$

$$= (f'h' + a'b'c'f'g' + a'b'd'e'h')(c'g' + a'e'g' + b'c'd'e' + a'b'd'e'),$$

$$= c'f'g'h' + a'e'f'g'h' + b'c'd'e'f'h' + a'b'c'f'g' + a'b'd'e'h'.$$

$$= abde, bcd, ag, deh, cfg.$$

Prime Compatibility Classes Computation

| | maximal compatibles | class set |
|----|---------------------|-----------------------|
| 1 | {a,b,d,e} | \emptyset |
| 2 | {b,c,d} | {{a,b}, {a,g}, {d,e}} |
| 3 | {c,f,g} | {{c,d}, {e,h}} |
| 4 | {d,e,h} | {{a,b}, {a,d}} |
| 11 | {a,g} | \emptyset |

| | remaining prime compatibles | class set |
|----|--------------------------------|----------------|
| 5 | {b,c} | \emptyset |
| 6 | {c,d} | {{a,g}, {d,e}} |
| 7 | {c,f} | {{c,d}} |
| 8 | {c,g} | {{c,d}, {f,g}} |
| 9 | {f,g} | {{e,h}} |
| 10 | {d,h} | \emptyset |
| 12 | {f} | \emptyset |

Setting Up the Covering Problem

■ Covering clauses: One clause for each state

- For state a, the only two compatibles that cover it are 1 and 11. $(c_1 + c_{11})$

■ Closure Constraints

- Prime 2 ($\{b, c, d\}$) requires $\{(a,b), (a, g), (d, e)\}$.

(a,b) is found in $\{a,b,d,e\} (c_1)$
 (a,g) is found in $\{a,g\} (c_{11})$
 (d,e) is found in $\{a,b,d,e\} (c_1)$ and $\{d,e,h\} (c_4)$.

$c_2 \Rightarrow c_1$
 $c_2 \Rightarrow c_{11}$
 $c_2 \Rightarrow (c_1 + c_4)$

$(c'_2 + c_1) (c'_2 + c_{11}) (c'_2 + c_1 + c_4)$

■ Covering problem formulation

$$(c_1 + c_{11})(c_1 + c_2 + c_5)(c_2 + c_3 + c_5 + c_6 + c_7 + c_8)(c_1 + c_2 + c_4 + c_6 + c_{10})$$

$$(c_1 + c_4)(c_3 + c_7 + c_9 + c_{12})(c_3 + c_8 + c_9 + c_{11})(c_4 + c_{10})$$

$$(c'_2 + c_1)(c'_2 + c_{11})(c'_2 + c_1 + c_4)(c'_3 + c_2 + c_6)$$

$$(c'_3 + c_4)(c'_4 + c_1)(c'_4 + c_1)(c'_6 + c_{11})(c'_6 + c_1 + c_4)$$

$$(c'_7 + c_2 + c_6)(c'_8 + c_2 + c_6)(c'_8 + c_3 + c_9)(c'_9 + c_4) = 1.$$

Reduced Table

- Minimum cost solution: $c_1=c_4=c_5=c_9=1$.
- Reduced table is not unique. It will lead to different implementations with different cost.

| | x_1 | x_2 | x_3 | x_4 | x_5 | x_6 | x_7 |
|---|---------|---------|-------|---------|---------|---------|-------|
| 1 | 1,0 | {1,4},1 | 1,0 | 1,1 | 1,0 | 1,1 | 1,1 |
| 4 | 1,1 | {1,4},0 | 1,1 | {1,5},0 | {1,5},0 | {1,4},- | 1,1 |
| 5 | {1,5},0 | {1,4},1 | 1,1 | — | 1,- | 1,1 | 9,0 |
| 9 | {1,5},0 | 5,1 | -1 | 4,1 | 9,1 | 9,0 | 9,0 |

| | x_1 | x_2 | x_3 | x_4 | x_5 | x_6 | x_7 |
|---|-------|-------|-------|-------|-------|-------|-------|
| 1 | 1,0 | 1,1 | 1,0 | 1,1 | 1,0 | 1,1 | 1,1 |
| 4 | 1,1 | 1,0 | 1,1 | 1,0 | 1,0 | 1,- | 1,1 |
| 5 | 1,0 | 1,1 | 1,1 | — | 1,- | 1,1 | 9,0 |
| 9 | 1,0 | 5,1 | -1 | 4,1 | 9,1 | 9,0 | 9,0 |

State Encoding

- **Determine a binary encoding of the states ($|S|=n_s$) that optimize machine implementation**
 - Area
 - Cycle-time
 - Power dissipation
 - Testability
- **Assume D-type registers.**
- **Circuit complexity is related to**
 - Number of storage bits n_b used for state representation
 - Size of combinational component
- **There are $2^{n_b}! / (2^{n_b} - n_s)!$ possible encodings**
- **Implementation Modeling**
 - Two-level circuits.
 - Multiple-level circuits.

Two-Level Circuit Models

■ Sum of product representation.

- PLA implementation.

■ Area


- # of products (rows) \times # I/Os (columns).

■ Delay

- Twice # of products (2 column length) plus # I/Os (1 row length).

■ Note

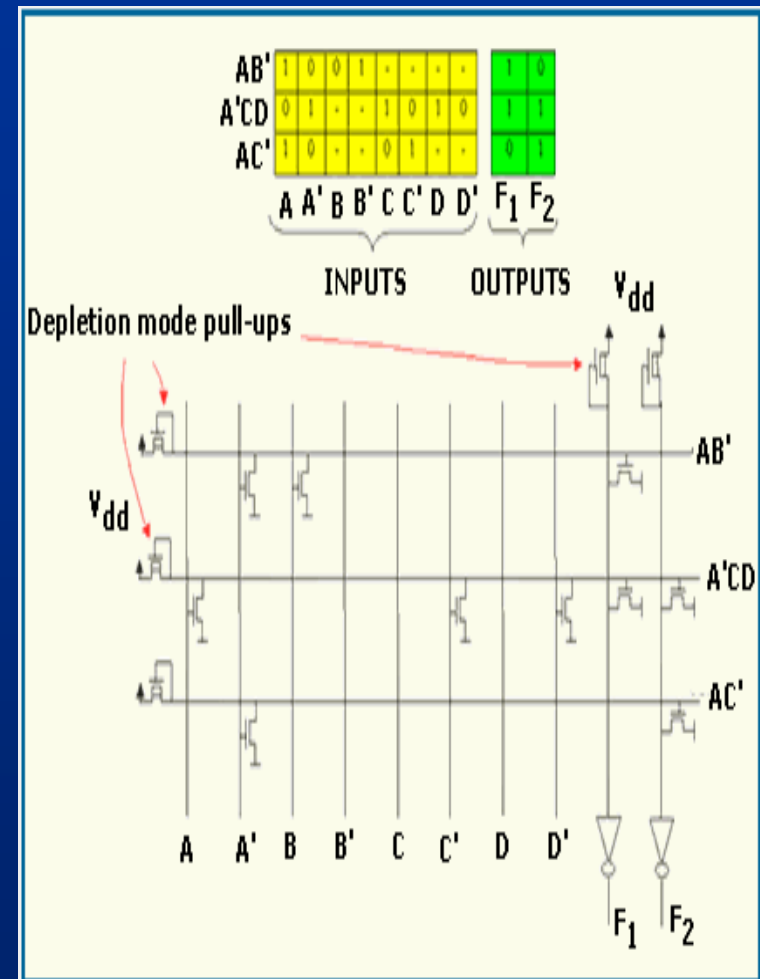- # products considered as the size of a minimum implementation.
- # I/Os depends on encoding length.



State Encoding for Two-Level Models


- Early work focused on use of minimum-length codes i.e. using $n_b = \lceil \log_2 n_s \rceil$.
- Most classical heuristics are based on reduced dependency criterion
 - Encode states so that state variables have least dependencies on those representing previous states.
 - Correlates weakly with minimality of sum-of-products representation.
- Symbolic minimization of state table.
 - Equivalent to minimizing the size of sum-of-products form related to all codes that satisfy the corresponding constraints.
- Constrained encoding problems.
 - Exact and heuristic methods.

Symbolic Minimization

- Minimization of Boolean functions where codes of inputs and/or outputs are not specified.
- Minimize tables of symbols rather than binary tables.
- Extension to bvi and mvi function minimization.
- Reduce the number of rows of a table, that can have symbolic fields.
- Reduction exploits
 - Combination of input symbols in the same field.
 - Covering of output symbols.
- Applications
 - Encoding of op-codes.
 - State encoding of finite-state machines.
- Problems
 - Input encoding.
 - Output encoding.
 - Mixed encoding.

Input Encoding Example

| ad-mode | op-code | control |
|---------|---------|---------|
| INDEX | AND | CNTA |
| INDEX | OR | CNTA |
| INDEX | JMP | CNTA |
| INDEX | ADD | CNTA |
| DIR | AND | CNTB |
| DIR | OR | CNTB |
| DIR | JMP | CNTC |
| DIR | ADD | CNTC |
| IND | AND | CNTB |
| IND | OR | CNTD |
| IND | JMP | CNTD |
| IND | ADD | CNTC |

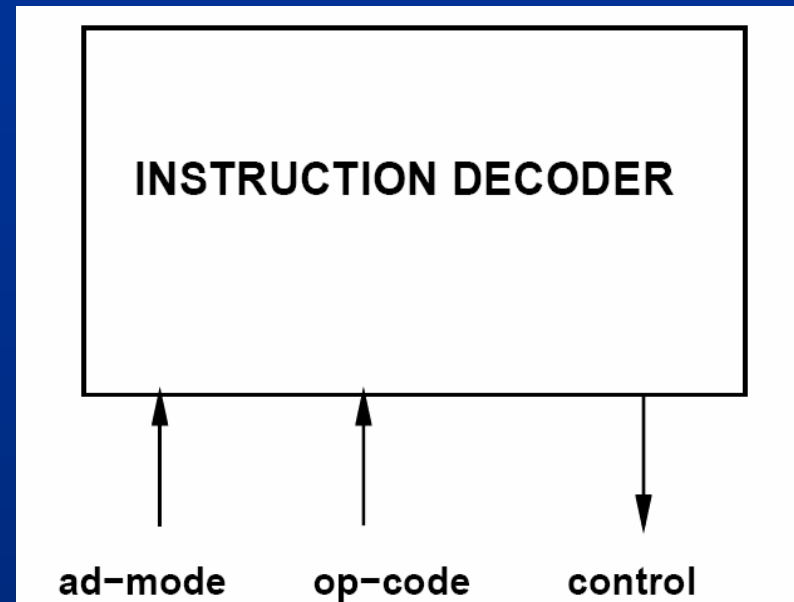

Replace symbols by binary strings to minimize corresponding covers

Definitions

- **Symbolic cover**

- List of symbolic implicants.
- List of rows of a table.

- **Symbolic implicant**

- Conjunction of symbolic literals.

- **Symbolic literals**

- Simple: one symbol.
- Compound: the disjunction of some symbols.

Input Encoding Problem

- **Degrees of freedom in encoding the symbols.**
- **Goal**
 - Reduce size of the representation.
- **Approach**
 - Encode to minimize number of rows.
 - Encode to minimize number of bits.
- **Represent each string by 1-hot codes.**
- **Minimize table with mvi minimizer.**
- **Interpret minimized table**
 - Compound mvi-literals.
 - Groups of symbols.

Input Encoding Example ...

Input Encoding Problem

| ad-mode | op-code | control |
|---------|---------|---------|
| INDEX | AND | CNTA |
| INDEX | OR | CNTA |
| INDEX | JMP | CNTA |
| INDEX | ADD | CNTA |
| DIR | AND | CNTB |
| DIR | OR | CNTB |
| DIR | JMP | CNTC |
| DIR | ADD | CNTC |
| IND | AND | CNTB |
| IND | OR | CNTD |
| IND | JMP | CNTD |
| IND | ADD | CNTC |

Encoded Cover

| | | |
|-----|------|------|
| 100 | 1000 | 1000 |
| 100 | 0100 | 1000 |
| 100 | 0010 | 1000 |
| 100 | 0001 | 1000 |
| 010 | 1000 | 0100 |
| 010 | 0100 | 0100 |
| 010 | 0010 | 0010 |
| 010 | 0001 | 0010 |
| 001 | 1000 | 0100 |
| 001 | 0100 | 0001 |
| 001 | 0010 | 0001 |
| 001 | 0001 | 0010 |

Minimum Cover

| | | |
|-----|-------------|------|
| 100 | 1111 | 1000 |
| 010 | 1100 | 0100 |
| 001 | 1000 | 0100 |
| 010 | 0011 | 0010 |
| 001 | 0001 | 0010 |
| 001 | 0110 | 0001 |

... Input Encoding Example

Minimum Symbolic Cover

| | | |
|-------|----------------|------|
| INDEX | AND,OR,JMP,ADD | CNTA |
| DIR | AND,OR | CNTB |
| IND | AND | CNTB |
| DIR | JMP,ADD | CNTC |
| IND | ADD | CNTC |
| IND | OR,JMP | CNTD |

Minimum Cover

| | | |
|-----|-------------|------|
| 100 | 1111 | 1000 |
| 010 | 1100 | 0100 |
| 001 | 1000 | 0100 |
| 010 | 0011 | 0010 |
| 001 | 0001 | 0010 |
| 001 | 0110 | 0001 |

■ Examples of

- Simple literal: AND
- Compound literal: AND,OR

Input Encoding Problem

- Transform minimum symbolic cover into minimum bv-cover.
- Map symbolic implicants into bv implicants (one to one).
- Compound literals
 - Encode corresponding symbols so that their supercube does not include other symbol codes.
- Replace encoded literals into cover.

Example

■ Compound literals

- AND,OR,JMP,ADD
- AND,OR
- JMP,ADD
- OR,JMP


■ Valid code

- {AND 00, OR 01, JMP 11, ADD 10}


■ Replacement in cover

| | | |
|------|---|----|
| 1111 | → | ** |
| 1100 | → | 0* |
| 1000 | → | 00 |
| 0011 | → | 1* |
| 0010 | → | 10 |
| 0110 | → | *1 |

Valid code

 

Invalid code

 

Input Encoding Algorithms

■ Problem specification

• Constraint matrix **A**

- One row for each constraint (literal) and one column for each symbol
- $a_{ij} = 1$ iff symbol j belongs to literal i .

■ Solution sought for

• Encoding matrix **E**

- As many rows as the symbols.
- Encoding length n_b .

■ Constraint matrix

$$\mathbf{A} = \begin{matrix} & \text{AND} & \text{OR} & \text{JMP} & \text{ADD} \\ \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \end{bmatrix} & \text{AND,OR} \\ & \text{JMP,ADD} \\ & \text{OR,JMP} \end{matrix}$$

■ Encoding matrix

$$\mathbf{E} = \begin{matrix} \begin{bmatrix} 0 & 0 \\ 0 & 1 \\ 1 & 1 \\ 1 & 0 \end{bmatrix} & \text{AND} \\ & \text{OR} \\ & \text{JMP} \\ & \text{ADD} \end{matrix}$$

Input Encoding Problem

- Given **constraint matrix A**
 - Find **encoding matrix E**
 - satisfying all input encoding constraints (due to compound literals)
 - With minimum number of columns (bits).
- An encoding matrix **E** satisfies the encoding constraints by **A** if for each row **a^T** of **A**
 - The supercube of rows of **E** corresponding to 1's in **a^T** does not intersect any of the rows of **E** corresponding to 0's in **a^T** .
- Identity matrix is always a valid encoding.
 - 1-hot encoding
- **Theorem:** Given a constraint matrix **A** , the encoding matrix **$E=A^T$** satisfies the constraints of **A** .

Dichotomy Theory

■ Dichotomy

- Two sets (L, R).
- Bipartition of a subset of the symbol set.

■ Encoding

- Set of columns of E.
- Each column corresponds to a bipartition of symbol set.

■ Rationale

- Encoding matrix is equivalent to a set of bipartitions.
- Each row of the constraint matrix implies some choice on the codes i.e. induces a bipartition.

Dichotomies

- **Dichotomy associated with row a^T of A**
 - A set pair (L, R)
 - L has the symbols with the **1s** in a^T
 - R has the symbols with the **0s** in a^T
- **Seed dichotomy associated with row a^T of A**
 - A set pair (L, R)
 - L has the symbols with the **1s** in a^T
 - R has **one** symbol with a 0 in a^T
- **Dichotomy associated with constraint $a^T = 1100$**
 - ($\{\text{AND, OR}\}; \{\text{JMP, ADD}\}$).
- **The corresponding seed dichotomies are**
 - ($\{\text{AND, OR}\}; \{\text{JMP}\}$)
 - ($\{\text{AND, OR}\}; \{\text{ADD}\}$).

Definitions

■ Compatibility

- (L_1, R_1) and (L_2, R_2) are compatible if
 - $L_1 \cap L_2 = \emptyset$ and $R_1 \cap R_2 = \emptyset$ or
 - $L_1 \cap R_2 = \emptyset$ and $R_1 \cap L_2 = \emptyset$.

■ Covering

- Dichotomy (L_1, R_1) covers (L_2, R_2) if
 - $L_1 \supseteq L_2$ and $R_1 \supseteq R_2$ or
 - $L_1 \supseteq R_2$ and $R_1 \supseteq L_2$.

■ Prime dichotomy

- Dichotomy that is not covered by any compatible dichotomy of a given set.

■ Union of two compatible dichotomies is a dichotomy covering both with smallest left and right blocks.

Exact Input Encoding

- **Compute all prime dichotomies.**
- **Form a prime/seed dichotomy table.**
- **Find minimum cover of seeds by primes.**
- **Prime dichotomies can be computed based on Compatibility graphs of seed dichotomies by**
 - Finding largest clique covering each edge
- **An encoding can be found based on**
 - Compatibility graphs of seed dichotomies by a clique covering
 - Conflict graphs of seed dichotomies by a graph coloring

Example ...

Encoding matrix


$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \end{bmatrix}$$

Seed dichotomies

| | | |
|-------|--|---------------------------|
| s_1 | | ({ AND,OR } ; { JMP }) |
| s_2 | | ({ AND,OR } ; { ADD }) |
| s_3 | | ({ JMP,ADD } ; { AND }) |
| s_4 | | ({ JMP,ADD } ; { OR }) |
| s_5 | | ({ OR,JMP } ; { AND }) |
| s_6 | | ({ OR,JMP } ; { ADD }) |

Prime Dichotomies

| | | |
|-------|--|------------------------------|
| p_1 | | ({ AND,OR } ; { JMP,ADD }) |
| p_2 | | ({ OR,JMP } ; { AND,ADD }) |
| p_3 | | ({ OR,JMP,ADD } ; { AND }) |
| p_4 | | ({ AND,OR,JMP } ; { ADD }) |

 

... Example

■ Table

| | s_1 | s_2 | s_3 | s_4 | s_5 | s_6 |
|-------|-------|-------|-------|-------|-------|-------|
| p_1 | 1 | 1 | 1 | 1 | 0 | 0 |
| p_2 | 0 | 0 | 0 | 0 | 1 | 1 |
| p_3 | 0 | 0 | 1 | 0 | 1 | 0 |
| p_4 | 0 | 1 | 0 | 0 | 0 | 1 |

■ Minimum cover: p_1 and p_2

■ Encoding

$$E = \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}$$

AND
OR
JMP
ADD

| | |
|-------|--------------------------------|
| p_1 | ({ AND, OR } ; { JMP, ADD }) |
| p_2 | ({ OR, JMP } ; { AND, ADD }) |

Heuristic Encoding

- Determine dichotomies of rows of A.

- Column-based encoding

- Construct E column by column.

- Iterate

- Determine maximum compatible set.
- Find a compatible encoding.
- Use it as column of E.

- Dichotomies

| | | |
|-------|--|------------------------------|
| d_1 | | ({ AND,OR } ; { JMP,ADD }) |
| d_2 | | ({ JMP,ADD } ; { AND,OR }) |
| d_3 | | ({ OR,JMP } ; { AND,ADD }) |

- First two dichotomies are compatible.
- Encoding column $[1100]^T$ satisfies d_1 , d_2 .
- Need to satisfy d_3 . Second encoding column $[0110]^T$.

$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \end{bmatrix}$$

$$\mathbf{E} = \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}$$


Output and Mixed Encoding

■ Output encoding

- Determine encoding of output symbols.

■ Mixed encoding

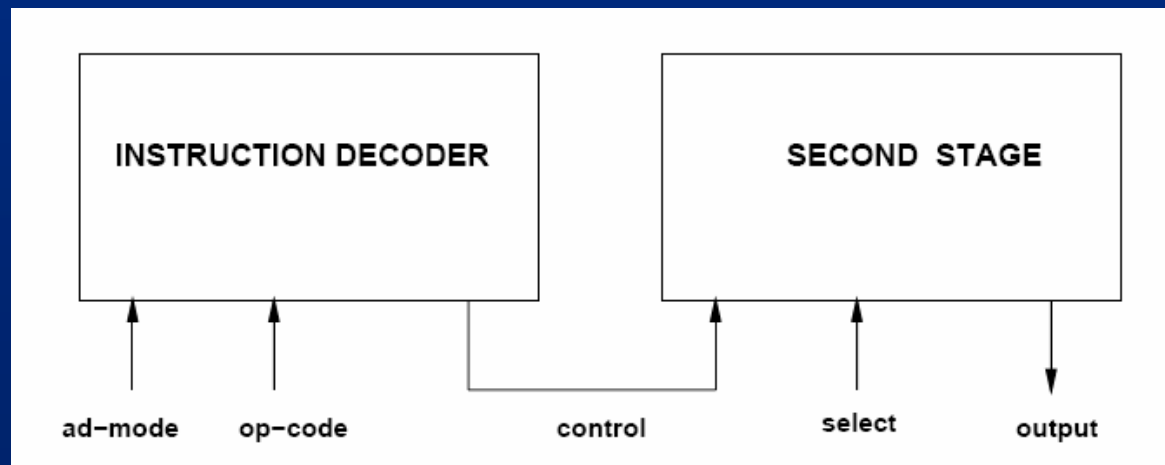- Determine both input and output encoding
- Examples
 - Interconnected circuits.
 - Circuits with feedback.



Symbolic Minimization

- Extension to mvi-minimization.
- Accounts for
 - Covering relations.
 - Disjunctive relations.
- Exact and heuristic minimizers.
- Minimum symbolic cover computed before

| | | |
|-------|----------------|------|
| INDEX | AND,OR,JMP,ADD | CNTA |
| DIR | AND,OR | CNTB |
| IND | AND | CNTB |
| DIR | JMP,ADD | CNTC |
| IND | ADD | CNTC |
| IND | OR,JMP | CNTD |

- Can we use fewer implicants?
- Can we merge implicants?

Covering Relations Example

- Assume the code of CNTD covers the codes of CNTB and CNTC.

| | | |
|-------|----------------|------|
| INDEX | AND,OR,JMP,ADD | CNTA |
| DIR | AND,OR | CNTB |
| IND | AND | CNTB |
| DIR | JMP,ADD | CNTC |
| IND | ADD | CNTC |
| IND | OR,JMP | CNTD |

| | | |
|-----|------|------|
| 100 | 1111 | 1000 |
| 010 | 1100 | 0100 |
| 001 | 1000 | 0100 |
| 010 | 0011 | 0010 |
| 001 | 0010 | 0010 |
| 001 | 0110 | 0001 |

- Possible codes

- CNTA = 00, CNTB = 01,
- CNTC = 10 and CNTD = 11.

| | | |
|-----|------|------|
| 100 | 1111 | CNTA |
| 011 | 1100 | CNTB |
| 011 | 0011 | CNTC |
| 001 | 0110 | CNTD |

Disjunctive Relations Example

- Assume the code of CNTD is the OR of the codes of CNTB and CNTC.

| | | | | | |
|-------|----------------|------|-----|------|------|
| INDEX | AND,OR,JMP,ADD | CNTA | 100 | 1111 | 1000 |
| DIR | AND,OR | CNTB | 010 | 1100 | 0100 |
| IND | AND | CNTB | 001 | 1000 | 0100 |
| DIR | JMP,ADD | CNTC | 010 | 0011 | 0010 |
| IND | ADD | CNTC | 001 | 0010 | 0010 |
| IND | OR,JMP | CNTD | 001 | 0110 | 0001 |

- Possible codes**

- CNTA = 00, CNTB = 01,
- CNTC = 10 and CNTD = 11.

| | | |
|-----|------|------|
| 100 | 1111 | CNTA |
| 010 | 1100 | CNTB |
| 010 | 0011 | CNTC |
| 001 | 1110 | CNTB |
| 001 | 0111 | CNTC |

Output Encoding Algorithms

- Often solved in conjunction with input encoding.
- Exact algorithms
 - Prime dichotomies compatible with output constraints.
 - Construct prime/seed table.
 - Solve covering problem.
- Heuristic algorithms
 - Construct E column by column.
- **Compatibility**
 - (L_1, R_1) and (L_2, R_2) are compatible if $L_1 \cap R_2 = \emptyset$ and $R_1 \cap L_2 = \emptyset$.
- **Covering**
 - Dichotomy (L_1, R_1) covers (L_2, R_2) if $L_1 \supseteq L_2$ and $R_1 \supseteq R_2$.
- Prime dichotomies need to cover at least one element of all seed pairs.

Example ...

- Input constraint matrix of second stage

$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix}$$

- Output constraint matrix of first stage

$$\mathbf{B} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \end{bmatrix}$$

- Assume the code of CNTD covers the codes of CNTB and CNTC.

... Example ...

- Seed dichotomies associated with A

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix}$$

$$B = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \end{bmatrix}$$


S_{1A} : ({CNTA, CNTB} ; {CNTC})
 S_{1B} : ({CNTC} ; {CNTA, CNTB})
 S_{2A} : ({CNTA, CNTB} ; {CNTD})
 S_{2B} : ({CNTD} ; {CNTA, CNTB})
 S_{3A} : ({CNTB, CNTD} ; {CNTA})
 S_{3B} : ({CNTA} ; {CNTB, CNTD})
 S_{4A} : ({CNTB, CNTD} ; {CNTC})
 S_{4B} : ({CNTC} ; {CNTB, CNTD})

- Seed dichotomies s_{2A} and s_{4B} are not compatible with B.
- Note that only one of the seed dichotomies S_{iA} or S_{iB} needs to be covered and not both.

... Example ...

- Prime dichotomies compatible with B

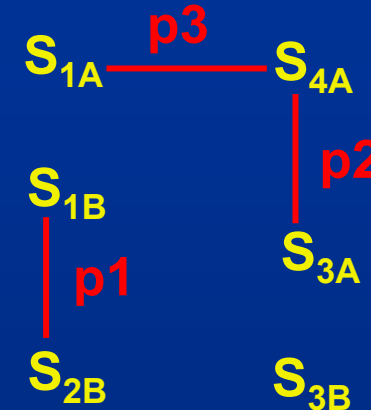P1: ({CNTC, CNTD}; {CNTA, CNTB})
 P2: ({CNTB, CNTD}; {CNTA, CNTC})
 P3: ({CNTA, CNTB, CNTD}; {CNTC})
 P4: ({CNTA}; {CNTB, CNTD})



- Cover: p_1 and p_2
- Encoding matrix

$$E = \begin{bmatrix} 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{bmatrix}$$

S_{1A} : ({CNTA, CNTB}; {CNTC})
 S_{1B} : ({CNTC}; {CNTA, CNTB})
 ~~S_{2A} : ({CNTA, CNTB}; {CNTD})~~
 S_{2B} : ({CNTD}; {CNTA, CNTB})
 S_{3A} : ({CNTB, CNTD}; {CNTA})
 S_{3B} : ({CNTA}; {CNTB, CNTD})
 S_{4A} : ({CNTB, CNTD}; {CNTC})
 ~~S_{4B} : ({CNTC}; {CNTB, CNTD})~~

... Example

- Heuristic encoding considers the dichotomy pairs associated with each row

d_{1A} : ({CNTC, CNTD} ; {CNTA, CNTB})
 ~~d_{1B} : ({CNTA, CNTB} ; {CNTC, CNTD})~~
 d_{2A} : ({CNTB, CNTD} ; {CNTA, CNTC})
 ~~d_{2B} : ({CNTA, CNTC} ; {CNTB, CNTD})~~

- Dichotomies d_{1B} and d_{2B} do not satisfy output constraints.
- Dichotomies d_{1A} and d_{2A} are not compatible and considered one at a time yielding two-column encoding.


$$A = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix}$$

$$B = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 \end{bmatrix}$$

$$E = \begin{bmatrix} 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{bmatrix}$$

State Encoding of Finite-State Machines

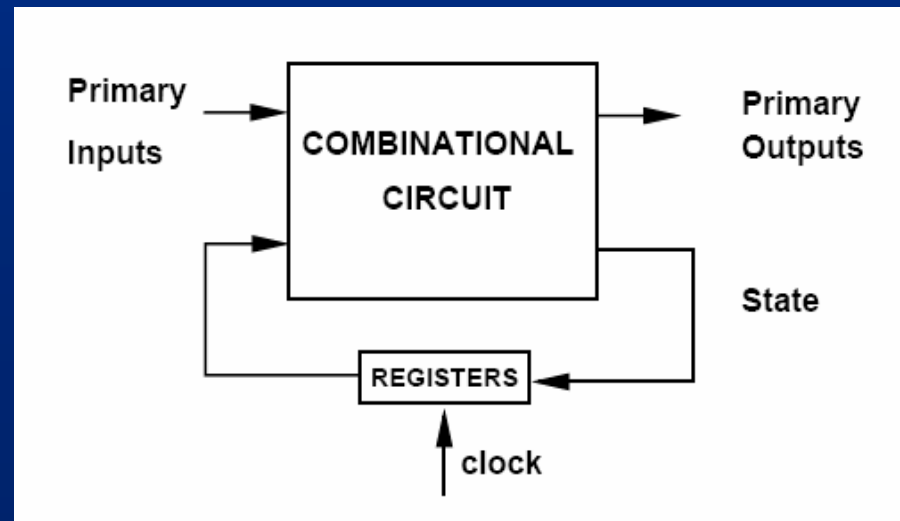- Given a (minimum) state table of a finite-state machine
 - Find a consistent encoding of the states
 - that preserves the cover minimality
 - with minimum number of bits.
- The state set must be encoded while satisfying simultaneously both input and output constraints.



Example ...

| INPUT | P-STATE | N-STATE | OUTPUT |
|-------|----------------|----------------|--------|
| 0 | s ₁ | s ₃ | 0 |
| 1 | s ₁ | s ₃ | 0 |
| 0 | s ₂ | s ₃ | 0 |
| 1 | s ₂ | s ₁ | 1 |
| 0 | s ₃ | s ₅ | 0 |
| 1 | s ₃ | s ₄ | 1 |
| 0 | s ₄ | s ₂ | 1 |
| 1 | s ₄ | s ₃ | 0 |
| 0 | s ₅ | s ₂ | 1 |
| 1 | s ₅ | s ₅ | 0 |

Minimum Symbolic Cover

| | | | |
|---|--|----------------|---|
| * | s ₁ s ₂ s ₄ | s ₃ | 0 |
| 1 | s ₂ | s ₁ | 1 |
| 0 | s ₄ s ₅ | s ₂ | 1 |
| 1 | s ₃ | s ₄ | 1 |

Covering Constraints

- s₁ and s₂ cover s₃
- s₅ is covered by all other states.

Encoding Constraint Matrices

$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

$$\mathbf{B} = \begin{bmatrix} 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

... Example ...

After Implicant Merging:

| | | | |
|---|--------|----|---|
| 0 | s1, s2 | s3 | 0 |
| 1 | s2 | s1 | 1 |
| 1 | s3 | s4 | 1 |
| 0 | s4, s5 | s2 | 1 |
| 1 | s1, s4 | s3 | 0 |
| 0 | s3 | s5 | 0 |
| 1 | s5 | s5 | 0 |

If $s1 \supseteq s3$ and $s2 \supseteq s3$:

| | | | |
|---|------------|----|---|
| * | s1, s2, s4 | s3 | 0 |
| 1 | s2 | s1 | 1 |
| 1 | s3 | s4 | 1 |
| 0 | s4, s5 | s2 | 1 |
| 0 | s3 | s5 | 0 |
| 1 | s5 | s5 | 0 |

| INPUT | P-STATE | N-STATE | OUTPUT |
|-------|---------|---------|--------|
| 0 | s1 | s3 | 0 |
| 1 | s1 | s3 | 0 |
| 0 | s2 | s3 | 0 |
| 1 | s2 | s1 | 1 |
| 0 | s3 | s5 | 0 |
| 1 | s3 | s4 | 1 |
| 0 | s4 | s2 | 1 |
| 1 | s4 | s3 | 0 |
| 0 | s5 | s2 | 1 |
| 1 | s5 | s5 | 0 |

Last two rows, output is 0 => no impact on output equation. If s5 is covered by all other states, a minimal code will have s5 assigned the 0 code, i.e. no impact on next state equations => last two rows can be eliminated.

| | | | |
|---|------------|----|---|
| * | s1, s2, s4 | s3 | 0 |
| 1 | s2 | s1 | 1 |
| 1 | s3 | s4 | 1 |
| 0 | s4, s5 | s2 | 1 |

... Example

■ Encoding matrix (one row per state)

$$E = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 0 & 1 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

Covering Constraints

- s1 and s2 cover s3
- s5 is covered by all other states.

■ Encoded cover of combinational component

| | | | |
|---|-----|-----|---|
| * | 1** | 001 | 0 |
| 1 | 101 | 111 | 1 |
| 0 | *00 | 101 | 1 |
| 1 | 001 | 100 | 1 |

| | | | |
|---|-------------|-------|---|
| * | $s_1s_2s_4$ | s_3 | 0 |
| 1 | s_2 | s_1 | 1 |
| 0 | s_4s_5 | s_2 | 1 |
| 1 | s_3 | s_4 | 1 |

Limitation of Symbolic Minimization and Constrained Encoding

- The minimum-length solution compatible with a set of constraints may require bits larger than $\lceil \log_2 n_s \rceil$.
- **Example:** Consider an FSM whose minimal symbolic cover is:
 - 00 s1, s2 s3 100
 - 01 s2, s3 s1 010
 - 10 s1, s3 s2 001
- **Satisfaction of input constraints requires at least 3 bits.**
 - e.g. s1=100, s2=010, s3=001
 - PLA size is 3 rows and 11 columns (2 PI+3 PS+3 NS+3 PO)
- **Assume we do not satisfy first input constraint**
 - 2 bits are sufficient
 - PLA size is 4 rows and 9 columns (2 PI+2 PS+2 NS+3 PO)

State Encoding for Multiple-Level Models

- Logic network representation.
- **Area**: # of literals.
- **Delay**: Critical path length.
- Encoding based on **cube-extraction** heuristics [Mustang-Devadas].
- **Rationale**
 - When two (or more) states have a transition to the same next-state
 - Keep the distance of their encoding short.
 - Extract a large common cube.
- **Exploit first stage of logic.**
- **Works fine because most FSM logic is shallow.**

Example

- **5-state FSM (3-bits).**
 - $s1 \rightarrow s3$ with input i .
 - $s2 \rightarrow s3$ with input i' .
- **Encoding**
 - $s1 \rightarrow 000 = a'b'c'$.
 - $s2 \rightarrow 001 = a'b'c$.
- **Transition**
 - $i a'b'c' + i' a'b'c = a'b' (ic + i'c')$
 - **6 literals instead of 8.**

Algorithm

■ Examine all state pairs

- Complete graph with $|V| = |S|$.

■ Add weight on edges

- Model desired code proximity.
- The higher the weight the lower the distance.

■ Embed graph in the Boolean space.

- Objective is to minimize the cost function

$$\sum_{i=1}^{N_s} \sum_{j=i+1}^{N_s} \text{Weight}(v_i, v_j) * \text{Dist}(v_i, v_j)$$

■ Difficulties

- The number of occurrences of common factors depends on the next-state encoding.
- The extraction of common cubes interact with each other.

Mustang Algorithm Implementation ...

■ Fanout-oriented algorithm

- Consider *state fanout* i.e. next states and outputs.
- Assign closer codes to pair of states that have same next state transition or same output.
- *Maximize the size of the most frequent common cubes.*

$$M_{k,l}^P = \sum_{i=1}^{m_o} (P_{k,i}^o * P_{l,i}^o) + \frac{n_E}{2} \sum_{i=1}^{n_s} (P_{k,i}^s * P_{l,i}^s)$$

$P_{k,i}^o$ is the number of times state k is represented in output i ,

$P_{k,i}^s$ is number of times state k is represented in state i ,

m_o is the number of outputs,

n_s is the number of states,

n_E is the number of encoding bits.

... Mustang Algorithm Implementation ...

■ Fanin-oriented algorithm

- Consider *state fan-in* i.e. present states and inputs.
- Assign closer codes to pair of states that have transition from same present state or same input.
- *Maximize the frequency of the largest common cubes.*

$$M_{k,l} = \sum_{i=1}^{ni} (P_{k,i}^{ON} * P_{l,i}^{ON}) + (P_{k,i}^{OFF} * P_{l,i}^{OFF}) + n_b * \sum_{i=1}^{ns} (P_{k,i}^S * P_{l,i}^S)$$

$P_{k,i}^{ON}$: number of occurrences of input i in equation of state k

$P_{k,i}^{OFF}$: number of occurrences of input \bar{i} in equation of state k

$P_{k,i}^S$: number of occurrences of state i in equation of state k

... Mustang Algorithm Implementation

```

-0 st0 st0 0
11 st0 st0 0
01 st0 st1 -
0- st1 st1 1
11 st1 st0 0
10 st1 st2 1
1- st2 st2 1
00 st2 st1 1
01 st2 st3 1
0- st3 st3 1
11 st3 st2 1
    
```

Fig. 1. Example FSM.

 


Fig. 5. Graph generated by fanout-oriented algorithm.

 


Fig. 6. Graph generated by fanin-oriented algorithm.

Synchronous Logic Network ...


■ Synchronous Logic Network

- Variables.
- Boolean equations.
- Synchronous delay annotation.


■ Synchronous network graph

- Vertices \leftrightarrow equations \leftrightarrow I/O , gates.
- Edges \leftrightarrow dependencies \leftrightarrow nets.
- Weights \leftrightarrow synch. delays \leftrightarrow registers.

... Synchronous Logic Network

 

(a)

 

(b)

$$a^{(n)} = i^{(n)} \oplus i^{(n-1)}$$

$$b^{(n)} = i^{(n-1)} \oplus i^{(n-2)}$$

$$c^{(n)} = a^{(n)}b^{(n)}$$

$$d^{(n)} = c^{(n)} + d'^{(n-1)}$$

$$e^{(n)} = d^{(n)}e^{(n-1)} + d'^{(n)}b'^{(n)}$$

$$v^{(n)} = c^{(n)}$$


$$s^{(n)} = e^{(n-1)}$$

Approaches to Synchronous Logic Optimization

- **Optimize combinational logic only.**
- **Optimize register position only**
 - Retiming.
- **Optimize overall circuit**
 - Peripheral retiming.
 - Synchronous transformations
 - Algebraic.
 - Boolean.

Retiming ...

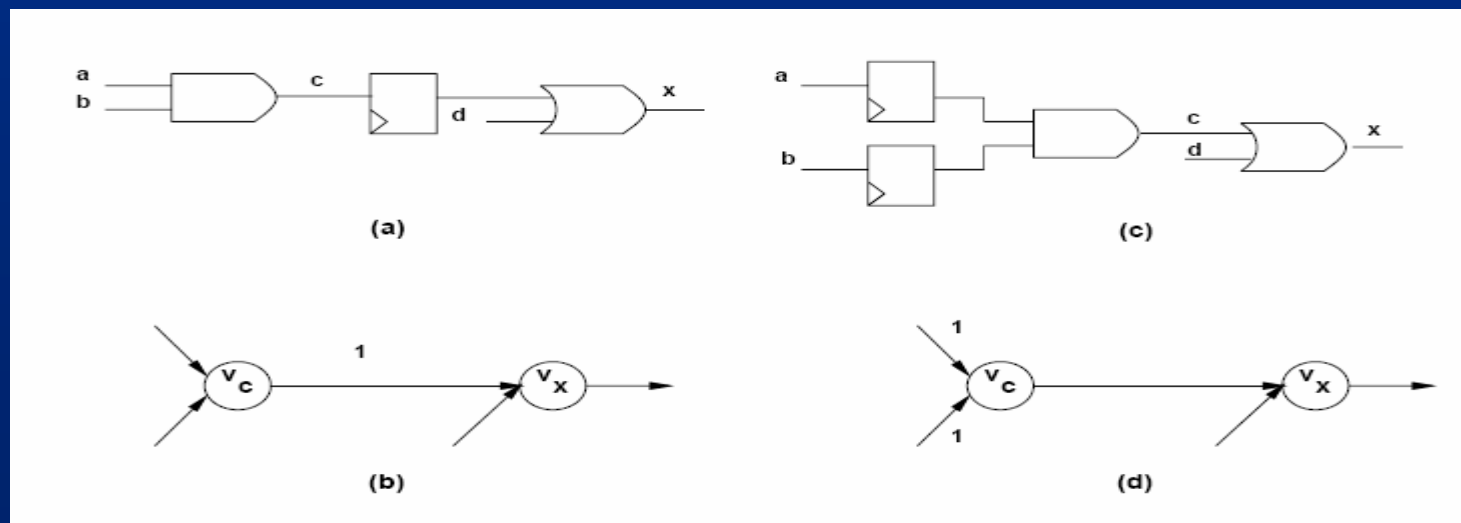- Minimize cycle-time or area by changing register positions.
- Do not modify combinational logic.
- Preserve network structure
 - Modify weights.
 - Do not modify graph structure.



... Retiming ...

- **Global optimization technique [Leiserson].**
- **Changes register positions**
 - affects area
 - changes register count.
 - affects cycle-time
 - changes path delays between register pairs.
- **Solvable in polynomial time.**
- **Assumptions**
 - Vertex delay is constant: No fanout delay dependency.
 - Graph topology is invariant: No logic transformations.
 - Synchronous implementation
 - Cycles have positive weights.
 - Edges have non-negative weights.

... Retiming ...

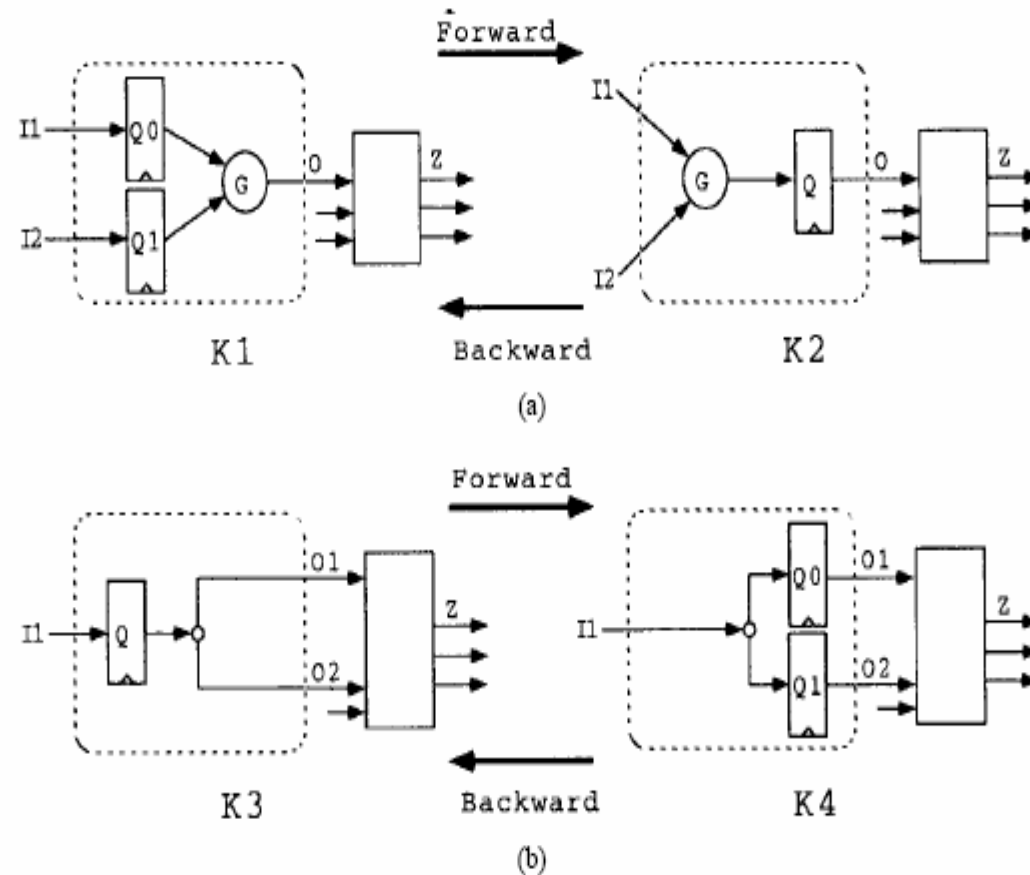


Fig. 1. (a) Retiming forward/backward across a single-output combinational gate and (b) retiming forward/backward across a fanout stem.

... Retiming ...


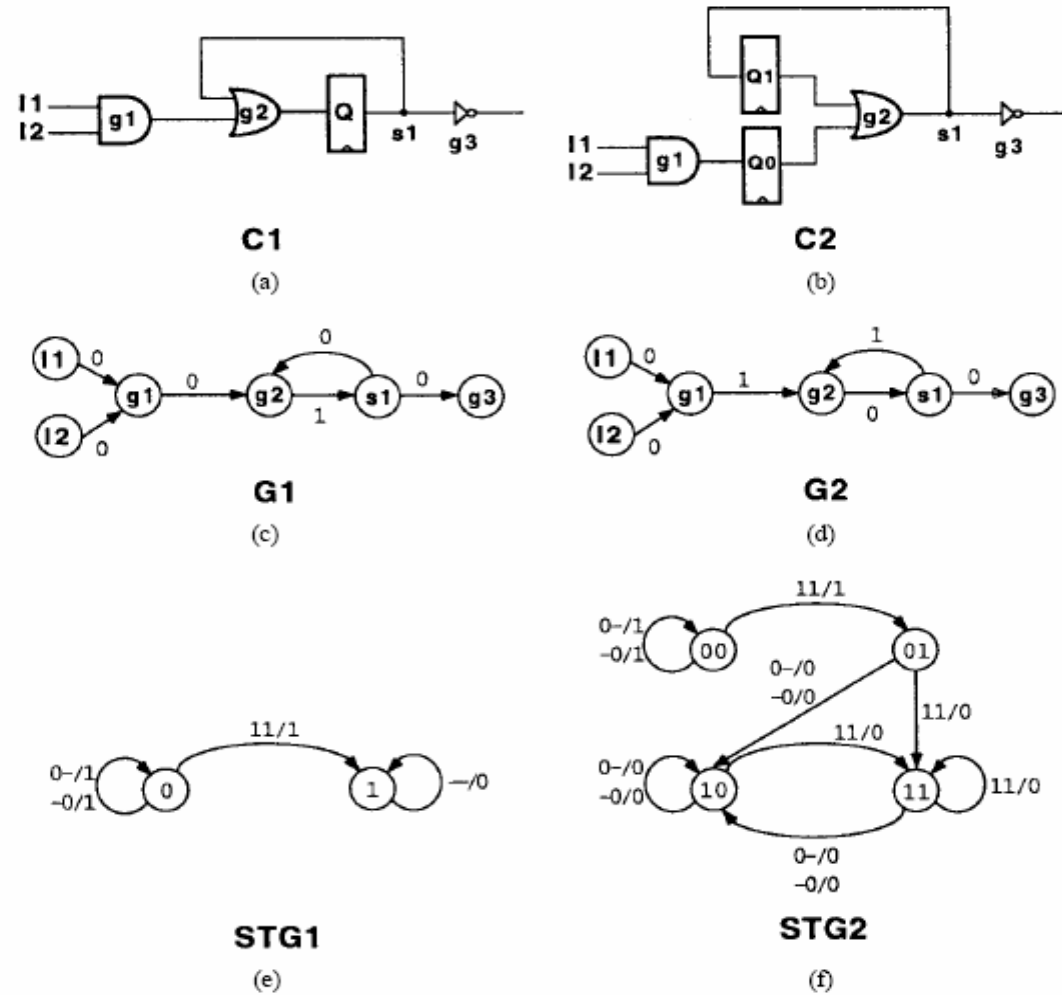



Fig. 2. An example of a backward retiming move across a single-output combinational gate.

... Retiming

 


L1

(a)

 


L2

(b)

 

(c)

 



(d)

Fig. 3. An example of a forward retiming move across a fanout stem.

... Retiming ...

■ Retiming of a vertex

  - Moving registers from output to inputs or vice versa
- Integer
 - Positive value: from outputs to inputs
 - Negative value: from inputs to outputs



■ Retiming of a network

- Vector of vertex retiming.



■ Definitions

- $w(v_i, v_j)$ – weight of edge (v_i, v_j) .

- Retiming of an edge (v_i, v_j) : $\tilde{w}_{ij} = w_{ij} + r_j - r_i$.

 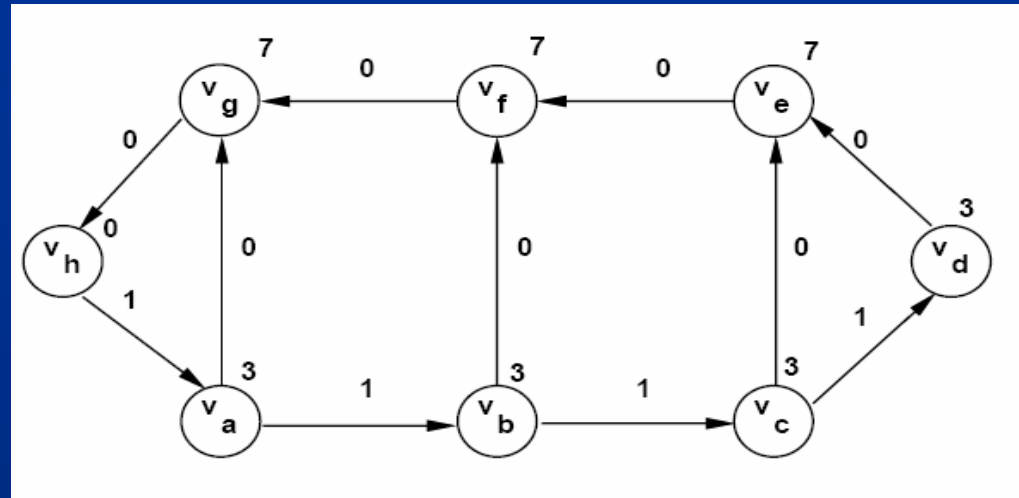Example

- Node values indicate delay.
- Retiming vector
 - $[a\ b\ c\ d\ e\ f\ g\ h] = [0\ 0\ -1\ -1\ -1\ 0\ 1\ 1]$
 - $[a\ b\ c\ d\ e\ f\ g\ h] = - [1\ 1\ 2\ 2\ 2\ 1\ 0\ 0] = [1\ 1\ 0\ 0\ 0\ 1\ 2\ 2]$
- Original critical path is $(v_d, v_e, v_f, v_g, v_h) = 24$ units
- Retimed critical path is $(v_b, v_c, v_e) = 13$ units





Behavior and Testability Preservation under Retiming ...

- A **synchronizing sequence** for a machine is an input sequence that brings the machine to a known and unique state determined without knowledge of output response or initial state of the machine.
- An interesting class of synchronizing sequences allows the state reached after applying the synchronizing sequence to be either a single state or a set of equivalent states.
- A synchronizing sequence (or a test) derived based on pessimistic 3-valued simulation is called **structural**; otherwise, it is called **functional**.
 - functional synchronizing sequences (or tests) correspond to those derived based on the state transition graph of a circuit.

... Behavior and Testability Preservation under Retiming ...

Theorem 1: Let K' be a circuit resulting from a retiming of K . If a structural synchronizing sequence I synchronizes K to a state q , then I synchronizes K' to a state q' equivalent to q .

 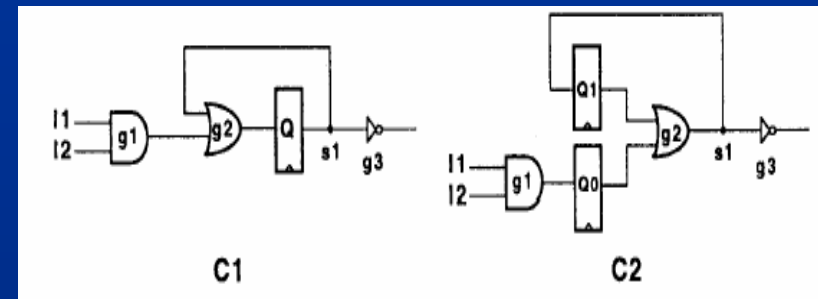
Theorem 2: Let K' be a circuit resulting from a retiming of K , and let V be a sequence of input vectors of length equal to the maximum number of backward retiming moves across any controlling gate in K . If a structural synchronizing sequence I synchronizes K to a single state, then the sequence $\langle I, V \rangle$ synchronizes K and K' to single and equivalent states.




- **Vector 11 synchronizes C1 to a single state and C2 to an equivalent set of states.**
- **Any of the vectors (11, 00), (11, 01), (11, 10), (11, 11) synchronizes C2 to a single equivalent state.**

... Behavior and Testability Preservation under Retiming ...

 
Theorem 3: Let K' be a circuit resulting from a retiming of K , and let P be a sequence of arbitrary input vectors of length equal to the maximum number of forward retiming moves across any fan-out stem node in K . If a functional synchronizing sequence I synchronizes K to a state q , then the sequence $\langle P, I \rangle$ synchronizes K' to a state q' equivalent to q .




L1
(a)

 

L2
(b)

 

(c)

 


(d)

- **Vector 11 is a functional synchronizing sequence for L1 but not for L2.**
- **Any of the vectors (00, 11), (01, 11), (10, 11), (11, 11) is a synchronizing sequence for L2.**

... Behavior and Testability Preservation under Retiming


Theorem 5: Let K' be a circuit resulting from a retiming of K , and let P be a sequence of arbitrary vectors of length equal to the maximum number of forward retiming moves across any node in K . For every fault f' in K' , there exists a corresponding fault f in K such that if T is a test for f in K , then the sequence $\langle P, T \rangle$ is a test for f' in K' .

 Corollary 1: Retiming preserves single stuck-at fault testability.



H 1

(a)

 

H 2

(b)

Fig. 6. An example illustrating that retiming may not preserve single stuck-at fault testability under a hardware reset or a global reset state assumption.