

COE 202, Fall 2016

Verilog Assignment 1: Modeling Boolean Functions

Due: Thursday, November 10, at 11 am (during class time)

1. Write a Verilog description of a circuit specified by the following Boolean functions:

$$x = a(cd + b) + bc'$$

$$y = (a \oplus b)(c + d')$$

$$z = ((a + b)(c + d'))'$$

- a) Use continuous assignment statements to describe the above equations. Do not assign any delay to x , y , or z .
- b) Use gate-level description to describe the above equations without modification. Use a NAND gate for the output z . Assign a delay of 1ns to a NOT gate, a delay of 2ns to AND, NAND, OR, and a delay of 3ns to XOR.
- c) Write a test bench to test the two modules of parts (a) and (b). Exhaustive testing should be used. All the sixteen possible combinations of inputs a , b , c , and d should be used to produce outputs x , y , and z .
- d) Run the simulator. Examine the waveforms to verify the correctness of outputs x , y , and z . Record the delays of x , y , and z for the gate-level description. Save different snapshots of the waveforms.
- e) Submit a report (Word document) that should contain:
 - i. The Verilog module descriptions of parts (a) and (b)
 - ii. The test benches of parts (a) and (b)
 - iii. The timing diagrams (waveforms) taken directly as snapshots from the simulator. Have as many snapshots as needed to cover all the test cases.
 - iv. Discussion about the time delays of outputs x , y , and z .

A soft copy of the report and Verilog code should be submitted on Blackboard and a hard copy should be submitted in class.

Important Note: the Verilog code and simulation results should be your own individual work. Detected cheating cases (copying) will receive a grade of zero, including those who shared their work with others.