

COE 202, Fall 2016

Verilog Assignment 2

Due: Thursday, January 5, at 11 am (during class time)

Q1. Modeling a simple ALU

It is required to design an ALU circuit that receives two 16-bit input numbers **A[15:0]** and **B[15:0]**, and produces a 16-bit output **Z[15:0]** and a carry output **Cout**. The circuit implements the following functions based on the values of the 3-bit selection input **S[2:0]**:

Select Input S[2:0]	Function
0 0 0	$Z = A + B$
0 0 1	$Z = A - B$
0 1 0	$Z = A + B + 1$
0 1 1	$Z = A - B - 1$
1 0 0	$Z = A \& B$
1 0 1	$Z = A \mid B$
1 1 0	$Z = A \wedge B$
1 1 1	$Z = \sim(A \mid B)$

For the last four logic functions, the output **Cout** should be zero.

- [4 marks] Show the block diagram design of your circuit using components like Adder, Multiplexor, etc. as needed. Use only one adder in your solution.
- [5 marks] Model the Adder and the Multiplexor modules in Verilog separately using continuous assignment statements.
- [5 marks] Model the ALU by instantiating components according to your block diagram.
- [6 marks] Write a Verilog test bench to test your design and verify its correctness by simulation. Show snapshots of your simulation to demonstrate its correctness. For each function, test at least 2 input combinations of your choice to demonstrate correct functionality of the ALU.

Q2. Modeling a Synchronous Sequential Circuit

It is required to design a synchronous sequential circuit that receives a serial input **X** (bit stream) and produces a serial output **Z**. The output **Z** is set to **1** when the circuit detects either the sequence **1010** or the sequence **1001**. Assume that the detection of sequences is overlapping. The flip-flops should have an asynchronous reset input to reset the circuit to its initial state. The following is an example of an input/output bit stream:

Input Bit Stream X	1 0 1 0 1 0 0 1 0 1 0 0 0
Output Bit Stream Z	0 0 0 1 0 1 0 1 0 0 1 0 0

- a) [5 marks] Design a **Mealy** state diagram of the sequence detector.
- b) [5 marks] Derive the next state and output equations and draw a circuit diagram of the sequential circuit using minimal number of D flip flops and logic.
- c) [7 marks] Write a structural Verilog model of your sequential circuit by first modeling the D Flip-Flop as a separate module. Then, instantiate the D Flip-Flops and model the next state and output equations using continuous assign statements.
- d) [5 marks] Write a test bench that tests your structural Verilog model in (c) using the above input sequence. Verify that your circuit produces the correct output. Show snapshots of the generated waveforms in your report.
- e) [5 marks] Write a behavioral Verilog model that models your state diagram in (a).
- f) [3 marks] Use the test bench developed in (d) to test the correctness of your behavioral model developed in (e). Verify that your behavioral model produces the correct output. Show snapshots of the generated waveforms in your report.

This assignment can be solved either individually, or as a group of two students. Include snapshots of simulation output to illustrate the correctness of your circuit. Submit your solution as a word document along with the Verilog code.

A Soft copy of the word document and Verilog code should be submitted on Blackboard. In addition, a hard copy of the word document should be submitted in class.