

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 141 (Fall 2014)
Major Exam II
Saturday November 29, 2014

Time: 150 minutes, Total Pages: 11

Name: _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	17	
2	14	
3	10	
4	12	
5	12	
Total	65	

Question 1

For the given K-map representing the Boolean function F, answer the following questions:

AB/CD	00	01	11	10
00		1		
01		1	1	1
11	1	1		1
10	1	1		1

- (i) Which one of the following is an Implicant of F:

Term	$A'C'$	$A'BD$	AC	$A'B'C'$	BCD'
Implicant (Y/N)					

- (ii) Which one of the following is a Prime Implicant (PI) of F:

Term	AC'	$A'BC$	$BC'D$	$C'D$	AD'
PI (Y/N)					


- (iii) Which one of the following is an Essential Prime Implicant (EPI) of F:

	$C'D$	$A'BC$	$A'C'$	$BC'D$	AD'
EPI (Y/N)					

- (iv) Obtain a simplified sum-of-product (SOP) expression for F.

- (v) The following Boolean expression $F = AD + A'C'D'$ is a simplified version of the expression $F = A'B'C'D' + ABCD + AB'C'D$. Are there any don't care conditions? If so, what are they?

- (vi) Implement the circuit given below using only 2-input NAND gates. Redraw the circuit to obtain a multi-level NAND circuit implementation. Assume that only the true form of each input variable is available.

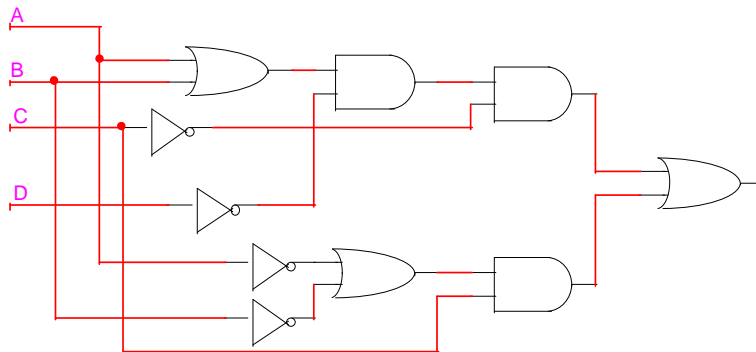

Question 2.

(14 Points)

(i) Fill in all blank cells in the two tables below.

Binary	Equivalent decimal value with the binary interpreted as:			
	Unsigned number	Signed-magnitude number	Signed-1's complement number	Signed-2's complement number
10110110				

Decimal	Binary representation in 8 bits:		
	Signed-magnitude representation	Signed-1's complement representation	Signed-2's complement representation
+ 100			
- 100			

(ii) Show how the following arithmetic operations are performed using 5-bit signed 2's-complement system. Check for overflow and mark clearly any overflow occurrences.

$\begin{array}{r} 01001 \\ - 11110 \\ \hline \end{array}$	(i)	$\begin{array}{r} 10100 \\ + 11100 \\ \hline \end{array}$	(ii)
Overflow: Yes/No		Overflow: Yes/No	
$\begin{array}{r} 11111 \\ + 11111 \\ \hline \end{array}$	(iii)	$\begin{array}{r} 01101 \\ - 11101 \\ \hline \end{array}$	(iv)
Overflow: Yes/No		Overflow: Yes/No	

Question 3.**(10 points)**

- (i) It is required to design a combinational circuit that receives a 4-bit input number, $X_3X_2X_1X_0$, and computes the number of leading zero's in the input. For example, if the input $X_3X_2X_1X_0=0111$ or $X_3X_2X_1X_0=0100$, the output should produce a result indicating that there is a single leading zero. Construct the truth table of the circuit. You do not need to derive the Boolean expressions of the outputs. (5 points)
- (ii) Using a block diagram of the design of the 4-bit leading-zero detector circuit in (i) and any other needed MSI blocks (e.g. Adder, Comparator, Multiplexer, Decoder, etc.), design a combinational circuit that receives an 8-bit input number, $X_7X_6X_5X_4X_3X_2X_1X_0$, and computes the number of leading zero's in the input. (5 points)

Question 4.**(12 Points)**

Using *only* the following modules:

- One 2-to-4 Decoder with enable,
- One 4-to-1 MUX,
- A maximum of five 1-to-2 DeMUXs /Decoders, and
- The minimum number of 2-input NAND gates (*if needed*)

Implement the following assuming that signals are available only in the “True” but not the complement form:

- (i) A 3-to-8 Decoder (you may use this decoder as a black-box in solving (ii) and/or (iii) below)
- (ii) $F1(a,b) = ab + a'b'$
- (iii) $F2(a,b,c) = m_0 + m_1 + m_2 + m_4 + m_7$

Label all your signals (inside and outside MSI components).


Question 5.

(12 Points)


It is required to design an n -bit magnitude comparator. The circuit receives two n -bit unsigned numbers A and B and produces two outputs GT and EQ as given in the table to the right.

	GT	EQ
IF $A > B$	1	0
IF $A = B$	0	1
IF $A < B$	0	0

The input operands are processed in a bitwise manner *starting with the most significant bit (MSB)*. The comparator circuit is constructed using n identical copies of the basic 1-bit cell shown to the right. Cell i processes the i^{th} input bits (A_i and B_i) together with information passed to it from its predecessor cell (GT_{i+1} and EQ_{i+1}). It produces two output bits (GT_i and EQ_i). The cell output $GT_i = 1$ iff $(A_{n-1} A_{n-2} \dots A_{i+1} A_i > B_{n-1} B_{n-2} \dots B_{i+1} B_i)$ and $EQ_i = 1$ iff $(A_{n-1} A_{n-2} \dots A_{i+1} A_i = B_{n-1} B_{n-2} \dots B_{i+1} B_i)$.

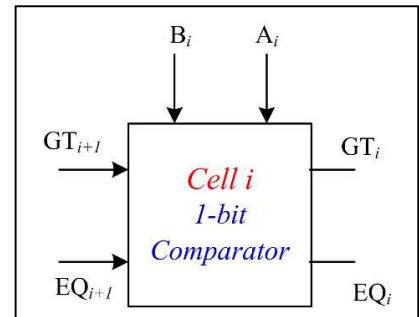

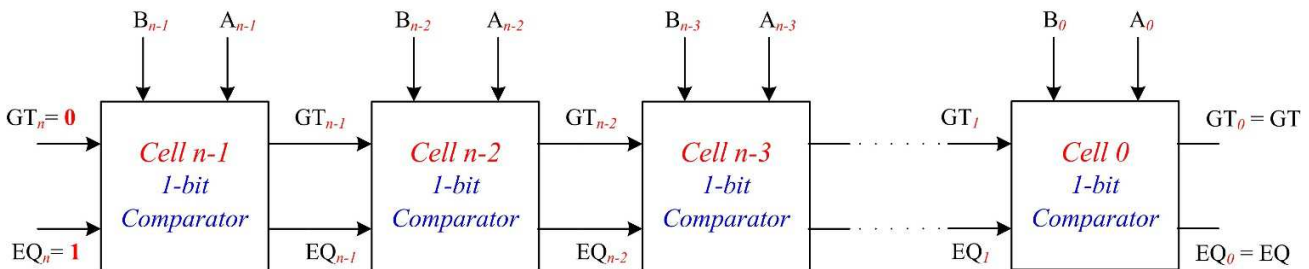
The Figure below shows the n -bit comparator circuit implemented using n copies of the basic 1-bit cell. The output of the n -bit comparator is that of the n^{th} cell copy (cell 0; the least-significant). Note that the inputs GT_n and EQ_n to the first cell (cell $n-1$; the most significant) are set to **0 and 1** respectively as there are no more significant bits.




Boolean expressions of the outputs of cell i and its gate-level implementation are given below:

$$GT_i = GT_{i+1} + A_i \bar{B}_i EQ_{i+1}, \text{ and } EQ_i = (A_i \odot B_i) \cdot EQ_{i+1}$$

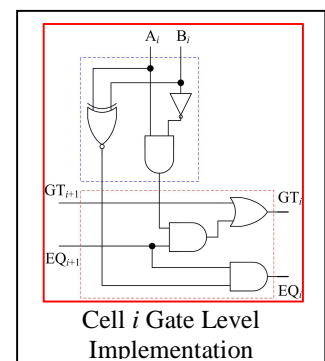Assuming that the **XOR** and **XNOR** gates have a delay of 2τ while all **OTHER** gates (including inverters) have a delay of 1τ , calculate:



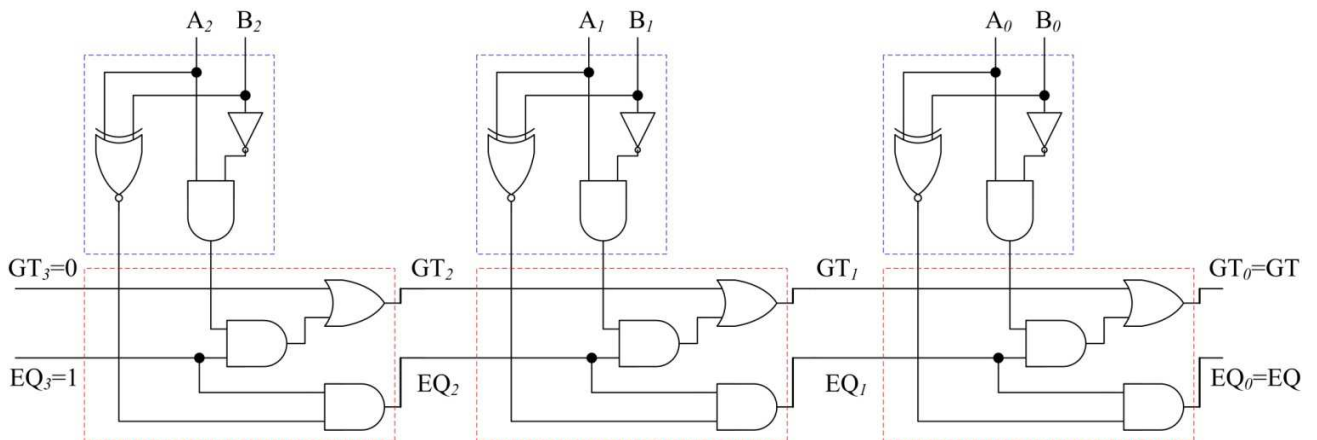
(i) The worst case delay of the 3-bit comparator (as a function of τ) shown below (4 Points)



(ii) The worst case delay of an n -bit comparator (as a function of n and τ) (3 Points)

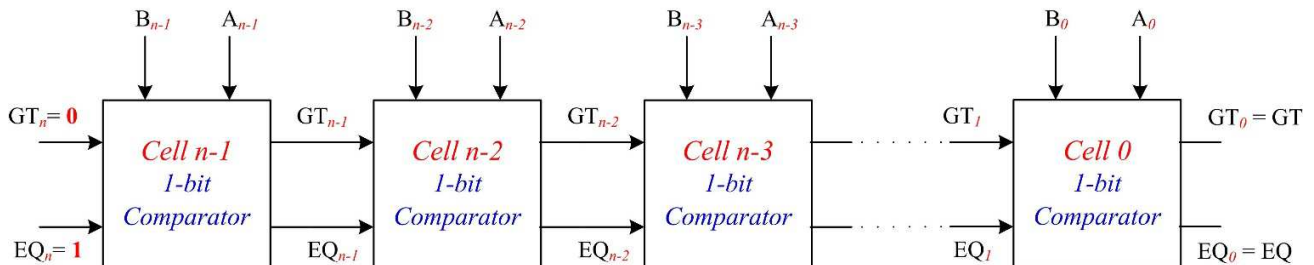- (iii) Suggest a design for a cascadeable 3-bit comparator with lookahead capability. What is the worst case delay of this unit (using the same delay model of 2τ for XOR/XNOR gates and 1τ for all other gates (irrespective of their fanin)? (5 Points)

For convenience, the comparator circuit and Boolean expressions of the cell are repeated here.



Boolean expressions of the outputs of cell i and its gate-level implementation are given below:

$$GT_i = GT_{i+1} + A_i \bar{B}_i EQ_{i+1}, \text{ and}$$

$$EQ_i = (A_i \odot B_i) \cdot EQ_{i+1}$$