

Behavioral Modeling in Verilog

COE 202

Digital Logic Design

Dr. Muhamed Mudawar

King Fahd University of Petroleum and Minerals

Presentation Outline

- ❖ Introduction to Dataflow and Behavioral Modeling
- ❖ Verilog Operators
- ❖ Module Parameters
- ❖ Modeling Adders, Comparators, Multiplexers
- ❖ Always Block with Sensitivity List
- ❖ Procedural Statements: IF and CASE
- ❖ Modeling Decoder, Priority Encoder, and ALU

Verilog Four-Valued Logic

❖ Verilog Value Set consists of four basic values:

0 – represents a logic zero, or false condition

1 – represents a logic one, or true condition

X – represents an unknown logic value

Z – represents a high-impedance value

x or **X** represents an unknown or uninitialized value

z or **Z** represents the output of a disabled tri-state buffer

Nets and Variables

Verilog has two major data types:

1. **Net data types:** are connections between parts of a design

2. **Variable data types:** can store data values

❖ The **wire** is a net data type (physical connection)

✧ A wire cannot store the value of a procedural assignment

✧ However, a wire can be driven by continuous assignment

❖ The **reg** is a variable data type

✧ Can store the value of a procedural assignment

✧ However, cannot be driven by continuous assignment

✧ Other variable types: **integer**, **time**, **real**, and **realtime**

Modeling Circuits in Verilog

Four levels of modeling circuits in Verilog

1. Gate-Level Modeling

Lowest-level modeling using Verilog primitive gates

2. Structural Modeling using module instantiation

Describes the structure of a circuit with modules at different levels

3. Dataflow Modeling using concurrent assign statements

Describes the flow of data between input and output

4. Behavioral Modeling using procedural blocks and statements

Describes what the circuit does at a higher level of abstraction

Can also mix different models in the same design

Dataflow and Behavioral Modeling

❖ Dataflow Modeling using Continuous Assignment

- ✧ Used mostly for describing Boolean equations and combinational logic
- ✧ Verilog provides a rich set of operators
- ✧ Can describe: adders, comparators, multiplexers, etc.
- ✧ Synthesis tool can map a dataflow model into a target technology

❖ Behavioral Modeling using Procedural Blocks and Statements

- ✧ Describes what the circuit does at a functional and algorithmic level
- ✧ Encourages designers to rapidly create a prototype
- ✧ Can be verified easily with a simulator
- ✧ Some procedural statements are synthesizable (Others are NOT)

Continuous Assignment

- ❖ The **assign** statement defines continuous assignment
- ❖ Syntax: **assign** [**#delay**] *net_name* = *expression*;
- ❖ Assigns *expression* value to *net_name* (wire or output port)
- ❖ The optional **#delay** specifies the delay of the assignment
- ❖ Continuous assignment statements are **concurrent**
- ❖ Can appear in any order inside a module
- ❖ Continuous assignment can model combinational circuits
- ❖ Describes the flow of data between input and output

Verilog Operators

Bitwise Operators

<code>~a</code>	Bitwise NOT
<code>a & b</code>	Bitwise AND
<code>a b</code>	Bitwise OR
<code>a ^ b</code>	Bitwise XOR
<code>a ~^ b</code>	Bitwise XNOR
<code>a ^~ b</code>	Same as <code>~^</code>

Arithmetic Operators

<code>a + b</code>	ADD
<code>a - b</code>	Subtract
<code>-a</code>	Negate
<code>a * b</code>	Multiply
<code>a / b</code>	Divide
<code>a % b</code>	Remainder

Relational Operators

<code>a == b</code>	Equality
<code>a != b</code>	Inequality
<code>a < b</code>	Less than
<code>a > b</code>	Greater than
<code>a <= b</code>	Less or equal
<code>a >= b</code>	Greater or equal

Reduction Operators

<code>&a</code>	AND all bits
<code> a</code>	OR all bits
<code>^a</code>	XOR all bits
<code>~&a</code>	NAND all bits
<code>~ a</code>	NOR all bits
<code>~^a</code>	XNOR all bits

Shift Operators

<code>a << n</code>	Shift Left
<code>a >> n</code>	Shift Right

Miscellaneous Operators

<code>sel?a:b</code>	Conditional
<code>{a, b}</code>	Concatenate

Reduction operators produce a 1-bit result

Relational operators produce a 1-bit result

`{a, b}` concatenates the bits of `a` and `b`

Bit Vectors in Verilog

- ❖ A Bit Vector is multi-bit declaration that uses a single name
- ❖ A Bit Vector is specified as a Range **[msb:lsb]**
- ❖ **msb** is *most-significant bit* and **lsb** is *least-significant bit*
- ❖ Examples:

```
input  [15:0] A;    // A is a 16-bit input vector
```

```
output [0:15] B;   // Bit 0 is most-significant bit
```

```
wire   [3:0] W;   // Bit 3 is most-significant bit
```

- ❖ **Bit select:** **W[1]** is bit **1** of W
- ❖ **Part select:** **A[11:8]** is a 4-bit select of A with range **[11:8]**
- ❖ The part select range must be consistent with vector declaration

Reduction Operators

```
module Reduce
```

```
( input [3:0] A, B, output X, Y, Z );
```

```
// A, B are input vectors, X, Y, Z are 1-bit outputs
```

```
// X = A[3] | A[2] | A[1] | A[0];
```

```
assign X = |A;
```

```
// Y = B[3] & B[2] & B[1] & B[0];
```

```
assign Y = &B;
```

```
// Z = X & (B[3] ^ B[2] ^ B[1] ^ B[0]);
```

```
assign Z = X & (^B);
```

```
endmodule
```

Concatenation Operator { }

```
module Concatenate
```

```
( input [7:0] A, B, output [7:0] X, Y, Z );
```

```
// A, B are input vectors, X, Y, Z are output vectors
```

```
// X = A is right-shifted 3 bits using { } operator
```

```
assign X = {3'b000, A[7:3]};
```

```
// Y = A is right-rotated 3 bits using { } operator
```

```
assign Y = {A[2:0], A[7:3]};
```

```
// Z = selecting and concatenating bits of A and B
```

```
assign Z = {A[5:4], B[6:3], A[1:0]};
```

```
endmodule
```

Integer Literals (Constant Values)

❖ Syntax: [**size**][**'base**]**value**

size (optional) is the number of bits in the value

'base can be: **'b**(binary), **'o**(octal), **'d**(decimal), or **'h**(hex)

value can be in binary, octal, decimal, or hexadecimal

❖ If the **'base** is not specified then decimal **value**

❖ Examples:

8'b1011_1101 (8-bit binary), **'hA3F0** (16-bit hexadecimal)

16'o56377 (16-bit octal), **32'd999** (32-bit decimal)

❖ The underscore **_** can be used to enhance readability of **value**

❖ When **size** is fewer bits than **value**, upper bits are truncated


Ripple Carry Adder

- ❖ Using **identical copies** of a full adder to build a large adder

- ❖ The **cell** (iterative block) is a **full adder**

Adds 3 bits: a_i , b_i , c_i Computes: Sum s_i and Carry-out c_{i+1}

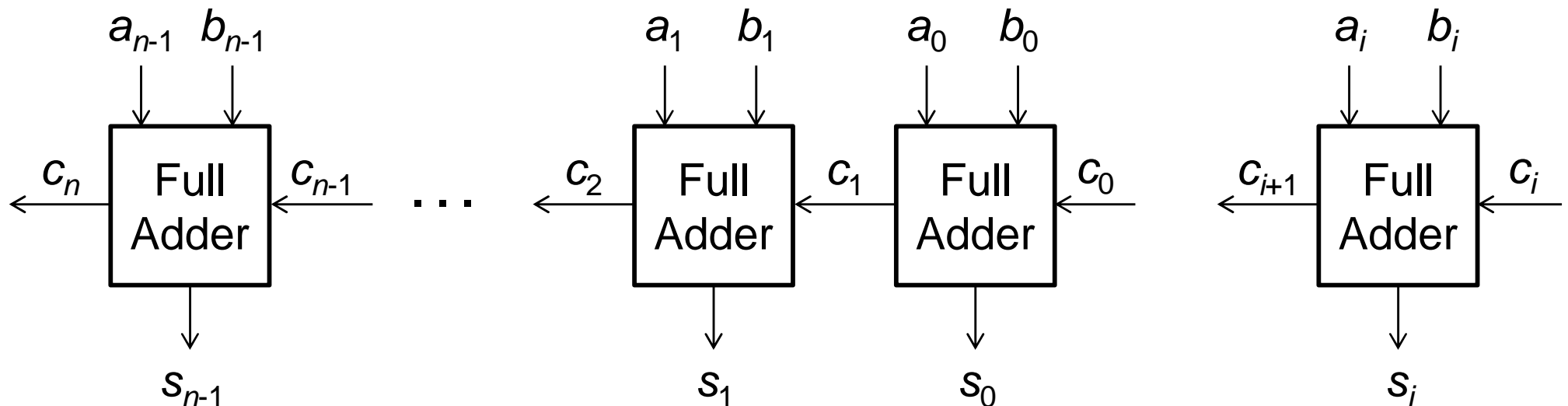- ❖ Carry-out of cell i becomes carry-in to cell $(i+1)$



16-Bit Adder with Array Instantiation

```
// Input ports: 16-bit a and b, 1-bit cin (carry input)
// Output ports: 16-bit sum, 1-bit cout (carry output)

module Adder_16 (input [15:0] a, b, input cin,
                output [15:0] sum, output cout);

    wire [16:0] c; // carry bits
    assign c[0] = cin; // carry input
    assign cout = c[16]; // carry output

    // Instantiate an array of 16 Full Adders
    // Each instance [i] is connected to bit select [i]

    Full_Adder FA [15:0] (a[15:0], b[15:0], c[15:0],
                        c[16:1], sum[15:0]);

endmodule
```

Array Instantiation of identical modules by a single statement

16-Bit Adder with Continuous Assignment

```
// Input ports: 16-bit a and b, 1-bit cin (carry input)
// Output ports: 16-bit sum, 1-bit cout (carry output)
```

```
module Adder_16 (input [15:0] a, b, input cin,
                 output [15:0] sum, output cout);
```

```
    wire [16:0] c;           // carry bits
    assign c[0] = cin;      // carry input
    assign cout = c[16];    // carry output
```

```
// assignment of 16-bit vectors
```

```
assign sum[15:0] = (a[15:0] ^ b[15:0]) ^ c[15:0];
assign c[16:1]   = (a[15:0] & b[15:0]) |
                  (a[15:0] ^ b[15:0]) & c[15:0];
```

```
endmodule
```

16-bit Adder with the + Operator

```
module Adder16
  ( input [15:0] A, B, input cin,
    output [15:0] Sum, output cout );

  // A and B are 16-bit input vectors
  // Sum is a 16-bit output vector
  // {cout, Sum} is a concatenated 17-bit vector
  // A + B + cin is 16-bit addition + input carry
  // The + operator is translated into an adder

  assign {cout, Sum} = A + B + cin;

endmodule
```


Modeling a Parametric n-bit Adder

```
// Parametric n-bit adder, default value for n = 16
module Adder #(parameter n = 16)
    ( input [n-1:0] A, B, input cin,
      output [n-1:0] Sum, output cout );

    // A and B are n-bit input vectors
    // Sum is an n-bit output vector

    // The + operator is translated into an n-bit adder
    // Only one assign statement is used

    assign {cout, Sum} = A + B + cin;

endmodule
```

Instantiating Adders of Various Sizes

```
// Instantiate a 16-bit adder (parameter n = 16)
```

```
// A1, B1, and Sum1 must be 16-bit vectors
```

```
Adder #(16) adder16 (A1, B1, Cin1, Sum1, Cout1);
```

```
// Instantiate a 32-bit adder (parameter n = 32)
```

```
// A2, B2, and Sum2 must be 32-bit vectors
```

```
Adder #(32) adder32 (A2, B2, Cin2, Sum2, Cout2);
```

```
// If parameter is not specified, it defaults to 16
```

```
Adder adder16 (A1, B1, Cin1, Sum1, Cout1);
```

Modeling a Magnitude Comparator

```
// n-bit magnitude comparator, No default value for n
```

```
module Comparator #(parameter n)
```

```
(input [n-1:0] A, B,
```

```
output GT, EQ, LT);
```

```
// A and B are n-bit input vectors (unsigned)
```


```
// GT, EQ, and LT are 1-bit outputs
```

```
assign GT = (A > B);
```

```
assign EQ = (A == B);
```

```
assign LT = (A < B);
```

```
endmodule
```

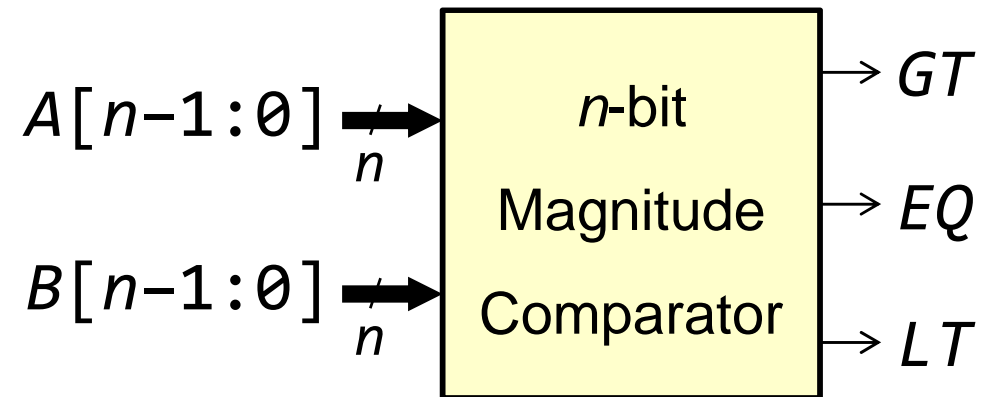

Instantiating Comparators of Various Sizes

```
// Instantiate a 16-bit comparator (n = 16)  
// A1 and B1 must be declared as 16-bit vectors  
Comparator #(16) comp16 (A1, B1, GT1, EQ1, LT1);
```

```
// Instantiate a 32-bit comparator (n = 32)  
// A2 and B2 must be declared as 32-bit vectors  
Comparator #(32) comp32 (A2, B2, GT2, EQ2, LT2);
```

```
// WRONG Instantiation: Must specify parameter n  
Comparator comp32 (A2, B2, GT2, EQ2, LT2);
```

Conditional Operator

❖ Syntax:

Boolean_expr ? True_expression : False_expression

If *Boolean_expr* is true then select *True_expression*

Else select *False_Expression*

❖ Examples:

```
assign max = (a>b)? a : b; // maximum of a and b
```

```
assign min = (a>b)? b : a; // minimum of a and b
```

❖ Conditional operators can be nested

Modeling a 2x1 Multiplexer

```
// Parametric 2x1 Mux, default value for n = 1
```

```
module Mux2 #(parameter n = 1)
```

```
( input [n-1:0] A, B, input sel,  
  output [n-1:0] Z);
```

```
// A and B are n-bit input vectors
```


```
// Z is the n-bit output vector
```

```
// if (sel==0) Z = A; else Z = B;
```

```
// Conditional operator used for selection
```

```
assign Z = (sel == 0)? A : B;
```

```
endmodule
```

 

Modeling a 4x1 Multiplexer

```
// Parametric 4x1 Mux, default value for n = 1
```

```
module Mux4 #(parameter n = 1)
```

```
( input [n-1:0] A, B, C, D,
```

```
input [1:0] sel,
```

```
output [n-1:0] Z );
```

```
// sel is a 2-bit vector
```


```
// Nested conditional operators
```

```
assign Z = (sel[1] == 0) ?
```

```
((sel[0] == 0) ? A : B) :
```

```
((sel[0] == 1) ? C : D);
```

```
endmodule
```

 

Behavioral Modeling

- ❖ Uses procedural blocks and procedural statements
- ❖ There are two types of **procedural** blocks in Verilog
 1. The **initial** block
 - ✧ Executes the enclosed statement(s) one time only
 2. The **always** block
 - ✧ Executes the enclosed statement(s) repeatedly until simulation terminates
- ❖ The body of the **initial** and **always** blocks is **procedural**
 - ✧ Can enclose one or more **procedural statements**
 - ✧ Procedural statements are surrounded by **begin ... end**
- ❖ Multiple procedural blocks can appear in any order inside a module and run in parallel inside the simulator

Example of Initial and Always Blocks

```
module behave;
  reg clk; // 1-bit variable
  reg [15:0] A; // 16-bit variable
  initial begin // executed once
    clk = 0; // initialize clk
    A = 16'h1234; // initialize A
    #200 $finish
  end
  always begin // executed always
    #10 clk = ~clk; // invert clk every 10 ns
  end
  always begin // executed always
    #20 A = A + 1; // increment A every 20 ns
  end
endmodule
```

Always Block with Sensitivity List

❖ Syntax:

```
always @(sensitivity List) begin  
    procedural statements  
end
```

❖ An **a**lways block can have a *sensitivity list*

❖ Sensitivity list is a list of signals: @(signal1, signal2, ...)

The sensitivity list triggers the execution of the **a**lways block

When there is a **change of value in any listed signal**

Otherwise, the **a**lways block does nothing until another change occurs on a signal in the sensitivity list

Sensitivity List for Combinational Logic

- ❖ For combinational logic, the sensitivity list **must include**:

ALL the signals that are read inside the **always** block

Example: **A**, **B**, and **sel** must be in the sensitivity list below:

```
always @(A, B, sel) begin  
    if (sel == 0) Z = A;  
    else Z = B;  
end
```

A, B, and sel are
read inside the
always block

- ❖ Combinational logic can also use: **@(*)** or **@***

@(*) is automatically sensitive to all the signals that are read inside the **always** block

If Statement

- ❖ The **if** statement is procedural
- ❖ Can only be used inside a procedural block
- ❖ Syntax:

if (*expression*) *statement*

[**else** *statement*]

- ❖ The **else** part is optional

A *statement* can be simple or compound

A *compound statement* is surrounded by **begin** ... **end**

- ❖ **if** statements can be nested
- ❖ Can be nested under **if** or under **else** part

Modeling a 2x1 Multiplexer

// Behavioral Modeling of a Parametric 2x1 Mux

```
module Mux2 #(parameter n = 1)
  ( input [n-1:0] A, B, input sel,
    output reg [n-1:0] Z);
```

```
// Output Z must be of type reg
```

```
// Sensitivity list = @(A, B, sel)
```


```
always @(A, B, sel) begin
```

```
  if (sel == 0) Z = A;
```

```
  else Z = B;
```

```
end
```

```
endmodule
```

 

Modeling a 3x8 Decoder

```
module Decoder3x8 (input [2:0] A, output reg [7:0] D);  
    // Sensitivity list = @(A)  
    always @(A) begin  
        if (A == 0)      D = 8'b00000001;  
        else if (A == 1) D = 8'b00000010;  
        else if (A == 2) D = 8'b00000100;  
        else if (A == 3) D = 8'b00001000;  
        else if (A == 4) D = 8'b00010000;  
        else if (A == 5) D = 8'b00100000;  
        else if (A == 6) D = 8'b01000000;  
        else              D = 8'b10000000;  
    end  
endmodule
```


Modeling a 4x2 Priority Encoder

```
module Priority_Encoder4x2
  (input [3:0] D, output reg V, output reg [1:0] A);
  // sensitivity list = @(D)
  always @(D) begin
    if (D[3])      {V, A} = 3'b111;
    else if (D[2]) {V, A} = 3'b110;
    else if (D[1]) {V, A} = 3'b101;
    else if (D[0]) {V, A} = 3'b100;
    else          {V, A} = 3'b000;
  end
endmodule
```

Modeling a Magnitude Comparator

```
// Behavioral Modeling of a Magnitude Comparator
```
 
```
module Comparator #(parameter n = 1)
  (input [n-1:0] A, B, output reg GT, EQ, LT);
  // Sensitivity list = @(A, B)
  always @(A, B) begin
    if (A > B)
      {GT, EQ, LT} = 'b100;
    else if (A == B)
      {GT, EQ, LT} = 'b010;
    else
      {GT, EQ, LT} = 'b001;
  end
endmodule
```



Case Statement

- ❖ The **case** statement is procedural (used inside **always** block)
- ❖ Syntax:

```
case (expression)  
    case_item1: statement  
    case_item2: statement  
    . . .  
    default:    statement  
endcase
```


The **default** case is optional

A *statement* can be simple or compound

A *compound statement* is surrounded by **begin** . . . **end**

Modeling a Mux with a Case Statement
 
```
module Mux4 #(parameter n = 1)
  ( input [n-1:0] A, B, C, D, input [1:0] sel,
    output reg [n-1:0] Z );
  // @(*) is @(A, B, C, D, sel)
  always @(*) begin
    case (sel)
      2'b00: Z = A;
      2'b01: Z = B;
      2'b10: Z = C;
      default: Z = D;
    endcase
  end
endmodule
```




Modeling a Multifunction ALU

// Behavioral Modeling of an ALU

```
module ALU #(parameter n = 16)
  ( input [n-1:0] A, B, input [1:0] F,
    output reg [n-1:0] Z, output reg Cout );
  // @(*) is @(A, B, F)
  always @(*) begin
    case (F)
      2'b00: {Cout,Z} = A+B;
      2'b01: {Cout,Z} = A-B;
      2'b10: {Cout,Z} = A&B;
      default: {Cout,Z} = A|B;
    endcase
  end
endmodule
```

ALU Symbol

 

Modeling a BCD to 7-Segment Decoder

```
module BCD_to_7Seg_Decoder
  ( input  [3:0] BCD, output reg [6:0] Seg )
  always @(BCD) begin
    case (BCD)
      0: Seg = 7'b1111110;      1: Seg = 7'b0110000;
      2: Seg = 7'b1101101;      3: Seg = 7'b1111001;
      4: Seg = 7'b0110011;      5: Seg = 7'b1011011;
      6: Seg = 7'b1011111;      7: Seg = 7'b1110000;
      8: Seg = 7'b1111111;      9: Seg = 7'b1111011;
      default: Seg = 7'b0000000;
    endcase
  end
endmodule
```

