

Registers and Counters

COE 202

Digital Logic Design

Dr. Muhamed Mudawar


King Fahd University of Petroleum and Minerals

Presentation Outline

- ❖ Registers
- ❖ Shift Registers and their Applications
- ❖ Ripple Counters
- ❖ Synchronous Counters


Register

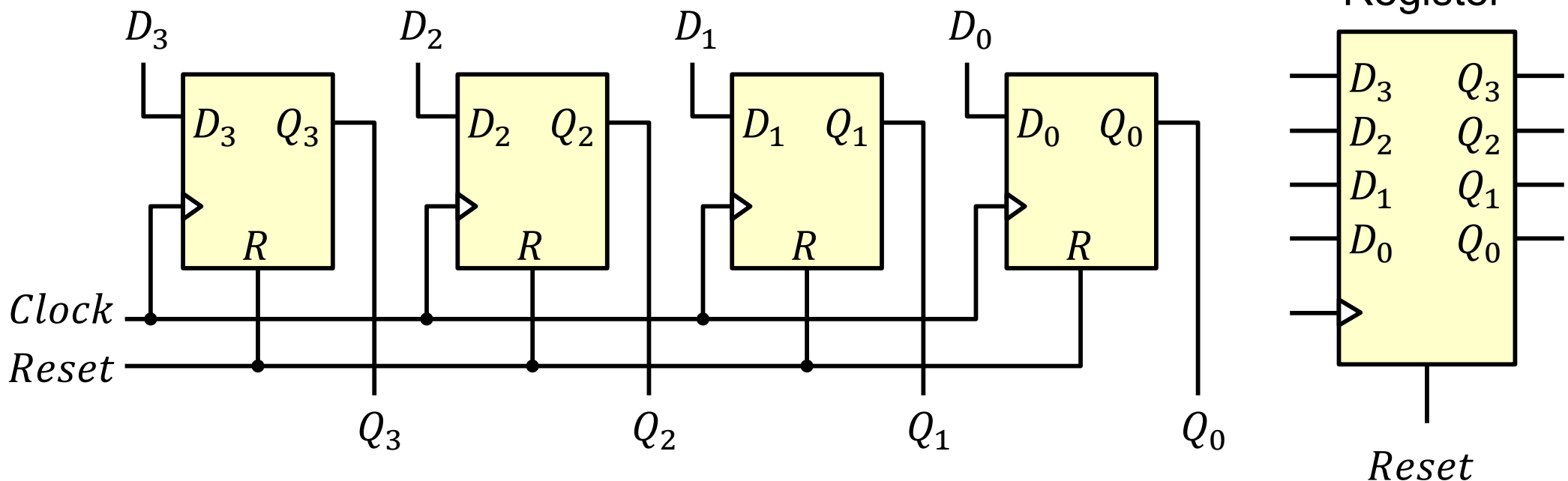- ❖ A register is a circuit capable of storing data
- ❖ An n -bit register consists of n Flip-Flops and stores n bits
- ❖ Common clock: data is loaded in parallel at the same clock edge
- ❖ Common reset: All Flip-Flops are reset in parallel



Register Load (or Enable)

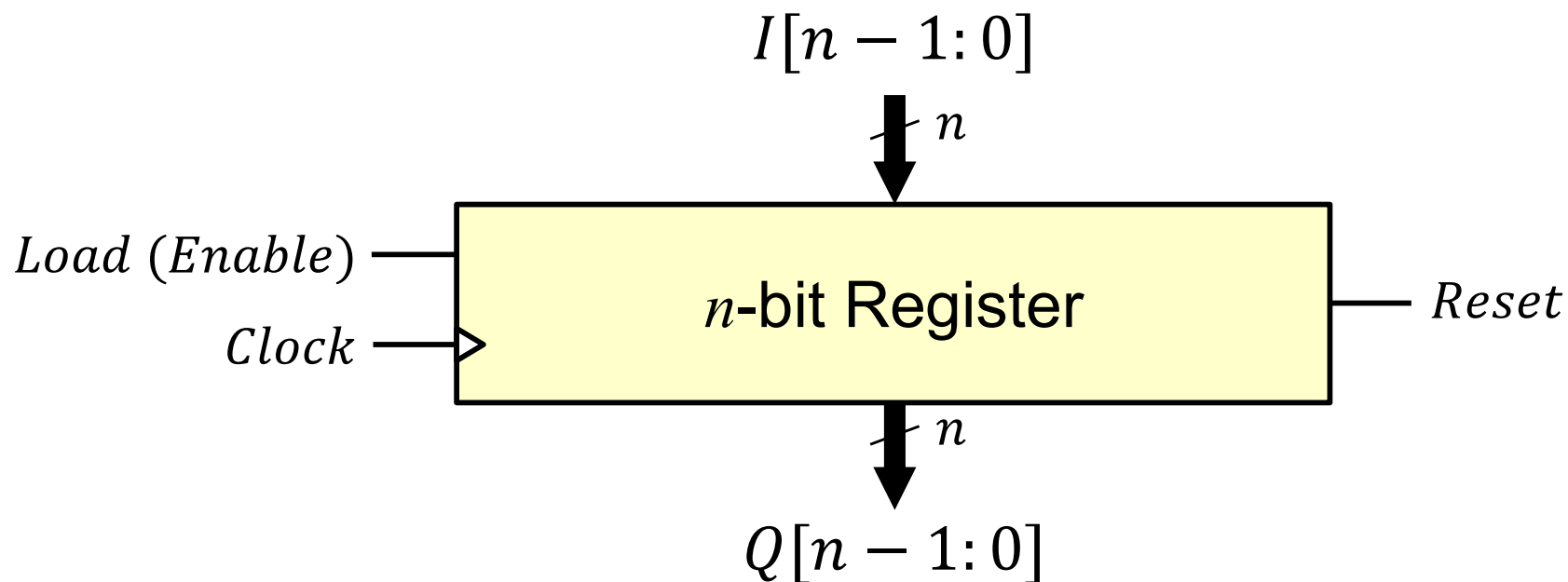- ❖ **Question:** How to control the loading of data into a register?
- ❖ **Solution:** Introduce a register Load (or Enable) signal
If the register is enabled, load the data into the register
Otherwise, do not change the value of the register
- ❖ **Question:** How to implement register Load?




Register with Parallel Load

❖ **Solution:** Add a mux at the D input of the register


❖ $D_i = Load \cdot I_i + \overline{Load} \cdot Q_i$

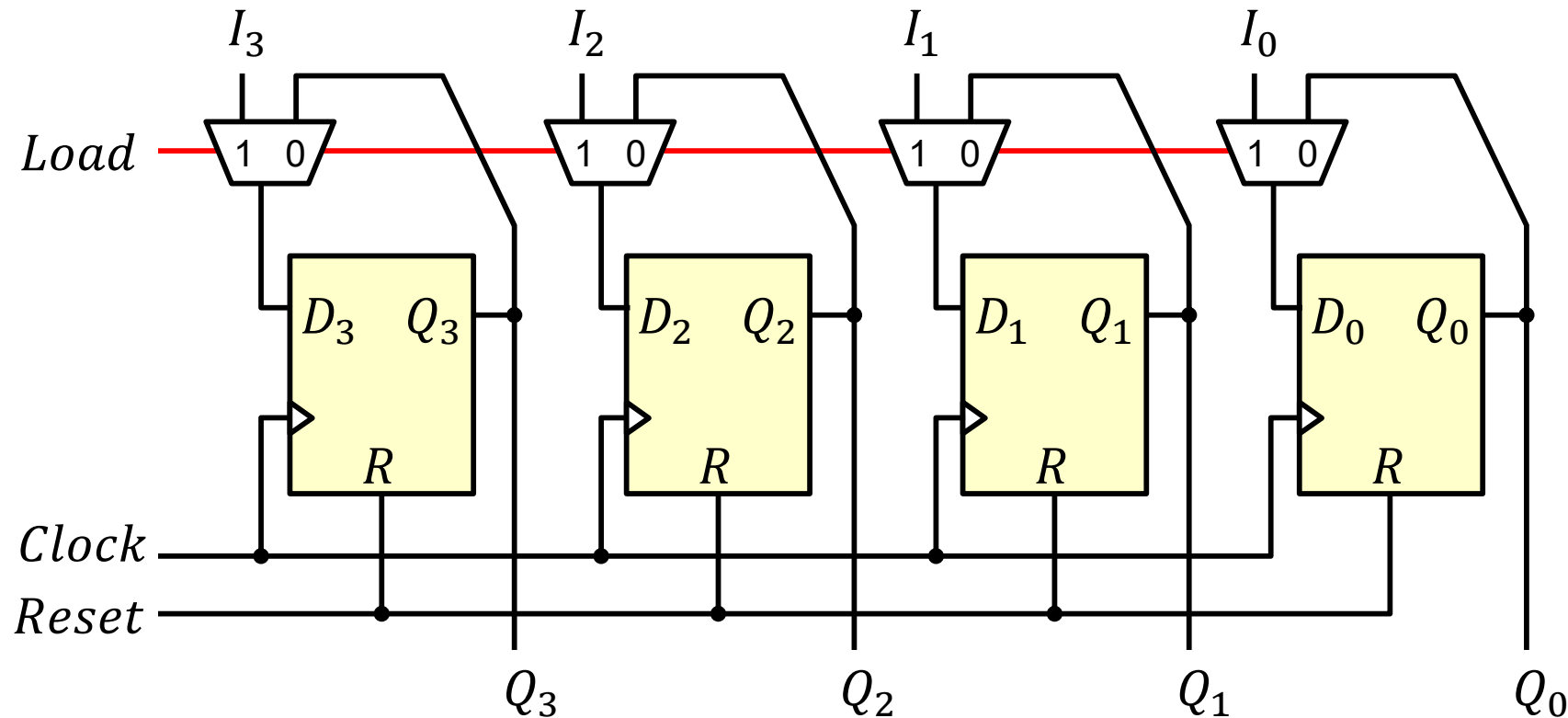❖ If $Load$ is **1** then $D_i = I_i$ If $Load$ is **0** then $D_i = Q_i$




Shift Registers

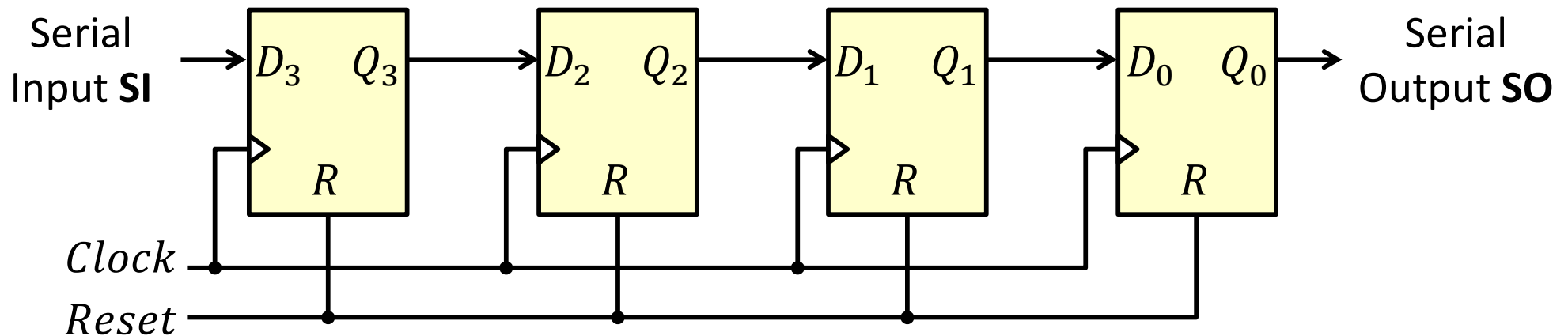- ❖ A shift register is a cascade of flip flops sharing the same clock
- ❖ Allows the data to be shifted from each flip-flop to its neighbor
- ❖ The output of a flip-flop is connected to the input of its neighbor
- ❖ Shifting can be done in either direction
- ❖ All bits are shifted simultaneously at the active edge of the clock



Right Shift Register


Timing of a Shift Register

 

Cycle	SI	Q3	Q2	Q1	Q0 = SO
T0	1	1	0	1	0
T1	0	1	1	0	1
T2	1	0	1	1	0
T3	1	1	0	1	1
T4	0	1	1	0	1
T5	1	0	1	1	0
T6	0	1	0	1	1

Shift Register with Parallel Output

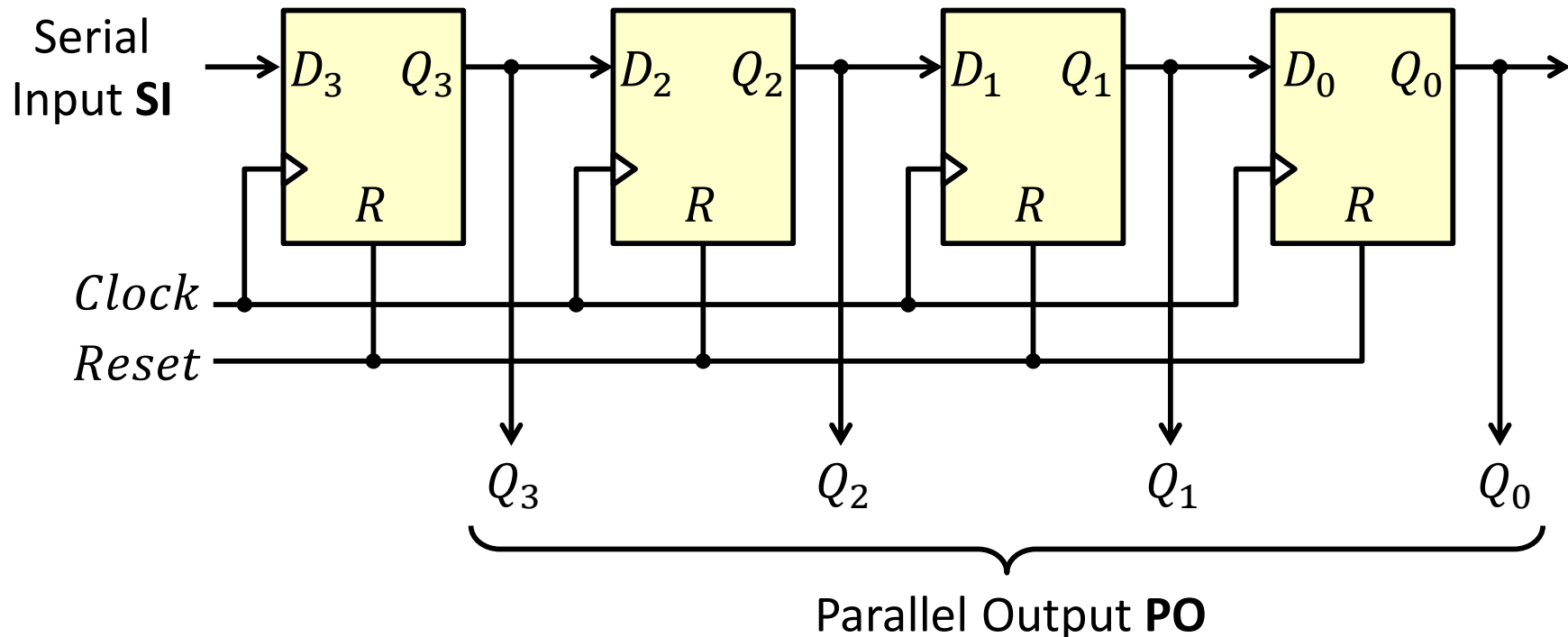
- ❖ The output of a shift register can be serial or parallel
- ❖ A Serial-In Parallel-Out (SIPO) shift register is shown below
- ❖ All flip-flop outputs can be read in parallel



Bit Serial Adder

- ❖ Adding two n -bit numbers A and B serially over n clock cycles
- ❖ A bit-serial adder can be implemented using
 1. A Full Adder
 2. A Flip-Flop to store the carry-out
 3. A Shift Register to store the n -bit sum

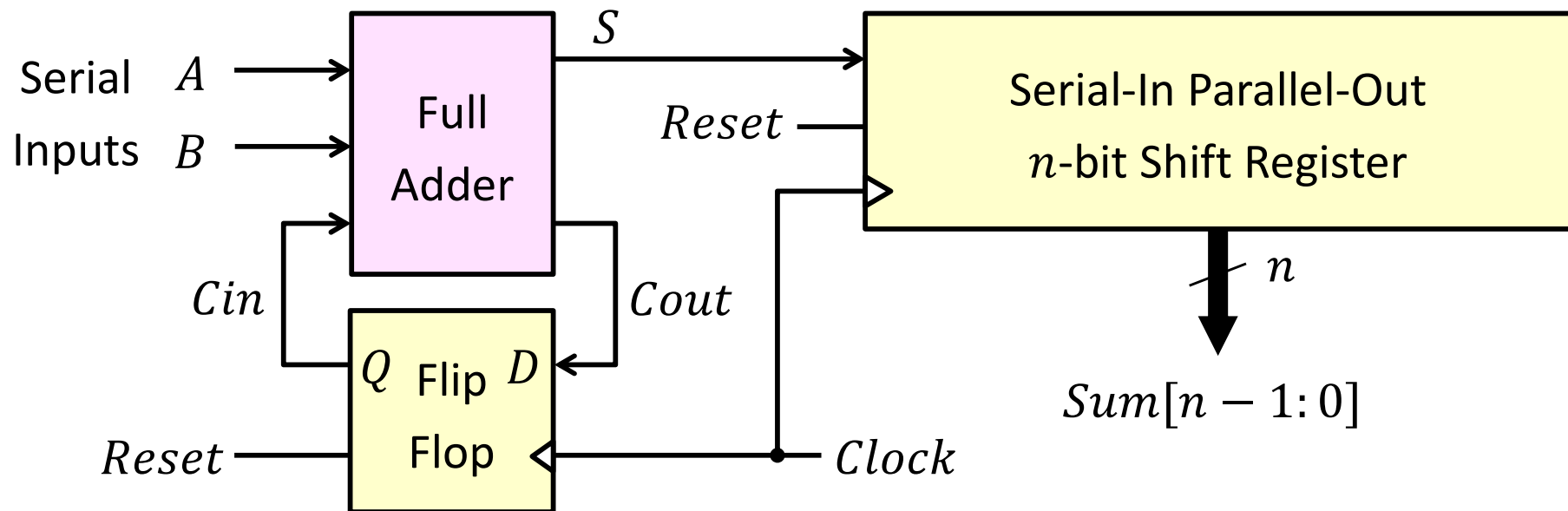Serial Addition
Starts at the
Least-significant bit




Sequence Detector with a Shift Register

- ❖ A sequence detector can be implemented using:

Left Shift Register (SIPO) + AND Gates

- ❖ Example: Detecting the sequences **1010** and **1100**

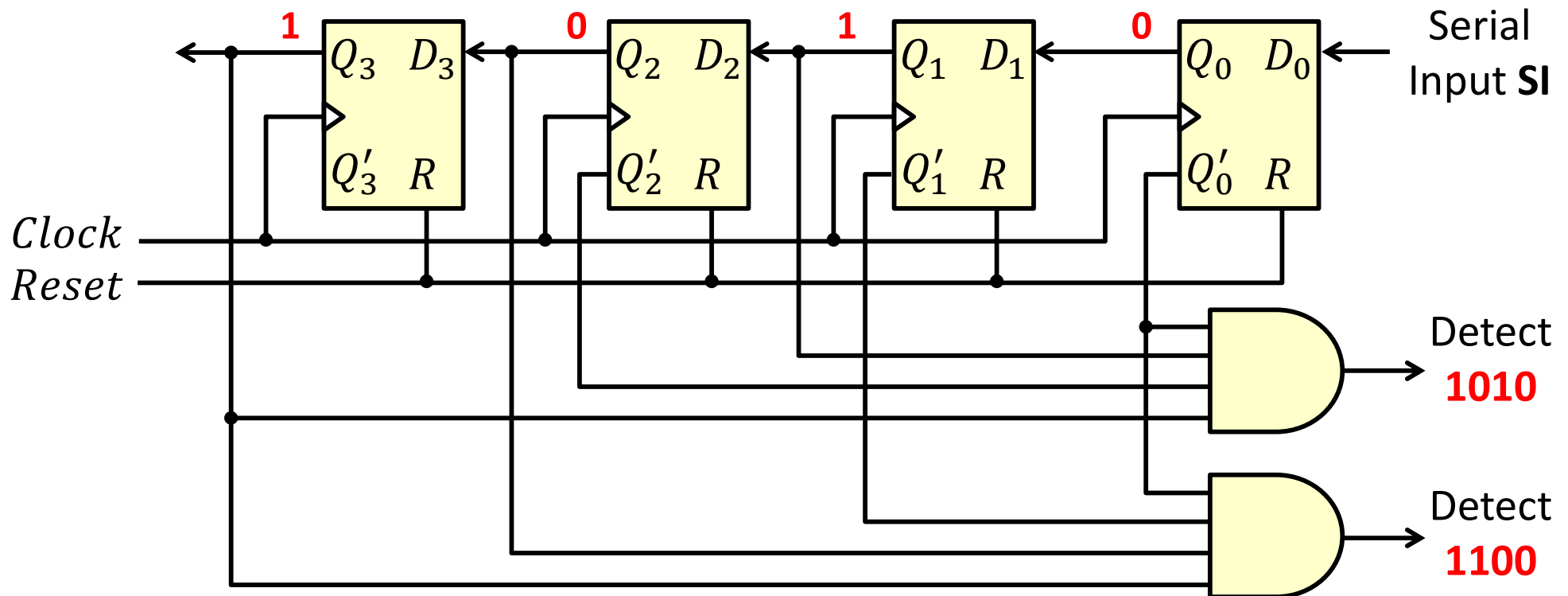Bits are shifted left starting at the most-significant bit




Parallel-In Serial-Out Shift Register

❖ A Parallel-In Serial-Out (PISO) Shift Register has:

- ❖ n parallel data input lines
- ❖ Serial Input
- ❖ Serial Output
- ❖ Control input s
- ❖ Clock input
- ❖ Reset input

❖ Two control functions:

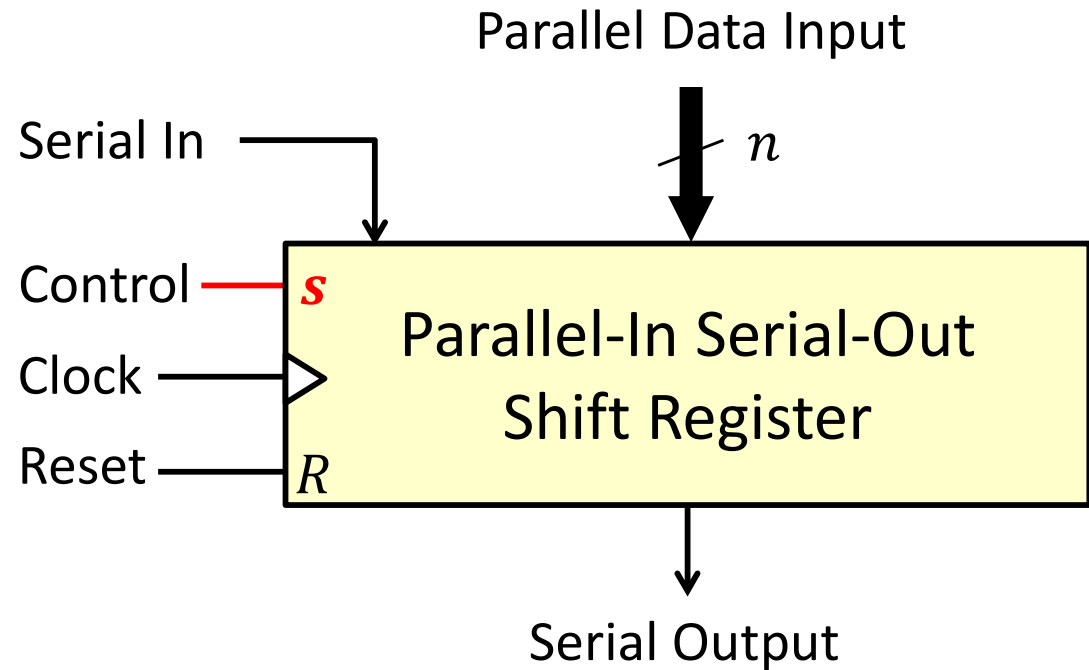- ❖ $s = 0 \rightarrow$ Shift Data
- ❖ $s = 1 \rightarrow$ Parallel Load n input bits




Parallel In Serial Out Shift Register

❖ Two control functions:

$s = 0$ → Shift

$s = 1$ → Load data

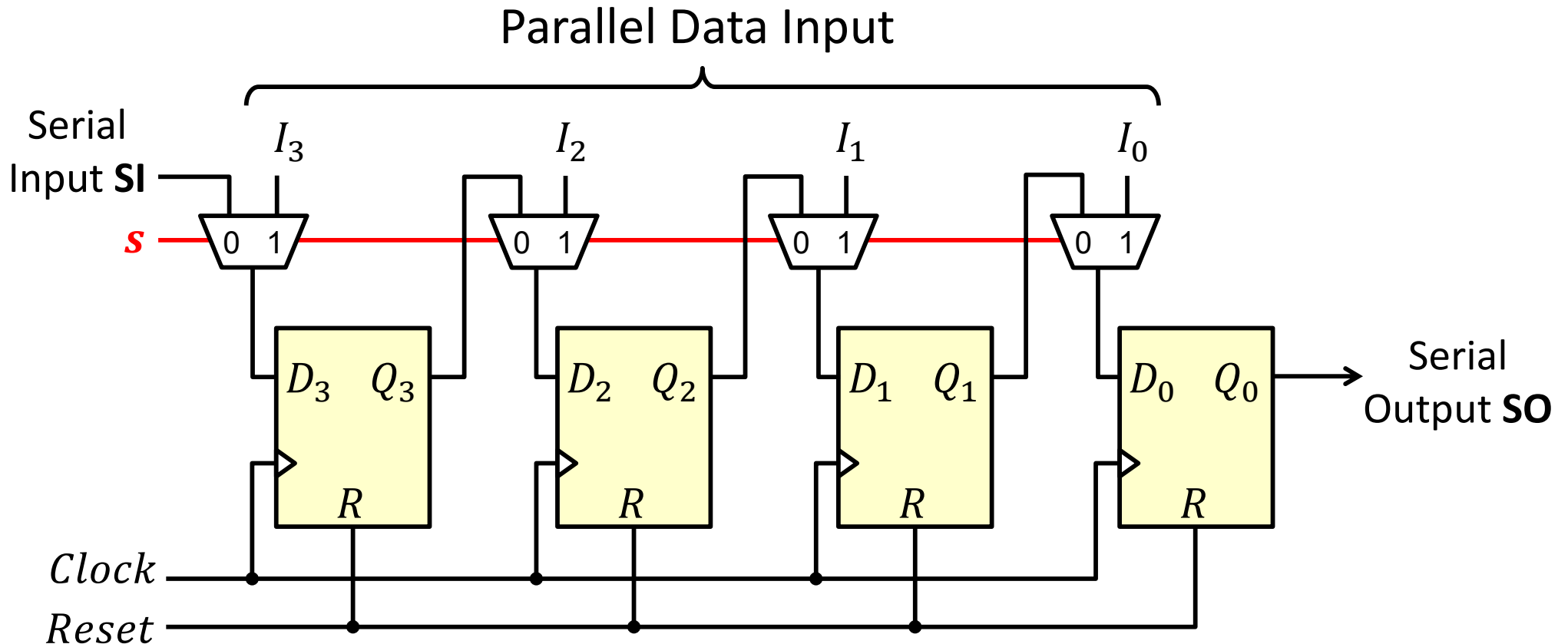


Universal Shift Register

❖ A Universal Shift Register has the following specification:


- ❖ n parallel data input and n output lines
- ❖ Right-shift and Left-shift Serial Inputs
- ❖ Two control input lines **s**
- ❖ Clock input
- ❖ Reset input

❖ Four control functions:

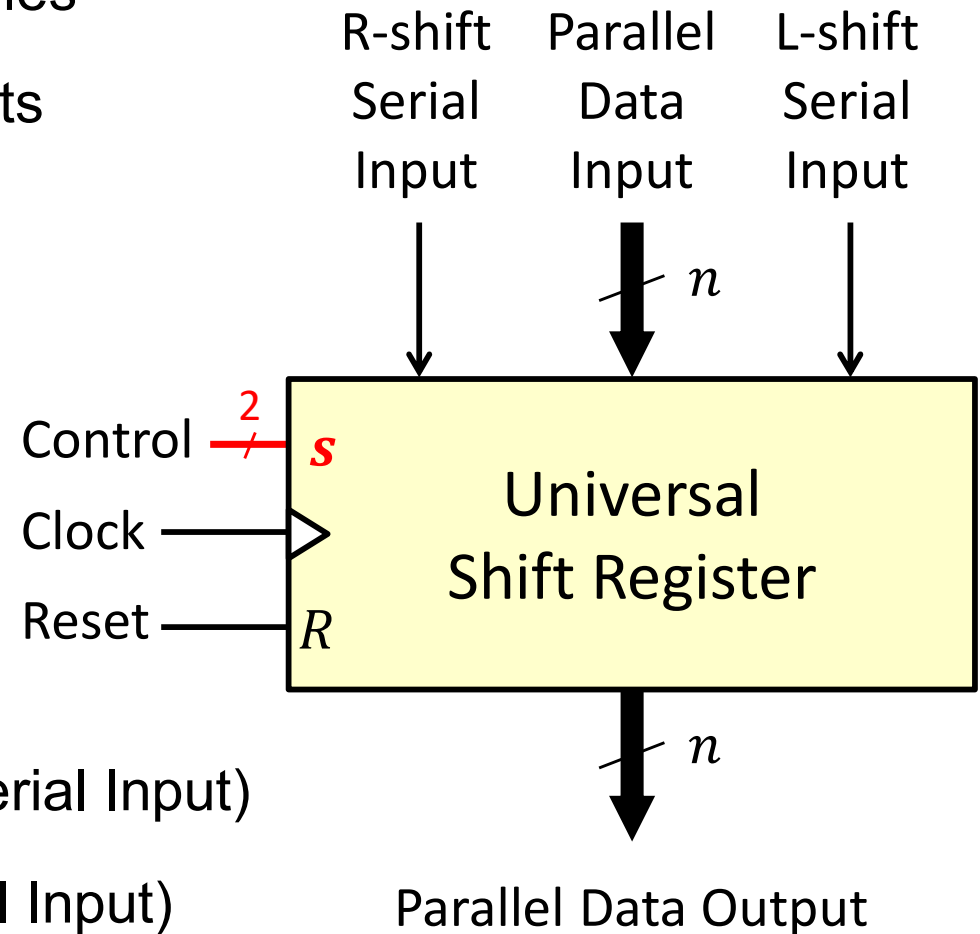- ❖ **s = 00** → No change in value
- ❖ **s = 01** → Shift Right (Right-Shift Serial Input)
- ❖ **s = 10** → Shift Left (Left-Shift Serial Input)
- ❖ **s = 11** → Parallel Load n input bits




Universal Shift Register Design

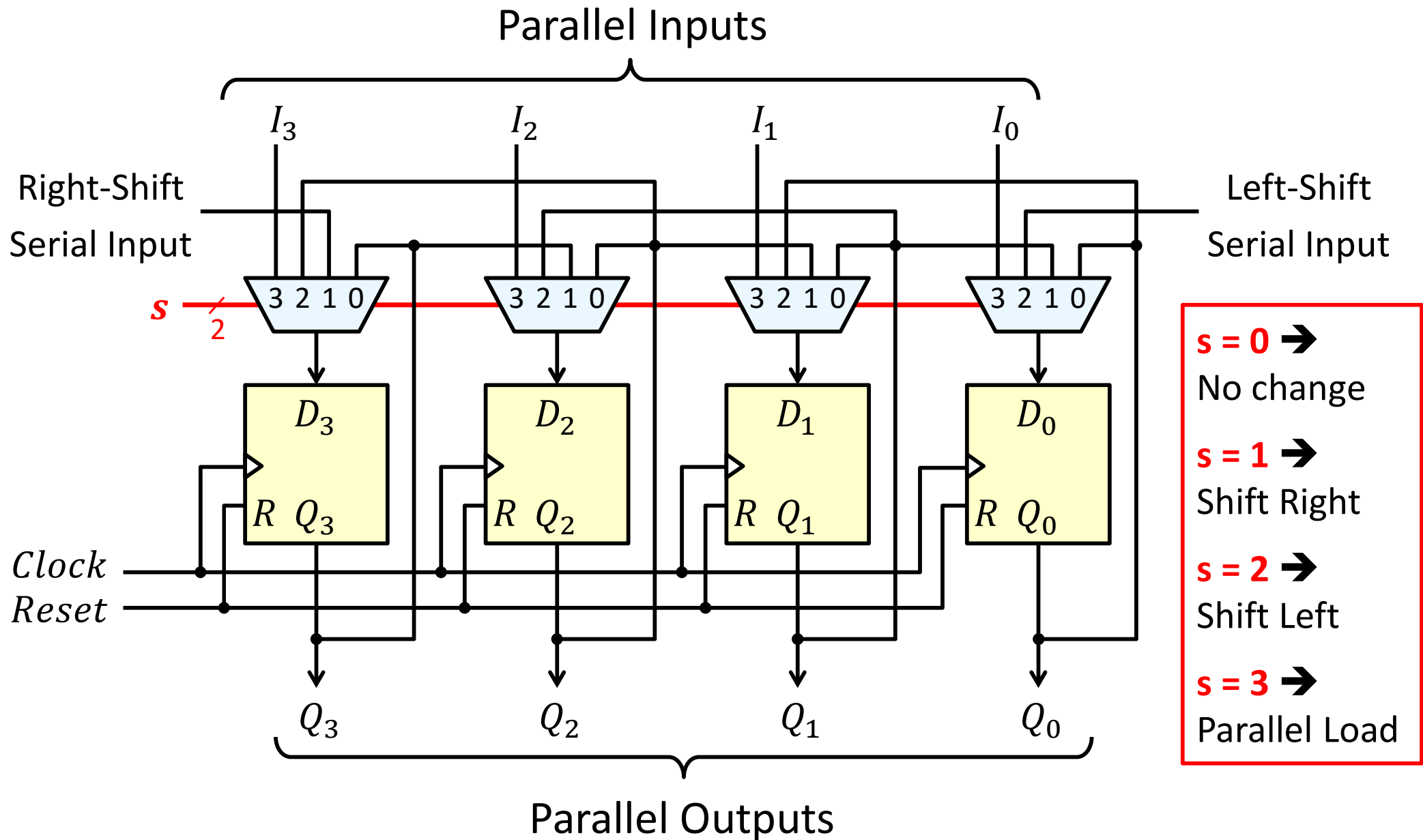

Counter

- ❖ Sequential circuit that goes through a specific sequence of states
- ❖ Output of the counter is the **count value**
- ❖ Modulo- N counter: goes through $0, 1, 2, \dots, (N - 1)$
- ❖ Modulo-8 binary counter: goes through $0, 1, 2, \dots, 7$
- ❖ Modulo-10 (BCD) counter: goes through $0, 1, 2, \dots, 9$
- ❖ Counting can be up or down
- ❖ Some Applications:

 - ✧ Timers
- ✧ Event Counting
- ✧ Frequency Division



Implementing Counters

Two Basic Approaches:

1. Ripple Counters

- ✧ The system clock is connected to the clock input of the first flip-flop (LSB)
- ✧ Each flip-flop output connects to the clock input of the next flip-flop
- ✧ Advantage: simple circuit and low power consumption
- ✧ Disadvantage: The counter is not truly synchronous
- ✧ No common clock to all flip-flops
- ✧ Ripple propagation delay as the clock signal propagates to the MSB

2. Synchronous Counters


- ✧ The system clock is connected to the clock input of ALL flip-flops
- ✧ Combinational logic is used to implement the desired state sequence

Ripple Counter

- ❖ Q_0 toggles at the positive edge of every cycle
- ❖ Q_1 toggles when Q_0 goes from 1 down to 0
- ❖ Q_2 toggles when Q_1 goes from 1 down to 0
- ❖ Q_3 toggles when Q_2 goes from 1 down to 0

Q3	Q2	Q1	Q0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

Counts Up
from 0 to 15
then back to 0

 

Ripple Counter (cont'd)


Up Count				Down Count			
Q_3	Q_2	Q_1	Q_0	Q'_3	Q'_2	Q'_1	Q'_0
0	0	0	0	1	1	1	1
0	0	0	1	1	1	1	0
0	0	1	0	1	1	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	0	1	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	0	1
1	0	1	1	0	1	0	0
1	1	0	0	0	0	1	1
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	0	0

$Q[3:0]$ is the Up Count


$Q'[3:0]$ is the Down Count

How to Count Down?

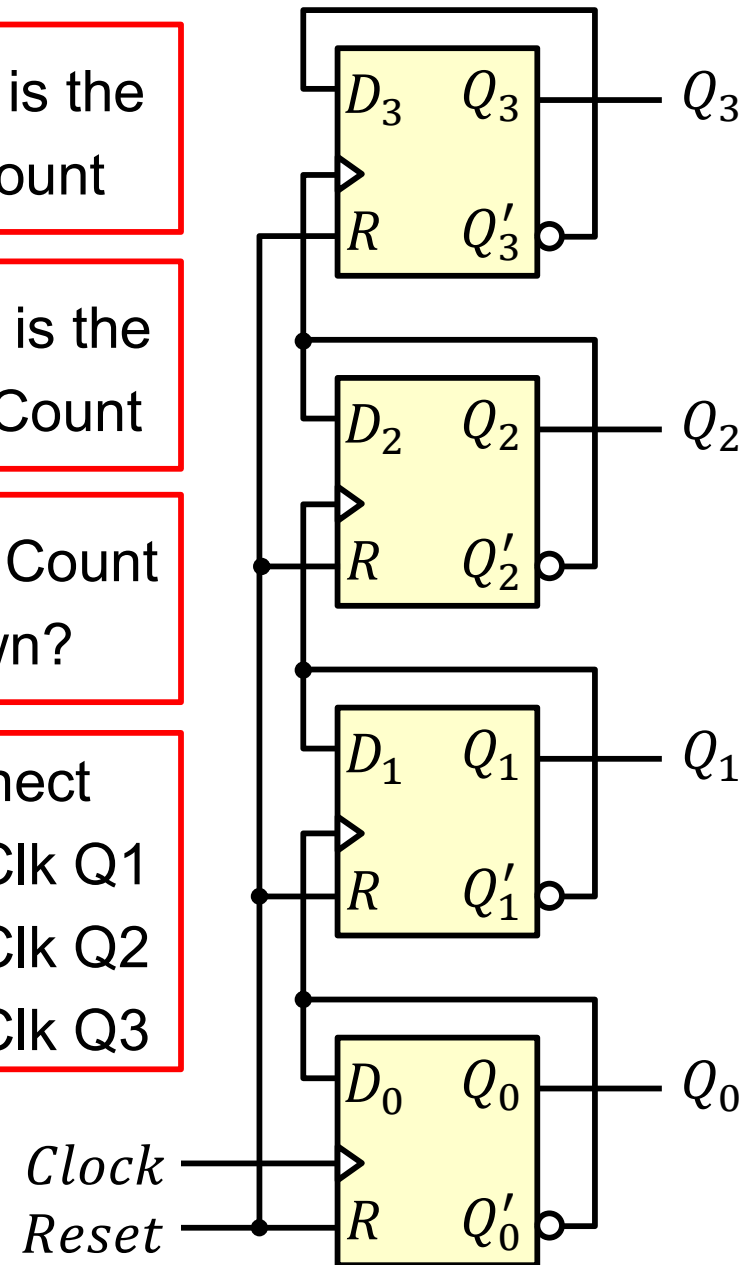Connect
 Q_0 to Clk Q_1
 Q_1 to Clk Q_2
 Q_2 to Clk Q_3



Timing of a Ripple Counter

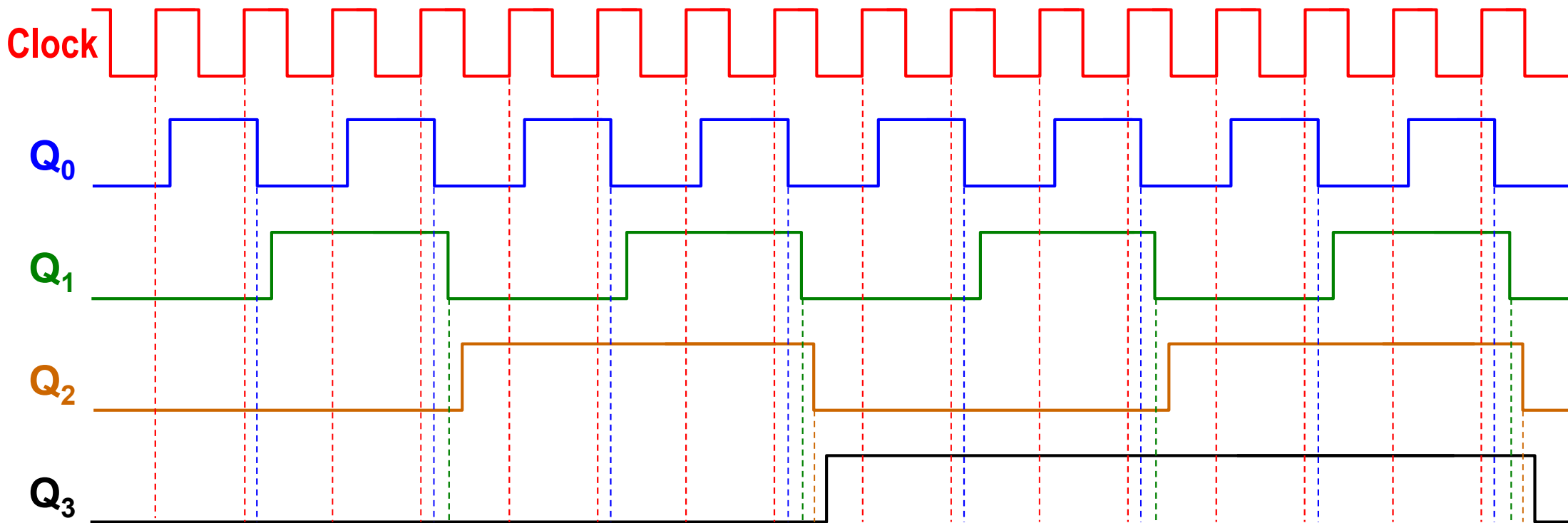

❖ Drawback of ripple counter:


Flip-flops are NOT driven by the same clock (Not Synchronous)

Q delay increases as we go from Q₀ to Q₃

Given $\Delta =$ flip-flop delay \rightarrow Delay of Q₀, Q₁, Q₂, Q₃ = Δ , 2Δ , 3Δ , 4Δ


Synchronous Counter

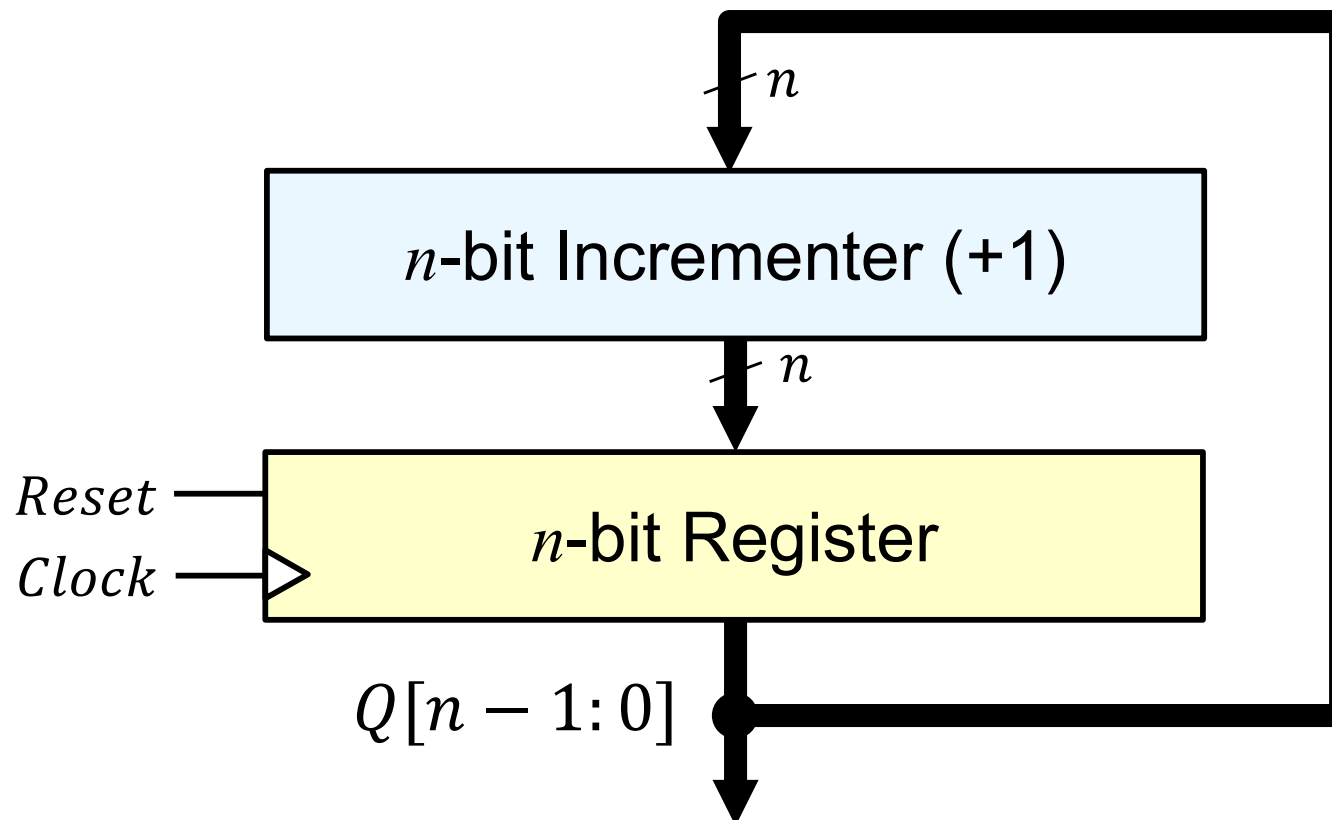- ❖ Avoid clock rippling
- ❖ n -bit Register with a **common clock** for all flip-flops
- ❖ n -bit Incrementer to generate next state (Up-Counter)



4-Bit Synchronous Counter with Enable

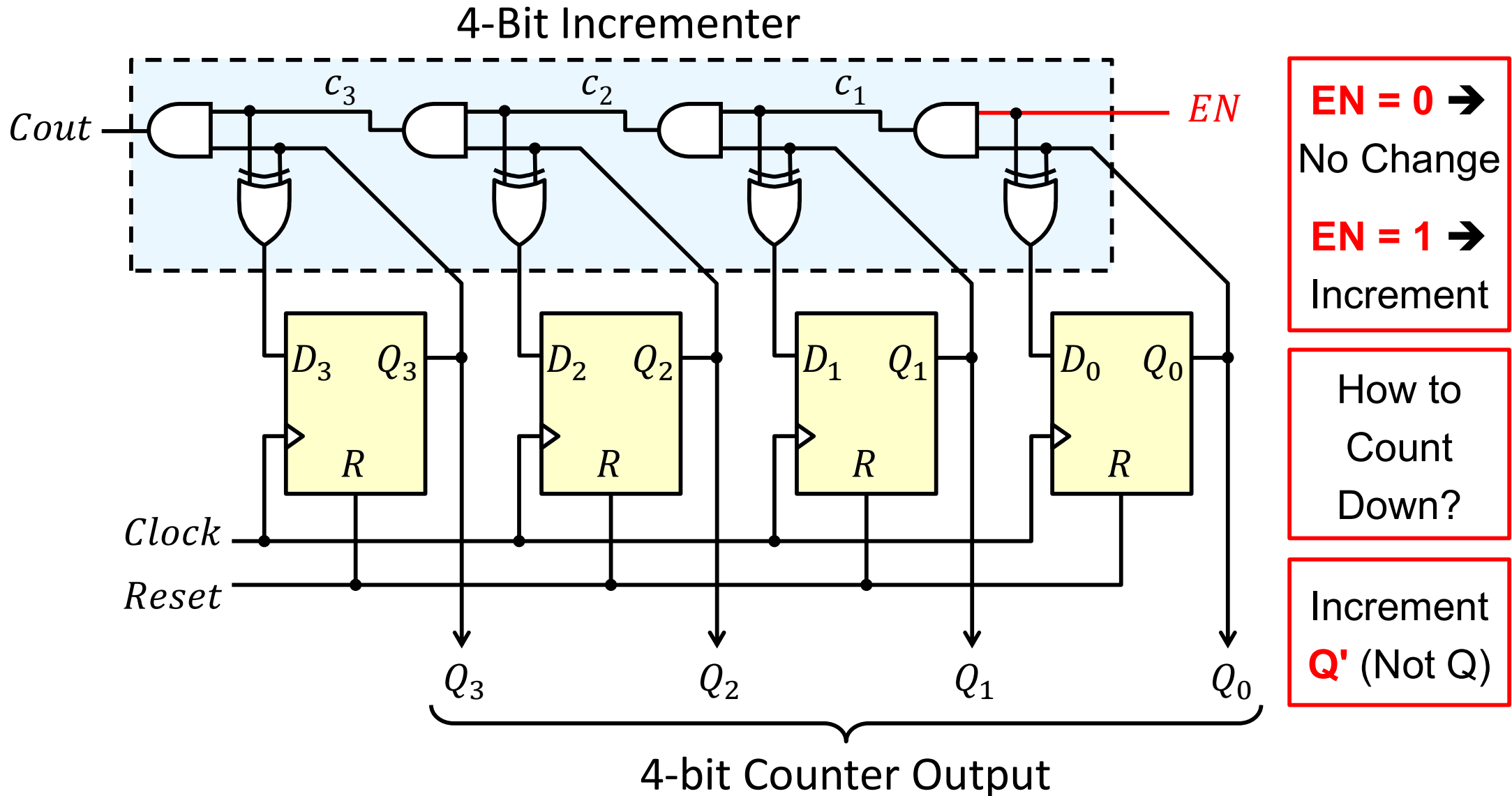- ❖ An incrementer is a reduced (contracted) form of an adder



Synchronous Counter (Counting Up)


Count Up			
Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Count Up

- ❖ When $Q_0 = 1$
Toggle (Complement) Q_1
- ❖ When $Q_0 = Q_1 = 1$
Toggle (Complement) Q_2
- ❖ When $Q_0 = Q_1 = Q_2 = 1$
Toggle (Complement) Q_3

4-Bit Synchronous Counter with T Flip-Flops

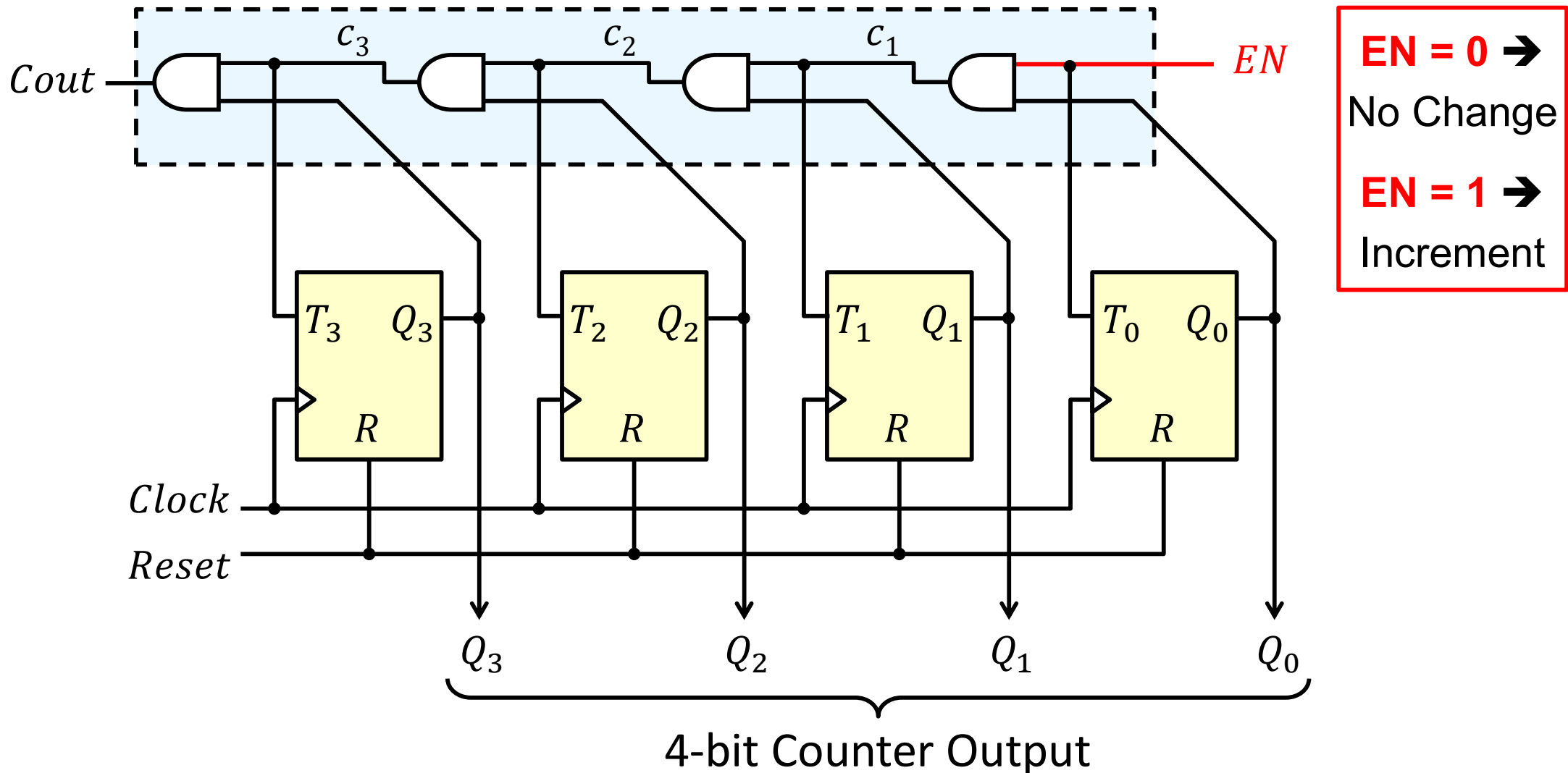- ❖ Toggle Q_1 when $c_1 = 1$, Toggle Q_2 when $c_2 = 1$, etc.




Synchronous Up-Down Counter (T Flip-Flops)


Count Down			
Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Count Down

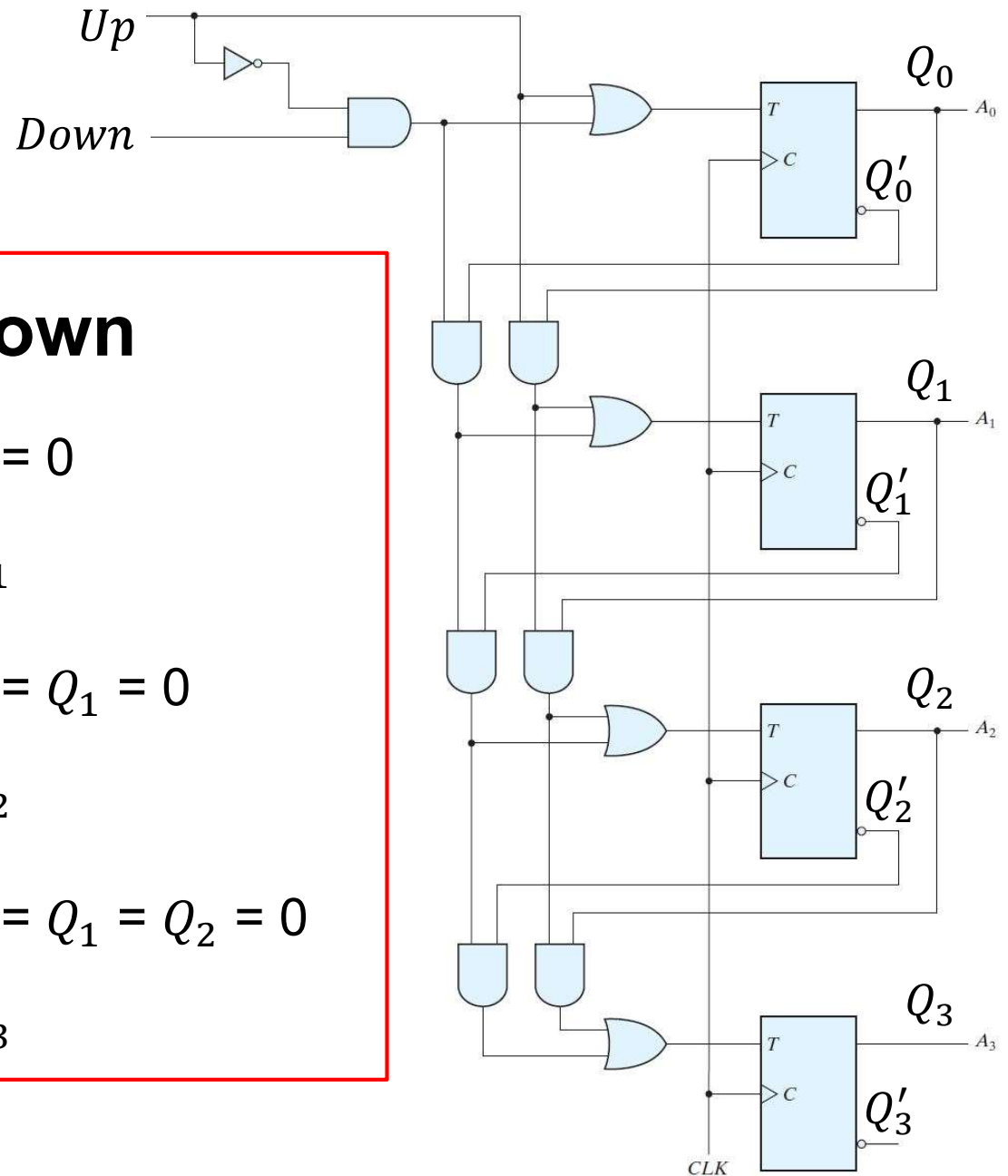- ❖ When $Q_0 = 0$
Toggle Q_1
- ❖ When $Q_0 = Q_1 = 0$
Toggle Q_2
- ❖ When $Q_0 = Q_1 = Q_2 = 0$
Toggle Q_3



Timing of a Synchronous Counter

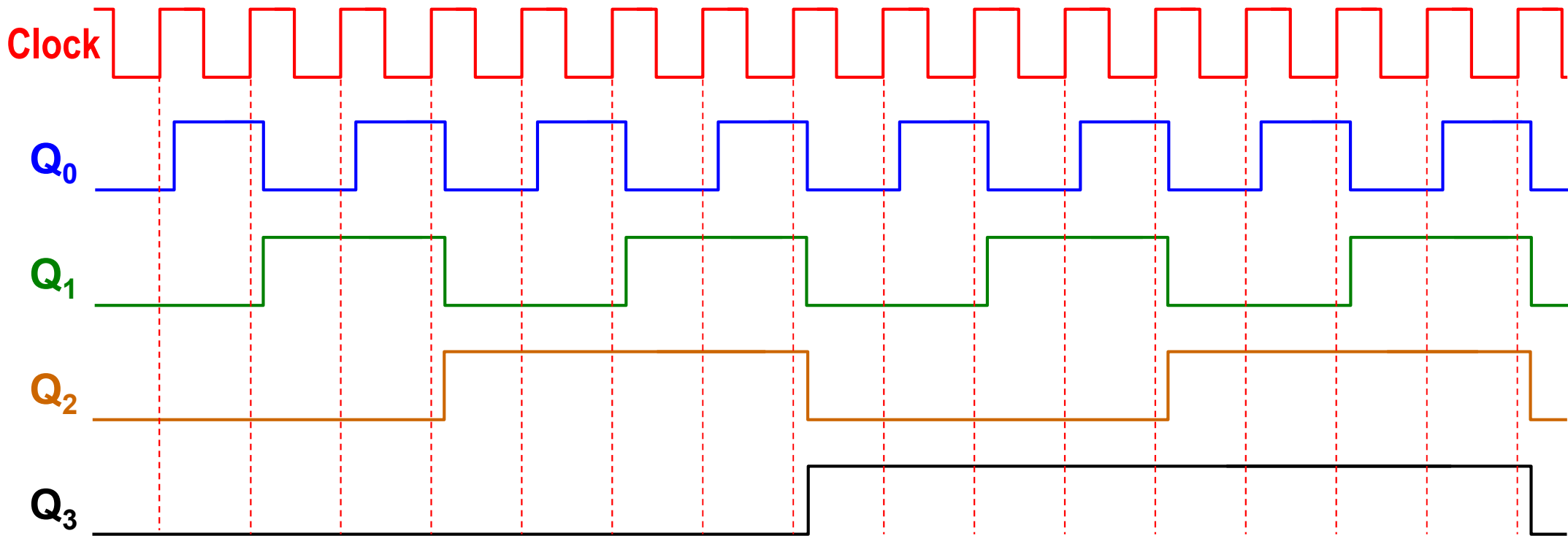


❖ Advantage of Synchronous counter:

ALL Flip-flops are driven by the **same clock**

Delay of all outputs is identical → Delay of $Q_0 = Q_1 = Q_2 = Q_3 = \Delta$

Frequency Division

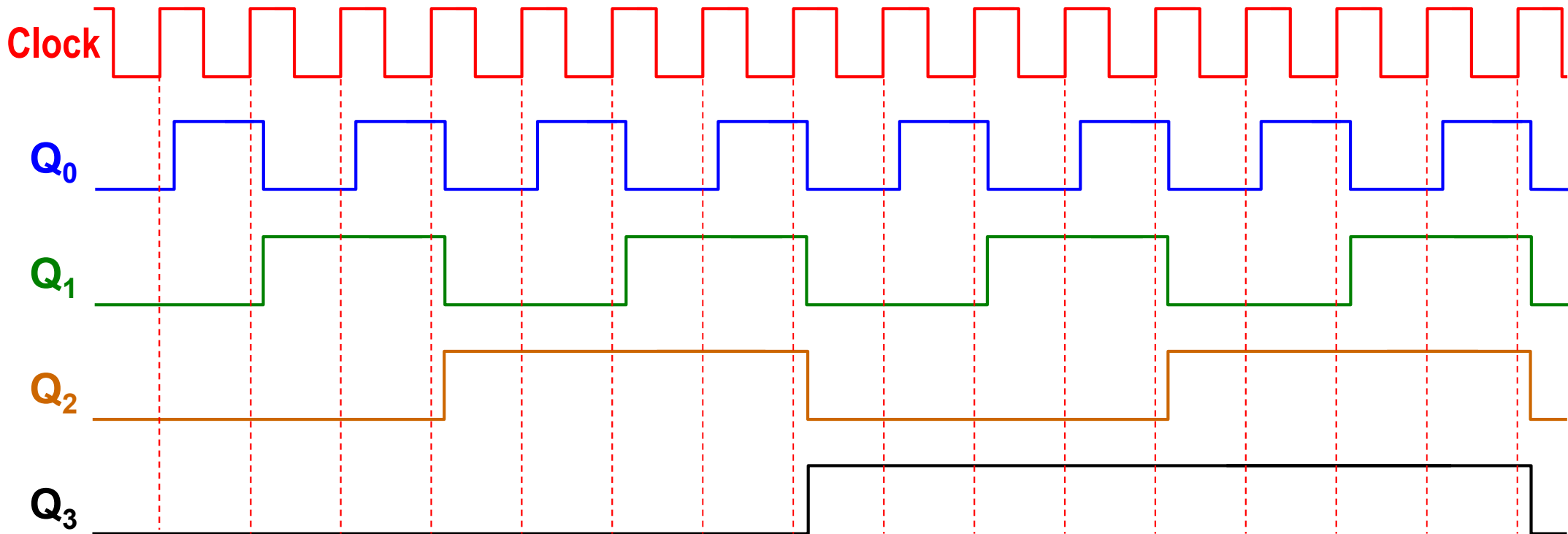
- ❖ A counter can be used as a frequency divider
- ❖ Counter is driven by a **Clock** with **frequency F**
- ❖ Output Q_0 Frequency = $F/2$, Output Q_1 Frequency = $F/4$
- ❖ Output Q_2 Frequency = $F/8$, Output Q_3 Frequency = $F/16$




BCD Counter

- ❖ **Problem:** Convert a 4-bit binary counter into a BCD counter
- ❖ **Solution:** When output reaches **9** then reset back to **0**
- ❖ **Asynchronous Reset:** Count to **10** and reset immediately

4-bit Counter with
Synchronous Reset

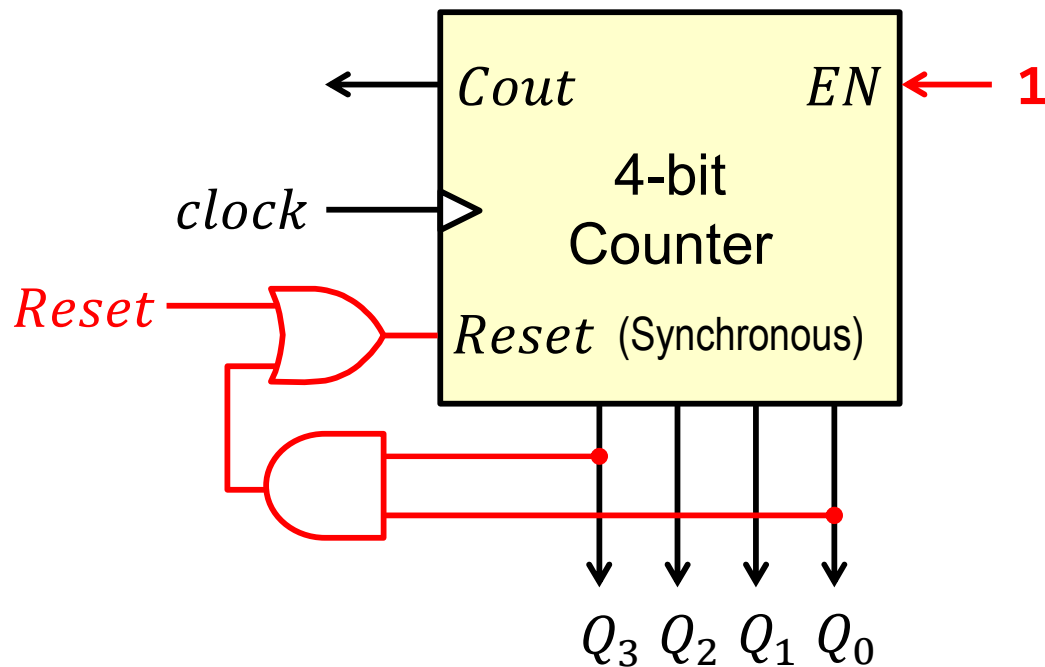


4-bit Counter with
Asynchronous Reset

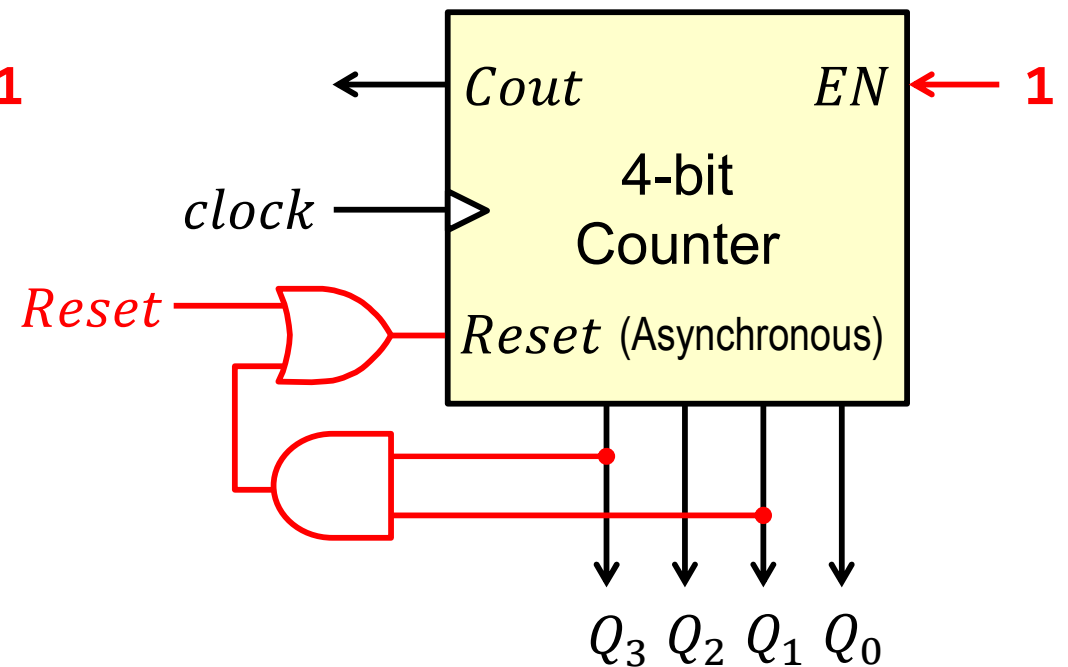

Building Larger Synchronous Counters

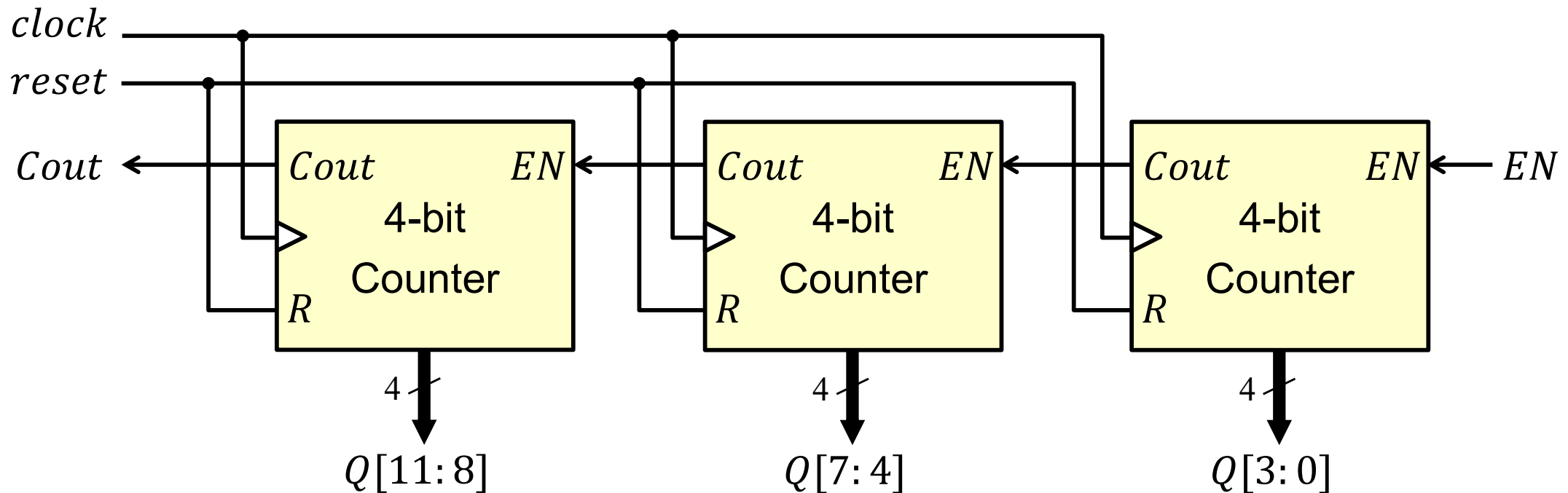
- ❖ Smaller counters can be used to build a larger counter
- ❖ Example: 12-bit counter designed using three 4-bit counters
 - Counts from **0** to **4095** ($2^{12} - 1$), then back to **0**
- ❖ The *Cout* of a 4-bit counter is used to enable the next counter




Synchronous Counter with Parallel Load

- ❖ Ability to load an initial binary number into the counter
 - ✧ Prior to the count operation
- ❖ Two control inputs:
 - ✧ **Load:** Initialize counter with input Data
 - ✧ **EN:** enables the counting

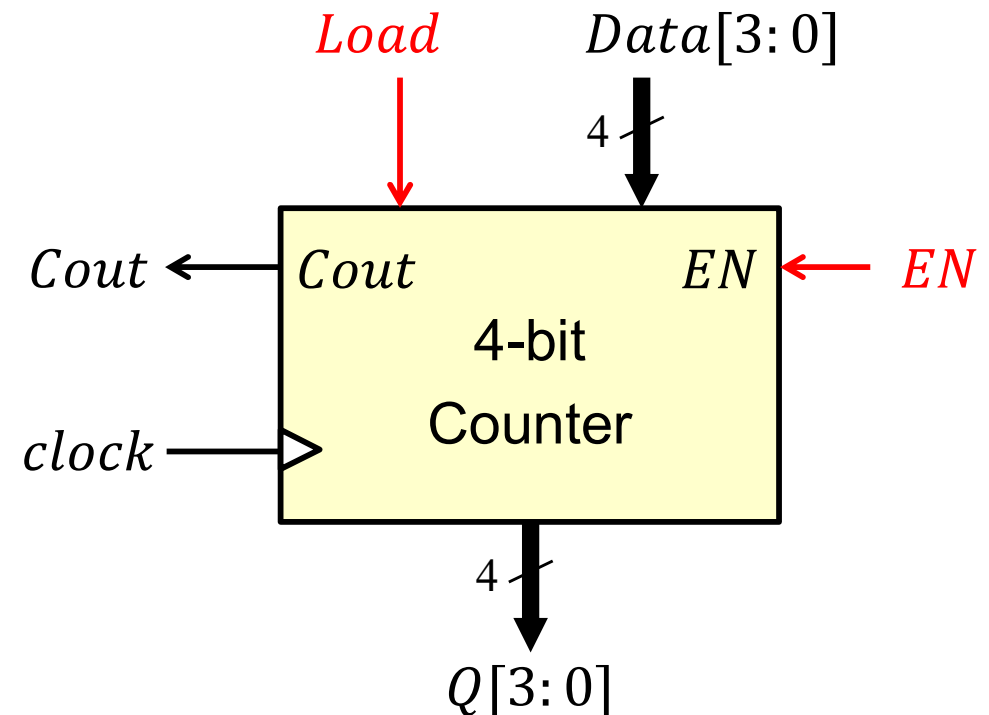Very useful in
implementing different
counting sequences




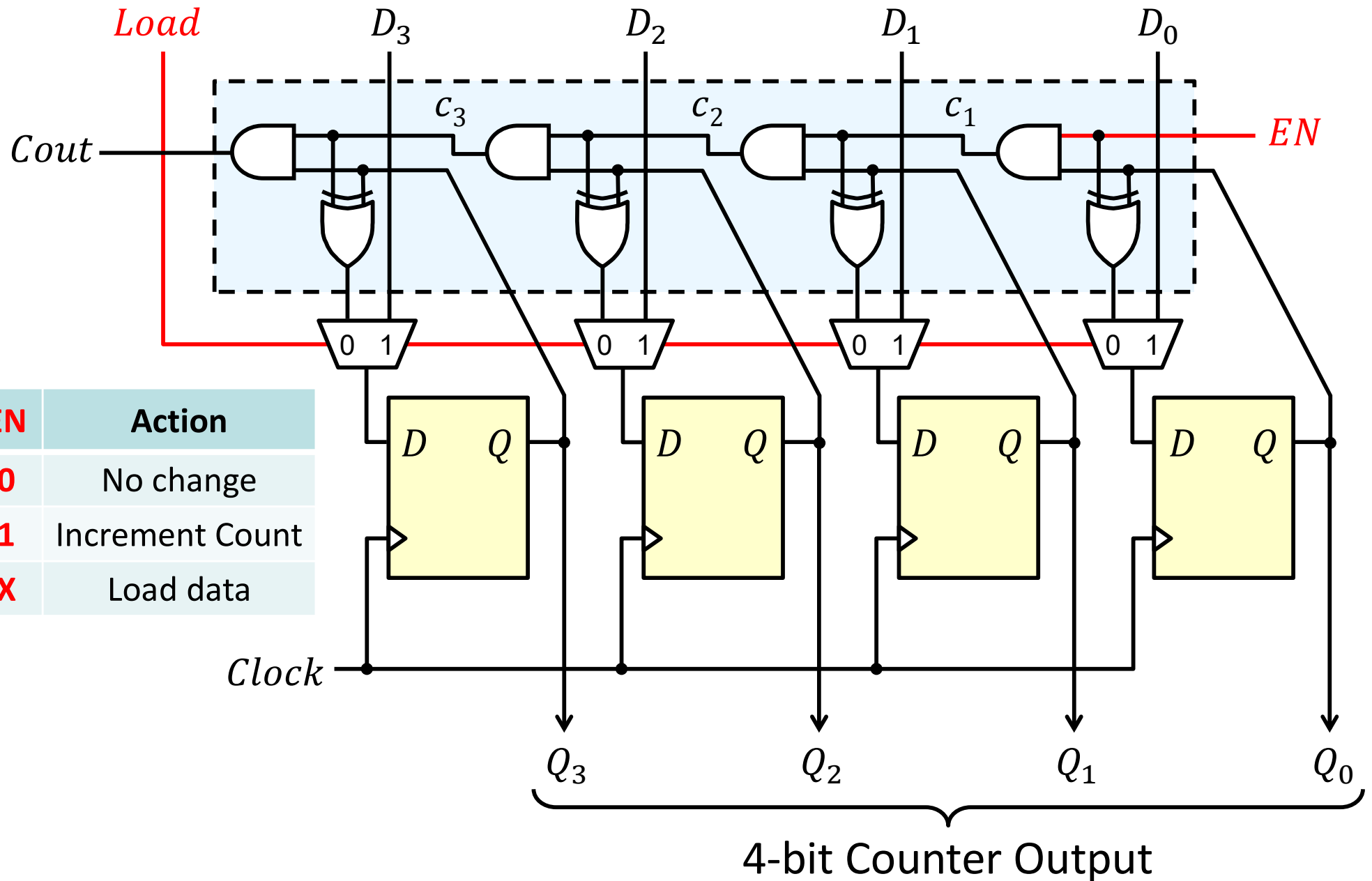Implementing a Counter with Parallel Load



3-to-12 Counter

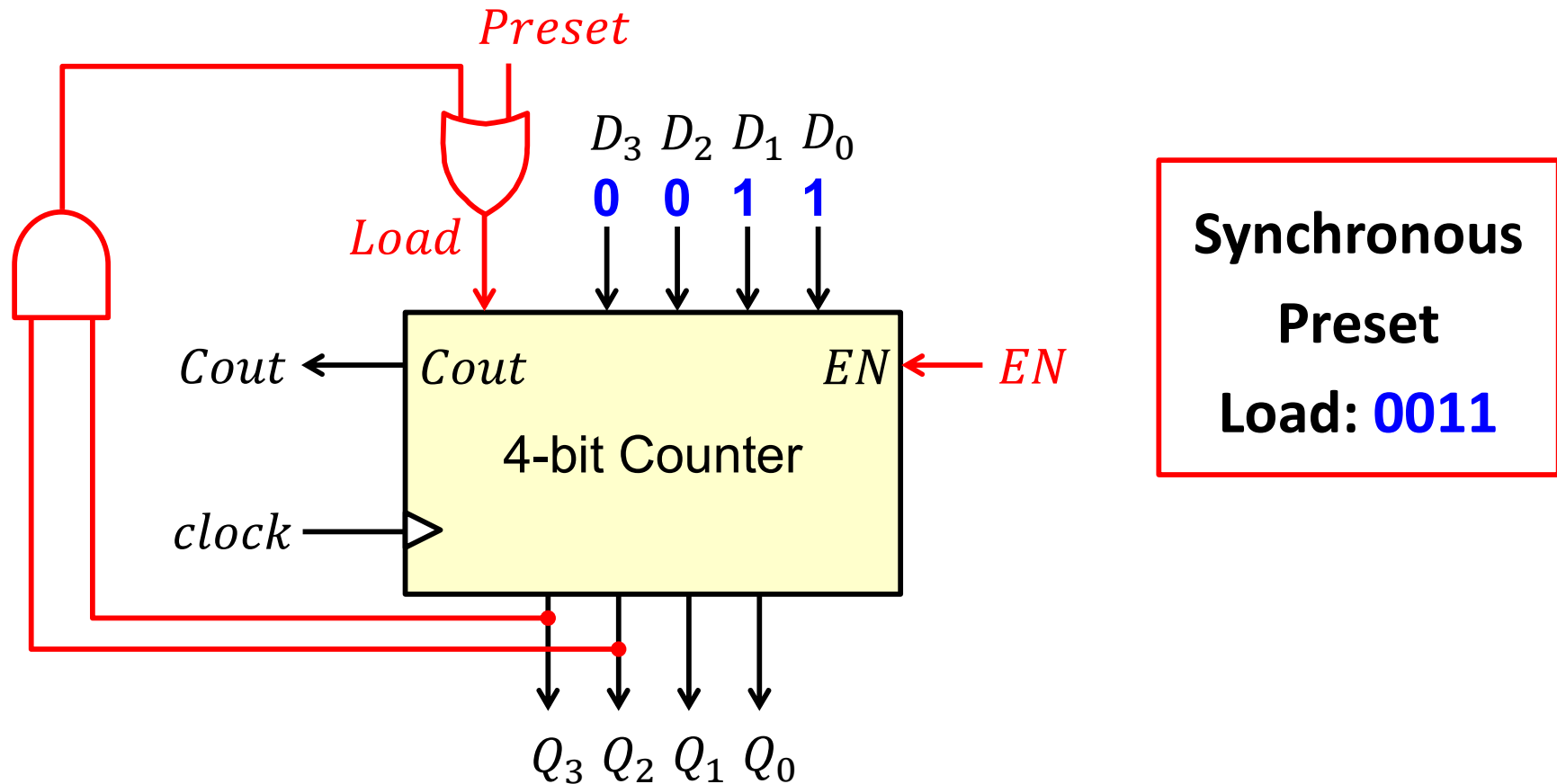- ❖ Convert a 4-bit binary counter **with load** into 3-to-12 counter
- ❖ **Solution:** Detect binary count **12** and then load **3**
- ❖ **Detect 12:** Binary count with $Q_3 = Q_2 = 1$



9-to-99 Counter

Problem: Use two 4-bit binary counters with parallel load and logic gates to build a counter that counts from **9** to **99 = 'b01100011**

Add a synchronous **Preset** input to initialize the counter to value **9**

