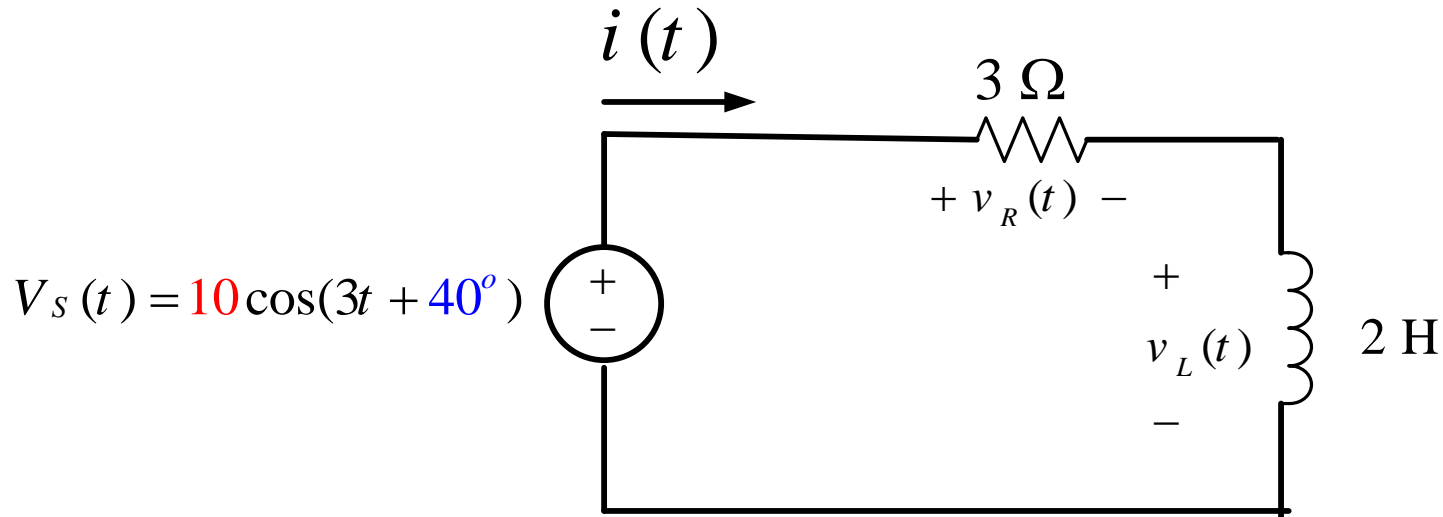


## 9.2 The Sinusoidal Response



$$\mathbf{KVL} \quad L \frac{di}{dt} + Ri = 10 \cos(3t + 40^\circ)$$

Solution for  $i(t)$  should be a sinusoidal of frequency 3

$$i(t) = 1.58 \cos(3t - 31.56^\circ)$$


$$v_R(t) = 3.1 \cos(3t - 31.56^\circ)$$

$$v_L(t) = 9.5 \cos(3t - 58.43^\circ)$$


We notice that only the **amplitude** and **phase** change

**In this chapter, we develop a technique for calculating the response directly without solving the differential equation**

## Time Domain

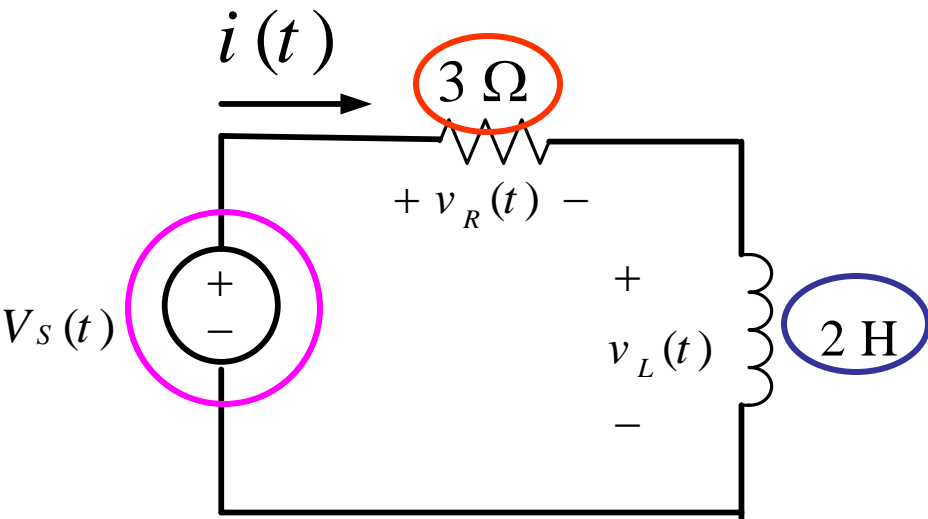

## Complex Domain

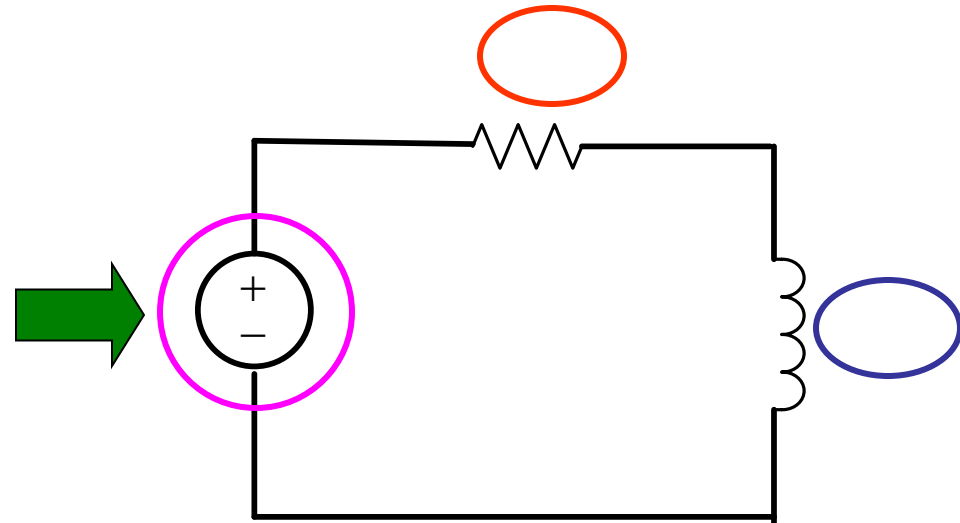

## Differential Equation

$$L \frac{di}{dt} + Ri = V_s(t)$$

## Algebraic Equation

### 9.3 The phasor

The **phasor** is a complex number that carries the **amplitude** and **phase** angle information of a sinusoidal function

The **phasor** concept is rooted in **Euler's** identity  $e^{\pm j\theta} = \cos(\theta) \pm j \sin(\theta)$

**Euler's** identity relates the complex exponential function to the trigonometric function

We can think of the **cosine** function as the **real part** of the complex exponential and the **sine** function as the imaginary part

$$\cos(\theta) = \Re\{e^{j\theta}\}$$

$$\sin(\theta) = \Im\{e^{j\theta}\}$$

**Because** we are going to use the cosine function on analyzing the sinusoidal steady-state we can apply

$$\cos(\theta) = \Re\{e^{j\theta}\}$$

$$e^{\pm j\theta} = \cos(\theta) \pm j \sin(\theta)$$

$$\cos(\theta) = \Re\{e^{j\theta}\}$$

$$\sin(\theta) = \Im\{e^{j\theta}\}$$

$$v = V_m \cos(\omega t + \phi) = V_m \Re\{e^{j(\omega t + \phi)}\} = V_m \Re\{e^{j\omega t} e^{j\phi}\}$$

We can move the coefficient  $V_m$  inside  $\longrightarrow v = \Re\{V_m e^{j\phi} e^{j\omega t}\}$

The quantity  $V_m e^{j\phi}$  is a complex number define to be the **phasor** that carries the amplitude and phase angle of a given sinusoidal function


### Phasor Transform

$$P\{V_m \cos(\omega t + \phi)\} = V_m e^{j\phi} = V$$

Were the notation  $P\{V_m \cos(\omega t + \phi)\}$

Is read “ the phasor transform of  $V_m \cos(\omega t + \phi)$

## The V-I Relationship for a Resistor

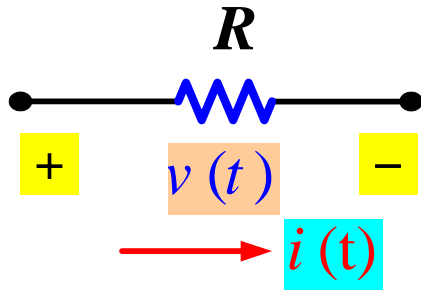

$$v(t) = Ri(t)$$


Let the current through the resistor be a **sinusoidal** given as  $i(t) = I_m \cos(\omega t + \theta_i)$


→  $v(t) = Ri(t) = R [I_m \cos(\omega t + \theta_i)] = RI_m [\cos(\omega t + \theta_i)]$

→  $v(t) = RI_m \left[ \cos(\omega t + \underbrace{\theta_i}_{\text{voltage phase}}) \right]$  Is also **sinusoidal** with

amplitude  $V_m = RI_m$  And phase  $\theta_v = \theta_i$

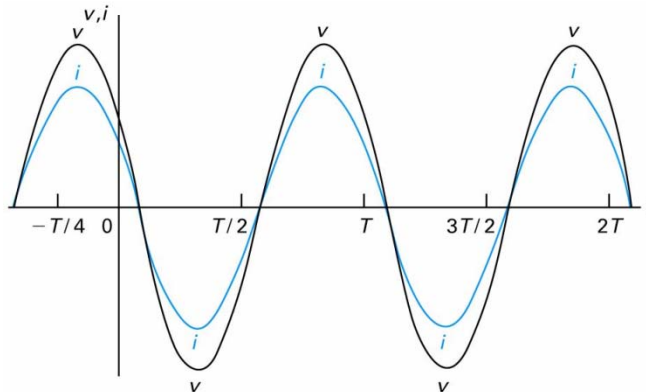
→ The sinusoidal voltage and current in a **resistor** are **in phase**



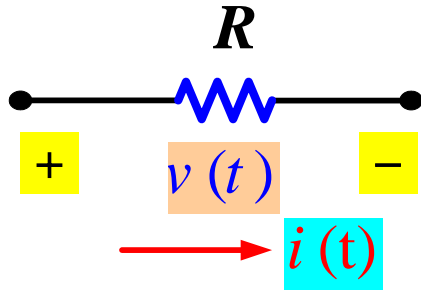

$$i(t) = I_m \cos(\omega t + \theta_i)$$
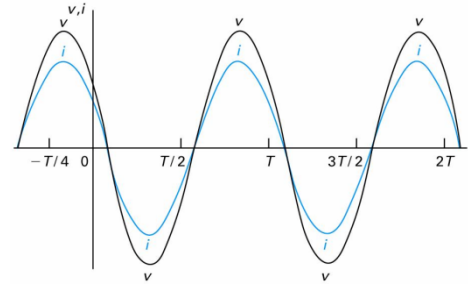
$$v(t) = RI_m [\cos(\omega t + \theta_i)]$$



Now let us see the phasor domain representation or phasor transform of the **current** and **voltage**

$$i(t) = I_m \cos(\omega t + \theta_i)$$

Phasor Transform


$$I = I_m e^{j\theta_i} = I_m \angle \theta_i$$

$$v(t) = RI_m [\cos(\omega t + \theta_i)]$$


Phasor Transform

$$V = RI_m e^{j\theta_i} = \underbrace{RI_m}_{V_m} \underbrace{\angle \theta_i}_{\theta_v} = RI$$

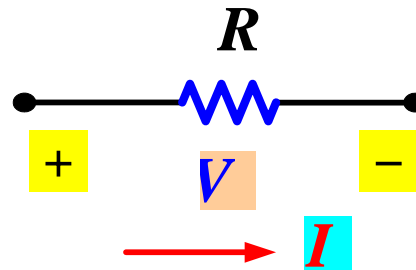
Which is Ohm's law on the **phasor** ( **or complex** ) domain




$$V = RI$$

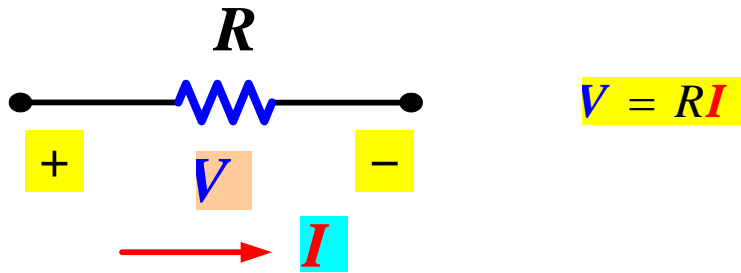

The voltage and the current are in phase

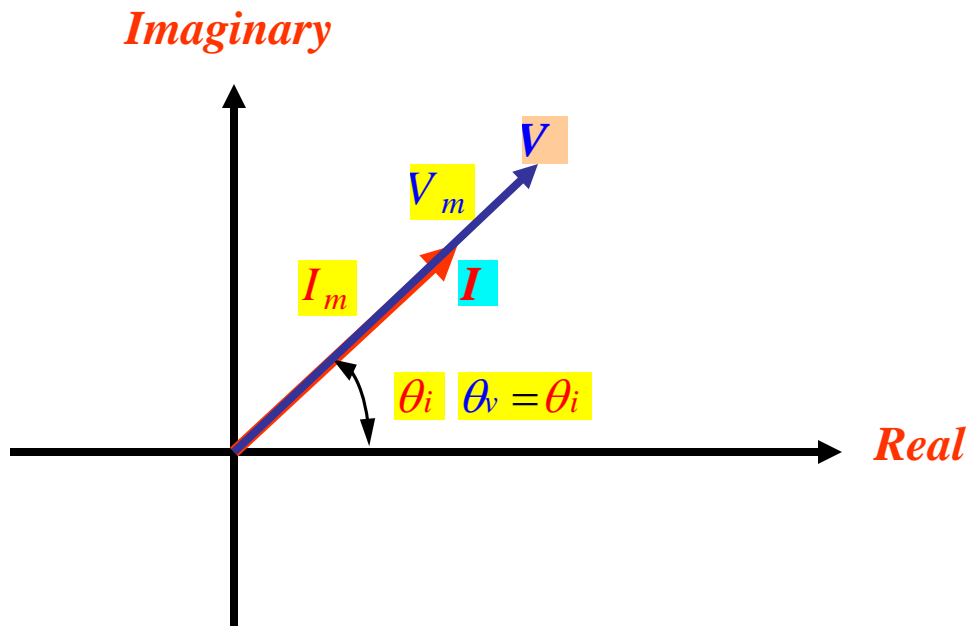

## The V-I Relationship for an Inductor

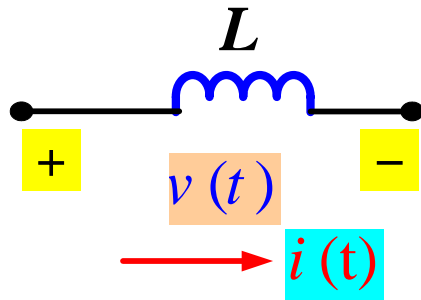


$$v(t) = L \frac{di(t)}{dt}$$

Let the current through the resistor be a **sinusoidal** given as

$$i(t) = I_m \cos(\omega t + \theta_i)$$
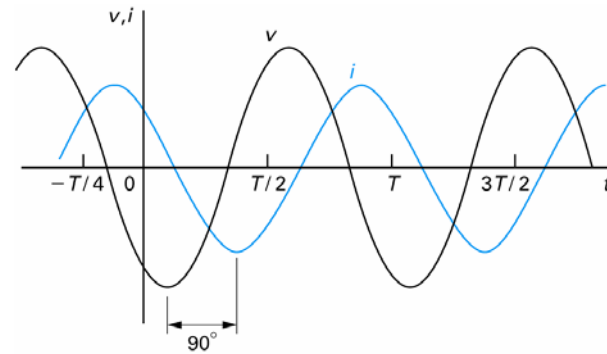
$$v(t) = L \frac{di(t)}{dt} = -\omega L I_m \sin(\omega t + \theta_i)$$




➡ The sinusoidal voltage and current in an **inductor** are **out of phase** by  **$90^\circ$**

The voltage **lead** the current by  **$90^\circ$**  or the current **lagging** the voltage by  **$90^\circ$**

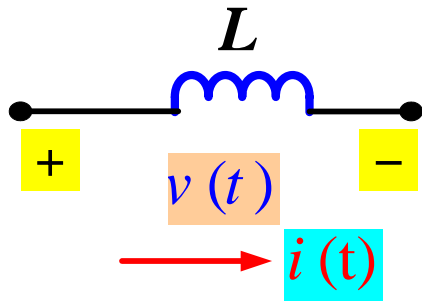
You can express the voltage **leading** the current by  **$T/4$  or  $1/4f$  seconds** where  **$T$**  is the period and  **$f$**  is the frequency





$$i(t) = I_m \cos(\omega t + \theta_i)$$
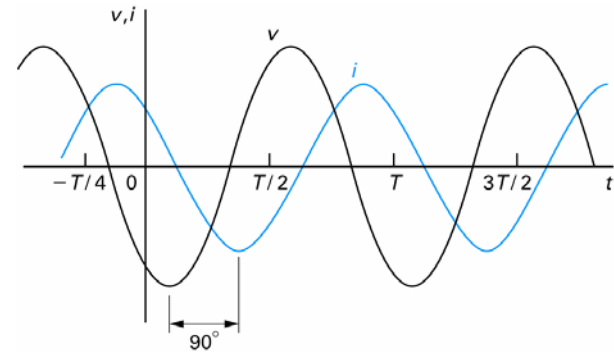
$$v(t) = -\omega L I_m \sin(\omega t + \theta_i)$$



Now we rewrite the sin function as a cosine function

(remember the phasor is defined in terms of a cosine function)

$$\Rightarrow v(t) = -\omega L I_m \cos(\omega t + \theta_i - 90^\circ)$$

The phasor representation or transform of the **current** and **voltage**

$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow I = I_m e^{j\theta_i} = I_m \angle \theta_i$$


$$v(t) = -\omega L I_m \cos(\omega t + \theta_i - 90^\circ) \Rightarrow V = -\omega L I_m e^{j(\theta_i - 90^\circ)} = -\omega L I_m e^{j\theta_i} \underbrace{e^{-j90^\circ}}_{=-j} = j \omega L I_m e^{j\theta_i}$$

But since  $j = 1 e^{j90^\circ} = 1 \angle 90^\circ$

$$\text{Therefore } V = j \omega L I_m e^{j\theta_i} = \omega L I_m e^{j90^\circ} e^{j\theta_i} = \omega L I_m e^{j(\theta_i + 90^\circ)} = \omega L I_m \angle (\theta_i + 90^\circ)$$
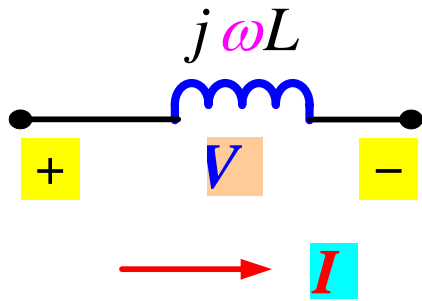
$$\Rightarrow V_m = \omega L I_m \text{ and } \theta_v = \theta_i + 90^\circ$$







$$V = j\omega LI$$

$$V_m = \omega LI_m \quad \text{and} \quad \theta_v = \theta_i + 90^\circ$$

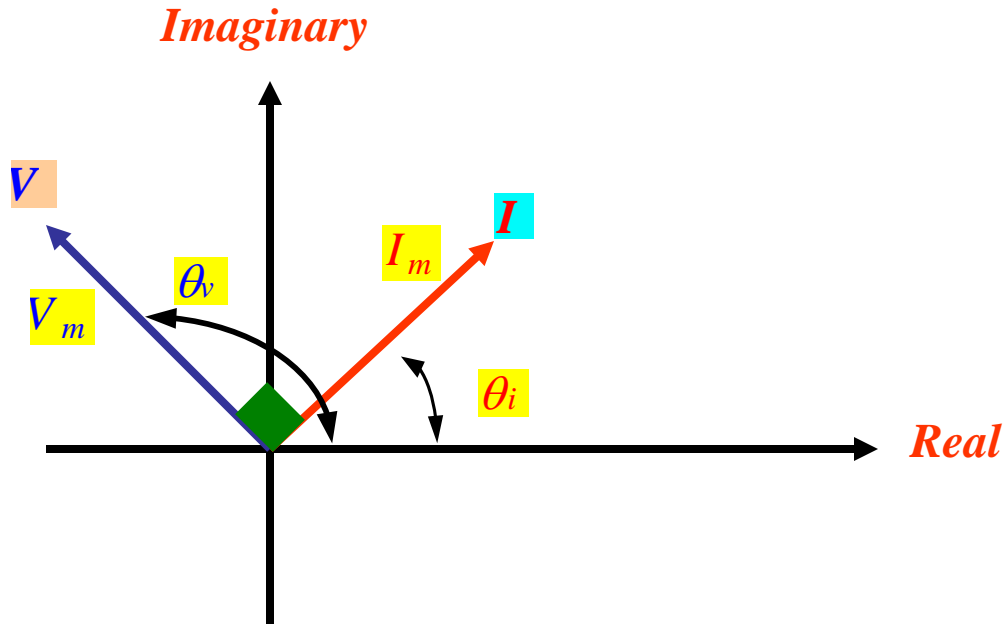The voltage **lead** the current by  $90^\circ$  or the current **lagging** the voltage by  $90^\circ$



## The V-I Relationship for a Capacitor

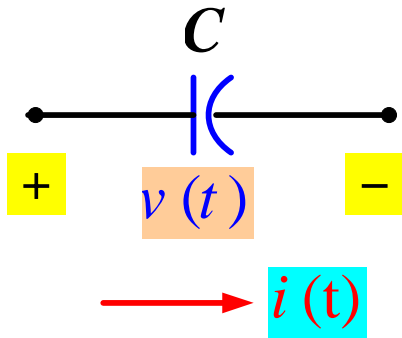


$$i(t) = C \frac{dv(t)}{dt}$$

Let the voltage across the capacitor be a **sinusoidal** given as

$$v(t) = V_m \cos(\omega t + \theta_v)$$

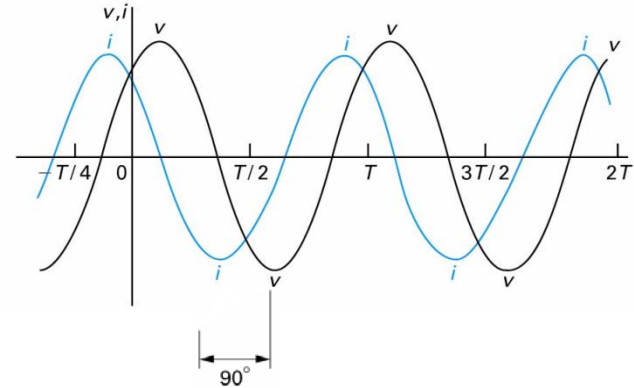
$$i(t) = C \frac{dv(t)}{dt} = -\omega C V_m \sin(\omega t + \theta_v)$$



➔ The sinusoidal voltage and current in an **inductor** are **out of phase** by  $90^\circ$


The voltage **lag** the current by  $90^\circ$  or the current **leading** the voltage by  $90^\circ$

# The V-I Relationship for a Capacitor

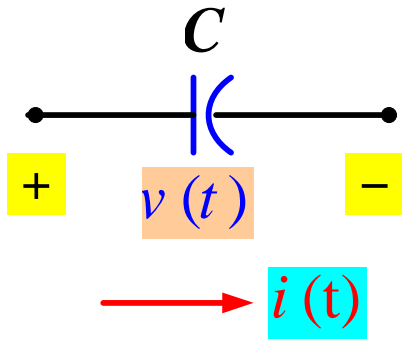

$$v(t) = V_m \cos(\omega t + \theta_v)$$
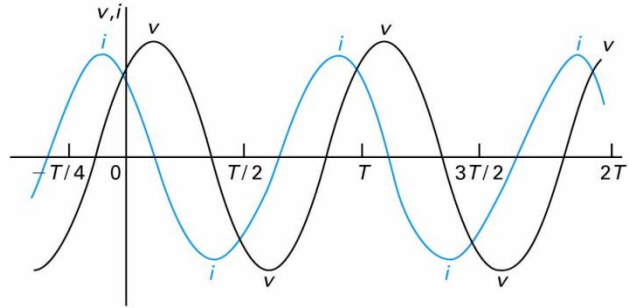
$$i(t) = -\omega C V_m \sin(\omega t + \theta_v)$$



The phasor representation or transform of the **voltage** and **current**


$$v(t) = V_m \cos(\omega t + \theta_v) \quad \Rightarrow \quad \mathbf{V} = V_m e^{j\theta_v} = V_m \angle \theta_v$$

$$i(t) = -\omega C V_m \sin(\omega t + \theta_v) = -\omega C V_m \cos(\omega t + \theta_v - 90^\circ) \quad \Rightarrow \quad \mathbf{I} = -\omega C V_m e^{j(\theta_v - 90^\circ)}$$

$$\Rightarrow \mathbf{I} = -\omega C V_m e^{j\theta_v} \underbrace{e^{j-90^\circ}}_{-j} = j\omega C V_m e^{j\theta_v} = j\omega C \mathbf{V}$$

$$\Rightarrow \mathbf{V} = \frac{\mathbf{I}}{j\omega C} = \frac{I_m e^{j\theta_i}}{\underbrace{j}_{e^{j90^\circ}} \omega C} = \frac{I_m e^{j(\theta_i - 90^\circ)}}{\omega C} = \underbrace{\frac{I_m}{\omega C}}_{V_m} \angle \underbrace{(\theta_i - 90^\circ)}_{\theta_v}$$

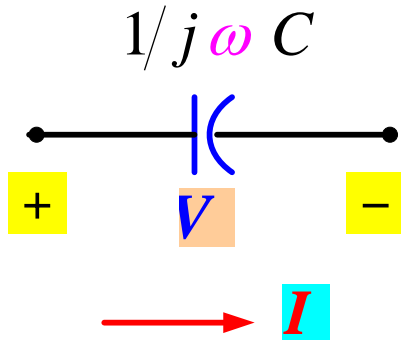
$$\Rightarrow V_m = \frac{I_m}{\omega C} \quad \text{and} \quad \theta_v = \theta_i - 90^\circ$$




$$V = \frac{I}{j\omega C}$$

$$V_m = \frac{I_m}{\omega C} \quad \text{and} \quad \theta_v = \theta_i - 90^\circ$$

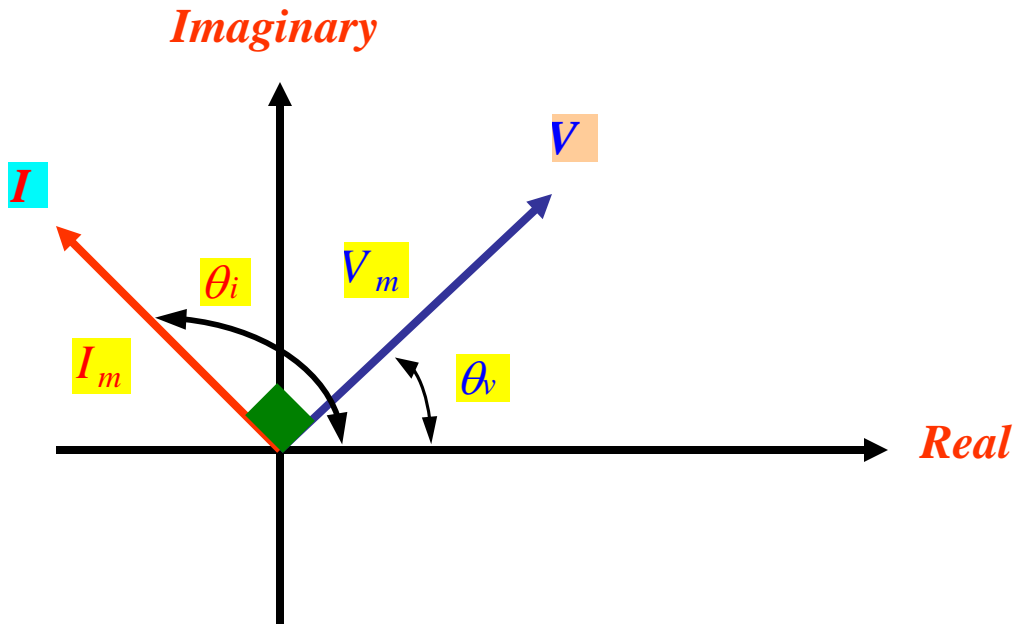The voltage **lag** the current by  $90^\circ$  or the current **lead** the voltage by  $90^\circ$




## Time-Domain

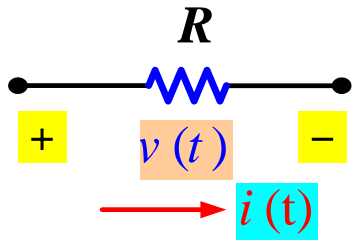

$$v(t) = Ri(t)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

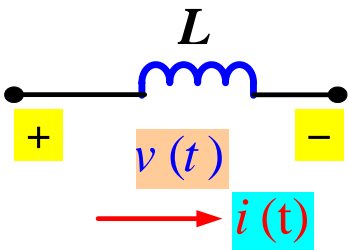
$$v(t) = RI_m [\cos(\omega t + \theta_i)]$$



$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$
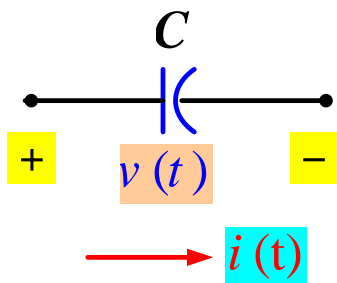
$$v(t) = -\omega LI_m \sin(\omega t + \theta_i)$$






$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = -\omega CV_m \sin(\omega t + \theta_v)$$

## Phasor (Complex or Frequency) Domain

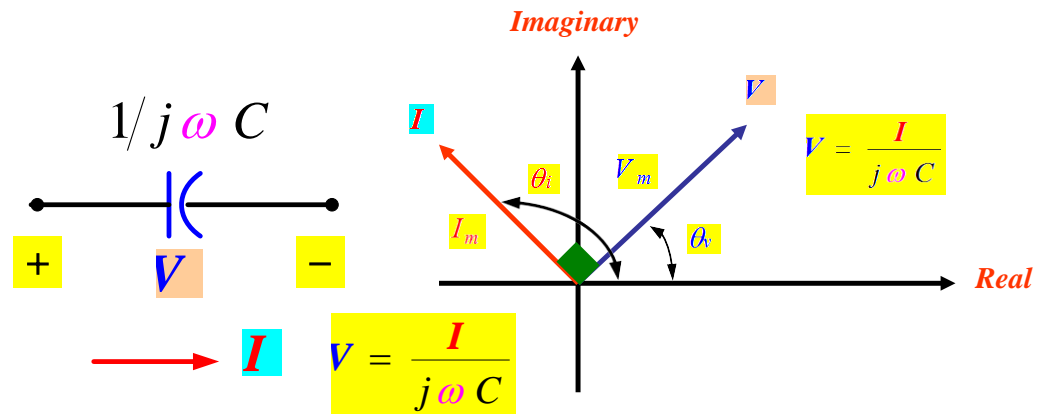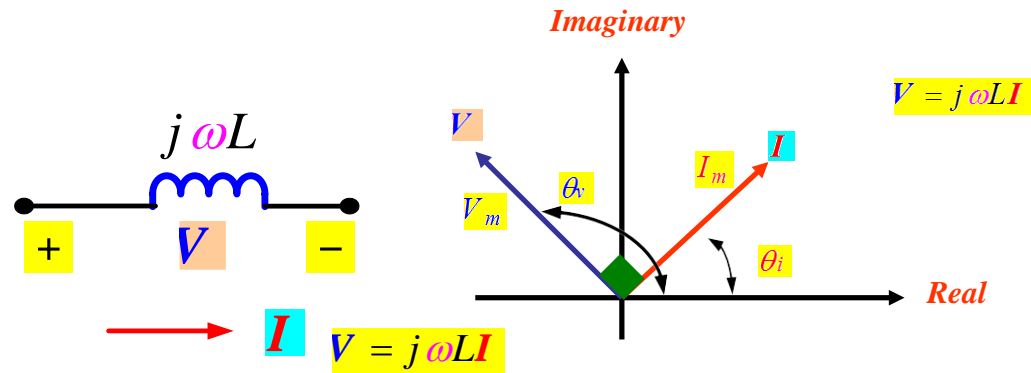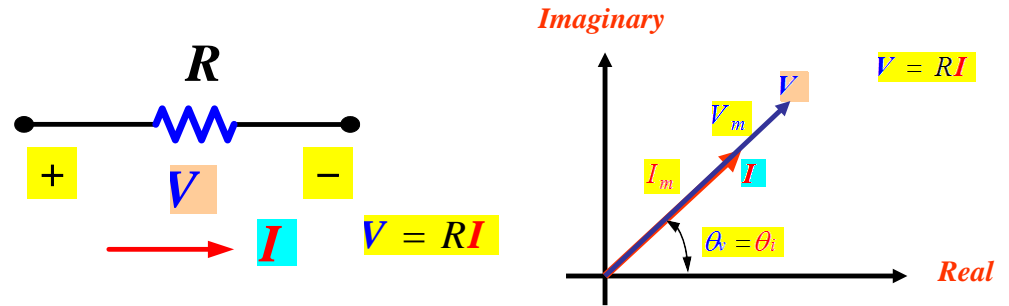

## Impedance and Reactance

The relation between the **voltage** and **current** on the **phasor** domain (**complex** or **frequency**) for the three elements R, L, and C we have

$$V = RI$$

$$V = j\omega LI$$

$$V = \frac{I}{j\omega C} = \frac{I}{j\omega C}$$

When we compare the relation between the **voltage** and **current**, we note that they are all of form:

$$V = ZI$$

Which state that the phasor voltage is some complex constant (Z) times the phasor current

This resemble (شبه) Ohm's law were the complex constant (Z) is called "**Impedance**" (أعاقه)

Recall on Ohm's law previously defined, the proportionality content R was real and called "**Resistant**" (مقاومه)

Solving for (Z) we have  $Z = \frac{V}{I}$

The **Impedance** of a resistor is  $Z_R = R$

The **Impedance** of an inductor is  $Z_L = j\omega L$

The **Impedance** of a capacitor is  $Z_C = \frac{1}{j\omega C}$

In all cases the impedance is measured in Ohm's  $\Omega$

$$V = RI$$

$$V = j\omega LI$$

$$V = \frac{1}{j\omega C} I$$

**Impedance**  $Z = \frac{V}{I}$

The **Impedance** of a resistor is  $Z_R = R$  In all cases the impedance is measured in Ohm's  $\Omega$

The **Impedance** of an inductor is  $Z_L = j\omega L$

The **Impedance** of a capacitor is  $Z_C = \frac{1}{j\omega C}$

The imaginary part of the impedance is called “**reactance**”

The **reactance** of a resistor is  $X_R = 0$

The **reactance** of an inductor is  $X_L = \omega L$

The **reactance** of a capacitor is  $X_C = \frac{-1}{\omega C}$

We note the “**reactance**” is associated with energy storage elements like the **inductor** and **capacitor**

Note that the impedance in general (*exception is the resistor*) is a function of frequency

At  $\omega = 0$  (DC), we have the following

$$Z_L = j\omega L = j(0)L = 0$$



short

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(0)C} = \infty$$




open



## 9.5 Kirchoff's Laws in the Frequency Domain ( Phasor or Complex Domain)

Consider the following circuit

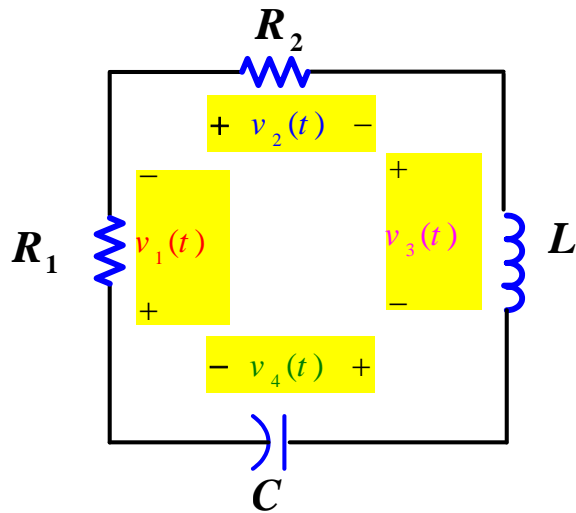

Phasor Transformation

$$v_1(t) = V_1 \cos(\omega t + \theta_1) \quad \longrightarrow \quad \mathbf{V}_1 = V_1 e^{j\theta_1}$$

$$v_2(t) = V_2 \cos(\omega t + \theta_2) \quad \longrightarrow \quad \mathbf{V}_2 = V_2 e^{j\theta_2}$$

$$v_3(t) = V_3 \cos(\omega t + \theta_3) \quad \longrightarrow \quad \mathbf{V}_3 = V_3 e^{j\theta_3}$$

$$v_4(t) = V_4 \cos(\omega t + \theta_4) \quad \longrightarrow \quad \mathbf{V}_4 = V_4 e^{j\theta_4}$$


KVL  $\longrightarrow$   $v_1(t) + v_2(t) + v_3(t) + v_4(t) = 0$

$$\longrightarrow V_1 \cos(\omega t + \theta_1) + V_2 \cos(\omega t + \theta_2) + V_3 \cos(\omega t + \theta_3) + V_4 \cos(\omega t + \theta_4) = 0$$

Using Euler Identity we have  $\Re\{V_1 e^{j\theta_1} e^{j\omega t}\} + \Re\{V_2 e^{j\theta_2} e^{j\omega t}\} + \Re\{V_3 e^{j\theta_3} e^{j\omega t}\} + \Re\{V_4 e^{j\theta_4} e^{j\omega t}\} = 0$

Which can be written as  $\Re\{V_1 e^{j\theta_1} e^{j\omega t} + V_2 e^{j\theta_2} e^{j\omega t} + V_3 e^{j\theta_3} e^{j\omega t} + V_4 e^{j\theta_4} e^{j\omega t}\} = 0$

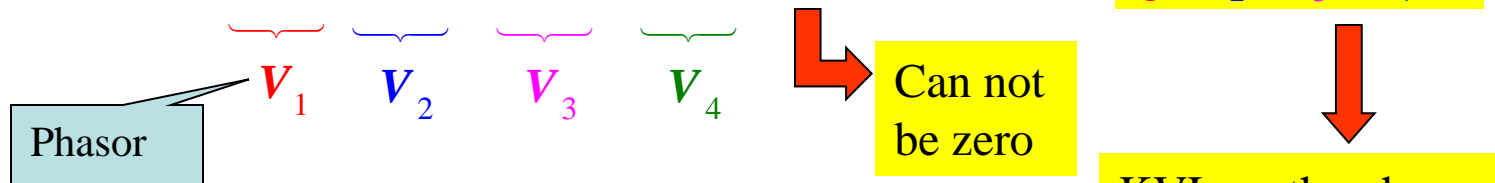Factoring  $e^{j\omega t} \longrightarrow \Re\{(V_1 e^{j\theta_1} + V_2 e^{j\theta_2} + V_3 e^{j\theta_3} + V_4 e^{j\theta_4}) e^{j\omega t}\} = 0 \longrightarrow V_1 + V_2 + V_3 + V_4 = 0$



So in general  $V_1 + V_2 + \dots + V_n = 0$

# Kirchhoff's Current Law

A similar derivation applies to a set of **sinusoidal** current summing at a node

$$i_1(t) = I_1 \cos(\omega t + \theta_1) \quad i_2(t) = I_2 \cos(\omega t + \theta_2) \quad \dots \quad i_n(t) = I_n \cos(\omega t + \theta_n)$$

Phasor  
Transformation

$$\mathbf{I}_1 = I_1 e^{j\theta_1}$$


$$\mathbf{I}_2 = I_2 e^{j\theta_2}$$

$$\mathbf{I}_n = I_n e^{j\theta_n}$$

KCL



$$i_1(t) + i_2(t) + \dots + i_n(t) = 0$$

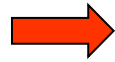


$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0$$

KCL on the phasor  
domain

## 9.6 Series, Parallel, and Delta-to Wye Simplifications

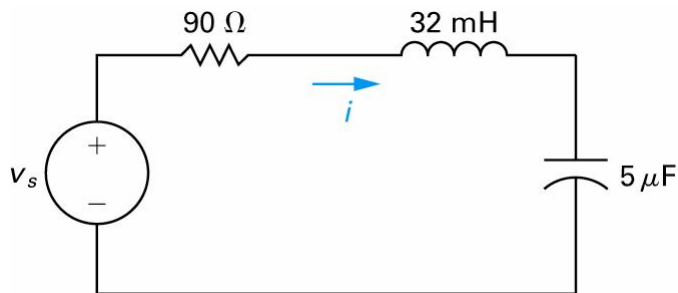**Example 9.6** for the circuit shown below the source voltage is sinusoidal




$$v_s(t) = 750 \cos(5000t + 30^\circ)$$



- (a) Construct the frequency-domain (phasor, complex) equivalent circuit ?  
 (b) Calculate the steady state current  $i(t)$  ?

The source voltage phasor transformation or equivalent  $\Rightarrow V_s = 750 e^{j30^\circ} = 750 \angle 30^\circ$

The **Impedance** of the inductor is  $Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160 \Omega$

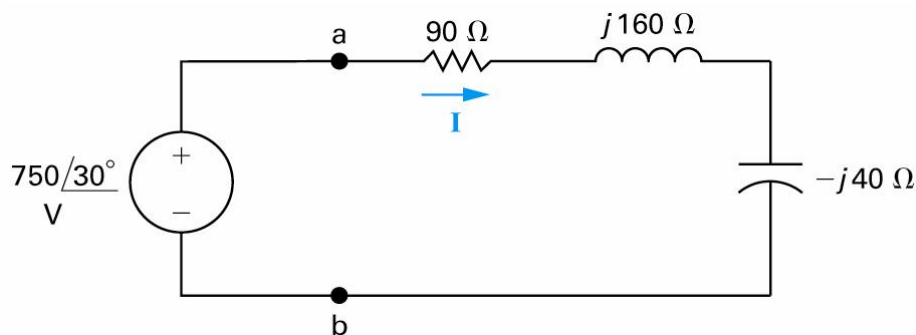The **Impedance** of the capacitor is  $Z_C = \frac{1}{j\omega C} = \frac{1}{j(5000)(5 \times 10^{-6})} = -j40 \Omega$



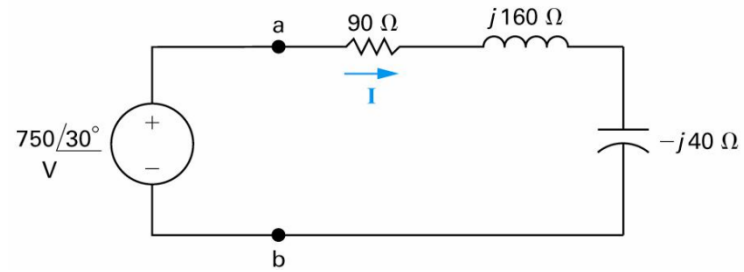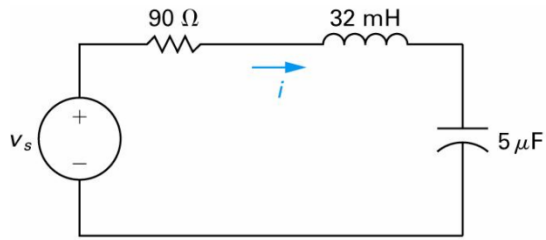

$$v_s(t) = 750 \cos(5000t + 30^\circ)$$


To Calculate the phasor current  $I$

$$I = \frac{V_s}{Z_{ab}} = \frac{750e^{j30^\circ}}{90 + j160 - j40} = \frac{750e^{j30^\circ}}{90 + j120} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A}$$



$$i(t) = 5 \cos(5000t - 23.13^\circ) \text{ A}$$
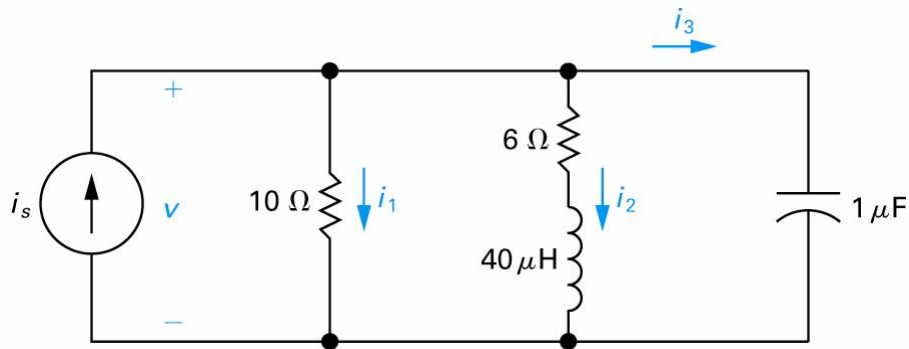
### Example 9.7 Combining Impedances in series and in Parallel





$$i_s(t) = 8\cos(200,000t) \text{ A}$$

(a) Construct the frequency-domain (phasor, complex) equivalent circuit ?

(b) Find the steady state expressions for  $v, i_1, i_2,$  and  $i_3$  ? ?

(a)

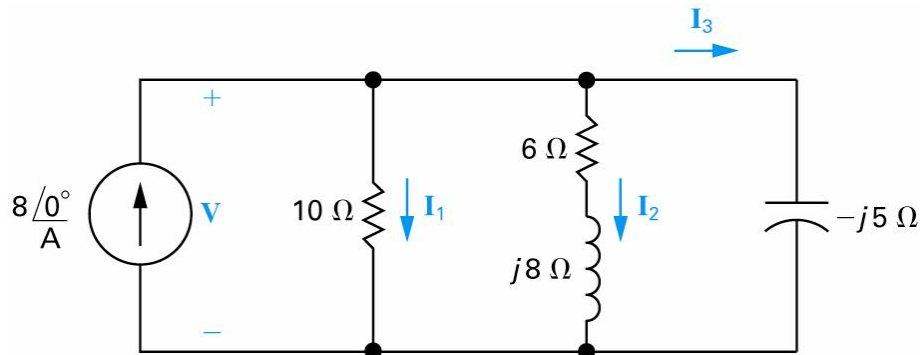

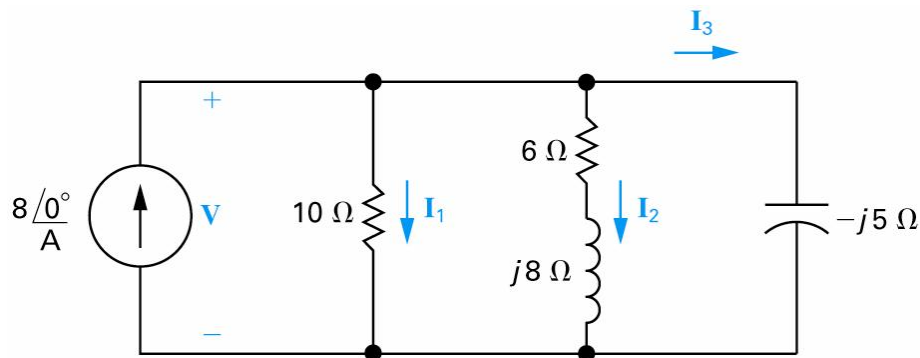

$$Y_1 = \frac{1}{10} = 0.1 \text{ S}$$

$$Y_2 = \frac{1}{6 + j8} = \frac{6 - j8}{100} = 0.06 - j0.08 \text{ S}$$

$$Y_3 = \frac{1}{-j5} = j0.2 \text{ S}$$

The admittance of the three branches is  $Y = Y_1 + Y_2 + Y_3 = 0.16 + j0.12 = 0.2 \angle 36.87^\circ \text{ S}$

$$Z = \frac{1}{Y} = 5 \angle -36.87^\circ \Omega \quad \mathbf{V} = Z\mathbf{I} = 40 \angle -36.87^\circ \text{ V} \quad \Rightarrow \quad v = 40 \cos(200,000t - 36.87^\circ) \text{ V}$$


$$\mathbf{I}_1 = \frac{40 \angle -36.87^\circ}{10} = 4 \angle -36.87^\circ = 3.2 - j2.4 \text{ A} \quad \Rightarrow \quad i_1 = 4 \cos(200,000t - 36.87^\circ) \text{ A}$$

$$\mathbf{I}_2 = \frac{40 \angle -36.87^\circ}{6 + j8} = 4 \angle -90^\circ = -j4 \text{ A} \quad \Rightarrow \quad i_2 = 4 \cos(200,000t - 90^\circ) \text{ A}$$

$$\mathbf{I}_3 = \frac{40 \angle -36.87^\circ}{5 \angle -90^\circ} = 8 \angle 53.13^\circ = 4.8 + j6.4 \text{ A} \quad \Rightarrow \quad i_3 = 8 \cos(200,000t + 53.13^\circ) \text{ A}$$

We check the computations  $\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 3.2 - j2.4 - j4 + 4.8 + j6.4 = \boxed{8 + j0} = \mathbf{I}$

## Delta-to Wye Transformations

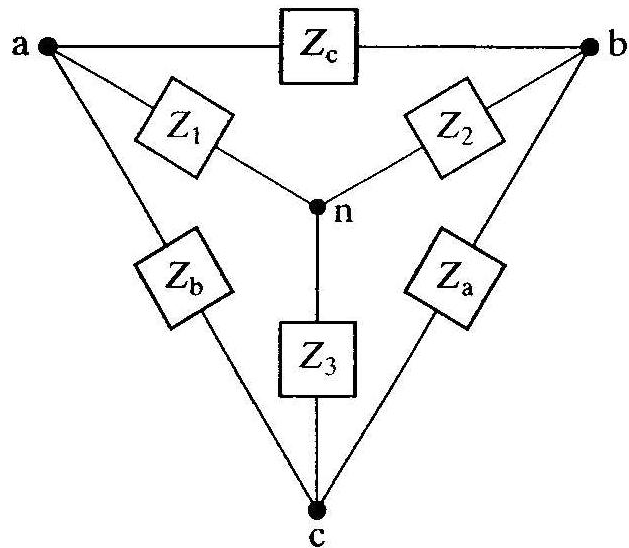

### $\Delta$ to Y

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

### Y to $\Delta$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$





$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$


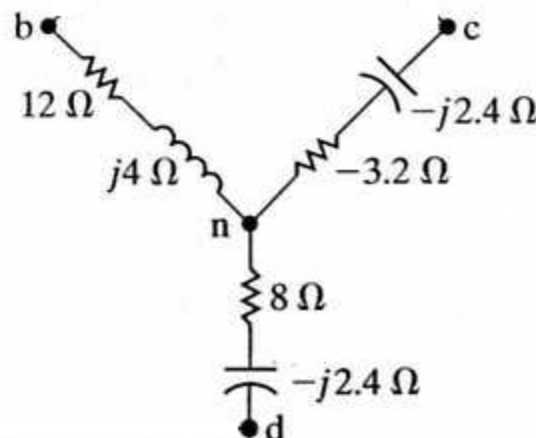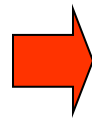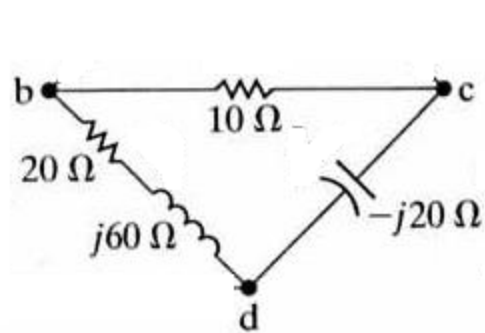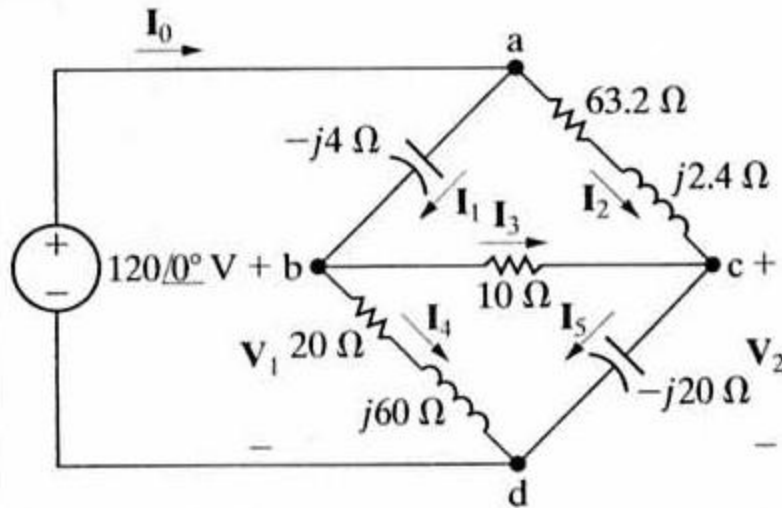
### Example 9.8

Use a  $\Delta$ -to-Y impedance transformation to find  $I_0, I_1, I_2, I_3, I_4, I_5, V_1,$  and  $V_2$  in the circuit




$$Z_1 = \frac{(20 + j60)(10)}{30 + j40} = 12 + j4 \Omega$$

$$Z_2 = \frac{10(-j20)}{30 + j40} = -3.2 - j2.4 \Omega$$

$$Z_3 = \frac{(20 + j60)(-j20)}{30 + j40} = 8 - j24 \Omega$$
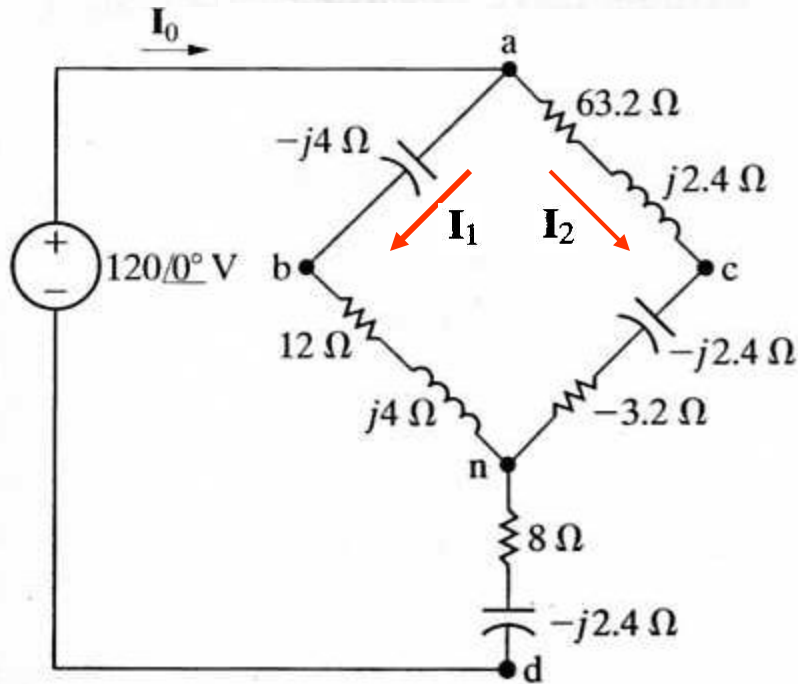
$$\mathbf{I}_0 = 4 \angle 53.13^\circ = 2.4 + j3.2 \text{ A}$$



$$\mathbf{V}_{nd} = (8 - j24)\mathbf{I}_0 = 96 - j32 \text{ V}$$

$$\mathbf{V} = \mathbf{V}_{an} + \mathbf{V}_{nd}$$

$$\mathbf{V}_{an} = 120 - 96 + j32 = 24 + j32 \text{ V}$$

$$\mathbf{I}_{abn} = \frac{24 + j32}{12} = 2 + j\frac{8}{3} \text{ A}$$

$$\mathbf{I}_{acn} = \frac{24 + j32}{60} = \frac{4}{10} + j\frac{8}{15} \text{ A}$$

the branch currents


$$\mathbf{I}_1 = \mathbf{I}_{abn} = 2 + j\frac{8}{3} \text{ A}$$

$$\mathbf{I}_2 = \mathbf{I}_{acn} = \frac{4}{10} + j\frac{8}{15} \text{ A}$$


check the calculations  $\mathbf{I}_1 + \mathbf{I}_2 = 2.4 + j3.2 = \mathbf{I}_0$

## 9.7 Source Transformations and Thevenin-Norton Equivalent Circuits


### Source Transformations

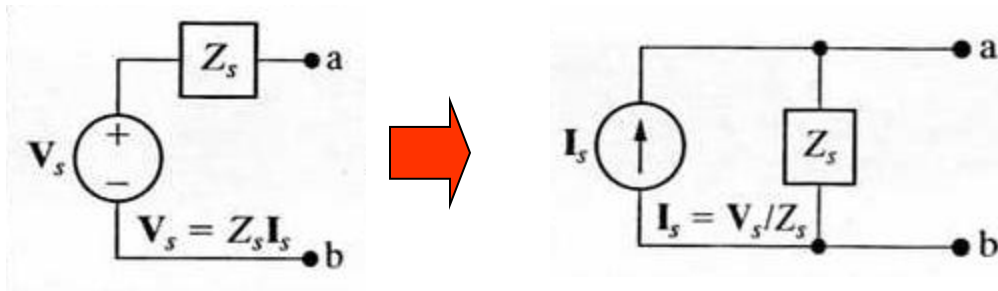


### Thevenin-Norton Equivalent Circuits

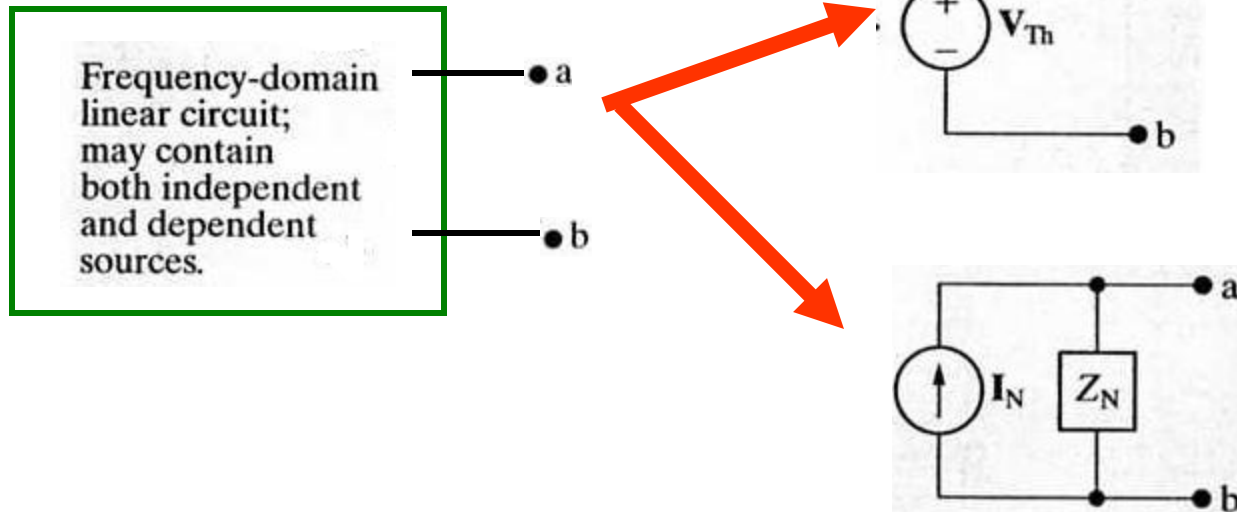

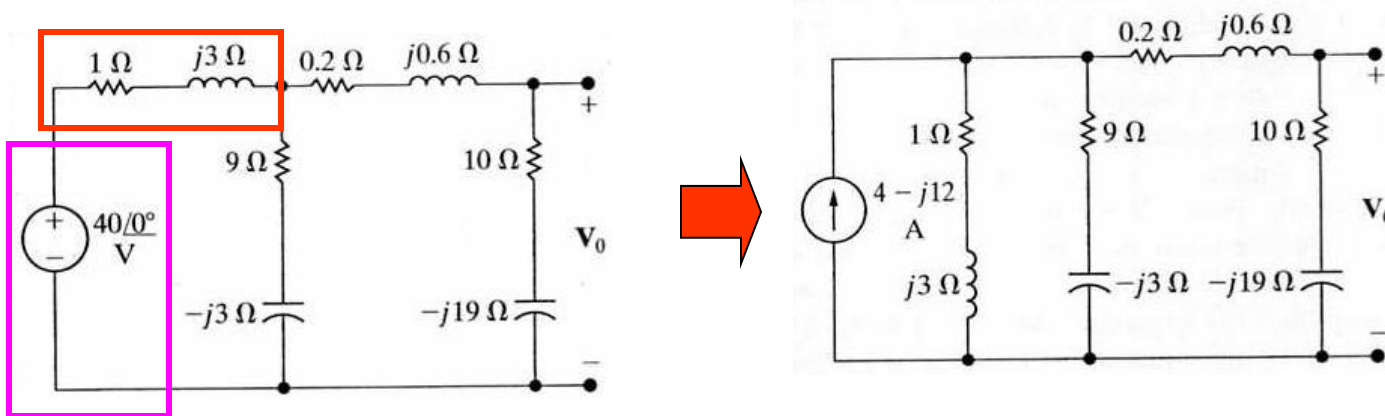**Example 9.9** Use the concept of source transformation to find the phasor voltage  $V_0$  in the circuit shown



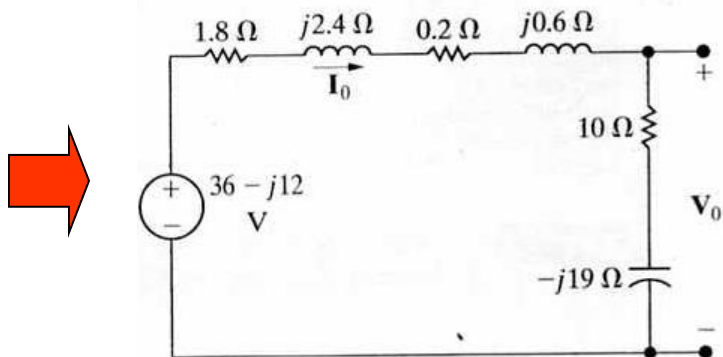
$$Z = \frac{(1 + j3)(9 - j3)}{10} = 1.8 + j2.4 \Omega,$$




$$\begin{aligned} I_0 &= \frac{36 - j12}{12 - j16} = \frac{12(3 - j1)}{4(3 - j4)} \\ &= \frac{39 + j27}{25} = 1.56 + j1.08 \text{ A.} \end{aligned}$$

$$V_0 = (1.56 + j1.08)(10 - j19) = 36.12 - j18.84 \text{ V}$$

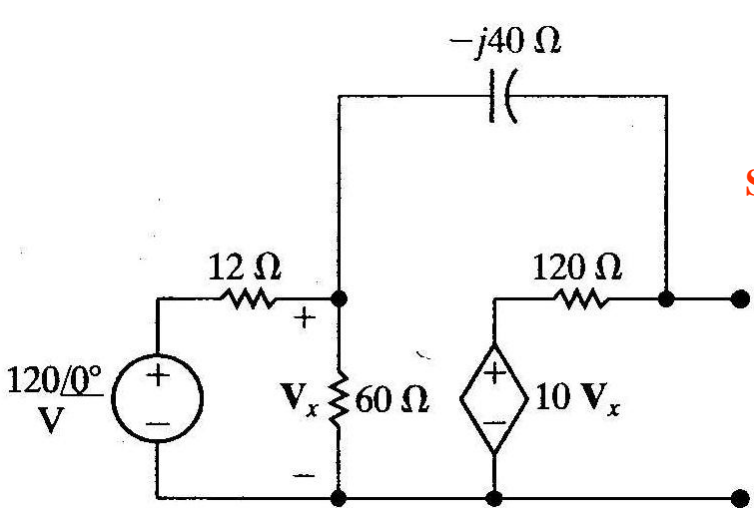**Example 9.10** Find the Thévenin equivalent circuit with respect to terminals a,b for the circuit shown



**Source Transformation**

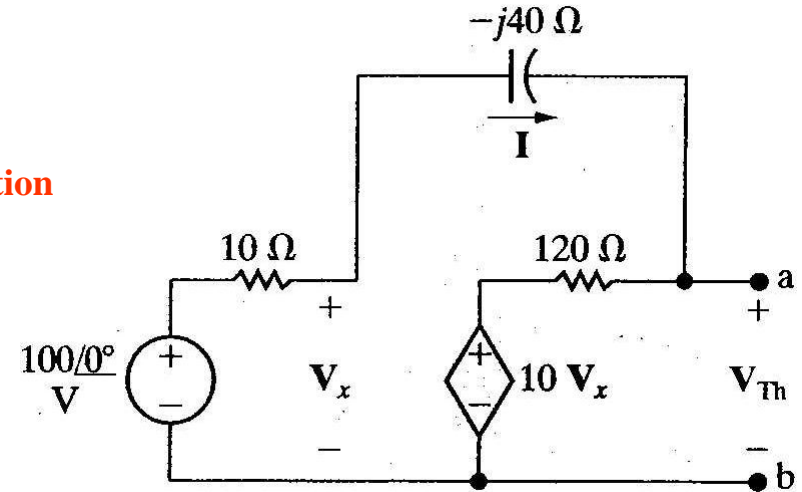

$$100 = 10I - j40I + 120I + 10V_x = (130 - j40)I + 10V_x$$



Since  $V_x = 100 - 10I$  then  $I = 18 \angle -126.87^\circ \text{ A}$

→  $V_x = 100 - 180 \angle -126.87^\circ = 208 + j144 \text{ V}$

→  $V_{Th} = 10V_x + 120I = 835.22 \angle -20.17^\circ \text{ V}$

**Next we find the Thevenin Impedance**

# Thevenin Impedance

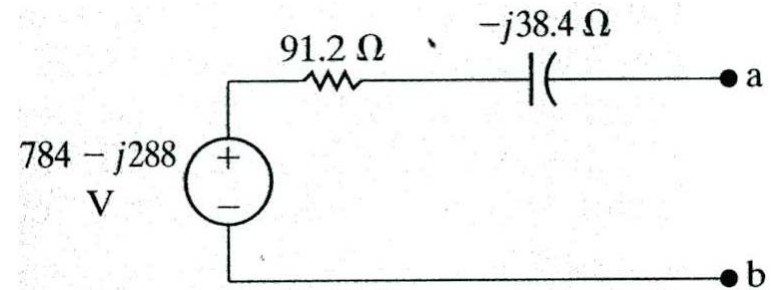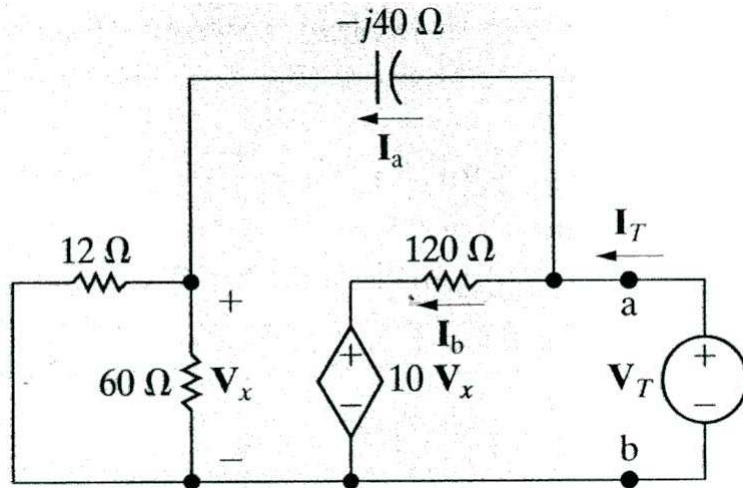


$$Z_{Th} = \frac{V_T}{I_T} \quad \text{Find } I_T \text{ in terms of } V_T \text{ then form the ratio } \frac{V_T}{I_T}$$

$$I_T = I_a + I_b \quad \text{Find } I_a \text{ and } I_b \text{ in terms of } V_T$$

$$I_a = \frac{V_T}{10 - j40}$$

$$V_x = 10I_a$$
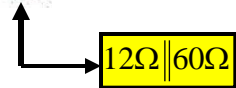
$$I_b = \frac{V_T - 10V_x}{120} = \frac{-V_T(9 + j4)}{120(1 - j4)}$$



$$I_T = I_a + I_b = \frac{V_T}{10 - j40} \left( 1 - \frac{9 + j4}{12} \right) = \frac{V_T(3 - j4)}{12(10 - j40)}$$



$$Z_{Th} = \frac{V_T}{I_T} = 91.2 - j38.4 \Omega$$



## 9.8 The Node-Voltage Method
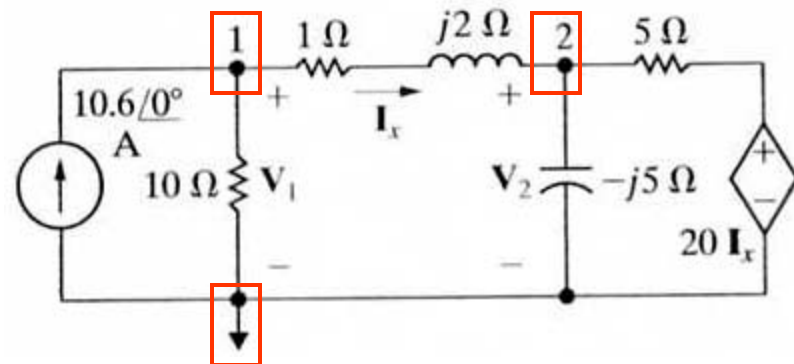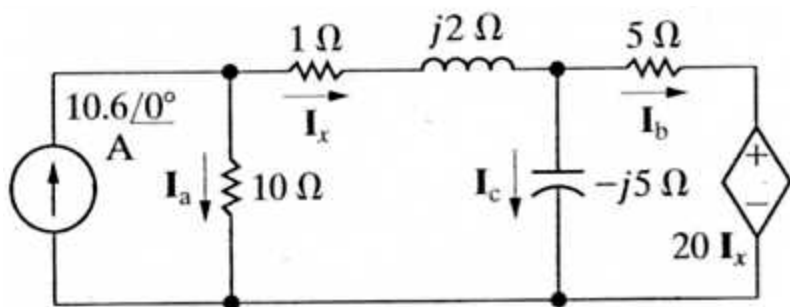
### Example 9.11

Use the node-voltage method to find the branch currents  $I_a$ ,  $I_b$ , and  $I_c$  in the circuit shown



**KCL at node 1**

$$-10.6 + \frac{V_1}{10} + \frac{V_1 - V_2}{1 + j2} = 0$$



$$V_1(1.1 + j0.2) - V_2 = 10.6 + j21.2 \quad (1)$$

**KCL at node 2**

$$\frac{V_2 - V_1}{1 + j2} + \frac{V_2}{-j5} + \frac{V_2 - 20I_x}{5} = 0$$

**Since**

$$I_x = \frac{V_1 - V_2}{1 + j2}$$




$$-5V_1 + (4.8 + j0.6)V_2 = 0 \quad (2)$$

**Two Equations and Two Unknown , solving**

$$V_1 = 68.40 - j16.80 \text{ V}$$

$$V_2 = 68 - j26 \text{ V}$$

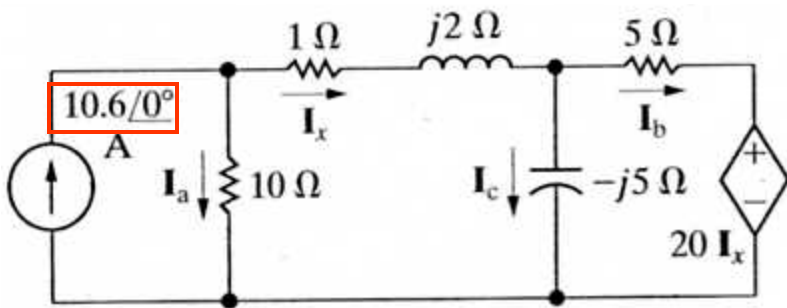

$$V_1 = 68.40 - j16.80 \text{ V}$$

$$V_2 = 68 - j26 \text{ V}$$

$$I_a = \frac{V_1}{10} = 6.84 - j1.68 \text{ A}$$

$$I_x = \frac{V_1 - V_2}{1 + j2} = 3.76 + j1.68 \text{ A}$$

$$I_b = \frac{V_2 - 20I_x}{5} = -1.44 - j11.92 \text{ A}$$

$$I_c = \frac{V_2}{-j5} = 6.84 - j1.68 + 3.76 + j1.68$$

### To Check the work



$$I_a + I_x = 6.84 - j1.68 + 3.76 + j1.68 = 10.6 \text{ A}$$

$$I_x = I_b + I_c = -1.44 - j11.92 + 5.2 + j13.6 = 3.76 + j1.68 \text{ A}$$



## 9.9 The Mesh-Current Method

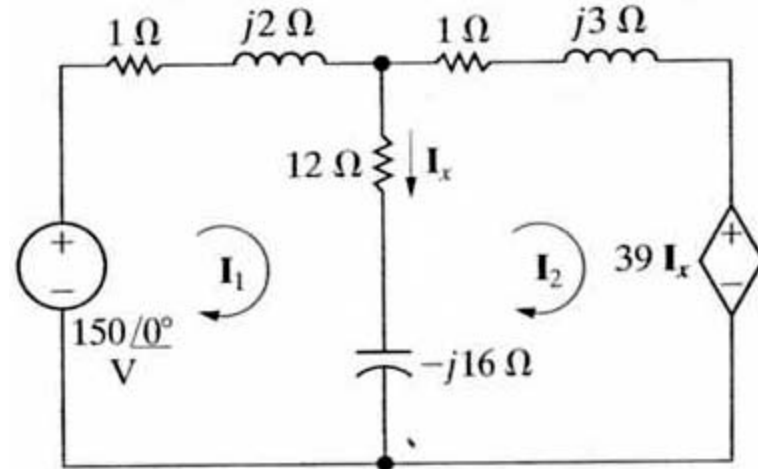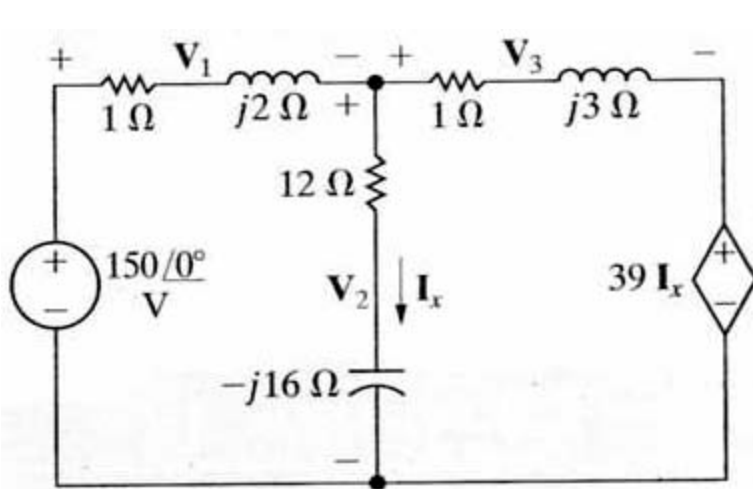**Example 9.12** Use the mesh-current method to find the voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown



**KVL at mesh 1**

$$150 = (1 + j2)I_1 + (12 - j16)(I_1 - I_2) \quad \rightarrow \quad 150 = (13 - j14)I_1 - (12 - j16)I_2$$

**KVL at mesh 2**

$$0 = (12 - j16)(I_2 - I_1) + (1 + j3)I_2 + 39I_x \quad \text{Since } I_x = I_1 - I_2 \quad (1)$$



$$\rightarrow \quad 0 = (27 + j16)I_1 - (26 + j13)I_2 \quad (2)$$

**Two Equations and Two Unknown , solving**

$$I_1 = -26 - j52 \text{ A}$$

$$I_2 = -24 - j58 \text{ A}$$

$$I_x = I_1 - I_2 = -2 + j6 \text{ A}$$

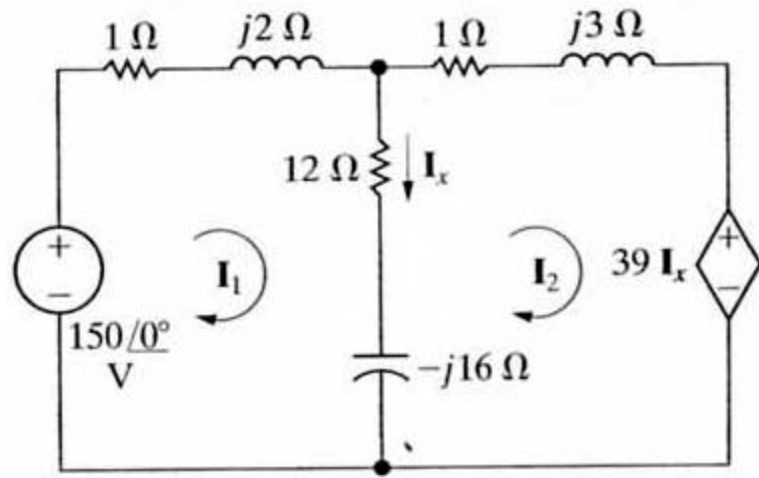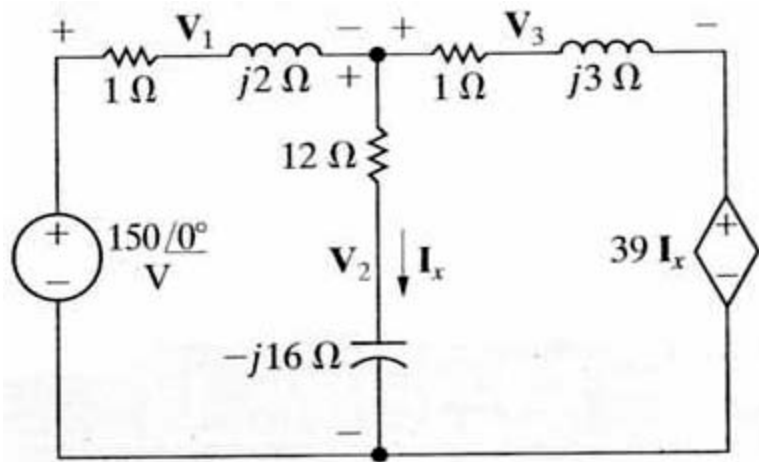

$$\mathbf{I}_1 = -26 - j52 \text{ A}$$

$$\mathbf{I}_2 = -24 - j58 \text{ A}$$

$$\mathbf{I}_x = -2 + j6 \text{ A}$$

$$\mathbf{V}_1 = (1 + j2)\mathbf{I}_1 = 78 - j104 \text{ V}$$

$$\mathbf{V}_2 = (12 - j16)\mathbf{I}_x = 72 + j104 \text{ V}$$

$$\mathbf{V}_3 = (1 + j3)\mathbf{I}_2 = 150 - j130 \text{ V}$$

## 9.12 The Phasor Diagram

the phasor quantities  $10 \angle 30^\circ$ ,  $12 \angle 150^\circ$ ,  $5 \angle -45^\circ$ , and  $8 \angle -170^\circ$

