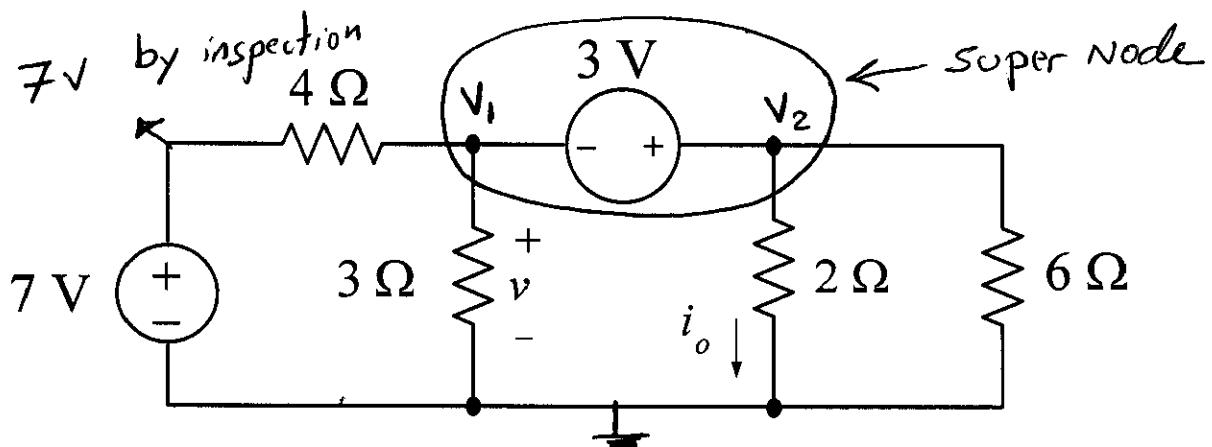


EE 201-06 – Winter 2012(112)  
Quiz 2

SER	ID	NAME	KEY
-----	----	------	-----



For the circuit shown above, using the nodal voltage method division method find  $v$  and  $i_o$ ?

Solution

KCL on Super Node

$$\frac{v_1 - 7}{4} + \frac{v_1}{3} + \frac{v_2}{2} + \frac{v_2}{6} = 0$$

X 12

$$3v_1 - 21 + 4v_1 + 6v_2 + 2v_2 = 0$$

$$7v_1 + 8v_2 = 21 \quad \text{--- (1)}$$

From Super Node       $v_2 - v_1 = 3 \quad \text{--- (2)}$

Solving (1) and (2)  $\Rightarrow v_1 = 12 \cancel{-} - 0.2 \text{ V}$   
 $v_2 = 2.8 \text{ V}$

$$\Rightarrow v = v_2 = -0.2 \text{ V}$$

$$i_o = \frac{v_2}{2} = \frac{2.8}{2} = 1.4 \text{ A}$$