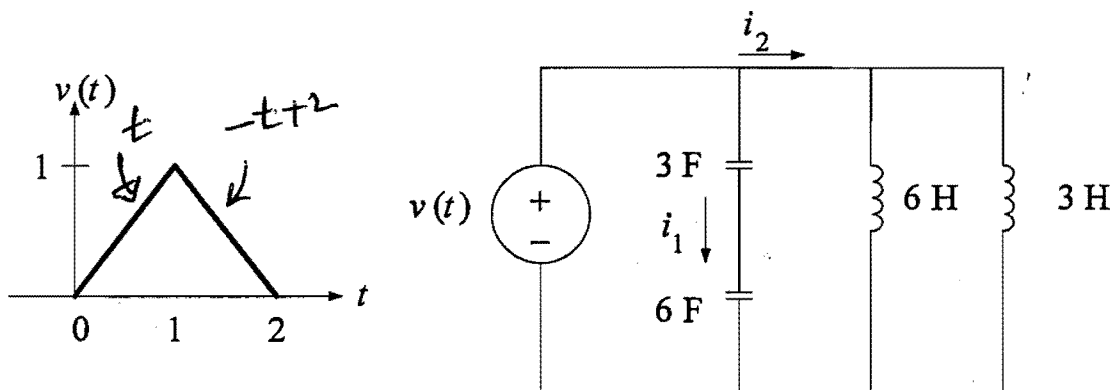



SER	ID	NAME
-----	----	------



For the circuit shown above, find:

(a) $i_1(t)$?

(b) $i_2(t)$?

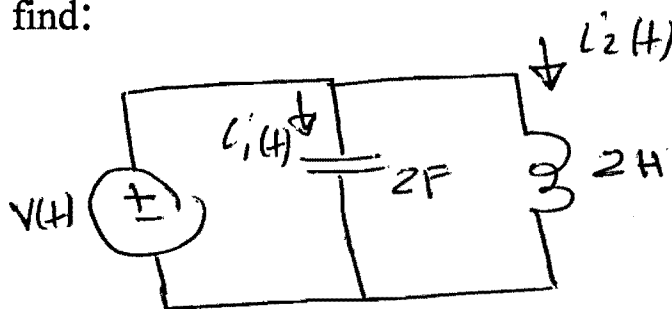

$$(a) \quad i_1(t) = C \frac{dv(t)}{dt} = 2 \begin{cases} 1 & 0 \leq t \leq 1 \\ -1 & 1 \leq t \leq 2 \end{cases}$$

$$= \begin{cases} 2 & 0 \leq t \leq 1 \\ -2 & 1 \leq t \leq 2 \end{cases}$$

$$(b) \quad i_2(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$t \leq 0 \quad i_2(t) = \frac{1}{2} \int_{-\infty}^0 0 d\tau = 0$$

$$\underline{0 < t \leq 1}$$

$$L_2'(t) = \frac{1}{2} \int_0^t t \, d\tau + \underbrace{L_2'(0)}_{= 0} = 0$$
$$= \frac{1}{2} \frac{t^2}{2} + 0 = \frac{t^2}{4}$$

$$\underline{1 \leq t \leq 2}$$

$$L_2'(t) = \frac{1}{2} \int_1^t (2 - \tau) \, d\tau + \underbrace{L_2'(1)}_{= \frac{1}{4}}$$

$$= \frac{1}{2} \left[2\tau - \frac{\tau^2}{2} \right]_1^t + \frac{1}{4}$$

$$= -\frac{t^2}{4} + t - \frac{1}{2}$$

$$\underline{t \geq 2} \quad L_2'(t) = \frac{1}{2} \int_2^t 0 \, d\tau + \underbrace{L_2'(2)}_{= \frac{1}{2}}$$

$$= \frac{1}{2}$$
