

TABLE OF CONTENTS

Expt No.	Title	Page
(1)	Resistor's and Ohm's Law.....	3
(2)	Kirchhoff's Laws.....	7
(3)	Computer Simulation of a D.C. Circuit.....	11
(4)	Current and Voltage Divider Rules.....	13
(5)	Superposition and Thevenin/Norton Theorems	16
(6)	Frequency Domain Analysis.....	20
(7)	Maximum Power Transfer.....	24
(8)	Average and RMS Values.....	28
	Appendix I (RESISTOR COLOR CODE).....	33
	Appendix II (LABORATORY REGULATIONS AND SAFETY RULES)	35