

EE 203 Electronics I

Quiz # 5

Name:

I.D.#

Sec.#04

Sketch a CMOS logic circuit using minimum number of transistors that realize the function: $Y = \overline{A(B + CDE)}$