

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS

Electrical Engineering Department

EE-416 Analog Filter Design

Instructor: Dr. Hussain Alzaher

Quiz # 5

Name: _____

I.D. # _____

Serial #: _____

Find the transfer function of the given circuit.

