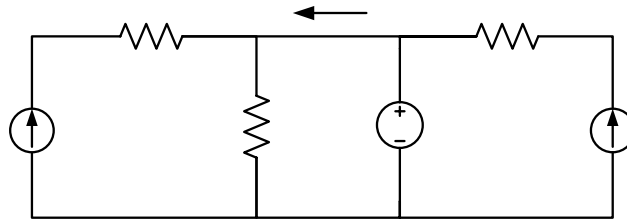


King Fahd University of Petroleum and Minerals
Electrical Engineering Department
EE201 Electric Circuits
Quiz # 1

Name:	I.D#	Sec.# 01
-------	------	----------

For the following single node circuit find,

- (a) Current i
- (b) The power associated with the 2A current source.



2

3A