

King Fahd University of Petroleum & Minerals
Department of Electrical Engineering

EE200-(01/03)

(101)



Homework # 5

1. Problem 4.3(a) in your textbook

Write the Boolean functions for the four outputs in terms of the input variables for the circuit shown in Fig. 4.26(section 4.11)

2. Problem 4.4(b) in your textbook

Design a combinational circuit with three inputs (x, y, z) and one output (F). The output is 1 when the binary value of the inputs is an odd number.

3. Problem 4.12(a) in your textbook

Design a half subtractor circuit with inputs x and y and outputs Difference (D) and Borrow (B). The circuit subtracts $x - y$ and places the difference in D and the borrow in B.

4. Problem 4.15 in your textbook

Derive the two-level Boolean expression for the output carry C_4 shown in the look ahead carry generator of Fig. 4.12.

5. Problem 4.28 in your textbook

Using a decoder and external gates, design the combinational circuit defined by the following three Boolean functions:

- a. $F_1 = x'y'z' + xz$, $F_2 = xy'z' + x'y$, and $F_3 = x'y'z + xy$
- b. $F_1 = (x + y')z$, $F_2 = y'z' + xy' + yz'$, and $F_3 = (x' + y)z$

4.3 (a) $Y_i = (A_i S' + B_i S)E'$ for $i = 0, 1, 2, 3$

4.4 (b) $F(x, y, z) = \sum(1, 3, 5, 7)$ Using $k - map$ $F = z$

4.12 (a)

x	y	B	D	$D = x'y + xy'$ $B = x'y$
0	0	0	0	
0	1	1	1	
1	0	0	1	
1	1	0	0	

4.15 $C_4 = G_3 + P_3 C_3 = G_3 + P_3(G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0)$


$= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$

4.28 (a)


$$F_1 = x(y + y')z = x'y'z' = \Sigma(0, 5, 7)$$

$$F_2 = xy'z' + x'y + x'y(z + z') = \Sigma(2, 3, 4)$$

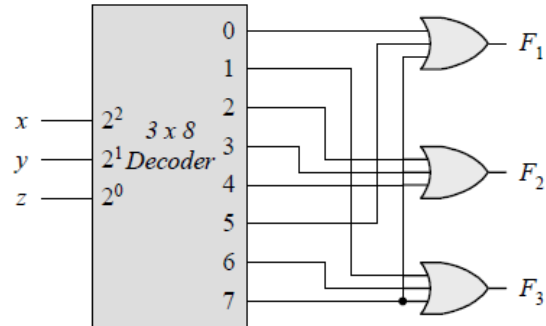
$$F_3 = x'y'z + xy(z + z') = \Sigma(1, 6, 7)$$





(b)

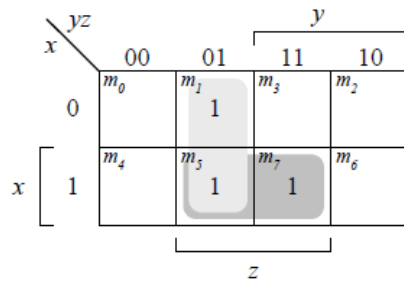

$$F_1 = y'z + xz = \Sigma(1, 5, 7)$$

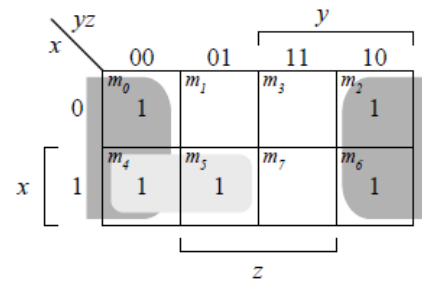
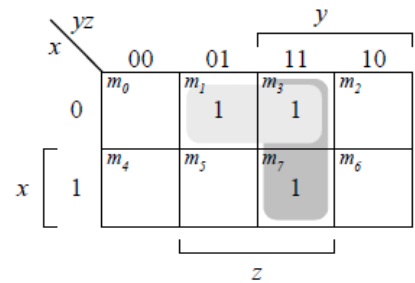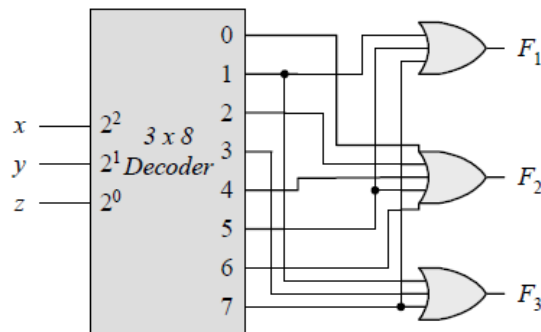
$$F_2 = y'z' + xy' + yz' = \Sigma(0, 2, 4, 5, 6)$$



$$F_3 = x'z + yz = \Sigma(1, 3, 7)$$