

**King Fahd University of Petroleum & Minerals**

Electrical Engineering Department

EE205: Electric Circuits II

**Dr. Ali Muqaibel**

HW2 : Natural & Step Response of RLC Circuits


**Problem 1:**

The current in the circuit in the figure is known to be

$$i(t) = B_1 e^{-80t} \cos 60t + B_2 e^{-80t} \sin 60t, t \geq 0.$$


The capacitor has a value of  $500\mu\text{F}$ ; the initial value of the current is zero, and the initial voltage on the capacitor is  $1\text{V}$ .

**Find the values of  $R, L, B_1,$  and  $B_2$ .**

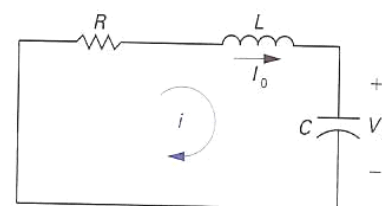


**Problem 2:**

The shown circuit has two switches which moves together (one opens and the other closes at the same time  $t=0$ ). Assume the circuit has been in the same condition for long time before switching at  $t=0$ . Find  $v_o(t)$  for  $t \geq 0$

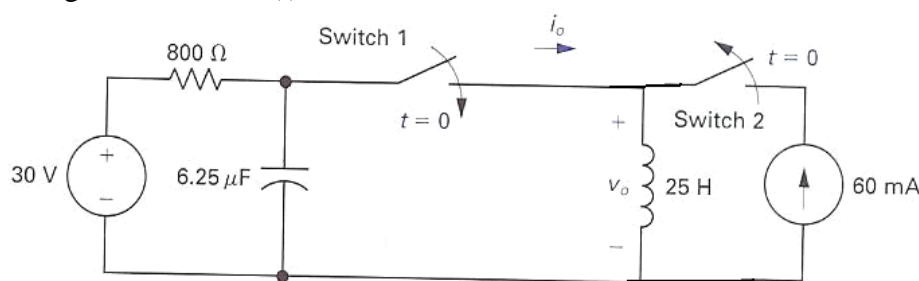

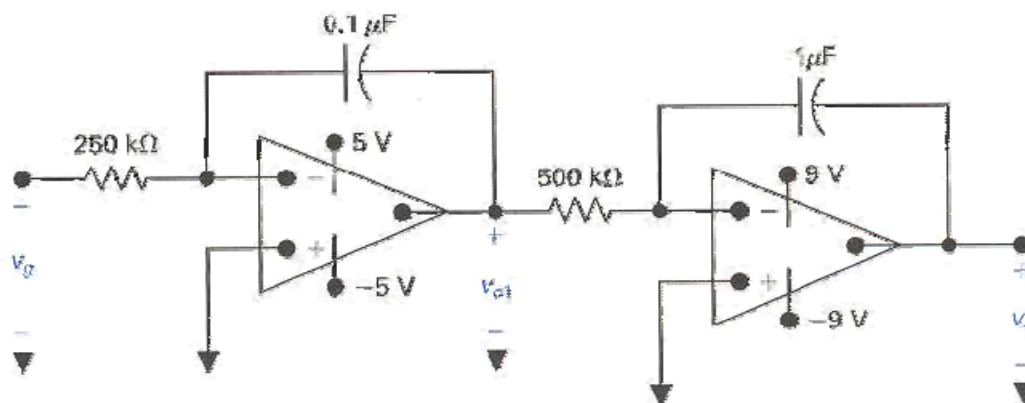**Problem 3:**

For the circuit shown in the Figure, the input voltage  $v_g$  jumps instantaneously from 0 to 25 mV



a) For the circuit shown in the figure. If  $v_{o1}(0)= 5\text{ V}$  and  $v_o(0)= 8\text{ V}$ , **show** that the equation for  $v_o(t)$  for  $0 \leq t < t_{sat}$  is given by

$$v_o(t) = t^2 - 10t + 8 \quad \text{V}$$

show details

b) How long is it before the circuit saturates?