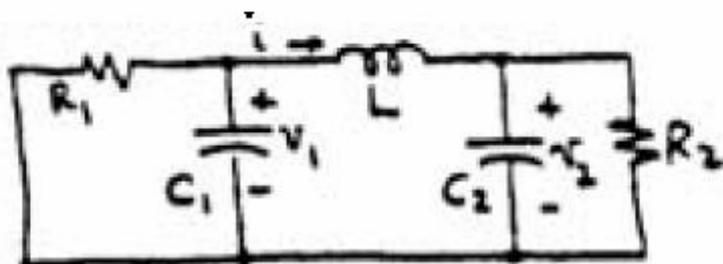


7.6



By KVL,

$$L \frac{di}{dt} + v_2 - v_1 = 0$$

$$\frac{di}{dt} = \frac{1}{L} v_1 - \frac{1}{L} v_2$$

By KCL,

$$C_1 \frac{dv_1}{dt} + \frac{v_1}{R} + i = 0$$


$$\frac{dv_1}{dt} = -\frac{1}{C_1} i - \frac{1}{RC_1} v_1$$

By KCL,

$$C_2 \frac{dv_2}{dt} + \frac{v_2}{R_2} = i$$

$$\frac{dv_2}{dt} = +\frac{1}{C_2} i - \frac{1}{R_2 C_2} v_2$$

7.9

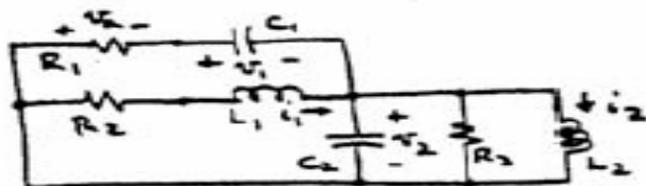

By KVL,

$$L_1 \frac{di_1}{dt} + v_2 + R_3 i_1 = 0$$

$$\frac{di_1}{dt} = -\frac{R_3}{L_1} i_1 - \frac{1}{L_1} v_2$$

By KVL,

$$L_2 \frac{di_2}{dt} = v_2$$

$$\frac{di_2}{dt} = \frac{1}{L_2} v_2$$

By KCL,


$$C_2 \frac{dv_2}{dt} + \frac{v_2}{R_3} + i_2 = i_1 + \frac{v_2}{R_1} = i_1 + \frac{-v_2 - v_1}{R_1}$$

$$C_2 \frac{dv_2}{dt} = i_1 - \frac{1}{R_1} v_1 - \left(\frac{1}{R_1} + \frac{1}{R_3}\right) v_2 - i_2$$

$$\frac{dv_2}{dt} = \frac{1}{C_2} i_1 - \frac{1}{C_2} i_2 - \frac{1}{R_1 C_2} v_1 - \left(\frac{1}{R_1 C_2} + \frac{1}{R_3 C_2}\right) v_2$$

By KCL, $C_1 \frac{dv_1}{dt} = \frac{v_1}{R_1} = -\frac{v_1 - v_2}{R_1} \Rightarrow \frac{dv_1}{dt} = -\frac{1}{R_1 C_1} v_1 - \frac{1}{R_1 C_1} v_2$
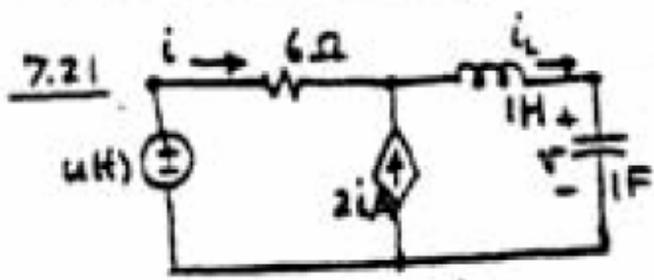
$$\frac{d}{dt} \begin{bmatrix} i_1 \\ i_2 \\ v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -\frac{R_3}{L_1} & 0 & 0 & -\frac{1}{L_1} \\ 0 & 0 & 0 & \frac{1}{L_2} \\ 0 & 0 & -\frac{1}{R_1 C_1} & -\frac{1}{R_1 C_1} \\ \frac{1}{C_2} & -\frac{1}{C_2} & -\frac{1}{R_1 C_2} & -\frac{1}{R_3 C_2} - \frac{1}{R_1 C_2} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ v_1 \\ v_2 \end{bmatrix}$$



By KCL, $i_L = 1 \frac{dv}{dt}$
 $\frac{dv}{dt} = i_L$


By KCL, $2i = i_L \Rightarrow i_L/3 = i$

By KVL,
 $u(t) = 6i + 1 \frac{di_L}{dt} + v$

$u(t) = 2i_L + \frac{di_L}{dt} + v$

$\frac{di_L}{dt} = -2i_L - v + u(t)$
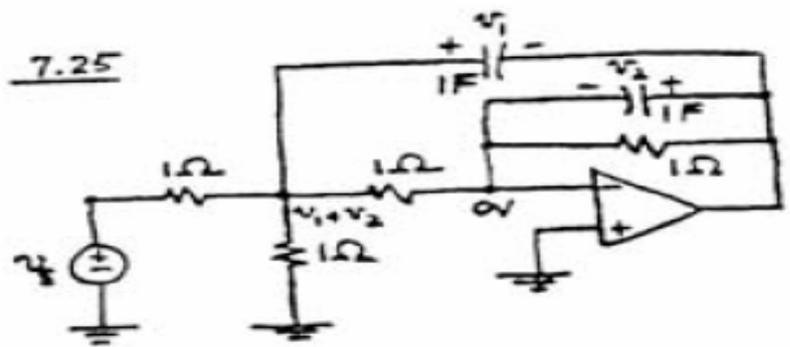
$$\frac{d}{dt} \begin{bmatrix} i_L \\ v \end{bmatrix} = \begin{bmatrix} -2 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u(t)$$



By KCL, $\frac{(v_1+v_2)-v_3}{1} + \frac{v_1+v_2}{1} + \frac{v_1+v_2}{1} + 1 \frac{dv_1}{dt} = 0$

$\frac{dv_1}{dt} = -3v_1 - 3v_2 + v_3$

By KCL, $\frac{v_1+v_2}{1} + \frac{v_2}{1} + 1 \frac{dv_2}{dt} = 0$

$\frac{dv_2}{dt} = -v_1 - 2v_2$

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -3 & -3 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} v_3$$

$$\frac{d}{dt} \begin{bmatrix} i_1 \\ v \end{bmatrix} = \begin{bmatrix} -\frac{24}{37} & -\frac{66}{37} \\ \frac{27}{37} & -\frac{9}{37} \end{bmatrix} \begin{bmatrix} i_1 \\ v \end{bmatrix} + \begin{bmatrix} \frac{60}{37} \\ -\frac{12}{37} \end{bmatrix} v_s$$



1. 4Ω resistor chosen for tree

2. i_1 and v are the state variables. v_1 and i_2 are assigned.

3. KVL: $\frac{1}{2} \frac{di_1}{dt} + v - v_1 = 0 \Rightarrow \frac{di_1}{dt} = -2v + 2v_1$

4. KCL: $\frac{1}{3} \frac{dv}{dt} + 4i = i_1 + i_2 \Rightarrow \frac{dv}{dt} = -12i + 3i_1 + 3i_2$

5. KVL: $2i + v_1 - v_s = 0 \Rightarrow 2i + v_1 = v_s$

$3i_2 + v - v_1 = 0 \Rightarrow 3i_2 - v_1 = -v$

6. KCL: $i + 4i = i_1 + i_2 + \frac{v}{4} \Rightarrow 20i - 4i_2 - v_1 = 4i_1$

7. $\Delta = \begin{vmatrix} 2 & 0 & 1 \\ 0 & 3 & -1 \\ 20 & -4 & -1 \end{vmatrix} = -6 - 60 - 8 = -74$ $\Delta_i = \begin{vmatrix} v_s & 0 & 1 \\ -v & 3 & -1 \\ 4i_1 & -4 & -1 \end{vmatrix} = -3v_s + 4v - 12i_1 - 4v_s = -12i_1 + 4v - 7v_s$

$\Delta_{i_2} = \begin{vmatrix} 2 & v_s & 1 \\ 0 & -v & -1 \\ 20 & 4i_1 & -1 \end{vmatrix} = 2v - 20v_s + 20v + 8i_1 = 8i_1 + 22v - 20v_s$ $\Delta_v = \begin{vmatrix} 2 & 0 & v_s \\ 0 & 3 & -v \\ 20 & -4 & 4i_1 \end{vmatrix} = 24i_1 - 60v_s - 8v$

$i = \frac{\Delta_i}{\Delta} = \frac{12}{74} i_1 - \frac{4}{74} v + \frac{7}{74} v_s$ $i_2 = \frac{\Delta_{i_2}}{\Delta} = -\frac{8}{74} i_1 - \frac{22}{74} v + \frac{20}{74} v_s$


8. $v_1 = \frac{\Delta_{v_1}}{\Delta} = -\frac{24}{74} i_1 + \frac{8}{74} v + \frac{60}{74} v_s$

$\frac{di_1}{dt} = -2v + 2(-\frac{24}{74} i_1 + \frac{8}{74} v + \frac{60}{74} v_s) = -\frac{24}{37} i_1 - \frac{66}{37} v + \frac{60}{37} v_s = \frac{di_1}{dt}$

$\frac{dv}{dt} = -12(\frac{12}{74} i_1 - \frac{4}{74} v + \frac{7}{74} v_s) + 3(-\frac{8}{74} i_1 - \frac{22}{74} v + \frac{20}{74} v_s)$

$= -\frac{144}{74} i_1 + \frac{48}{74} v - \frac{84}{74} v_s + \frac{332}{74} i_1 - \frac{24}{74} i_1 - \frac{66}{74} v + \frac{60}{74} v_s$

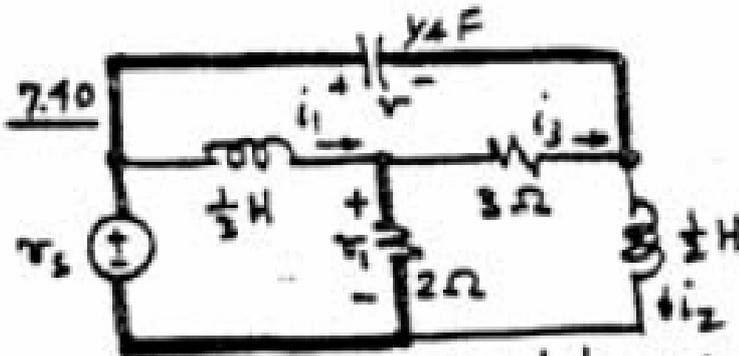$\frac{dv}{dt} = \frac{54}{37} i_1 - \frac{18}{37} v - \frac{24}{37} v_s = \frac{27}{37} i_1 - \frac{9}{37} v - \frac{12}{37} v_s = \frac{dv}{dt}$



1. 2Ω resistor
chosen for tree

2. i_1, i_2 and v are the state variables. i_2 and v_1 are assigned.

3. KVL: $\frac{1}{2} \frac{di_1}{dt} + v_1 - v_s = 0 \Rightarrow \frac{di_1}{dt} = -3v_1 + 3v_s$

$\frac{1}{2} \frac{di_2}{dt} - v_s + v = 0 \Rightarrow \frac{di_2}{dt} = -2v + 2v_s$

4. KCL: $\frac{1}{4} \frac{dv}{dt} + i_3 = i_2 \Rightarrow \frac{dv}{dt} = 4i_2 - 4i_3$

5. KVL: $3i_3 - v + v_s - v_1 = 0 \Rightarrow 3i_3 - v_1 = v - v_s$

6. KCL: $i_1 = \frac{v}{2} + i_3 \Rightarrow 2i_3 + v_1 = 2i_1$

$5i_3 = 2i_1 + v - v_s$

$i_3 = \frac{2}{5}i_1 + \frac{1}{5}v - \frac{1}{5}v_s$

$v_1 = 2i_1 - 2i_3$
 $= 2i_1 - 2\left(\frac{2}{5}i_1 + \frac{1}{5}v - \frac{1}{5}v_s\right)$

$v_1 = \frac{2}{5}i_1 - \frac{2}{5}v + \frac{2}{5}v_s$

8. $\frac{di_1}{dt} = -3\left(\frac{2}{5}i_1 - \frac{2}{5}v + \frac{2}{5}v_s\right) + 3v_s = -\frac{6}{5}i_1 + \frac{6}{5}v + \frac{3}{5}v_s = \frac{di_1}{dt}$

$\frac{dv}{dt} = 4i_2 - 4\left(\frac{2}{5}i_1 + \frac{1}{5}v - \frac{1}{5}v_s\right) = -\frac{8}{5}i_1 + 4i_2 - \frac{4}{5}v + \frac{4}{5}v_s = \frac{dv}{dt}$

$$\frac{d}{dt} \begin{bmatrix} i_1 \\ i_2 \\ v \end{bmatrix} = \begin{bmatrix} -\frac{6}{5} & 0 & 0 \\ 0 & 4 & 0 \\ -\frac{8}{5} & 0 & -\frac{4}{5} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ v \end{bmatrix} + \begin{bmatrix} \frac{3}{5} \\ 0 \\ \frac{4}{5} \end{bmatrix} v_s$$