

KFUPM-EE DEPT.
EE205: Circuits II-082
HW # 2: Due:

Problem 1:

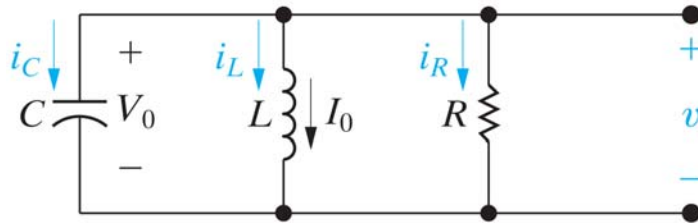


Figure: 08-01
Copyright © 2008 Pearson Prentice Hall, Inc.

The resistance, inductance, and capacitance in a parallel RLC circuit are 5000Ω , 1.25 H , and 8 nF , respectively.

- a) Calculate the roots of the characteristic equation that describe the voltage response of the circuit.
- b) Will the response be over-, under-, or critically damped?
- c) What value of R will yield a damped frequency of 6 krad/s ?
- d) What are the roots of the characteristic equation for the value of R found in (c) ?
- e) What value of R will result in a critically damped response?

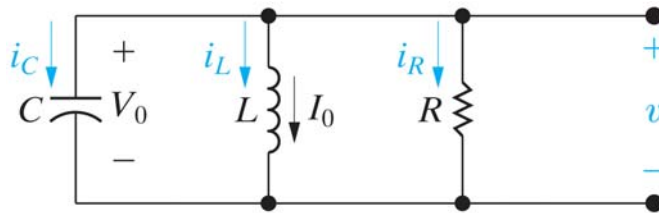
Problem 2:

Figure: 08-01
Copyright © 2008 Pearson Prentice Hall, Inc.

The initial value of the voltage v in the above circuit is zero, and the initial value of the capacitor current, $i_c(0^+)$ is 15 mA. The expression for the capacitor current is known to be:

$$i_c(t) = A_1 e^{-160t} + A_2 e^{-40t}, \quad t \geq 0^+$$

Where R is 200Ω .

- a) Find the value of α , ω_0 , L , C , A_1 , and A_2

$$\left(\text{Hint: } \frac{di_C(0)}{dt} = -\frac{di_L(0)}{dt} - \frac{di_R(0)}{dt} = \frac{v(0)}{L} - \frac{1}{R} i_C(0^+) \right)$$

- b) Find the expression for $v(t)$, $t \geq 0$
- c) Find the expression for $i_R(t)$, $t \geq 0$
- d) Find the expression for $i_L(t)$, $t \geq 0$

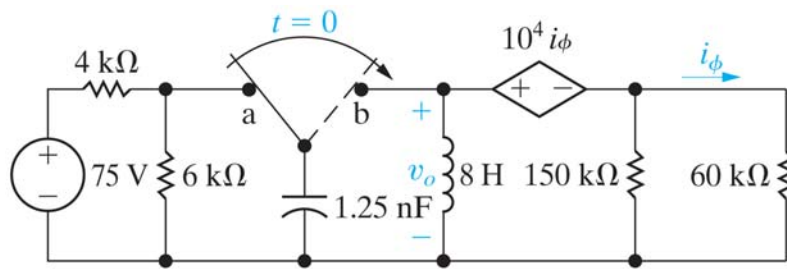
Problem 3:

Figure: 08-21-01P8.16

Copyright © 2008 Pearson Prentice Hall, Inc.

The switch in the above circuit has been in position for a long time. At $t = 0$, the switch moves instantaneously to position b. Find $v_o(t)$ for $t \geq 0$.

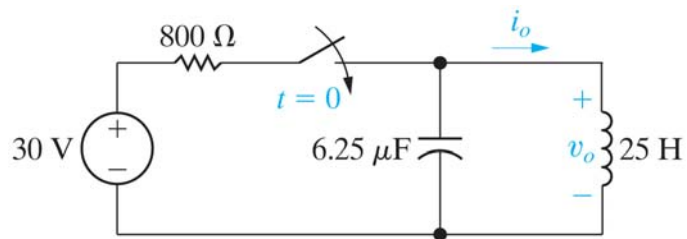
Problem 4:

Figure: 08-21-05P8.30

Copyright © 2008 Pearson Prentice Hall, Inc.

There is no energy stored in the circuit in the above Figure when the switch is closed at $t=0$. Find $v_o(t)$ for $t \geq 0$.

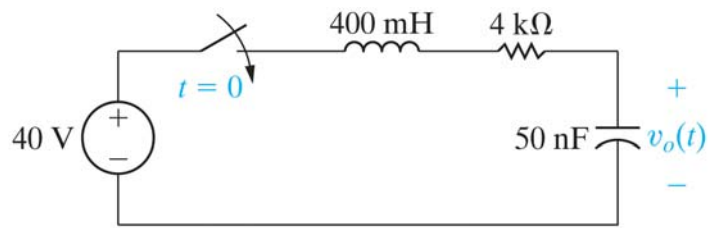
Problem 5:

Figure: 08-21-16P8.45

Copyright © 2008 Pearson Prentice Hall, Inc.

The initial energy stored in the circuit in the above Figure is zero, Find $v_o(t)$ for $t \geq 0$.