

KFUPM-EE DEPT.  
EE205: Circuits II-082  
**HW # 2: Solution**

Problem 1:

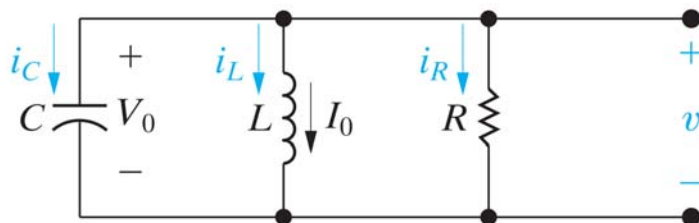


Figure: 08-01  
Copyright © 2008 Pearson Prentice Hall, Inc.

The resistance, inductance, and capacitance in a parallel RLC circuit are  $5000 \Omega$ ,  $1.25 \text{ H}$ , and  $8 \text{ nF}$ , respectively.

- Calculate the roots of the characteristic equation that describe the voltage response of the circuit.
- Will the response be over-, under-, or critically damped?
- What value of  $R$  will yield a damped frequency of  $6 \text{ krad/s}$ ?
- What are the roots of the characteristic equation for the value of  $R$  found in (c) ?
- What value of  $R$  will result in a critically damped response?

$$[\mathbf{a}] \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(10,000)(8)} = 12,500$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(1.25)(8)} = 10^8$$

$$s_{1,2} = -12,500 \pm \sqrt{(1.5625 - 1)10^8} = -12,500 \pm 7500$$

$$s_1 = -5000 \text{ rad/s}$$

$$s_2 = -20,000 \text{ rad/s}$$

[b] overdamped

$$[\mathbf{c}] \quad \omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \alpha^2 = \omega_o^2 - \omega_d^2 = 10^8 - 36 \times 10^6 = 0.64 \times 10^8$$

$$\alpha = 0.8 \times 10^4 = 8000$$

$$\frac{1}{2RC} = 8000; \quad \therefore R = \frac{10^9}{(16,000)(8)} = 7812.5 \Omega$$

$$[\mathbf{d}] \quad s_1 = -8000 + j6000 \text{ rad/s}; \quad s_2 = -8000 - j6000 \text{ rad/s}$$

$$[\mathbf{e}] \quad \alpha = 10^4 = \frac{1}{2RC}; \quad \therefore R = \frac{1}{2C(10^4)} = 6250 \Omega$$

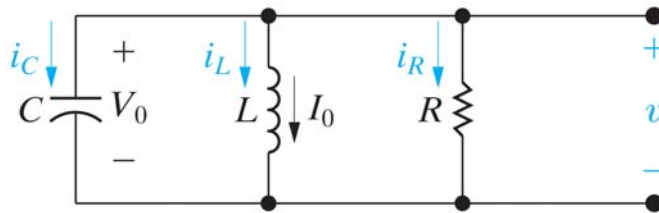
**Problem 2:**

Figure: 08-01  
Copyright © 2008 Pearson Prentice Hall, Inc.

The initial value of the voltage  $v$  in the above circuit is zero, and the initial value of the capacitor current,  $i_c(0^+)$  is 15 mA. The expression for the capacitor current is known to be:

$$i_c(t) = A_1 e^{-160t} + A_2 e^{-40t}, \quad t \geq 0^+$$

Where  $R$  is  $200 \Omega$ .

- a) Find the value of  $\alpha$ ,  $\omega_0$ ,  $L$ ,  $C$ ,  $A_1$ , and  $A_2$

$$\left( \text{Hint: } \frac{di_C(0)}{dt} = -\frac{di_L(0)}{dt} - \frac{di_R(0)}{dt} = \frac{v(0)}{L} - \frac{1}{R} i_C(0^+) \right)$$

- b) Find the expression for  $v(t)$ ,  $t \geq 0$   
 c) Find the expression for  $i_R(t)$ ,  $t \geq 0$   
 d) Find the expression for  $i_L(t)$ ,  $t \geq 0$

$$[\mathbf{a}] \quad 2\alpha = 200; \quad \alpha = 100 \text{ rad/s}$$

$$2\sqrt{\alpha^2 - \omega_0^2} = 120; \quad \omega_0 = 80 \text{ rad/s}$$

$$C = \frac{1}{2\alpha R} = \frac{1}{200(200)} = 25 \mu\text{F}$$

$$L = \frac{1}{\omega_0^2 C} = \frac{10^6}{(80)^2(25)} = 6.25 \text{ H}$$

$$i_C(0^+) = A_1 + A_2 = 15 \text{ mA}$$

$$\frac{di_C}{dt} + \frac{di_L}{dt} + \frac{di_R}{dt} = 0$$

$$\frac{di_C(0)}{dt} = -\frac{di_L(0)}{dt} - \frac{di_R(0)}{dt}$$

$$\frac{di_L(0)}{dt} = \frac{0}{6.25} = 0 \text{ A/s}$$

$$\frac{di_R(0)}{dt} = \frac{1}{R} \frac{dv(0)}{dt} = \frac{1}{R} \frac{i_C(0)}{C} = \frac{15 \times 10^{-3}}{(200)(25 \times 10^{-6})} = 3 \text{ A/s}$$

$$\therefore \frac{di_C(0)}{dt} = -3 \text{ A/s}$$

$$\therefore 160A_1 + 40A_2 = 3$$

$$4A_1 + A_2 = 75 \times 10^{-3}; \quad \therefore A_1 = 20 \text{ mA}; \quad A_2 = -5 \text{ mA}$$

$$\therefore i_C = 20e^{-160t} - 5e^{-40t} \text{ mA}, \quad t \geq 0$$

[b] By hypothesis

$$v = A_3e^{-160t} + A_4e^{-40t}, \quad t \geq 0$$

$$v(0) = A_3 + A_4 = 0$$

$$\frac{dv(0)}{dt} = \frac{15 \times 10^{-3}}{25 \times 10^{-6}} = 600 \text{ V/s}$$

$$-160A_3 - 40A_4 = 600; \quad \therefore A_3 = -5 \text{ V}; \quad A_4 = 5 \text{ V}$$

$$v = -5e^{-160t} + 5e^{-40t} \text{ V}, \quad t \geq 0$$

$$[c] i_R(t) = \frac{v}{200} = -25e^{-160t} + 25e^{-40t} \text{ mA}, \quad t \geq 0^+$$

$$[d] i_L = -i_R - i_C$$

$$i_L = 5e^{-160t} - 20e^{-40t} \text{ mA}, \quad t \geq 0$$

**Problem 3:**


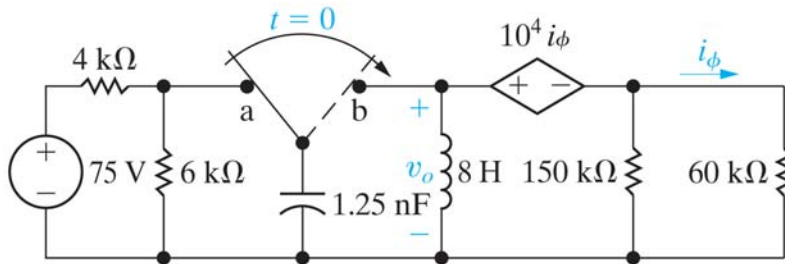


Figure: 08-21-01P8.16

Copyright © 2008 Pearson Prentice Hall, Inc.

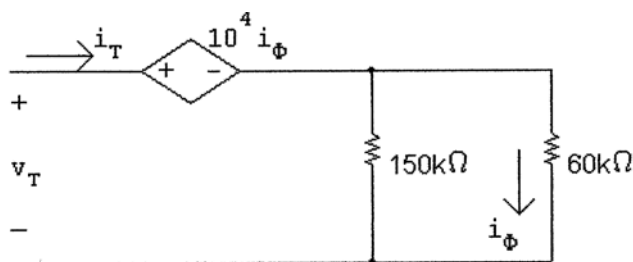The switch in the above circuit has been in position for a long time. At  $t = 0$ , the switch moves instantaneously to position b. Find  $v_o(t)$  for  $t \geq 0$ .



$$v_T = 10^4 i_T \frac{(150 \times 10^3)}{210 \times 10^3} + \frac{(150)(60)10^6}{210 \times 10^3} i_T$$

$$\frac{v_T}{i_T} = \frac{1500 \times 10^3}{210} + \frac{9000 \times 10^3}{210} = \frac{10,500}{210} \times 10^3 = 50 \text{ k}\Omega$$

$$V_o = \frac{75}{10}(6) = 45 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{45}{50,000} = -0.9 \text{ mA}$$

$$\frac{i_C(0)}{C} = \frac{-0.9}{1.25} \times 10^6 = -720 \times 10^3$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(8)(1.25)} = 10^8; \quad \omega_o = 10^4 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(50)(1.25) \times 10^3} = 8000 \text{ rad/s}$$

$$\omega_d = \sqrt{(100 - 64) \times 10^6} = 6000 \text{ rad/s}$$

$$v_o = B_1 e^{-8000t} \cos 6000t + B_2 e^{-8000t} \sin 6000t$$

$$v_o(0) = B_1 = 45 \text{ V}$$

$$\frac{dv_o}{dt}(0) = 6000B_2 - 8000B_1 = -720 \times 10^3$$

$$\therefore 6000B_2 = 8000(45) - 720 \times 10^3; \quad \therefore B_2 = -60 \text{ V}$$

$$v_o = 45e^{-8000t} \cos 6000t - 60e^{-8000t} \sin 6000t \text{ V}, \quad t \geq 0$$

Problem 4:


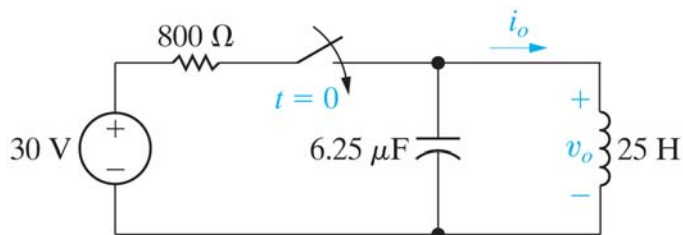


Figure: 08-21-05P8.30

Copyright © 2008 Pearson Prentice Hall, Inc.

There is no energy stored in the circuit in the above Figure when the switch is closed at  $t=0$ . Find  $v_o(t)$  for  $t \geq 0$ .

For  $t > 0$

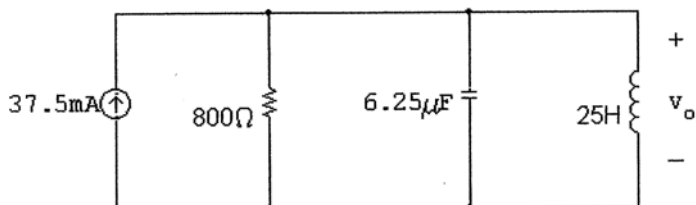

$$\alpha = \frac{1}{2RC} = 100; \quad \frac{1}{LC} = 6400$$

$$s_{1,2} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$V_f = 0; \quad v_o(0^+) = 0; \quad i_C(0^+) = 37.5 \text{ mA}$$

$$\therefore A'_1 + A'_2 = 0$$

$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{6.25 \times 10^{-6}} = 6000 \text{ V/s}$$

$$\frac{dv_o(0^+)}{dt} = -40A'_1 - 160A'_2$$

$$-40A'_1 - 160A'_2 = 6000$$

$$A_1' + 4A_2' = -150$$

$$A_1' + A_2' = 0$$

$$\therefore A_1' = 50 \text{ V}; \quad A_2' = -50 \text{ V}$$

$$v_o = 50e^{-40t} - 50e^{-160t} \text{ V}, \quad t \geq 0$$

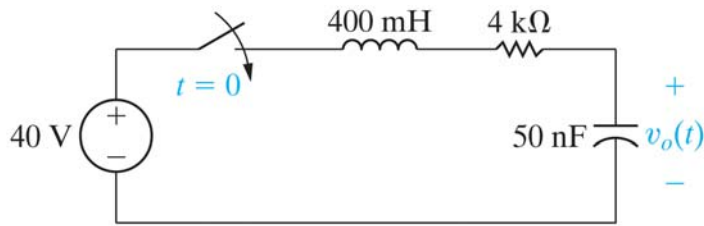
**Problem 5:**

Figure: 08-21-16P8.45

Copyright © 2008 Pearson Prentice Hall, Inc.

The initial energy stored in the circuit in the above Figure is zero, Find  $v_o(t)$  for  $t \geq 0$ .

$$\alpha = \frac{R}{2L} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{20} = 50 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 50 \times 10^6} = -5000 \pm j5000 \text{ rad/s}$$

$$v_o = V_f + B'_1 e^{-5000t} \cos 5000t + B'_2 e^{-5000t} \sin 5000t$$

$$v_o(0) = 0 = V_f + B'_1$$

$$v_o(\infty) = 40 \text{ V}; \quad \therefore B'_1 = -40 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = 5000B'_2 - 5000B'_1$$

$$\therefore B'_2 = B'_1 = -40 \text{ V}$$

$$v_o = 40 - 40e^{-5000t} \cos 5000t - 40e^{-5000t} \sin 5000t \text{ V}, \quad t \geq 0$$