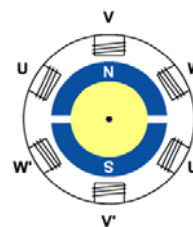




## CH11: Balanced Three-Phase Circuits

-Summary- ver 2.1


Dr. Ali Muqaibel



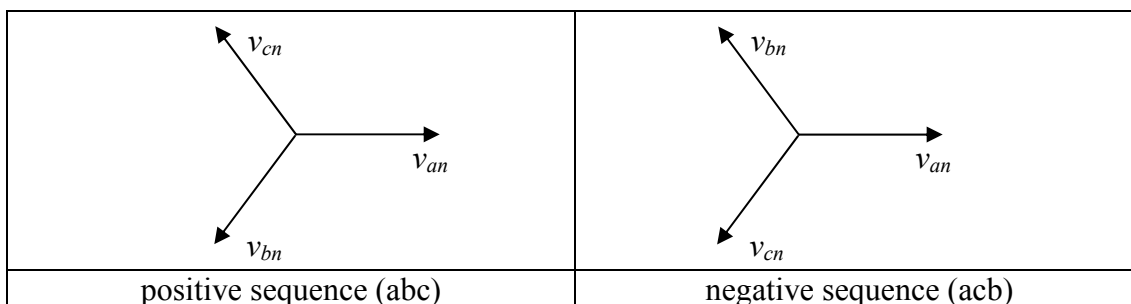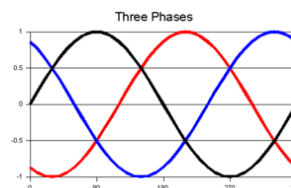- 3Ø circuits are important in power generation, transmission & distribution
- Balanced three – phase voltages or currents must be
  - sinusoidal with same f
  - same amplitude
  - out of phase by 120°



- circuits can operate (connected) in parallel only if they have the same sequence.
- Δ connection ==>  $V_L = V_\phi$
- Y connection ==>  $I_L = I_\phi$
- In balanced 3 Ø current in the neutral  $I_\phi = I_{aA} + I_{bB} + I_{cC} = 0$
- Transform any Δ→Y (if need be)  $Z_Y = Z_\Delta / 3$ .
- For Y-Y:
  - $|V_L| = \sqrt{3} |V_\phi|$
  - $V_L$  leads  $V_\phi$  by 30° for + sequence & lags by 30° for – sequence.

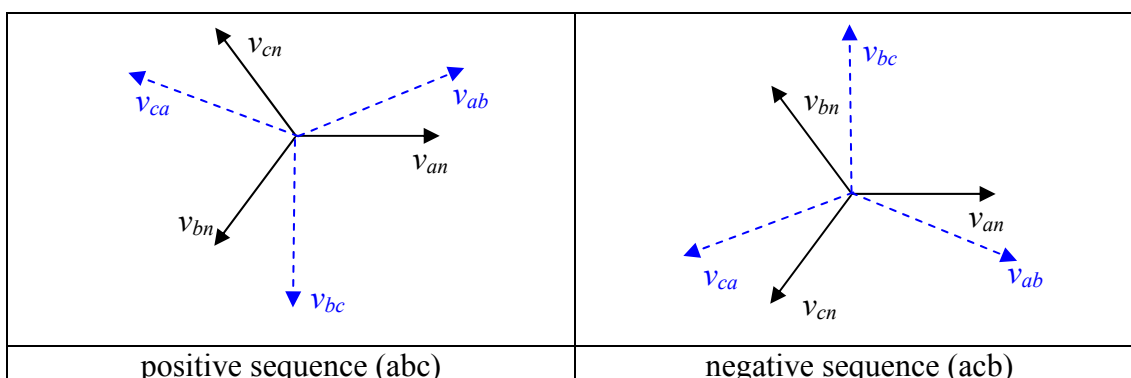

- For Y-Δ
  - Start by Δ →Y transformation (when needed)
  - $|I_L| = \sqrt{3} |I_\phi|$
  - $I_L$  lags  $I_\phi$  by 30° for + sequence and leads by 30° for – sequence
- For a sinusoidal waveform

$$v_{rms} = \frac{|V_{amp}|}{\sqrt{2}}$$

- for balanced 3  $\emptyset$  circuit
  - Average Power (watts)
 
$$P_{\emptyset} = P_A = P_B = P_C = V_{\emptyset} I_{\emptyset} \cos \theta_{\emptyset}, \quad P_T = 3P_{\emptyset}$$


$$P_T = \sqrt{3} V_L I_L \cos \theta_{\emptyset} \quad \dots\dots\dots \text{for Y or } \Delta$$
  - Reactive Power (VARs)
 
$$Q_{\emptyset} = V_{\emptyset} I_{\emptyset} \sin \theta_{\emptyset}$$
  - Complex Power or apparent power (VA)
 
$$S_{\emptyset} = V_{\emptyset} I_{\emptyset}^* = P_{\emptyset} + jQ_{\emptyset}$$

$$S_T = 3S_{\emptyset} = \sqrt{3} V_L I_L [\emptyset_{\emptyset}]$$
- Instantaneous power
 
$$P_T = P_A + P_B + P_C = 1.5 V_m I_m \cos \underline{\theta_{\emptyset}} = 3 V_{\emptyset} I_{\emptyset} \cos \theta_{\emptyset}$$
- Measuring Average Power with Two Wattmeters
 
$$W_1 = V_L I_L \cos(\theta_{\emptyset} + 30)$$

$$W_2 = V_L I_L \cos(\theta_{\emptyset} - 30)$$

$$P_T = W_1 + W_2 = \sqrt{3} V_L I_L \cos \theta_{\emptyset}$$
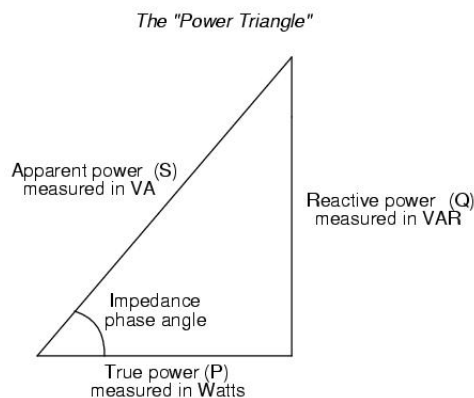
$$Q_T = \sqrt{3}(W_2 - W_1) = \sqrt{3} V_L I_L \sin \theta_{\emptyset}$$
- Capacitor banks can be used to reduce losses and control the voltage level



Note :

- This summary is meant to give an overview and it does **NOT** replace the book
- It is a matter of practice not just knowing the formula.
- Some variables represent vectors and some represent scalar values.

If you have any comment or correction please send to [muqaibel@kfupm.edu.sa](mailto:muqaibel@kfupm.edu.sa)

Prepared by  
Dr. Ali Muqaibel