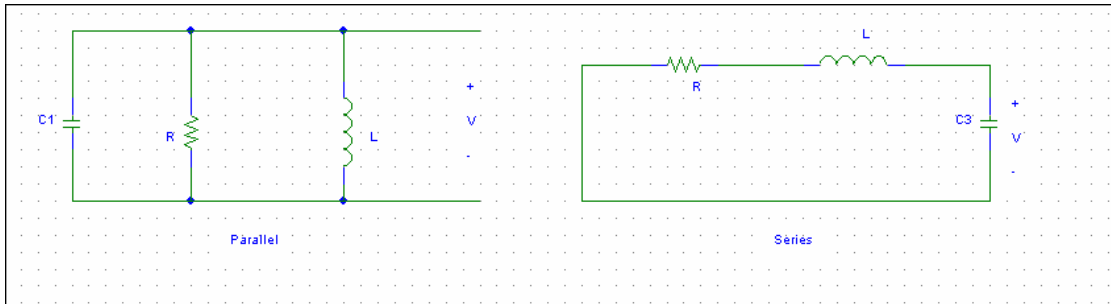


Summary for CH#8
Natural and Step Responses of RLC Circuits

- The **characteristic equation** of the following RLC circuits,



is:

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

where,

$$\alpha = \frac{1}{2RC} \text{ (parallel)}$$

$$\alpha = \frac{R}{2L} \text{ (series)}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ (for parallel \& series)}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$$

- Depending on the values of α^2 & ω_o^2 the natural and step response of the series & parallel RLC circuits can be classified as follow:

Type	Roots ($S_{1,2}$)	Condition
Overdamped	Real, distinct	$\alpha^2 > \omega_o^2$
Underdamped	Complex	$\alpha^2 < \omega_o^2$
Critically damped	Real, repeated	$\alpha^2 = \omega_o^2$


- **For natural response:**

Type	Equations	Initial Conditions
Overdamped	$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$x(0) = A_1 + A_2;$ $\frac{dx}{dt}(0) = \frac{i_c(0)}{C} = A_1 s_1 + A_2 s_2$
Underdamped	$x(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$	$x(0) = B_1;$ $\frac{dx}{dt}(0) = \frac{i_c(0)}{C} = -\alpha B_1 + \omega_d B_2,$ where: $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ (Warning !!)
Critically damped	$x(t) = (D_1 t + D_2) e^{-\alpha t}$	$x(0) = D_2$ $\frac{dx}{dt}(0) = \frac{i_c(0)}{C} = D_1 - \alpha D_2$

- **For step response:** (See examples 8.6-8.10)

Type	Equations	Initial Conditions
Overdamped	$x(t) = X_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}$	$x(0) = X_f + A'_1 + A'_2;$ $\frac{dx}{dt}(0) = \frac{i_c(0)}{C} = A'_1 s_1 + A'_2 s_2$
Underdamped	$x(t) = X_f + (B'_1 \cos \omega_d t + B'_2 \sin \omega_d t) e^{-\alpha t}$	$x(0) = X_f + B'_1;$ $\frac{dx}{dt}(0) = \frac{i_c(0)}{C} = -\alpha B'_1 + \omega_d B'_2,$
Critically damped	$x(t) = X_f + (D'_1 t + D'_2) e^{-\alpha t}$	$x(0) = X_f + D'_2$ $\frac{dx}{dt}(0) = \frac{i_c(0)}{C} = D'_1 - \alpha D'_2$

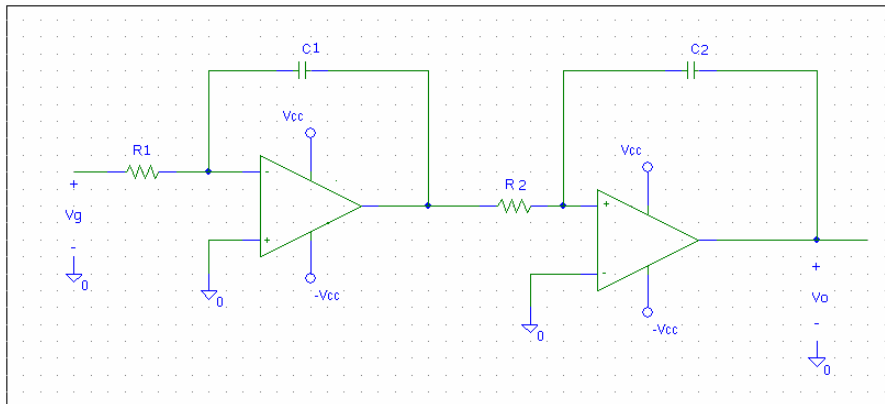Two Integrator Amplifier: (see example 8.13)



Applying KCL at the inverting terminals result in the following:

$$\frac{dv_o}{dt} = -\frac{1}{R_1 C_1} v_g \quad \text{--- 1}$$

$$\frac{dv_o}{dt} = -\frac{1}{R_2 C_2} v_{o1} \quad \text{Differentiating} \quad \Leftrightarrow \quad \frac{d^2 v_o}{dt^2} = -\frac{1}{R_2 C_2} \frac{dv_{o1}}{dt} \quad \text{--- 2}$$

From 1 & 2:

$$\frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g$$

• **Two Integrating Amplifiers with Feedback Resistors:**

The reason for adding the feedback resistors is the fact that the op amp in the integrating amplifier saturates because of the feedback capacitor's accumulation of charge. A resistor is placed in parallel with each feedback capacitor (C1 and C2) to overcome this problem.

$$\frac{d^2 v_o}{dt^2} + \left(\frac{1}{\tau_1} + \frac{1}{\tau_2} \right) \frac{dv_o}{dt} + \left(\frac{1}{\tau_1 \tau_2} \right) v_o = \frac{v_g}{R_a C_1 R_b C_2}$$

The characteristic equation :

$$s^2 + \left(\frac{1}{\tau_1} + \frac{1}{\tau_2} \right) s + \frac{1}{\tau_1 \tau_2} = 0$$

The roots :

$$s_1 = -\frac{1}{\tau_1}; s_2 = -\frac{1}{\tau_2}$$

Example 8.14 illustrates the analysis of the step response of two cascaded integrating amplifiers when the feedback capacitors are shunted with feedback resistors.