

**King Fahd University of Petroleum & Minerals**  
 Electrical Engineering Department  
 EE205: Electric Circuits II (031)

**Quiz 5**


Name: *KEY assume you know the approximation formula* ID#

Sec 01

For the practical tank circuit shown in the figure

$$R=0.002 \Omega, L=2 \text{ H, and } C=\frac{1}{50} \text{ F}$$

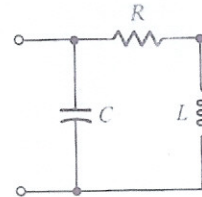- Find the resonance frequency of the circuit
- Find the quality factor of the circuit



a) *Assume high Quality coil*


$$\omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \cdot \frac{1}{50}}} = \boxed{5 \text{ rad/s}}$$

*CHECK the assumption.*

$$Q_{\text{coil}} = \frac{|X_s|}{R_s} = \frac{\omega L}{R_s} = \frac{5(2)}{0.002} = 5000 \gg 1 \text{ assumption is good.}$$

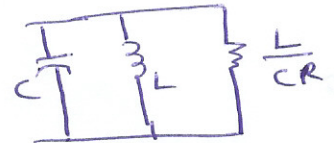b) *We can approximate the circuit to*

$$\text{the new } R_{\text{new}} = \frac{L}{CR} = \frac{2}{\frac{1}{50}(0.002)} = 50 \text{ k}\Omega$$



$$Q_{\parallel} = \omega_r RC = (5)(50 \text{ k})(\frac{1}{50}) = \boxed{5000}$$