
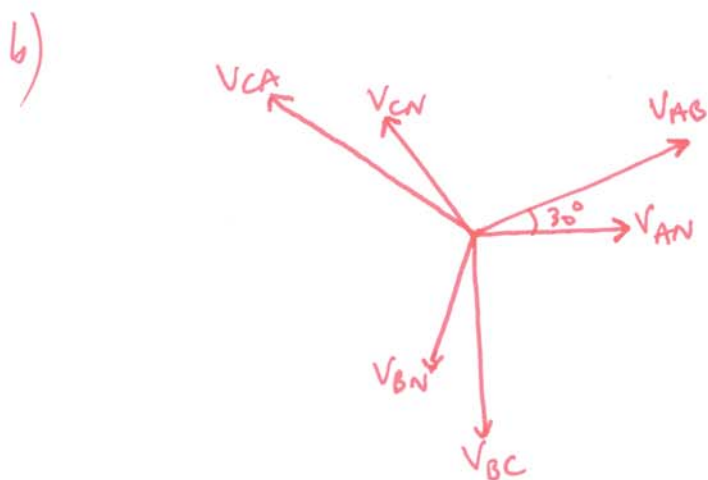


EE205 MT1

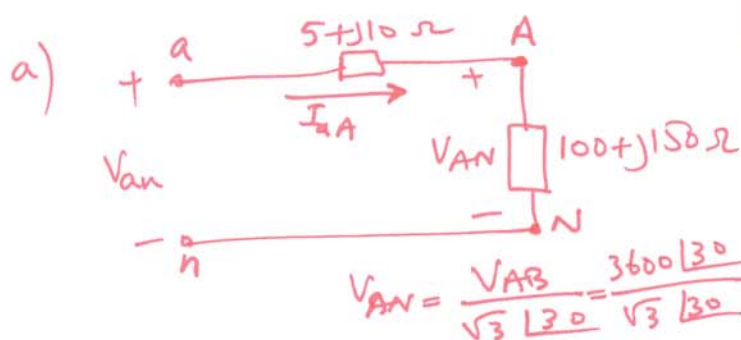Problem 1: [15 points]

A balanced three-phase load, Y-connected is $100 + j150 \Omega / \Phi$. The load is fed from a Y-connected source through a line that has an impedance of $5 + j10 \Omega / \Phi$. The Line-to-Line voltage V_{AB} at the Load terminals is $3600 \angle 30^\circ$ V. Assume a positive sequence.

- Construct the a-phase equivalent circuit of the system. Show all the details. [2pts]
- Draw the phasor diagram showing all phase voltages and Line voltages at the Load side. [3pts]
- Using the single phase equivalent circuit, calculate the line currents I_{aA} , I_{bB} , I_{cC} ? [3pts]
- Calculate the line voltage V_{ab} at the source? [3pts]
- Find the load complex power. [2pts]
- What is the efficiency of the system? (i.e. the ratio of the load real power to the source real power.) [2pts]



c)

$$I_{aA} = \frac{V_{AN}}{Z_{\phi}} = \frac{2078.5 \angle 0^\circ}{100 + j150} = \frac{2078.5}{180.28 \angle 56.31^\circ} = 11.53 \angle -56.31^\circ \text{ A}$$

$$I_{bB} = 11.53 \angle -176.31^\circ \text{ A}$$

$$I_{cC} = 11.53 \angle 63.69^\circ \text{ A}$$

d)

$$V_{ab} = \sqrt{3} \angle 30^\circ V_{an}$$

$$= \sqrt{3} \angle 30^\circ (V_{AN} + I_{aA}(5 + j10))$$

$$\underline{V_{an}} = I_{aA}(100 + 5 + j150 + j10)$$

$$= 11.53 \angle -56.31^\circ (105 + j160)$$

$$= 11.53 \times 191.38 \angle -56.31^\circ + 56.73^\circ$$

$$= 2206.57 \angle 0.42^\circ \text{ V}$$

$$V_{ab} = \sqrt{3} \angle 30^\circ \cdot 2206.57 \angle 0.42^\circ$$

$$= 3821.89 \angle 30.42^\circ \text{ V}$$

e)

$$S_{\phi} = V_{AN} I_{aA}^* = 2078.5 \angle 0^\circ \cdot 11.53 \angle 56.31^\circ$$

$$= 23965.11 \angle 56.31^\circ$$

$$= 13293.4 + j19940.2 \text{ VA}$$

f)

$$\eta = \frac{P_{\phi L}}{P_{\phi S}} = \frac{13293.4}{13956.96} \cdot 100\%$$

$$S_{\phi S} = V_{an} I_{aA}^* = 2206.57 \angle 0.42^\circ \cdot 11.53 \angle 56.31^\circ$$

$$= 25441.75 \angle 56.73^\circ$$

$$= 13956.96 + j2121.71$$

$$\eta = \frac{13293.4}{13956.96} \cdot 100\% = \underline{\underline{95.25\%}}$$

Problem 2: [15 points]

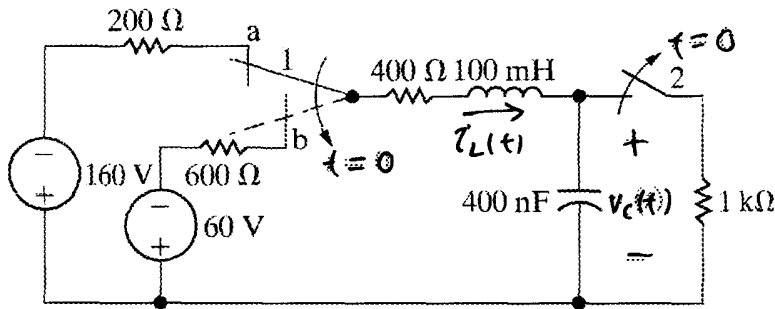


Figure: 08-21-20P8.52


Copyright © 2008 Pearson Prentice Hall, Inc.

The two switches in the above figure operate synchronously. When switch 1 is in position a, switch 2 is closed. When switch 1 is in position b, switch 2 is open. Switch 1 has been in position a for a long time. At $t = 0$, it moves instantaneously to position b.

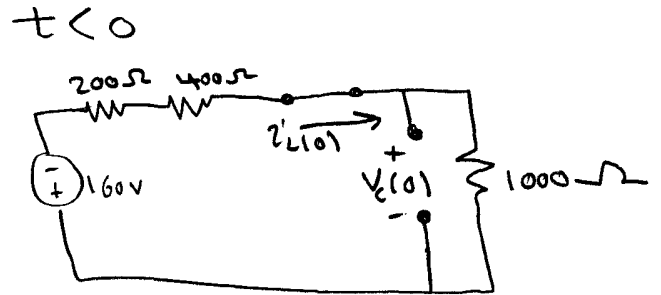2.1 Find $v_C(0)$, $i_L(0)$ [3pts]

$$i_L(0) = \frac{-160}{1600} = -100 \text{ mA}$$

$$v_C(0) = 1000 i_L(0) = -100 \text{ V}$$



2.2 Find $\frac{dv_C(0^+)}{dt}$, $\frac{di_L(0^+)}{dt}$ [3pts]

$$* C \frac{dv_C(t)}{dt} = i_L(t)$$


$$\Rightarrow \frac{dv_C(t)}{dt} = \frac{1}{C} i_L(t) = \frac{-100 \text{ mA}}{400 \text{ nF}}$$

$$\Rightarrow \frac{dv_C(0)}{dt} = -250,000 \text{ V/s}$$

$$* L \frac{di_L(t)}{dt} + v_C(t) + 60 + 1000 i_L(t) = 0$$

$$\Rightarrow L \frac{di_L(t)}{dt} = 100 - 60 + 100 = 140$$
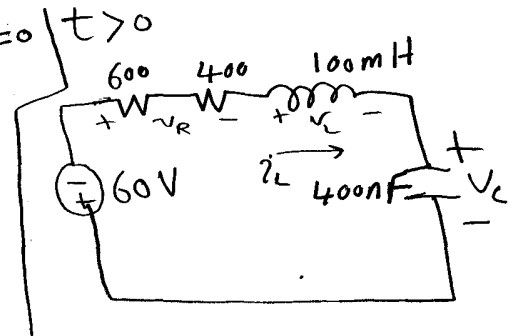
$$\Rightarrow \frac{di_L(t)}{dt} = \frac{140}{100 \text{ m}} = 1400 \text{ A/s}$$



2.3 Find α , ω_0 , s_1 , s_2 [2pts]

$$* \alpha = \frac{R}{2L} = \frac{1000}{200} \times 10^3 = 5000 \text{ rad/s}$$

$$* \omega_0^2 = \frac{1}{LC} = \frac{(10^9)(10^3)}{(100)(400)} = 25 \times 10^6$$

$$\Rightarrow \omega_0 = 5000 \text{ rad/s}$$

$$s_1 = s_2 = -\alpha = -5000 \text{ rad/s}$$

2.4 What is the type of the response for $t \geq 0$ [1pts]

Since $\alpha^2 = \omega_0^2 \Rightarrow$ Critically Damped

2.5 Find $v_c(t)$ for $t \geq 0$ [3pts]

$$v_c(t) = V_f + D_1 t e^{-5000t} + D_2 e^{-5000t}$$

* Find D_1 and D_2 from initial conditions

$$* v_c(0) = V_f + D_2 = -100 \text{ V}$$

$$\Rightarrow D_2 = v_c(0) - V_f = -100 + 60$$

$$\boxed{D_2 = -40 \text{ V}}$$

$$* \frac{dv_c(0)}{dt} = D_1 - 5000 D_2 = -250,000 \text{ V/s}$$

$$\Rightarrow D_1 = 5000 D_2 - 250,000$$

$$= 5000(-40) - 250,000$$

$$\boxed{D_1 = -450,000}$$

$$v_c(t) = -60 - 450,000 t e^{-5000t} - 40 e^{-5000t} \text{ V for } t \geq 0$$

2.6 Find $i_L(t)$ for $t \geq 0$ [3pts]

$$i_L(t) = C \frac{dv_c(t)}{dt}$$

$$= C \left[D_1 e^{-5000t} - 5000 D_1 t e^{-5000t} - 5000 D_2 e^{-5000t} \right]$$

$$= -5000 C D_1 t e^{-5000t} + [C D_1 - 5000 C D_2] e^{-5000t}$$

$$= -(5 \times 10^3)(400 \times 10^{-9})(-45 \times 10^4) t e^{-5000t} + [(400 \times 10^{-9})(-45 \times 10^4) - (5 \times 10^3)(400 \times 10^{-9})(-40)] e^{-5000t}$$

$$= 900 t e^{-5000t} + [-0.18 + 0.08] e^{-5000t}$$

$$i_L(t) = 900 t e^{-5000t} - 0.1 e^{-5000t} \text{ A, } t \geq 0$$




Problem 3: [15 points]

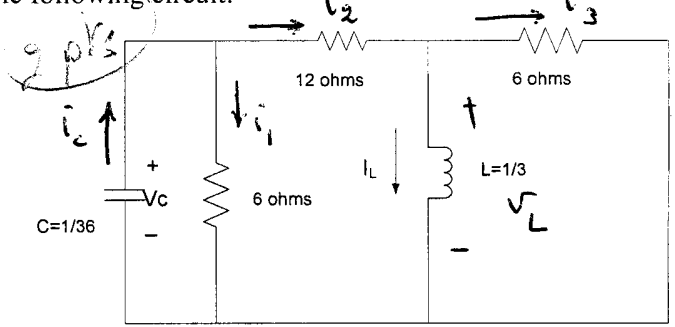Part A: [9pts]

Write down the state equations for the following circuit:

First, we have
$$\begin{cases} L \frac{di_L}{dt} = v_L \\ C \frac{dv_C}{dt} = -i_C \end{cases}$$



KVL:
$$\begin{cases} v_C = 6 i_1 \\ v_L = 6 i_3 \\ v_C = 12 i_2 + 6 i_3 \end{cases}$$

KCL:
$$\begin{cases} i_2 = i_3 + i_L \\ i_C = i_1 + i_2 \end{cases}$$

$$i_3 = \frac{1}{12} v_C - \frac{2}{3} i_L$$
, so that
$$L \frac{di_L}{dt} = 6 i_3 = -4 i_L + \frac{1}{3} v_C$$

$$\rightarrow -i_C = -i_1 - i_2 = -i_1 - i_3 - i_L = -\frac{1}{6} v_C - i_L - \frac{1}{12} v_C + \frac{2}{3} i_L$$

so that
$$C \frac{dv_C}{dt} = -\frac{1}{3} i_L - \frac{4}{12} v_C$$

Finally
$$\frac{d}{dt} \begin{bmatrix} i_L \\ v_C \end{bmatrix} = \begin{bmatrix} -12 & 1 \\ -12 & -8 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

Part B: [6pts]

Consider the following state equation with state vector $X(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$:

$$\frac{d}{dt} X(t) = AX(t), \text{ where } A = \begin{bmatrix} -12 & 1 \\ -12 & -8 \end{bmatrix}$$

Assume the initial conditions are $x_1(0) = 1$, and $x_2(0) = 1$.

Use the Euler numerical method to find $x_1(\Delta t)$, $x_2(\Delta t)$, and $x_1(2\Delta t)$, $x_2(2\Delta t)$, for $\Delta t = 0.1$

We have:
$$\begin{aligned} x_1[(h+1)\Delta t] &\approx x_1(h\Delta t) + [a_{11} x_1(h\Delta t) + a_{12} x_2(h\Delta t)] \cdot \Delta t \\ x_2[(h+1)\Delta t] &\approx x_2(h\Delta t) + [a_{21} x_1(h\Delta t) + a_{22} x_2(h\Delta t)] \cdot \Delta t \end{aligned}$$

with $\Delta t = 0.1$, $x_1(0) = x_2(0) = 1$
$$\begin{aligned} a_{11} &= -12 & a_{12} &= 1 \\ a_{21} &= -12 & a_{22} &= -8 \end{aligned}$$

we get
$$\begin{aligned} x_1(0.1) &= 1 + [-12 + 1] \times 0.1 = -0.1 \\ x_2(0.1) &= 1 + [-12 - 8] \times 0.1 = -1 \end{aligned}$$

$$\begin{aligned} x_1(0.2) &= -0.1 + [-12 \times -0.1 - 1] \times 0.1 = -0.08 \\ x_2(0.2) &= -1 + [1.2 + 8] \times 0.1 = -0.08 \end{aligned}$$