

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS**Electrical Engineering Department****EE-205 Electric Circuits II****Spring 2009/2010(092) First Major Exam****Duration : 90 min.****Dr. E. Hassan,****Dr. A. Muqaibel,****Dr. S. Al-Ghadban,****Dr. H. Masoudi (Coordinator)**

Name :

ID #

Section #

Key

Question	Grade
1 (10 points)	
2 (10 points)	
3 (10 points)	
Total (30 points)	

Notes :

- 1) Read the question very carefully.
- 2) Use a sketch to help you understand the question.
- 3) Write neatly.

Final

Question 1

Write the correct answer in the box shown. Only answers in the box below will be graded

Answers' Box

1. a	2. d	3. e	4. c
5. d	6. b	7. b	

Do NOT Circle or Mark the answer in the questions. If you do so, it is considered cheating.

(Parts 1 to 4: 1 points each; Parts: 5 to 7 two points each)

(only one answer is correct)

1) In a three-phase balanced system, if I_{aA} is $17+j10$ A, then for a negative sequence I_{cC} will be:

- a) $19.72 \angle -89.53^\circ$
- b) $17-j10$
- c) $19.72 \angle 30.46^\circ$
- d) $-17+j10$
- e) None of the above is correct

2) In a three phase balanced positive sequence Y-Y connected system, if V_{AN} is $120 \angle 0^\circ$ V at the load, then (for a negligible line impedance) V_{bc} at the source will be:


- a) $1/\sqrt{3}$ times in magnitude but leading by 90°
- b) $\sqrt{3}$ times in magnitude but lagging by 150°
- c) $\sqrt{3}$ times in magnitude but leading by 120°
- d) $\sqrt{3}$ times in magnitude but lagging by 90°
- e) None of the above is correct

3) The complete solution for the voltage across the capacitor in a series RLC circuit of the step response with a DC source consists of:

- a) The function of the same form as the natural response
- b) The final value of the response function
- c) The function of the same form as the natural response and the final value of the response function if R is greater than C
- d) The function of the same form as the natural response and the final value of the response function if R is equal to C
- e) None of the above is correct


4) Assume the parallel RLC circuit of the step response shown, with $I = 24$ mA. The solution for $i_l(t)$ is

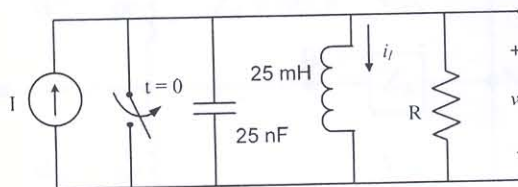- a) Over damped if $R = 625 \Omega$
- b) Under-damped if $R = 400 \Omega$
- c) Critically-damped if $R = 500 \Omega$
- d) All of the above are correct
- e) None of the above is correct




5) For the ideal Op-Amp circuit shown assume no energy in the capacitor before the switch is closed at $t = 0$. For $t \geq 0$, the Op-Amp

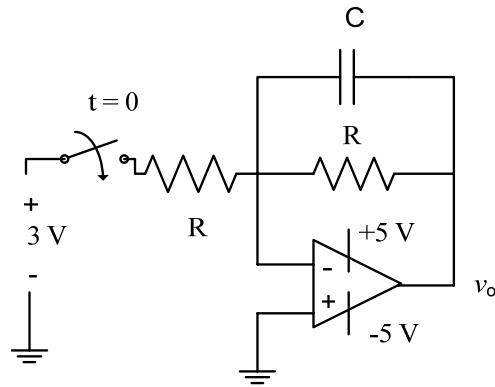- a) will saturate in 3 seconds
- b) will saturate in 5 seconds
- c) will saturate only if R is greater than C
- d) will never saturate
- e) None of the above is correct




6) Assume two balanced 3-phase systems. System A is a delta source with a phase voltage of V connected to a Y-load with a phase impedance of R. System B is a Y source of phase voltage V connected to a delta load of phase impedance of R. Comparing the total power absorbed by Load A and B, the following is true:

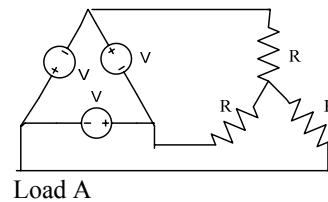- a) The power absorbed by load B is 18 times the power absorbed by load A
- b) The power absorbed by load B is 9 times the power absorbed by load A
- c) The power absorbed by load B is 6 times the power absorbed by load A
- d) The power absorbed by load B is 3 times the power absorbed by load A
- e) The power absorbed by load B is the same as the power absorbed by load A.




Load A

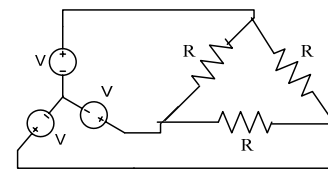

Load B


7) Using the two-wattmeter method, calculate the reading of each wattmeter in the given circuit if the phase voltage at the load is 120 V and $Z_\phi = 8 - j6 \Omega$.

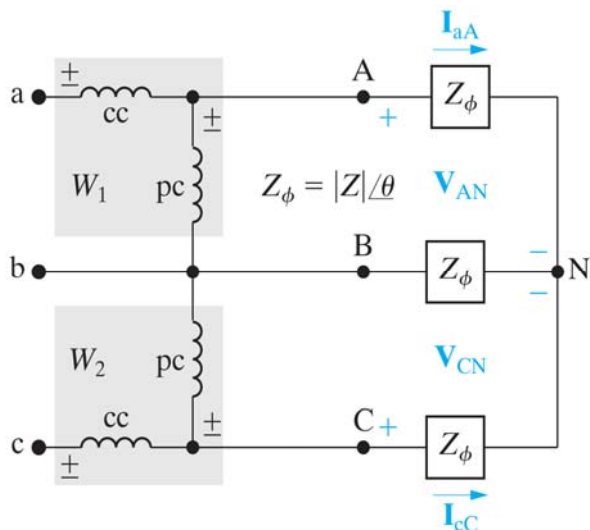- a) $W_1 = 979.75 \text{ W}$ and $W_2 = 2476.25 \text{ W}$
- b) $W_1 = 2476.25 \text{ W}$ and $W_2 = 979.75 \text{ W}$
- c) $W_1 = 565.66 \text{ W}$ and $W_2 = 1429.7 \text{ W}$
- d) $W_1 = 1429.7 \text{ W}$ and $W_2 = 565.66 \text{ W}$
- e) None of the above is correct



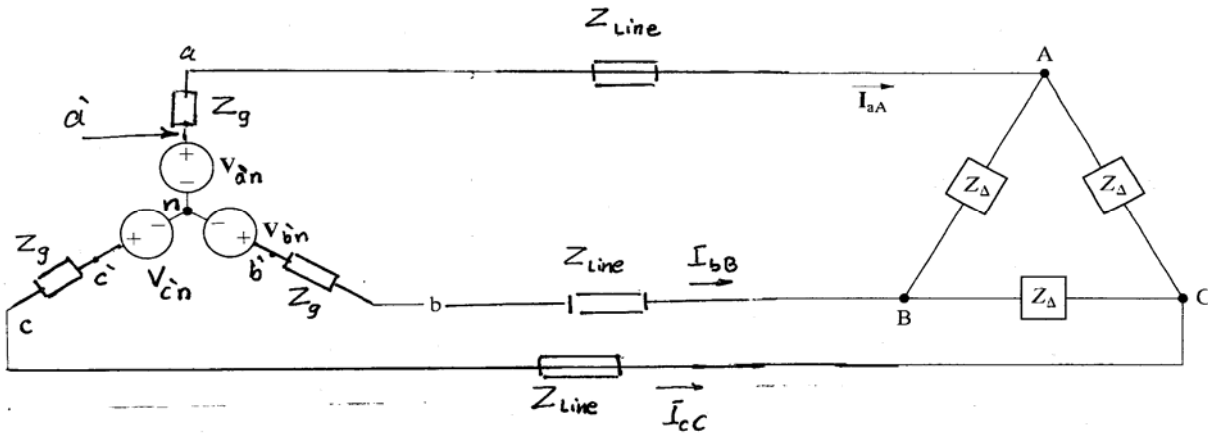Question 2 In a balanced positive sequence three phase Y- Δ connection shown, the followings are given:
 Line current $I_{aA} = 12 \angle 40^\circ$ Amp., line impedance $Z_{line} = 2 + j2$ ohms, Generator impedance $Z_g = 1 + j1$ ohms,
 and the power absorbed per phase is 800 Watts at a power factor = 0.8 lagging. Find:

- The complex phase voltage V_{AB}
- The complex load impedance Z_{Δ} .
- The complex open circuit generator voltage V_g (Equal to V_{an}).




$$P = |I_{an}|^2 \frac{|Z_{\Delta}|}{3} \cos \phi_2 \quad (2)$$

$$800 = (12)^2 \frac{|Z_{\Delta}|}{3} \times 0.8$$



$$|Z_{\Delta}| = 20.833$$

$$\phi_2 = 36.87^\circ \quad (1)$$

$$Z_{\Delta} = 20.833 \angle 36.87$$

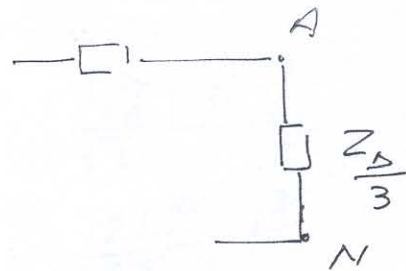
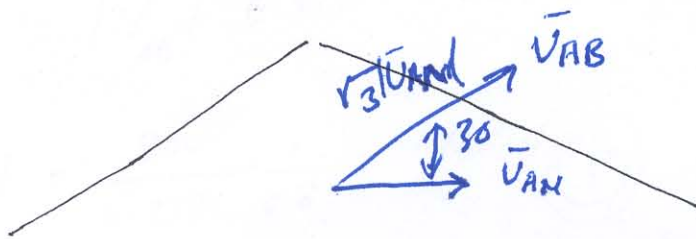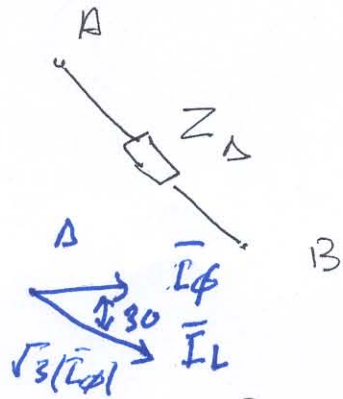
$$\bar{V}_{AB} = \bar{V}_{AN} \sqrt{3} \angle 30^\circ$$



$$V_{AN} = I_{AA} \frac{Z_{\Delta}}{3} \quad (2)$$

$$= 12 \angle 40 \times \frac{20.833 \angle 36.87}{3}$$

$$= 83.333 \angle 76.87^\circ \quad (1)$$

$$V_{AB} = \sqrt{3} V_{AN} \angle 30$$

$$= 144.33 \angle 106.87^\circ \quad (1)$$

$$I_{AA} = I_{AB} \sqrt{3} \angle -30$$

$$\therefore I_{AB} = \frac{12 \angle 40 \angle 30}{\sqrt{3}} \quad (2)$$

$$= 6.928 \angle 70^\circ$$

$$V_{AB} = I_{AB} Z_{\Delta}$$

$$= 6.928 \angle 70^\circ \times 20.833 \angle 36.87$$

$$= 144.33 \angle 106.87 \quad (2)$$

$$V_g = I_{AA} (Z_g + Z_{Line} + \frac{Z_{\Delta}}{3}) \quad (2) \quad \text{or} \quad I_{AA} (Z_g + Z_{Line}) + V_{AN}$$


$$\therefore V_g = 12 \angle 40 (1+j1 + 2+j2) + 83.333 \angle 76.87$$

$$= 133.9 \angle 79.95^\circ \quad (1)$$

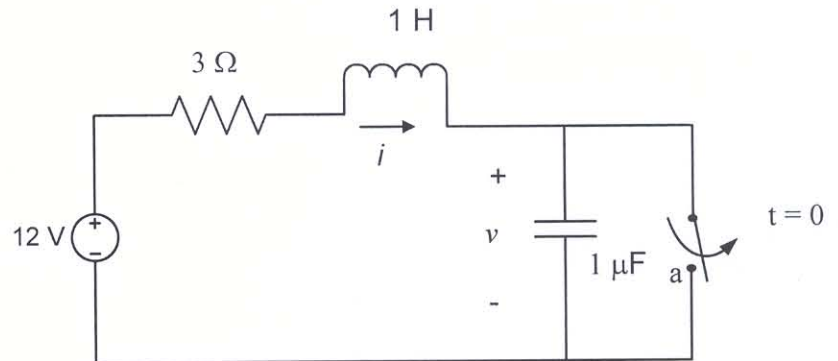Question 3 For the circuit shown, the switch has been closed for a long time before it is opened at $t=0$.

- ① a) Find $v(t)$ and $i(t)$ for $t < 0$

$$1 \left\{ \begin{array}{l} v = 0 \\ i = \frac{12}{3} = 4A \end{array} \right.$$



For $t \geq 0$ find (b to f):

- ② b) The second order differential equation in terms of $v(t)$

$$\text{KVL} \quad 3i + L \frac{di}{dt} + v = 12, \quad i = C \frac{dv}{dt}$$

$$3 \times 10^{-6} \frac{dv}{dt} + 10^{-6} \frac{d^2v}{dt^2} + v = 12$$

$$2 \quad \frac{d^2v}{dt^2} + 3 \frac{dv}{dt} + 10^6 v = 12 \times 10^6$$

- ① c) The roots of the characteristic equation that describes the voltage $v(t)$

$$\alpha = \frac{3}{2}, \quad \omega_0 = \sqrt{10^6} = 10^3, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} \approx 10^3$$

$$s_1 = -\frac{3}{2} + j10^3, \quad s_2 = -\frac{3}{2} - j10^3$$

- ① d) What is the type of the response? and specify why?

1 The response is underdamped

$$\text{because } \omega_0^2 > \alpha^2$$

$$v(t) = V_f + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$$

② e) Find $v(0^+)$ and $\frac{dv(0^+)}{dt}$

$$v(0^+) = 12 + B_1 = 0$$

$$\frac{dU(t)}{dt} = \frac{i(t)}{C} \Rightarrow \frac{i(0^+)}{C} = \frac{4}{1 \times 10^{-6}} = 4 \times 10^6 = \frac{dU(0^+)}{dt}$$

$$\frac{dU(t)}{dt} = B_1' (-\alpha e^{-\alpha t} \cos \omega_d t - \omega_d e^{-\alpha t} \sin \omega_d t) + B_2' (-\alpha e^{-\alpha t} \sin \omega_d t + \omega_d e^{-\alpha t} \cos \omega_d t)$$

$$\frac{dU(0^+)}{dt} = -\alpha B_1 + \omega_d B_2'$$

③ f) Find $v(t)$

$$v(t) = 12 + B_1' e^{-3/2t} \cos 10^3 t + B_2' e^{-3/2t} \sin 10^3 t$$

$$v(0^+) = 0 = 12 + B_1' \quad (1) \Rightarrow B_1' = -12$$

$$\frac{dU(0^+)}{dt} = 4 \times 10^6 = -\alpha B_1' + \omega_d B_2' = -\frac{3}{2} B_1' + 10^3 B_2'$$

$$B_2' = \frac{4 \times 10^6 - 12 \times \frac{3}{2}}{10^3} \approx 4000$$

$$v(t) = 12 - 12 e^{-3/2t} \cos 10^3 t + 4000 e^{-3/2t} \sin 10^3 t$$