


Name: KEY

Ver.1 & 2

← Two Quizzes.

The switch in the circuit shown has been closed for a long time. The switch opens at $t=0$. Find $v_o(t)$ and $i_o(t)$ for $t \geq 0$.


$t < 0$

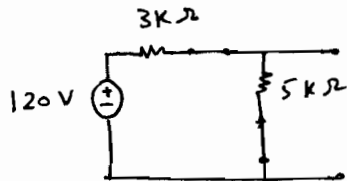

$$i_o(0^-) = \frac{120}{(3+5)k\Omega} = 15 \text{ mA}$$

$$v_o(0^-) = 120 \cdot \frac{5}{3+5} = 75 \text{ V}$$

for $t \geq 0$

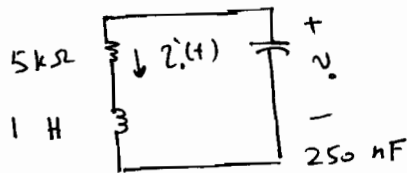

Series RLC circuit

$$i_c = C \frac{dv_o}{dt} = -i_o$$


$$\Rightarrow \frac{dv_o}{dt} = -\frac{i_o}{C}$$

$$\frac{dv_o}{dt}(0^+) = -\frac{i_o(0^+)}{C} = -\frac{15 \text{ mA}}{250 \text{ nF}} = -60,000 \text{ V/sec.}$$

By KVL

$$-v_o + 5k i_o + L \frac{di_o}{dt} = 0$$

$$L \frac{di_o}{dt} = v_o - 5k i_o$$

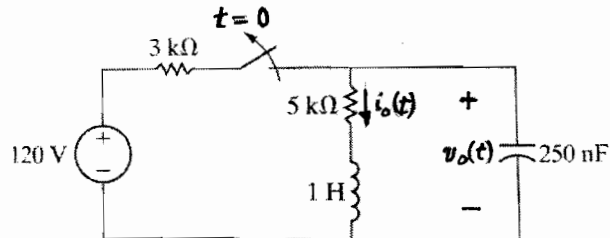

$$\frac{di_o}{dt}(0^+) = \frac{1}{L} (75 - 5k(15 \text{ mA})) = 75 - 75 = 0 \text{ A/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{5 \times 10^{-4}} = 2000$$

$$\alpha = \frac{R}{2L} = \frac{5k}{2} = 2500$$

$\alpha > \omega_0 \Rightarrow$ overdamped response.

$$v_o = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2500 \pm \sqrt{6250000 - 4 \times 10^6} = -2500 \pm 1500$$

$$s_1 = -4000, \quad s_2 = -1000$$

from the initial condition

$$75 = A_1 + A_2 \quad \text{--- (1)}$$

$$-60000 = -4000 A_1 - 1000 A_2$$

$$-60 = -4 A_1 - A_2 \quad \text{--- (2)}$$

$$15 = -3 A_1 \Rightarrow A_1 = -5 \quad \& \quad A_2 = 80$$

$$\Rightarrow v_o(t) = -5 e^{-4000t} + 80 e^{-1000t} \text{ V } t \geq 0$$

check i.c. $v_o(0) = -45 + 120 = 75$

$$i_o = -C \frac{dv_o}{dt} = -250 \text{ nF} [(-5)(-4000) e^{-4000t} + (80)(-1000) e^{-1000t}]$$

$$i_o(t) = -5 e^{-4000t} + 20 e^{-1000t} \text{ mA } t \geq 0$$

Another solution "same answer"
if we start with the current.

$$i(t) = A_3 e^{-4000t} + A_4 e^{-1000t}$$

$$i(0) = A_3 + A_4 = 15 \text{ mA} \quad \text{--- (1)}$$

$$0 = -4000 A_3 + 1000 A_4 \Rightarrow$$

$$\boxed{A_4 = -4 A_3} \quad \text{--- (2)}$$

Substitute (2) in (1)

$$A_3 - 4 A_3 = 15 \text{ mA}$$

$$\Rightarrow -3 A_3 = 15 \text{ mA}$$

$$\Rightarrow \boxed{A_3 = -5 \text{ mA}}$$

$$\boxed{A_4 = +20 \text{ mA}}$$

Same answer:

$$i(t) = -5 e^{-4000t} + 20 e^{-1000t} \text{ mA}$$

$$t \geq 0$$