


Turn Ratio = $1/13.5$

Voltage Gain = -3

take home answers

Name: KEY

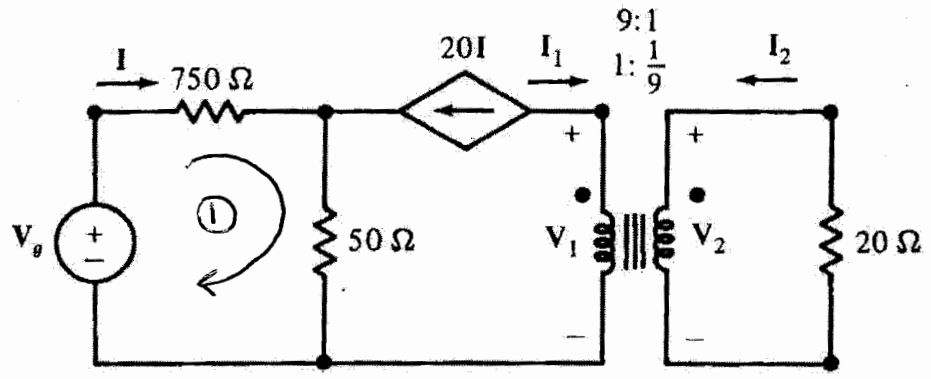For the given circuit calculate the voltage and power gains. The output voltage is V_2 .



By KVL loop ①

$$V_g = 750 \vec{I} + 50(21\vec{I})$$

$$= 1800 \vec{I} \quad \text{②}$$

$$\Rightarrow \vec{I} = \frac{V_g}{1800}$$

Also $\vec{I}_1 = -20\vec{I} = -20\left(\frac{V_g}{1800}\right)$

$$= -\frac{V_g}{90} \quad \text{①}$$

For the transformer

$$\vec{I}_2 = \frac{-\vec{I}_1}{1/9} = -9\vec{I}_1 \quad \text{②}$$

$$= -9\left(-\frac{V_g}{90}\right) = \frac{V_g}{10}$$

$$\Rightarrow \vec{V}_2 = -20\vec{I}_2 = -20\left(\frac{V_g}{10}\right) = -2V_g \quad \text{①}$$

$\frac{V_2}{V_g} = -2 \quad \text{①}$

The instantaneous power supplied by the independent voltage source

$$P_g = V_g i = V_g \left(\frac{V_g}{1800}\right) = \frac{V_g^2}{1800} \quad \text{①}$$

the power absorbed by the 20 Ohm load resistor is

$$P_r = \frac{V_2^2}{20} = \frac{(-2V_g)^2}{20} = \frac{1}{5} V_g^2 \quad \text{①}$$

Power Gain

$$\frac{P_r}{P_g} = \frac{(1/5)V_g^2}{V_g^2/1800} = 360 \quad \text{①}$$