

King Fahd University of Petroleum & Minerals
 Electrical Engineering Department
 EE207: Signals and Systems (081)
Quiz 6: Applications of Laplace Transforms

Serial #

- 1 points for not writing your serial number

Name: KEY

Ver.

For the op-amp circuit shown in the figure, suppose that $v_c(0) = 4V$ and $v_g(t) = \cos 2t u(t) V$.




(Tables are attached, If needed)

1) Redraw the circuit in Laplace domain.

Use the parallel Model for the capacitor.

2) Find $V_o(s)$

3) Find $v_o(t)$

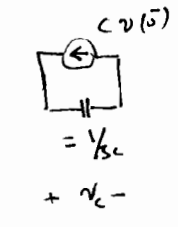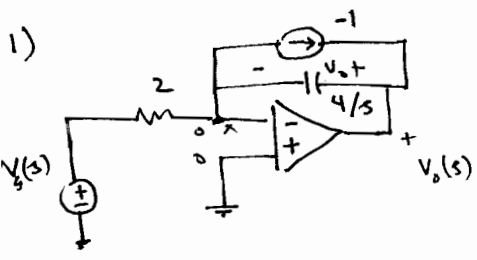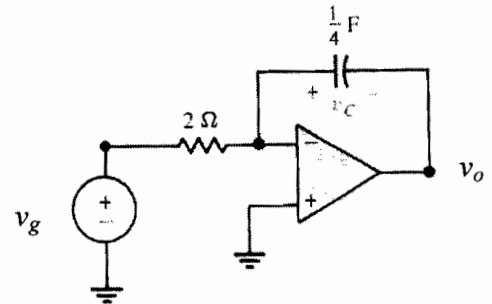

2) By KCL @ node x

$$\frac{V_g}{2} + 1 + \frac{v_o}{4/s} = 0$$

$$v_o = -\frac{4}{s} \left[1 + \frac{v_o}{2} \right]$$

$$v_o = -\frac{2}{s} \left[2 + V_g \right]$$

By Laplace Table.

$$\mathcal{L}[\cos 2t u(t)] = \frac{s}{s^2 + 2^2}$$

$$V_o(s) = -\frac{2}{s} \left[2 + \frac{s}{s^2 + 2^2} \right]$$

$$= -\frac{4}{s} - \frac{2}{s^2 + 2^2}$$

3) $v_o(t)$
 By inverse Laplace

$$\mathcal{L}^{-1}[V_o(s)] = -4 u(t) - \sin 2t u(t) \quad V$$

$$v_o(t) = -4 - \sin 2t \quad \checkmark \quad t \geq 0$$

$$= (-4 - \sin 2t) u(t) \quad \checkmark$$