

King Fahd University of Petroleum & Minerals

Electrical Engineering Department

EE 204_092 Fundamentals of Electric Circuits

Major Exam I
Wednesday, 24 March 2010
7:00 PM – 8:30 PM

| | |
|------------------------|--|
| Name (Capital Letters) | |
| ID Number | |
| Lecture Section Number | |
| Serial Number | |
| Lab Section Number | |







| Problem | Maximum | Score |
|---------|---------|-------|
| 1 | 6 | |
| 2 | 10 | |
| 3 | 6 | |
| 4 | 5 | |
| 5 | 10 | |
| 6 | 3 | |
| 7 | 5 | |
| 8 | 5 | |
| Total | 50 | |

SHOW ALL OF YOUR WORK IN A CLEAR NEAT WAY

Good luck!

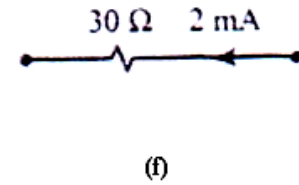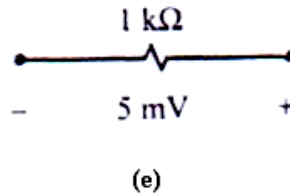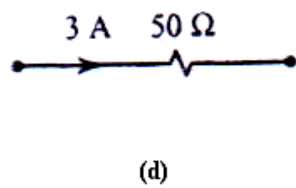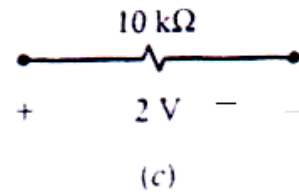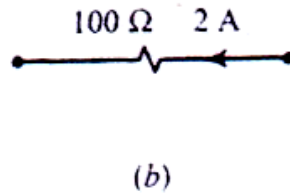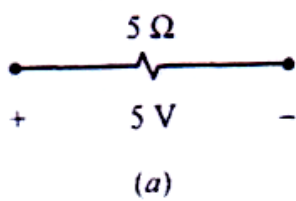Problem 1:

One of the parameters (current or voltage) is missing in the following resistors. Indicate the direction or polarity of the missing parameter in each figure and calculate its value in the table.




| Figure | Current | Voltage |
|--------|---------|---------|
| a | | 5V |
| b | 2A | |
| c | | 2V |
| d | 3A | |
| e | | 5mV |
| f | 2mA | |

Problem 2:


In the circuit below, boxes contain electric elements. State T for true, and F for False for the statements in the table. (We note A+B means A is in series with B; and A//B means A is in parallel with B.)

| | Statement | Put T or F |
|----|------------------|------------|
| 1 | A+B | |
| 2 | C//E | |
| 3 | D//F | |
| 4 | (C//E)+(F//D) | |
| 5 | C//B + D | |
| 6 | A+(C//E+D//F)//B | |
| 7 | A+C//E+(D//F//B) | |
| 8 | A+(C//E+D//F)//B | |
| 9 | A+C//E+D//F//B | |
| 10 | (C//E+D//F)//B | |

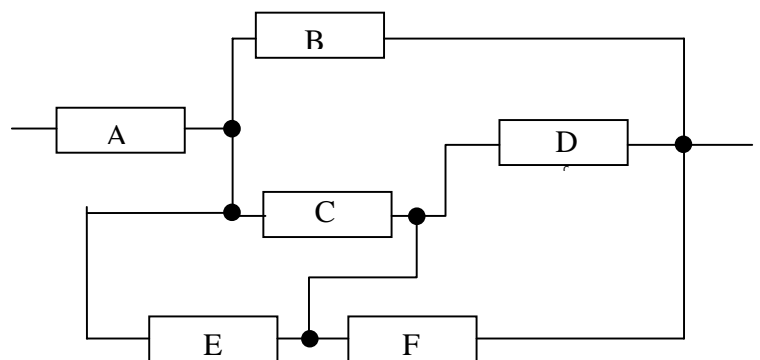

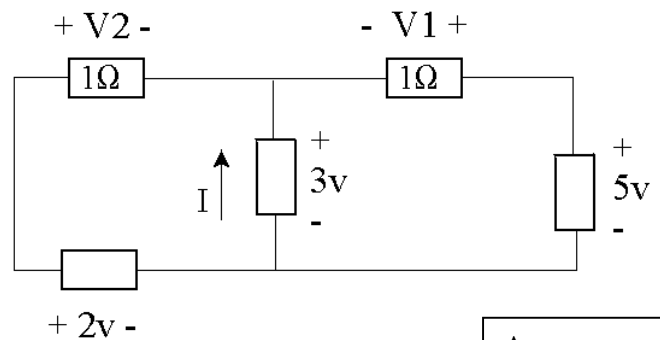Problem 3:


Consider the circuit shown below with electrical elements represented as boxes with voltages shown across the terminals of each. Determine the value of the voltages V_1, V_2 and the current I .



Answers:
 $V_1 =$
 $V_2 =$
 $I =$

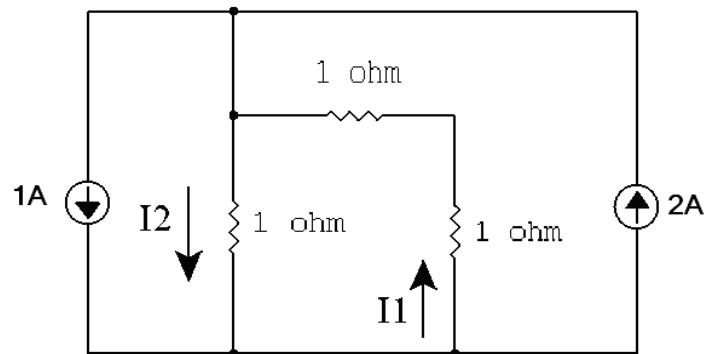Problem 4:


Use current dividers to find I_1 and I_2 in the circuit shown below:



Answers:
 $I_1 =$
 $I_2 =$

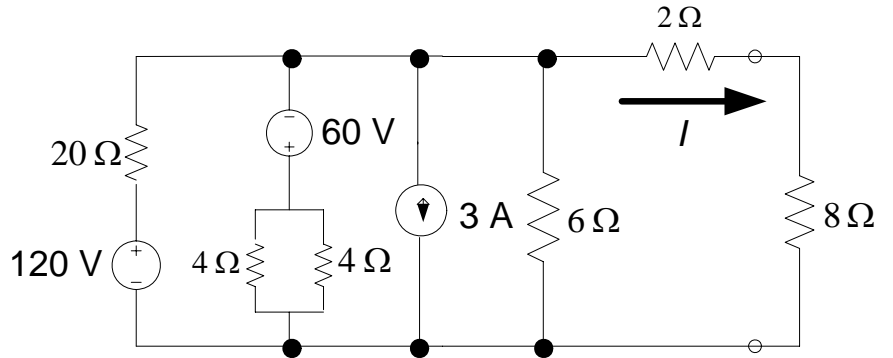Problem 5:


Use a series of source transformations to find the current I in the circuit shown below. (Redraw all steps of source transformations)



| |
|--|
| <p>Answer:</p> <p>$I =$</p> |
|--|

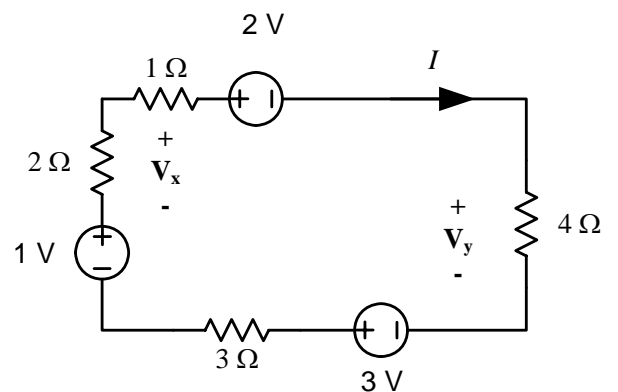Problem 6:


Determine I , V_x and V_y in the circuit shown?



| |
|--|
| <p>Put your answers here</p> <p>$I =$</p> <p>$V_x =$</p> <p>$V_y =$</p> |
|--|

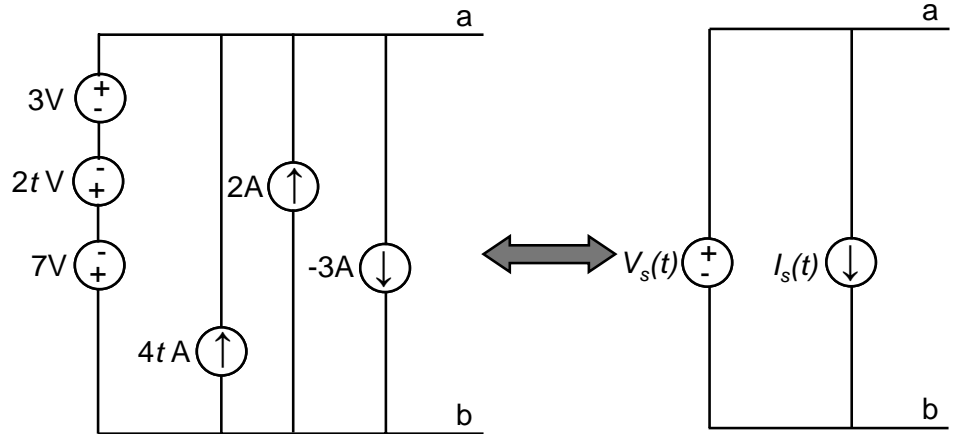Problem 7:


Reduce the circuit on the left to the circuit on the right to calculate $V_s(t)$ and $I_s(t)$ for $t = 0s, 3s$ and $5s$. Put the answers in the table shown. The time t is in seconds



| t | $V_s(t)$ | $I_s(t)$ |
|---|----------|----------|
| 0 | | |
| 3 | | |
| 5 | | |

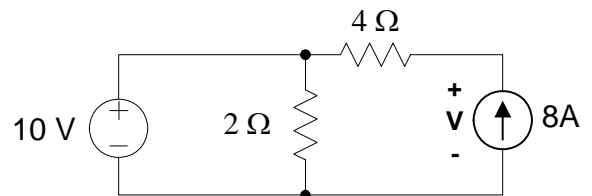Problem 8:

Determine the voltage V in the circuit using direct method and the power absorbed by the independent voltage source?



Put your answers here

$V =$

$P_{10V} =$