

King Fahd University of Petroleum & Minerals

Electrical Engineering Department

EE 204_092 Fundamentals of Electric Circuits

Major Exam II
5 May, 2010
7:00 PM – 8:30 PM

Name (Capital Letters)	
ID Number	
Lecture Section Number	
Serial Number	
Lab Section Number	


Problem	Maximum	Score
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
Total	60	

SHOW ALL OF YOUR WORK IN A CLEAR NEAT WAY

Good luck!

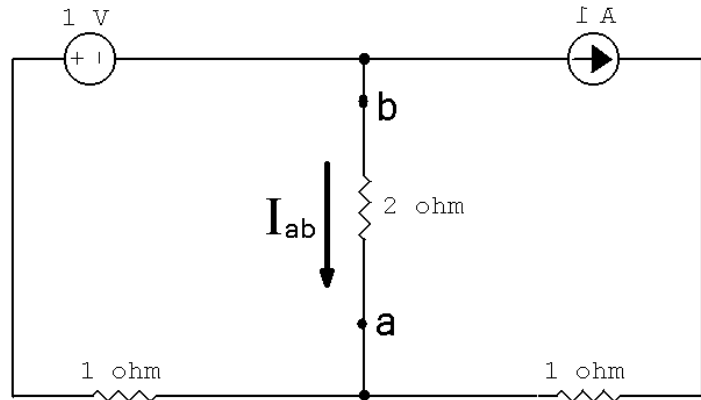Problem 1:

Find the Thevenin's equivalent of the circuit connected to the $2\ \Omega$ resistor between terminals a-b and use it to compute the current I_{ab} .




Put your answer here:

$I_{ab} =$

Problem 2:

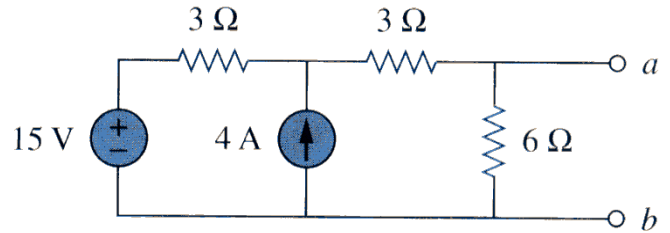- a) For the circuit shown below, find the value of the resistor to be connected between terminals a-b such that maximum power is transferred to it.
- b) Determine the value of the maximum power that can be transferred to the resistor found in part a




Put your answers here:

$R_L =$

$P_{R_L, \max} =$

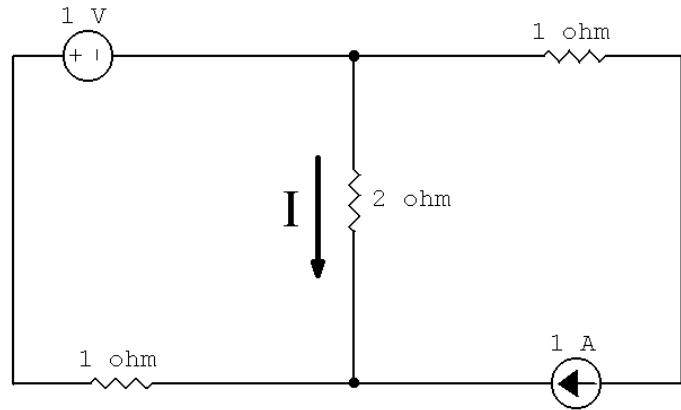Problem 3:

Use the principle of superposition to compute the current I in the circuit shown below,




Put your answer here

$I =$

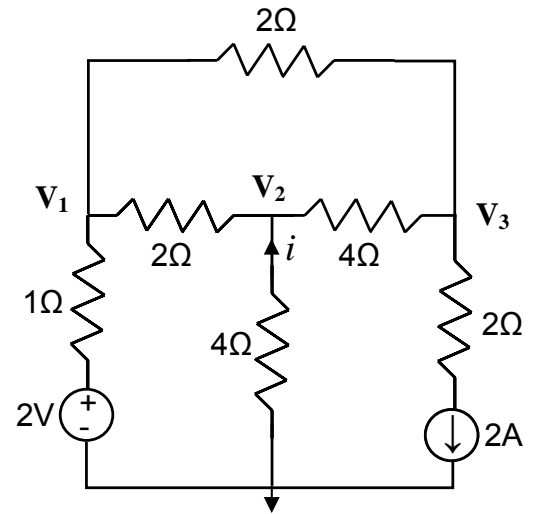Problem 4:


Calculate the current i in the circuit shown below using the node-voltage method.



Answer:
 $i =$

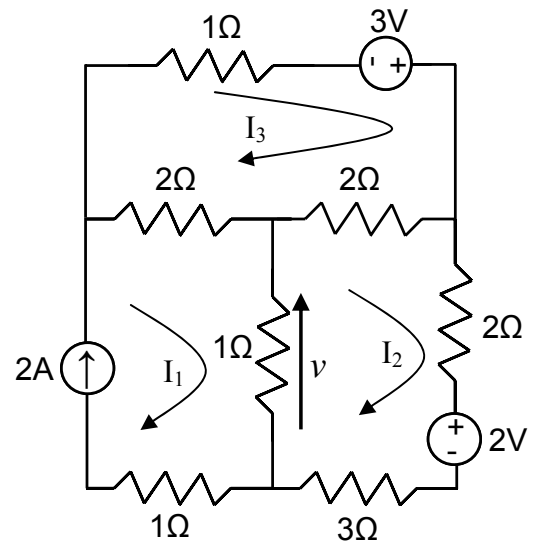Problem 5:

Calculate the voltage v in the circuit below using the mesh-current method.




Answer:
 $v =$

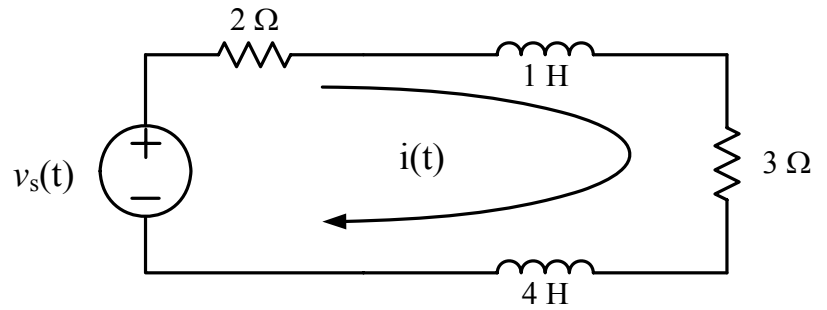Problem 6:

For the circuit shown, find $v_s(t)$ for all t , if $i(t)$ is defined by:

$$i(t) = \begin{cases} t & 0 \leq t \leq 2 \\ -t+4 & 2 \leq t \leq 4 \\ 0 & \text{elsewhere} \end{cases}$$



Answer: