



King Fahd University of Petroleum & Minerals

Electrical Engineering Department

EE 203 (102) – Final Exam

Tuesday, Jun 14, 2011

7:00-9:30 PM

Name	
ID	

	Dr. Oualid	Dr. Al-Gahtani	Dr. Al-Zaher	Dr. Wessam
Section	1 , 2	3, 6	4 , 5	7 , 8

Question	Grade
1 [25 Marks]	
2 [10 Marks]	
3 [15 Marks]	
4 [15 Marks]	
5 [20 Marks]	
6 [15 Marks]	
Total [100 Marks]	

Question: 1

A. [15 Marks]

For the circuit shown in Fig. 1, the transistors parameters are: $V_{TN} = 1V$, $\mu_n C_{ox} = 44.4\mu A/V^2$, $\lambda = 0$, and $L = 1\mu m$.

Assume Q1, Q2 and Q3 are identical.

- i) Determine the value of V_1 .
- ii) Design the transistors sizes (find W3) such that $V_2 = 3V$.
- iii) Determine the mode of operation of each transistor.

 


Fig 1

B. [10 Marks]

For the circuit shown in Fig 2,

- For the BJT assume $V_{BE} = 0.7V$ and neglect the base current (Large β)
- The NMOS transistor has $V_t = 1V$, $\lambda = 0$ and $\mu C_{ox} W/L = 2mA/V^2$.
- Assume Q1 is in saturation (pinch off) and Q2 is in active.

- i) Find the DC currents I_1 and I_2 .
- ii) Verify the assumption made for the mode of operations.

 



Fig 2

Question: 2

A.

[5 Marks]

 Draw a circuit that can convert 110V AC voltage to DC voltage of 10V.
(The values of the circuit components are not required)




B.

[5 Marks]

Using the constant-voltage model with $V_D = 0.7V$ plot the Input/output characteristics of the circuit shown below.

(Label all the critical voltage levels)

 


Question: 3

[15 Marks]

For the emitter follower shown, let $\beta=100$ and $R_{sig}=10k\Omega$.

- A. Calculate the collector current I_C .
- B. Draw its small signal equivalent circuit.
- C. Calculate the model parameters.
- D. Find the voltage gain v_o/v_{sig} .
- E. Find the input resistance.
- F. Find the output resistance

 


Question 4:

[15 Marks]

For the shown differential amplifier assume identical transistors with $V_1 = v_{cm} + v_{id}/2$ & $V_2 = v_{cm} - v_{id}/2$. Assume $\lambda = 0$.

 - A. Draw the small signal equivalent half-circuit for **the differential mode**
- B. Draw the small signal equivalent half-circuit for **the common mode**.
- C. If the output is taken single-ended (v_{o2} from M_2 drain), find the expressions of A_d , A_{cm} and **CMRR**.
- D. If the output is taken differentially ($v_{o2} - v_{o1}$), find the expressions of A_d , and A_{cm} .



Question: 5


A. [15 Marks]

For the shown pull-up network:

- i) Draw the corresponding pull-down network.
- ii) Write an expression for output Y in terms of the inputs A, B, C and D

$Y =$

 - iii) On each transistor, show the correct sizing $\frac{W}{L}$ of the pull-up network in terms of $p = \frac{W}{L}$ of the basic inverter



B. [5 Marks]

Design a pass-transistor logic (transmission gate) circuit to realize the following function:

The output Y equals to the input A if the input C is high and the output Y equals the input B if the input C is low.

[Draw the complete transistor level circuit]

Question: 6

[15 Marks]

For the shown ECL gate, assume all transistors are in active and neglect the base currents. If $V_R = -1.85V$, $I = 1mA$, $R = 2.3k\Omega$ and the all the transistors have $V_{BE} = 0.7V$ for a 1mA emitter current.

(a) What is the logic function performed at V_{o1} ?

(b) If V_B is sufficiently negative to turn Q_B off and V_A is connected to V_i , calculate

i. V_{IL} , and V_{IH} ?

ii. V_{OL} , and V_{OH} ?

iii. N_{MH} , and N_{ML} ?

