



King Fahd University of Petroleum and Minerals

Department of Electrical Engineering
EE 204 Fundamentals of Electric Circuits,
Second Semester (102)

Final Exam
Sunday, 12 June 2011
7:30 am – 10:00 am (150 minutes)

Name: _____

ID: _____

Section: _____

Instructors	Sections
Dr. Ahmad Yamani	1, 4, 6
Dr. Qureshi	2
Dr. Hammi	3
Dr. Adel Balghonaim	5
Mr. Noman Tasaduq	7
Dr. Wajih Abul Al-Saud	8, 10
Dr. Abdulmalik Zidouri	9, 11

Prob.	Score	Out of
1		5
2		5

Prob.	Score	Out of
3		9
4		9

Prob.	Score	Out of
5		9
6		9

Prob.	Score	Out of
7		8
8		10


Prob.	Score	Out of
9		8
10		10

Prob.	Score	Out of
11		6
12		12

Total		100
-------	--	-----

Good luck!

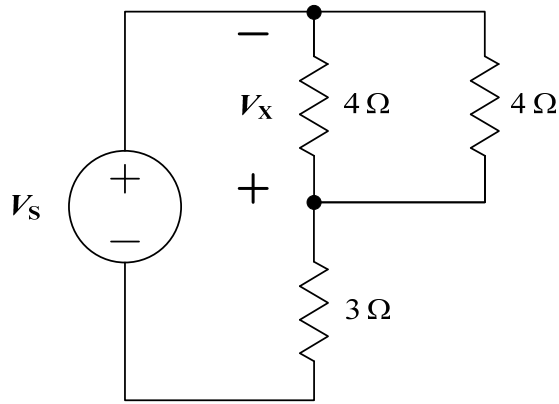
- (1) Using voltage division in the circuit below, we find that V_X is equal to:



- (A) $V_X = V_s \times \frac{4}{7}$
 (B) $V_X = -V_s \times \frac{4}{7}$
 (C) $V_X = -V_s \times \frac{2}{5}$
 (D) $V_X = -V_s \times \frac{2}{7}$
 (E) $V_X = -V_s \times \frac{4}{10}$
 (F) $V_X = V_s \times \frac{2}{5}$
 (G) Non of the above

The correct answer is ()

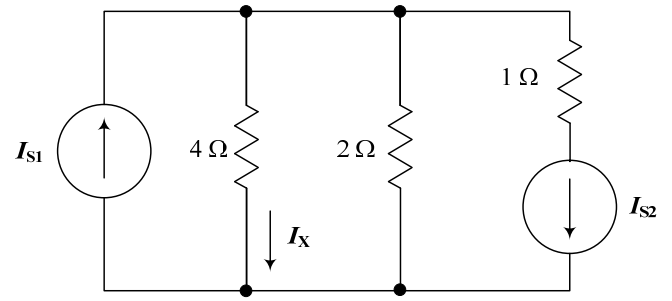
- (2) Using current division in the circuit below, we find that I_X is equal to:




- (A) $I_X = (I_{s1} - I_{s2}) \times \frac{3}{7}$
 (B) $I_X = (I_{s1} - I_{s2}) \times \frac{2}{6}$
 (C) $I_X = (I_{s1} - I_{s2}) \times \frac{2}{7}$
 (D) $I_X = (I_{s1}) \times \frac{2}{7}$
 (E) $I_X = (I_{s2} - I_{s1}) \times \frac{2}{6}$
 (F) $I_X = (I_{s2} - I_{s1}) \times \frac{4}{6}$
 (G) Non of the above

The correct answer is ()

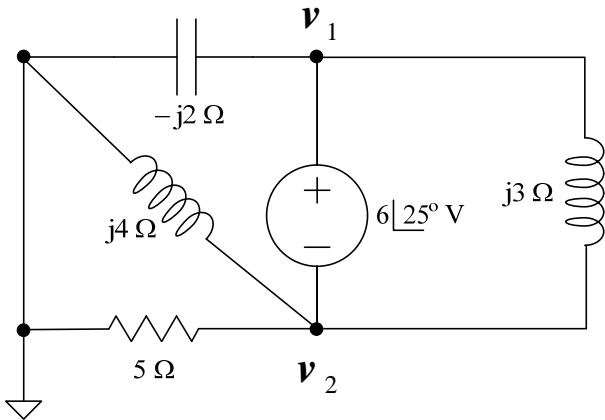- (3) Write all NODE-VOLTAGE equations necessary to solve for the node voltage in the circuit.
- Your equations should be in terms of the node voltages only.
 - Do not simplify or solve the equations.
 - You will lose marks for missing or extra equations.



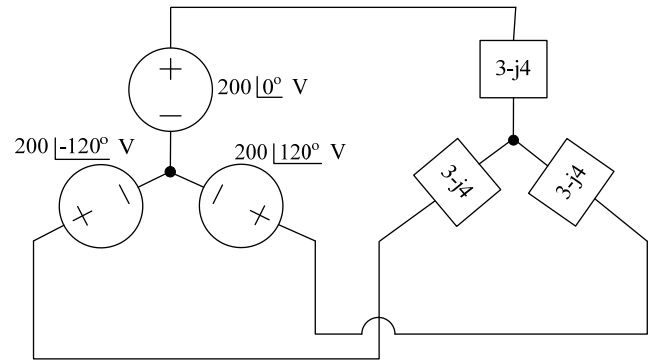
- (4) For the BALANCED 3-phase system shown below, find the total average power $P_{3\text{-phase}}$ consumed in the 3-phase load (The voltages of the source are RMS values).



$P_{3\text{-phase Load}} =$


W

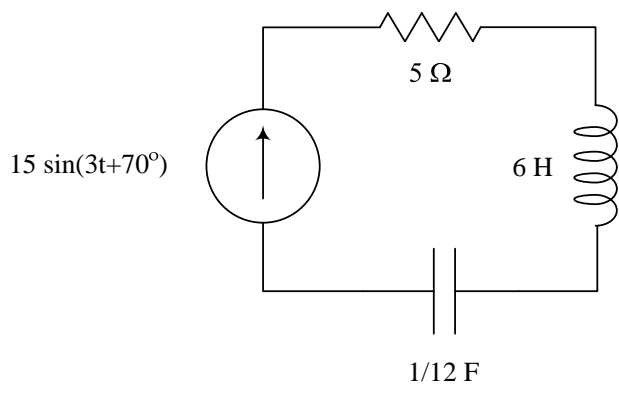(5) Find the complex power of the source \hat{P}_{source} .




$\hat{P}_{source} =$	VA
----------------------	----

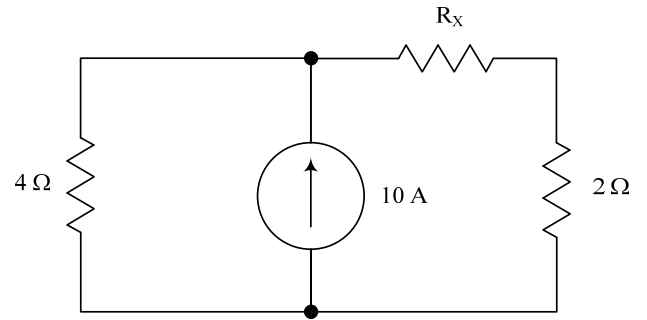(6) The current source generates 300 W of power. Find the power delivered to the resistor R_X .




$P_{R_X} =$	W
-------------	---

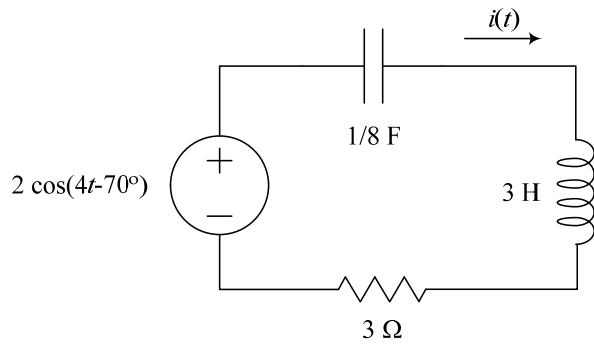(7) Find the current $i(t)$ shown in the circuit below.




$i(t) =$ A

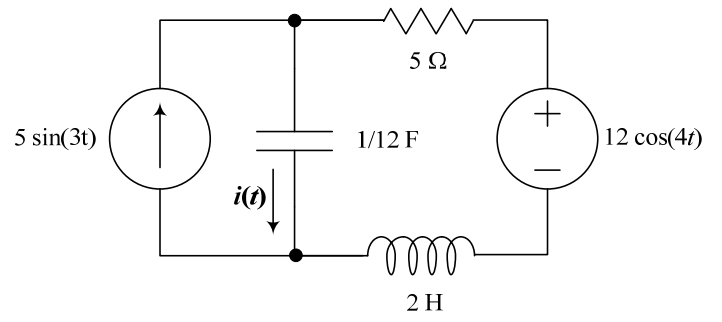(8) In the following circuit, find the current $i(t)$.




$i(t) =$

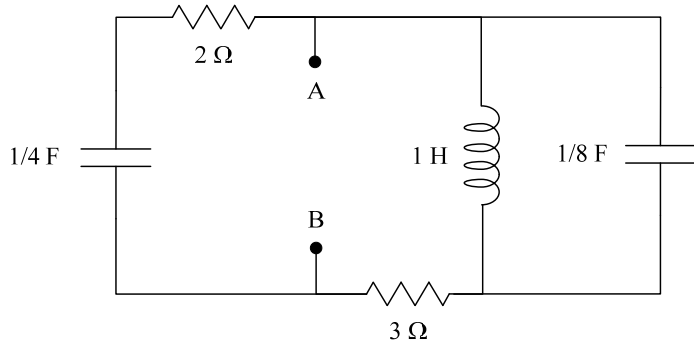(9) Given that the circuit below operates at a frequency $\omega = 4 \text{ rad/s}$, find the equivalent impedance Z seen between points A and B.




$Z =$

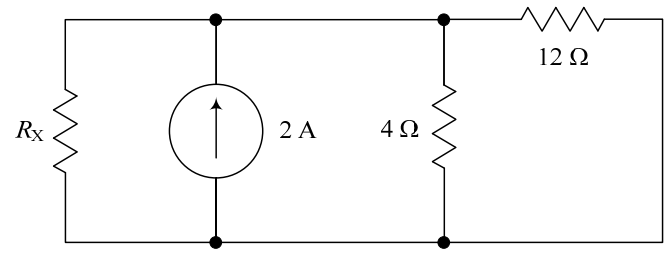(10) Find ALL values of resistance R_x that will make the power consumed by it to be equal to 1 W.




Values of R_x are Ω

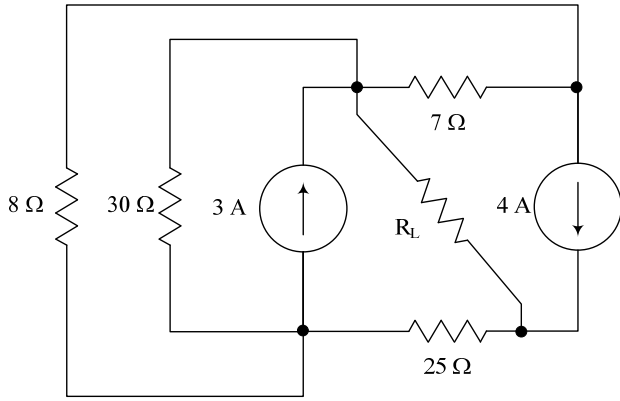(11) Find R_L that will absorb the maximum power from the circuit (DO NOT find the maximum power).



$R_L =$ Ω

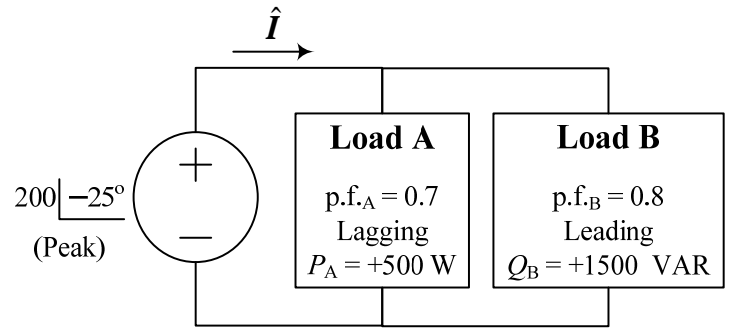(12) Load A and Load B are connected in parallel across a voltage source $200 \angle -35^\circ$ V (peak). Load A has a leading power factor (p.f.) of 0.7 with real power of +500 W. Load B has a lagging p.f. of 0.8 with reactive power +1500 VAR. Determine the current \hat{I} .



$\hat{I} =$ A