

King Fahd University



of Petroleum & Minerals

**Electrical Engineering Department
EE 204 Fundamentals of Electric Circuits
Second Semester (102)**

**Exam I
Wednesday, 16 March 2011
6:30 pm – 8:00 pm**

Name: _____

ID: _____

Section: _____

Instructors	Sections
Dr. Ahmad Yamani	1, 4, 6
Dr. Qureshi	2
Dr. Hammi	3
Dr. Adel Balghonaim	5
Mr. Noman Tasaduq	7
Dr. Wajih Abul Al-Saud	8, 10
Dr. Abdulmalik Zidouri	9, 11


Problem	Score	Out of
1		40
2		30
3		30
Total		100

Good Luck

Problem 1


a) In the following circuit, find

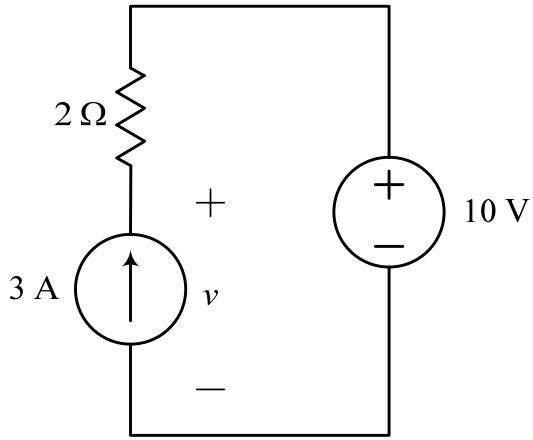- (i) the voltage v .
- (ii) the power associated with the 3A current source P_{3A} .




v	V
P_{3A}	W

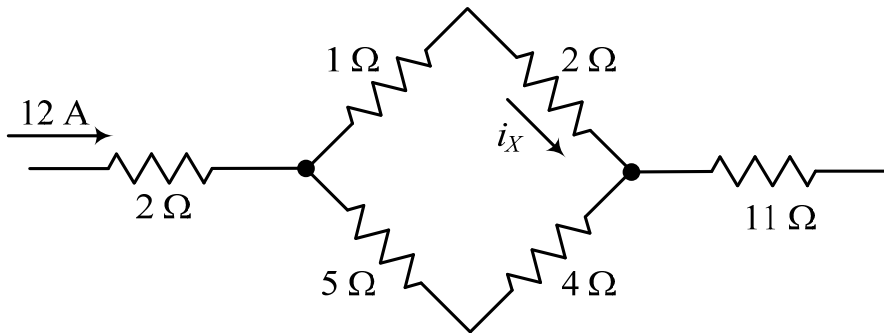b) Use current division to find the current i_X .




i_X	A
-------	---

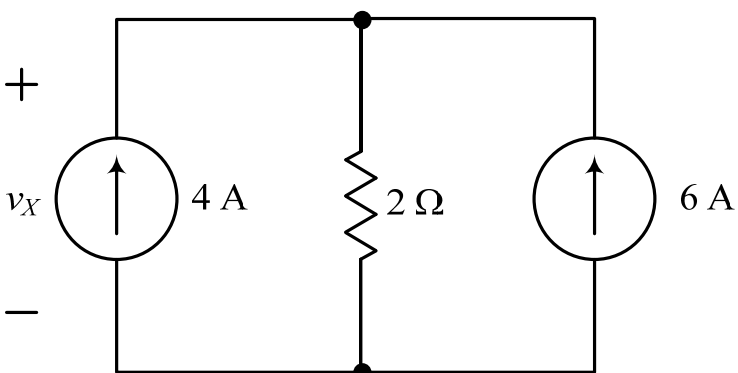c) Find the voltage v_X in the following circuit.



v_X	V
-------	---

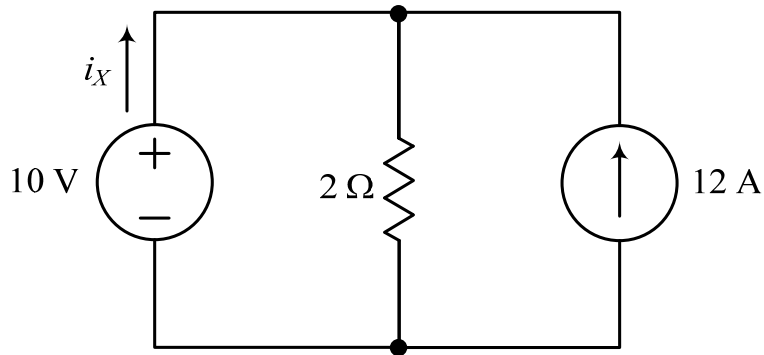
d) Find the current i_x in the following circuit.



i_x	A
-------	---


e) In the following circuit, find

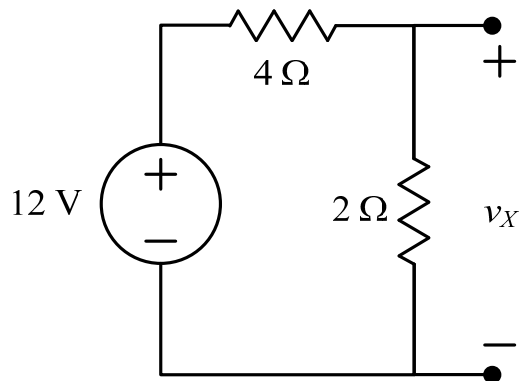- (i) the voltage v_x .
- (ii) the power associated with the 12V voltage source P_{12V} .



v_x	V
P_{12V}	W

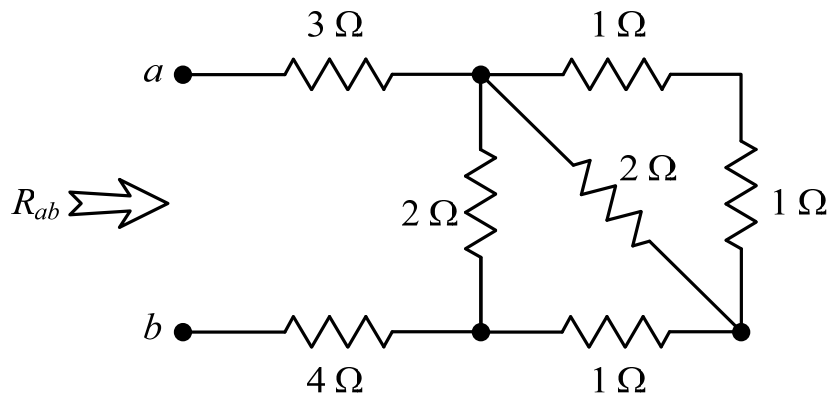
f) Find the equivalent resistance R_{ab} in the following.



R_{ab}	Ω
----------	---



g) In the following circuit, which of these statements is true

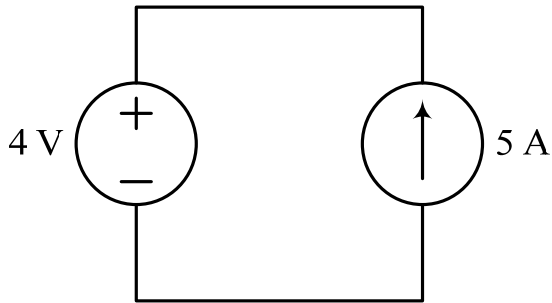- 1) Both sources are supplying 20 W of Power.
- 2) Both sources are absorbing 20 W of power.
- 3) The power in both sources is zero because no resistors exist to absorb the power.
- 4) The voltage source is supplying 20 W and the current source is absorbing 20 W.
- 5) The voltage source is absorbing 20 W and the current source is supplying 20 W.
- 6) It is not possible to determine the power supplied or absorbed by the two sources because no resistors exist in the circuit.
- 7) This circuit is invalid and the two sources should not be connected in this form.



Correct Statement	
-------------------	--

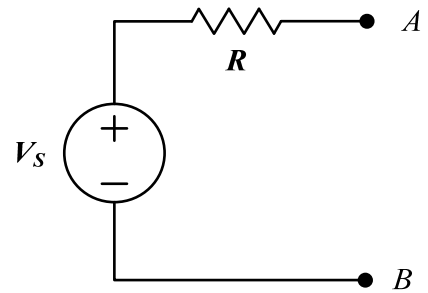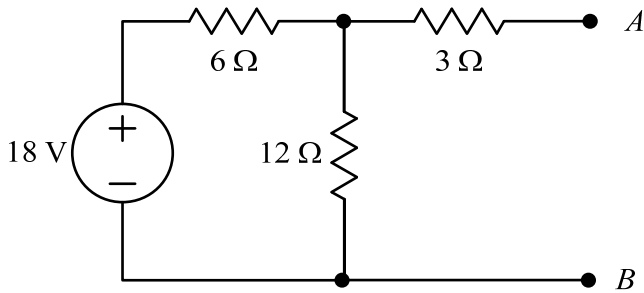h) Use source transformation to find the values of resistor R and voltage of the source V_S that make the two circuits seen between points A and B equivalent to each other.




V_S		V
R		Ω

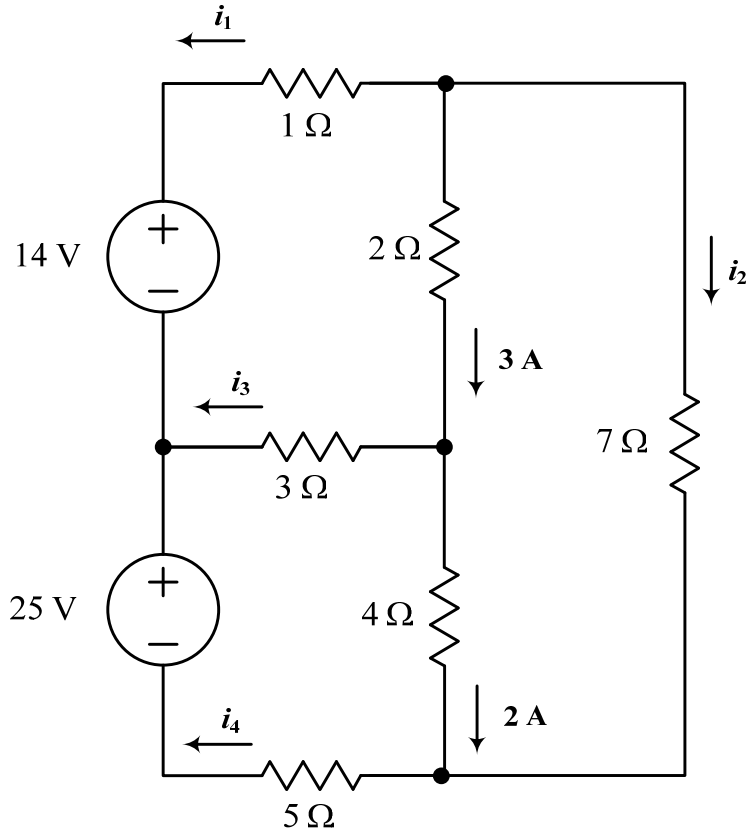Problem 2

In the following circuit,

- Find the currents i_1 , i_2 , i_3 , and i_4 .
- Find the powers associated with the two voltage sources (P_{14V} and P_{25V}).
- Find the powers in all resistors and determine if the law of conservation of power is satisfied or not (show your work).



i_1		A
i_2		A
i_3		A
i_4		A
P_{14V}		W
P_{25V}		W
Conservation of Power Satisfied?		

Problem 3

Using circuit reduction methods (series and parallel combination of resistors), find the value of the current i in the following circuit.

