

King Fahd University of Petroleum & Minerals

Electrical Engineering Department
EE 204 Fundamentals of Electric Circuits
First Semester (111)

Exam I
Wednesday, 12 October 2011
6:00 PM – 7:30 PM

Name: _____

ID: _____

Section: _____

Instructors

Dr. S. AL-AHMADI

Dr. M BIN SAEED

Dr. A. YAMANI

Dr. Z. AL-AKHDAR

Mr. T NOMAN

Dr. M MOHANDES

Dr. O. HAMMI

Problem	Score	Out of
1		10
2		10
3		10
Total		30


Good Luck!!

Problem 1

For the circuit shown,


- a) (5pts.) Determine the voltage V_x .
- b) (4pts) Calculate the power absorbed by the 60V voltage source.
- c) (1pt.) Is the 50V voltage source supplying or absorbing power?

a) $V_x =$
b) $P_{60V} =$
c) The 50V voltage source is : (circle the correct answer)
supplying absorbing

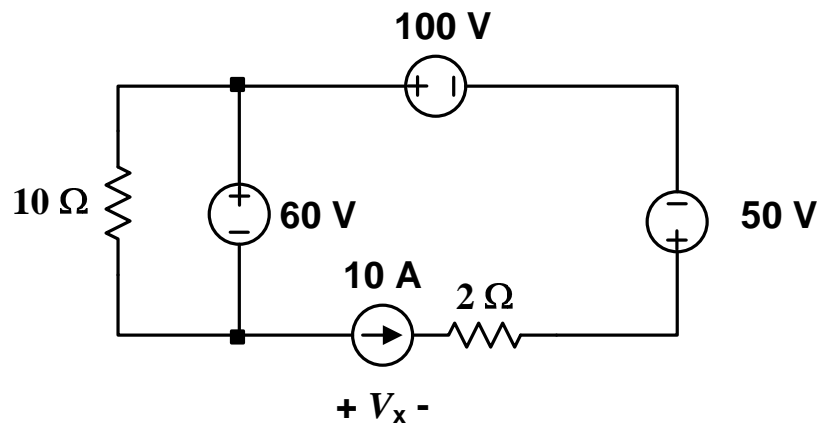


Problem 2

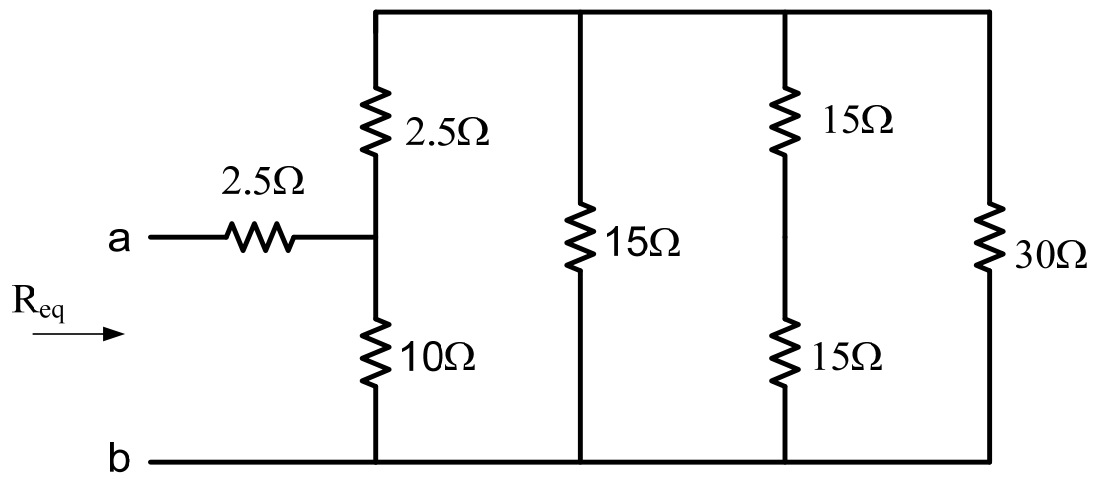a) (5 pts.) For the circuit shown below, determine the equivalent resistance R_{eq} between the terminals a and b.



$R_{eq} =$

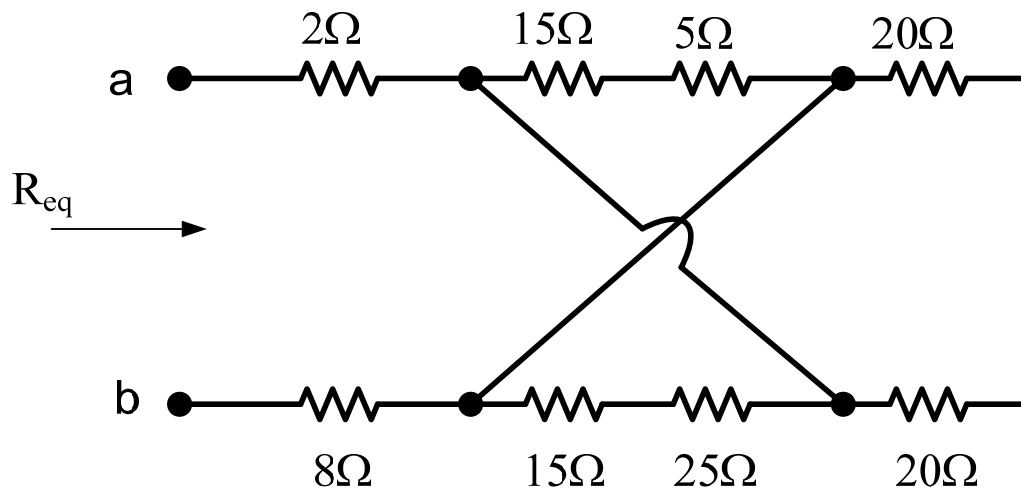b) (5 pts.) For the circuit shown below, determine the equivalent resistance R_{eq} between the terminals a and b.




$R_{eq} =$

Problem 3

a)

1. (2 pts.) Use **source transformation** to reduce the circuit shown to a single-node pair circuit, then

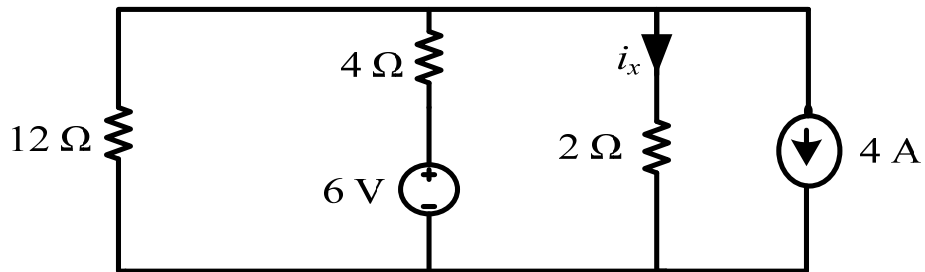2. (2 pts.) use **current division rule (CDR)** in the circuit obtained in part (1) to determine the current i_x .




$i_x =$

b)

1. (3 pts.) Use **source transformations** to reduce the circuit shown to a single loop circuit, then

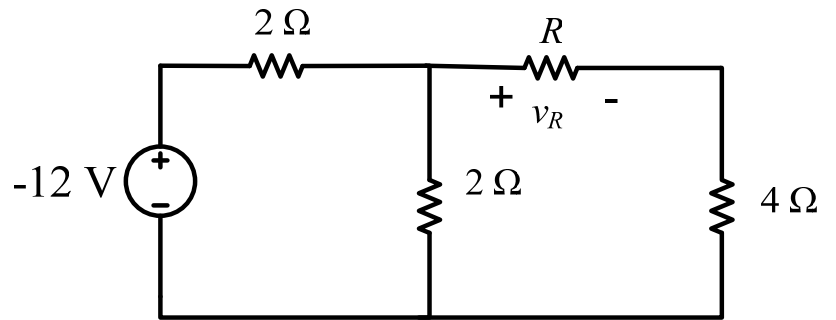2. (3 pts.) use **voltage division rule (VDR)** in the circuit obtained in part (1) to determine the value of the resistor R such that $v_R = -4 \text{ V}$.



$R =$