



King Fahd University of Petroleum & Minerals
Electrical Engineering Department
Winter 2012 (112)

EE 203 – Exam I
Saturday, March 3, 2012
6:00-7:30 PM

Name	
ID	

	Dr. M. Al-Gahtani	Dr. H. Al-Zaher	Dr. O. Hammi	Dr. W. Mesbah	Dr. H. Ragheb
Section	3 and 6	5	1, 4 and 8	7	2

Problem	Grade
1 (6 points)	
2 (6 points)	
3 (6 points)	
4 (6 points)	
5 (6 points)	
Total (30 points)	

Question 1:

For the circuit shown in Figure 1, the op amp is ideal.

- a) Find the range of values of σ for which the closed loop gain is such that $|G| \leq 20$ V/V.
Where the close loop gain is given by $(G=v_o/v_{in})$ [2 points]
- b) For $v_{in}=0.5\sin(1000t)$ V, find the maximum output current i_o when $\sigma=0.1$. [3 points]
- c) Determine the input resistance. [1 points]

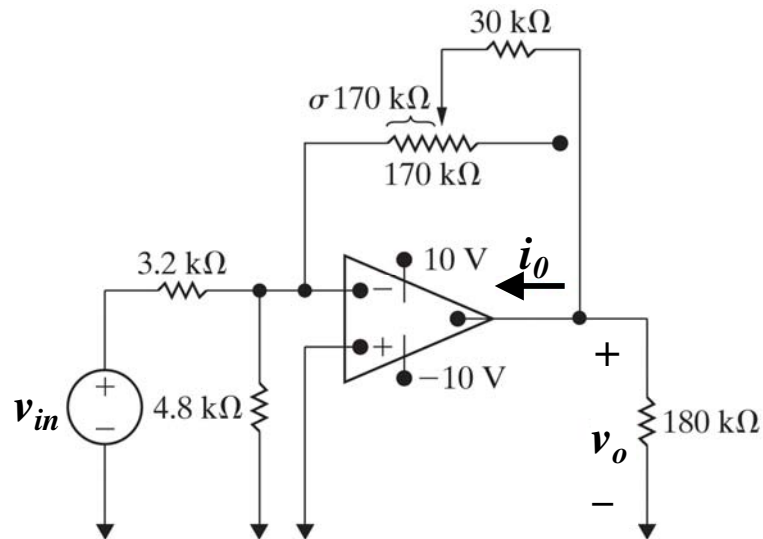


Figure 1

Question 2:

For the circuit shown in Figure 2, assume that all diodes have a constant voltage drop model with $V_D=0.7\text{ V}$. Calculate I and V_a , and determine the mode of operation of each diode (ON or OFF) in the following cases: **(Verify your Solution)** [6 points]

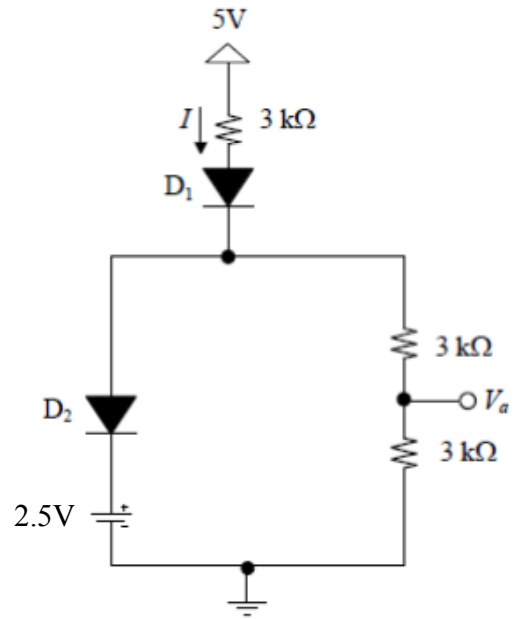


Figure 2

Question 3:

A 10-V Zener diode is used to regulate the voltage across a variable load resistor as shown in Figure 3. The input voltage varies between 13 and 16 V. The load current varies from 0 to 85 mA. The minimum Zener current is 15 mA.

- a) Calculate the maximum value of R . [3 points]
b) Calculate the maximum power dissipated by the diode for $R=40\Omega$. [3 points]

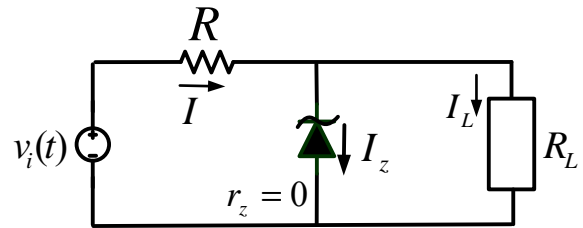


Figure 3

Question 4:

The rectifier circuit shown in Figure 4 is designed to deliver 30 volt DC to $100\ \Omega$ load with ripple voltage equal to 8% of the DC voltage

- a) Specify the value of n .
- b) Specify the value of C .

[3 points]

[3 points]

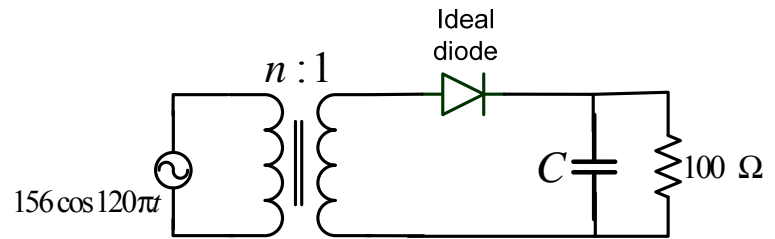


Figure 4

Question 5:

Draw the voltage transfer characteristics (**and show all key values**) for the circuit shown in Figure 5, assume the diodes are identical and have a constant voltage drop model with $V_D = 0.6 \text{ V}$. **[6 points]**

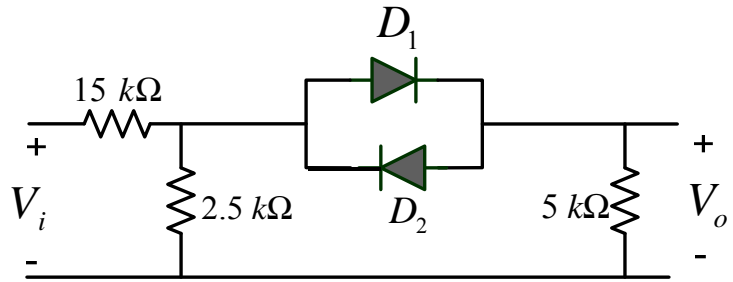


Figure 5

