



King Fahd University of Petroleum & Minerals  
Electrical Engineering Department  
Winter 2012 (112)

EE 203 – Exam II  
Wednesday, April 18, 2012  
6:00-7:30 PM

Name	
ID	

	Dr. M. Al-Gahtani	Dr. H. Al-Zaher	Dr. O. Hammi	Dr. W. Mesbah	Dr. H. Ragheb
Section	3 and 6	5	1, 4 and 8	7	2

Problem	Grade
1 (12 points)	
2 (12 points)	
3 (6 points)	
<b>Total (30 points)</b>	

**Problem 1 - A:**


For the circuit below, assuming the MOSFET operates in saturation (pinch off) mode and has  $V_t=2\text{V}$  and  $\mu_n C_{ox} W/L=0.8\text{mA/V}^2$ .

a) Determine  $I_D$ ,  $V_D$ , and  $V_S$ .

[5 points]

b) Verify the assumption on the transistor's mode of operation.


[1 points]

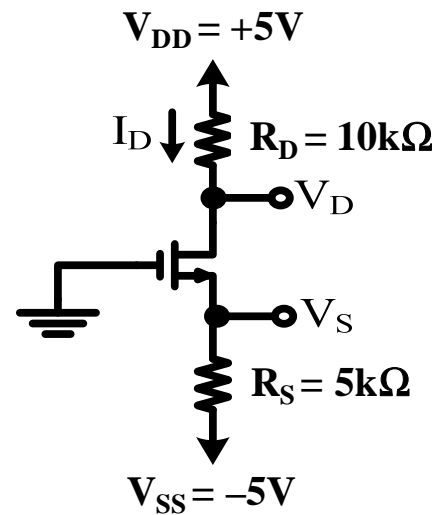

**Problem 1 - B:**

Design the below so that the MOSFET operates in saturation (pinch off) mode with  $I_D=0.5\text{mA}$  and  $V_D=3\text{V}$ . The MOSFET has  $V_t=-1\text{V}$  and  $k_pW/L=1\text{mA/V}^2$ .

- a) Given that  $R_{G1}=2\text{M}\Omega$ , find the values of  $R_{G2}$  and  $R_D$ . [4 points]  
b) Find  $R_D$  such that the transistor will work at the edge of saturation (pinch off). [2 points]

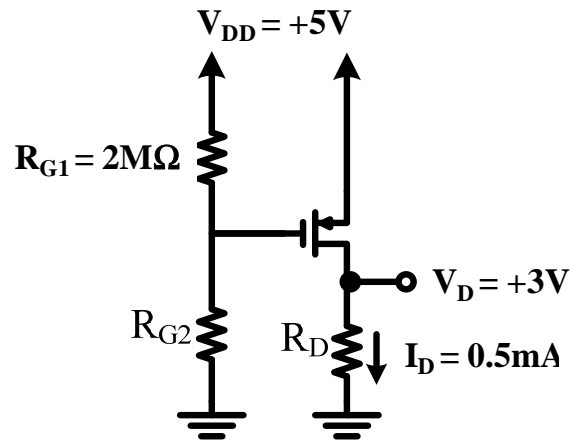


**Problem 2 - A:**

For the circuit shown below, the NMOS transistor operates into saturation (pinch off) mode. The transistor has channel length modulation ( $\lambda \neq 0$ )

a) What type of amplifiers is this? [2 points]

b) Draw the small-signal equivalent model for the whole circuit using the small signal  $\pi$ -model. [4 points]

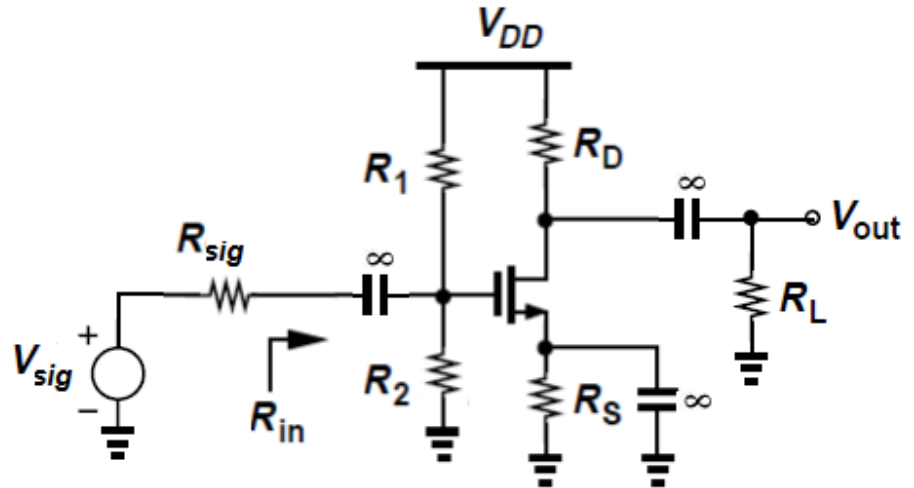


**Problem 2 - B:**

For the amplifier circuit shown below,  $\lambda=0$ ,  $I_A=1\text{mA}$ ,  $V_{tn}=1\text{V}$ , and  $k_n W/L=2\text{mA/V}^2$ .

- a) What type of amplifiers is this? [1 point]
- b) Calculate the amplifier transconductance ( $g_m$ ). [2 points]
- c) Derive the expression of the overall voltage gain ( $v_{out}/v_{sig}$ ) [3 points]

Note that  $v_{sig}$  is an AC source and all other sources are DC.

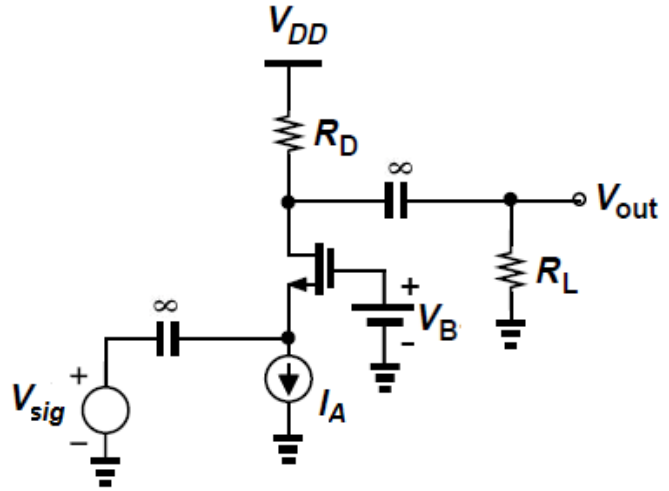

**Problem 3:**

The transistor in the circuit below has  $\beta=100$  and  $V_{BE(on)}=0.7V$ .

a) Find  $I_E$ ,  $I_C$ ,  $V_E$  and  $V_C$ ? Start the analysis by assuming that the transistor works in the active mode. [4 points]

b) Verify the mode of operation of the transistor. [2 points]

