



EE 203: Electronics I

Instructors: **Dr. H. Al-Zaher** (sections 1, 5)
Dr. M. Al-Gahtani (sections 3, 6)
Mr. N. Tasadduq (sections 4)
Dr. O. Hammi (sections 7)
Dr. H. Ragheb (sections 8)

Examination: Final Exam

Date : May 19, 2013

Time: 8:00-10:30 AM

Student Name:	
Student Number:	
Section Number:	

Problem 1	20	
Problem 2	20	
Problem 3	20	
Problem 4	20	
Problem 5	20	
Total	100	

Answer all questions showing all steps. More than one answer for the same problem are given zero mark.


Problem (1) [20 points]

Part 1: Select the correct answer in the following multiple choice questions (MCQs) [1 Mark each].

MCQ 1:

Compared to the inverting op-amp, the main advantage of the non-inverting op-amp shown in the circuit below is:

- A. its high output impedance.
- B. its high input impedance.
- C. its low output impedance.
- D. its positive gain.

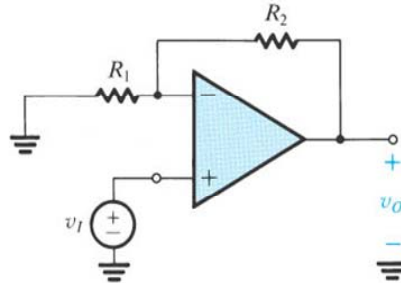

MCQ 2:

The instrumentation amplifier is a high performance version of:

- A. The inverting amplifier.
- B. The non-inverting amplifier.
- C. The difference amplifier.
- D. The weighted summer amplifier.

MCQ 3:

Peak inverse voltage for a diode is

- A. Maximum voltage across the diode working in forward direction.
- B. Maximum voltage across the diode working in the reverse direction.
- C. Minimum voltage across the diode working in the reverse direction.
- D. None of the above.

MCQ 4:

The BJT can be used as an amplifier if:

- A. The EB junction is reverse biased and CB junction is forward biased.
- B. The EB junction is forward biased and CB junction is reverse biased.
- C. The EB junction is forward biased and CB junction is forward biased.
- D. The EB junction is reverse biased and CB junction is reverse biased.

MCQ 5:

Which of the following amplifier configurations has high input resistance and low output resistance ?

- A. Common Emitter amplifier.
- B. Common Emitter amplifier with R_s .
- C. Common base amplifier.
- D. Common collector amplifier.

MCQ 6:


Which of the following relation is correct for BJT in saturation mode?

- A. $I_c = \beta I_B$
- B. $I_c < \beta I_B$
- C. $I_c > \beta I_B$
- D. $\beta I_c < I_B$

MCQ 7:

The sizes of PMOS transistors with input A and B in terms of the size of PMOS transistor of the basic inverter **p** are:

- A. $M_A=1p, M_B=1p$
- B. $M_A=1p, M_B=2p$
- C. $M_A=2p, M_B=1p$
- D. $M_A=2p, M_B=2p$

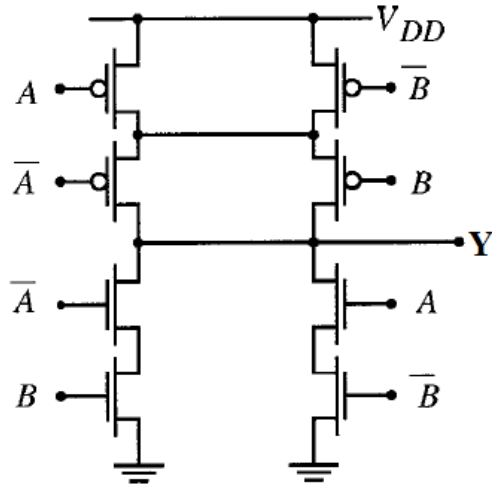

MCQ 8:


When the MOSFET operates in triode region it has a resistance r_{DS} which is:

- A. Proportional to (W/L) .
- B. Proportional to $1/(W/L)$.
- C. Proportional to $(W/L)^2$.
- D. Proportional to $1/(W/L)^2$.

MCQ 9:

Biasing the MOSFET as shown in the figure will place the transistor in:


- A. In the border between saturation (pinch-off) and triode regions.
- B. In the saturation (pinch-off) region when R_D is greater than R_G .
- C. In the saturation (pinch-off) region when V_{DD} is greater than V_t .
- D. In the saturation (pinch-off) region when R_D is less than R_G .

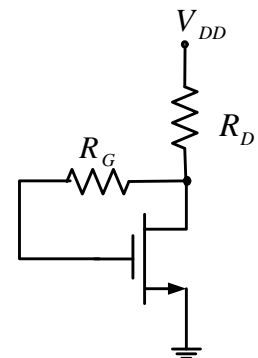

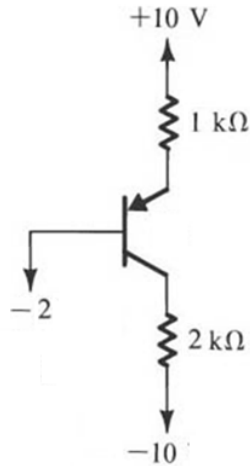Part 2: Fill in the blank (FIB) with correct values:


FIB 1 [4 Marks]:

The transistor in the circuit below has $\beta=100$, $V_{EB}(\text{on}) = 0.7\text{V}$ and $V_{ES}(\text{sat}) = 0.2\text{V}$. Given that the transistor is working in saturation, then the collector voltage $V_C = \dots\dots\dots$



FIB 2 [4 Marks]:

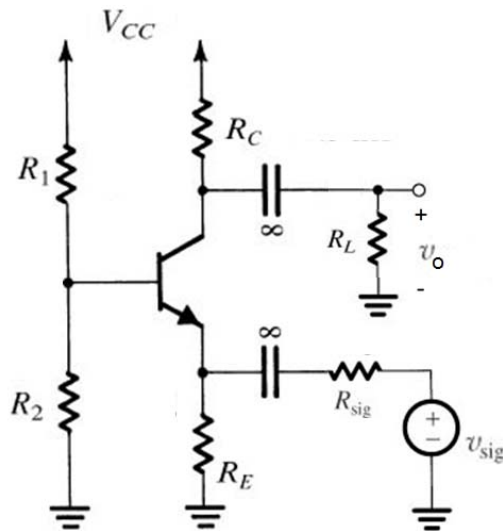The input resistance of the amplifier is given by $R_{in} = \dots\dots\dots$



FIB 3 [3 Marks]:

The VTC of an inverter is shown below, determine corresponding

$V_{OH} = \dots\dots\dots V$


$V_{OL} = \dots\dots\dots V$

$V_{IL} = \dots\dots\dots V$

$V_{IH} = \dots\dots\dots V$


$V_{NMH} = \dots\dots\dots V$

$V_{NML} = \dots\dots\dots V$

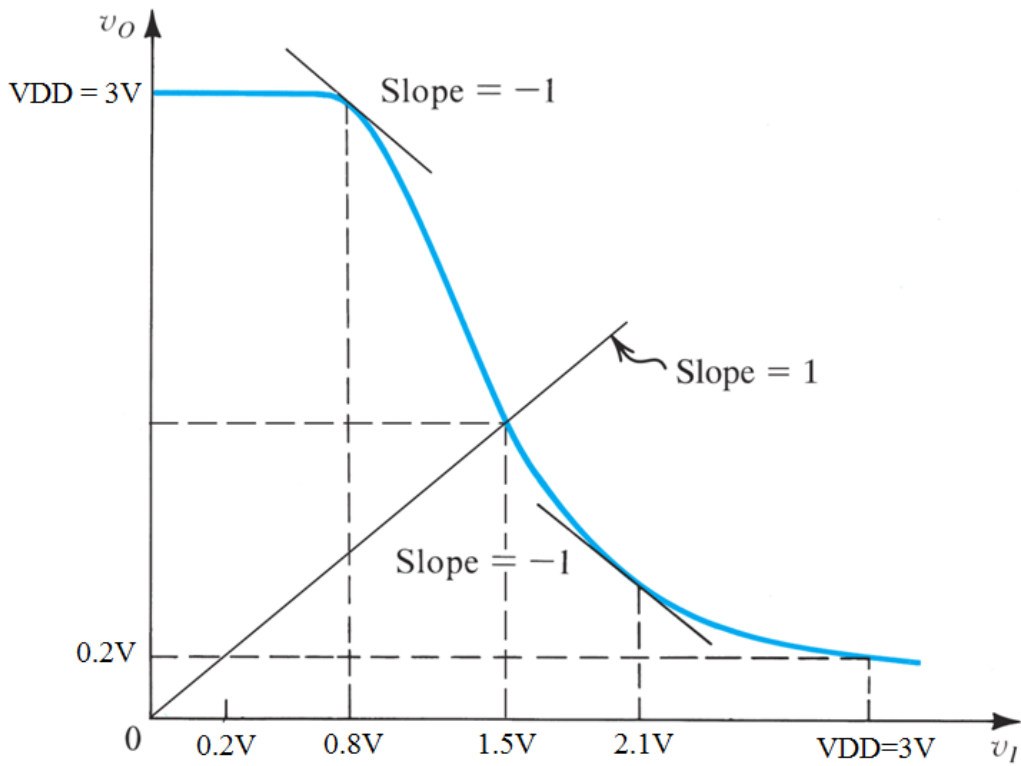


Problem (2) [20 points]

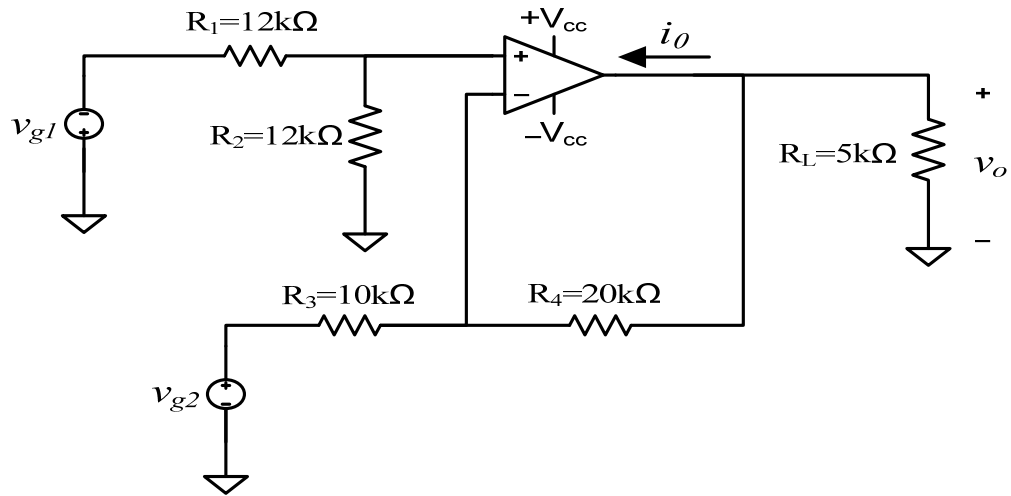A. For the ideal op-amp circuit show in the figure,
Find the expression of the output voltage v_o as a function of the input voltages v_{g1} and v_{g2} .



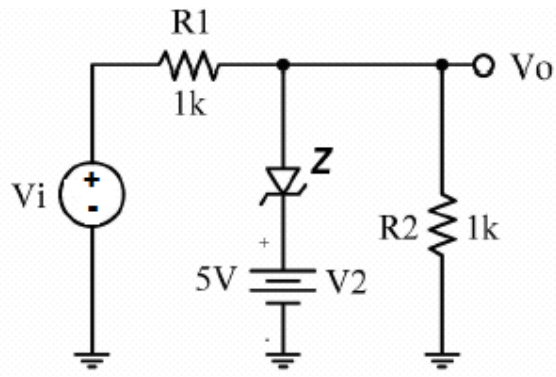B. For the circuit shown below, assume that the zener diode has $V_z=3.3V$ and $r_z=0\Omega$ when reverse biased, and has a $0.7V$ drop when forward biased. Fill the following table for values of V_o for different values of input voltage V_i .




V_i	V_o
-8V	
0V	
8V	

Problem (3) [20 points]

The CMOS in the amplifier circuit shown below has $V_t = 1.5 \text{ volt}$, $k'_n \frac{W}{L} = 2 \text{ mA/V}^2$. The current $I_D = 0.81 \text{ mA}$ and $R_D = R_L = R_s = 2 \text{ k}\Omega$. Neglecting the output resistance r_o of the transistor, determine:

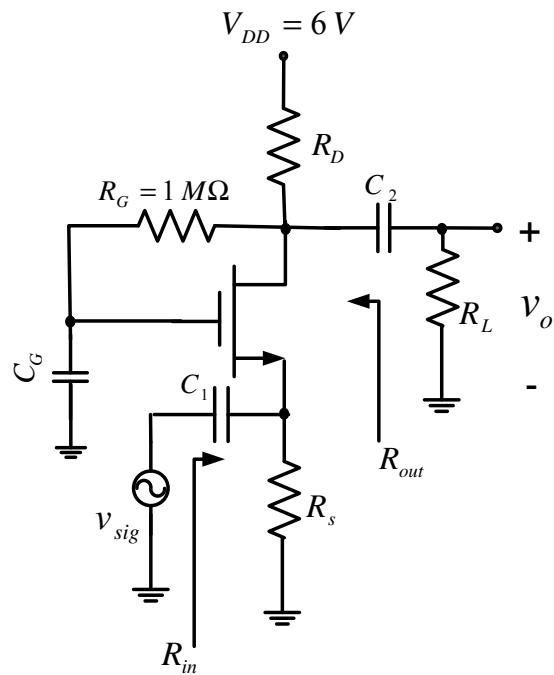- (a) DC biasing voltages (V_{GS} , V_{DS}).
- (b) Draw the small signal equivalent circuit.
- (c) The input resistance R_{in} .
- (d) The voltage gain v_o / v_{sig} .
- (e) The output resistance R_o .




Problem (4) [20 points]

Consider the circuit shown below, with the BJT transistor operating in active region. Select the value of the DC current ' I ' and the value of the resistor ' R_C ' such that:


$$R_{in} = 5k\Omega, \frac{v_{out}}{v_{sig}} = -75 \frac{V}{V},$$

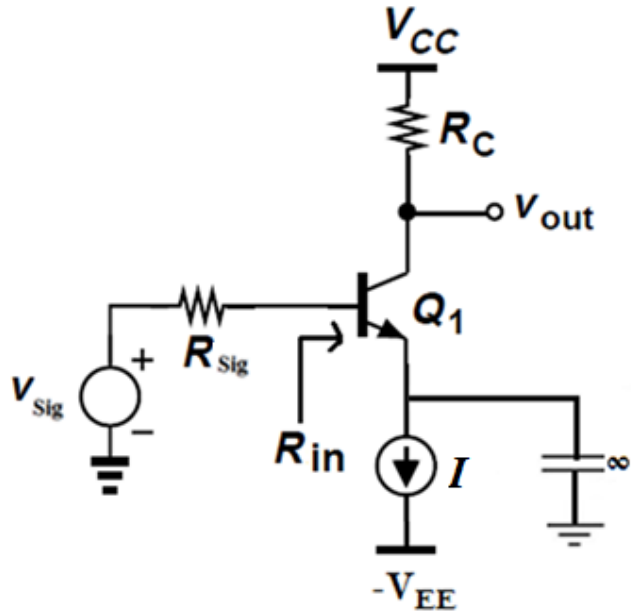Neglect r_o and assume $\beta=100$, $R_{sig}=1k\Omega$ and $V_{CC} = V_{EE} = 5V$.



Problem (5) [20 points]

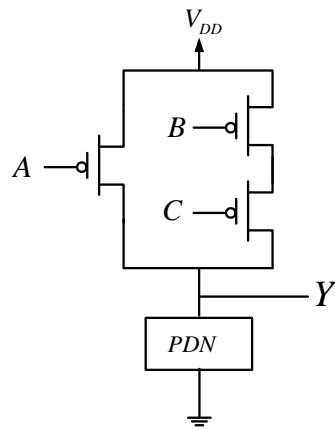1. In addition to Fan-In and Fan-Out, list another four of the main design parameters of logic gates.
 - (i)
 - (ii)
 - (iii)
 - (iv)
2. Determine the logic function Y realized by the given logic gate.



3. Design a CMOS logic gate with minimum number of transistors to implement the function X. Then expand the design to implement the logic function Y with minimum number of transistors as well.

$$X = \overline{(A + B).C}$$

$$Y = \overline{((A + B).C.D) + E}$$

4. Design a 2 by 1 multiplexer using pass transistor logic (Transmission gates) that selects one of four inputs from A and B depending on the selection bit S1.

Draw the complete circuits shown all transistors including the inverter.