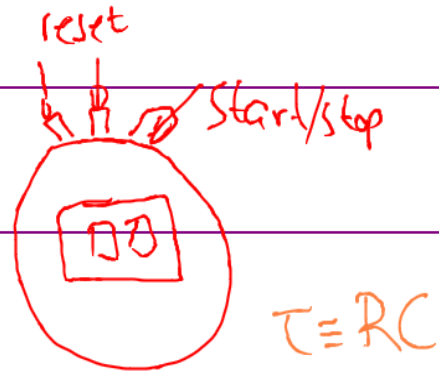


Stopwatch




q, C, V
 $C \equiv q/V$
 $V = q/C$
 $q = CV$
 $Q = C\varepsilon$



charging of capacitor

$q(t) = Q(1 - e^{-t/\tau})$

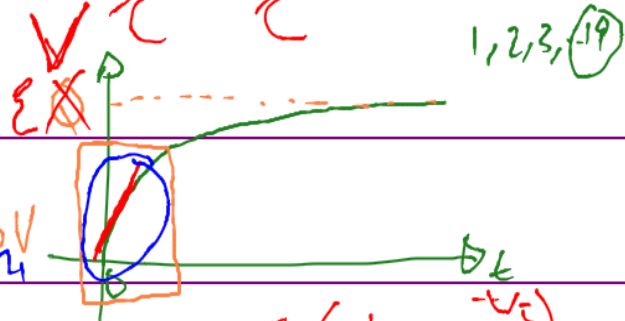

approximation

$e^x = 1 + \frac{x}{1!} + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$

$e^{-t/\tau} \approx 1 - \frac{t/\tau}{1!} + \frac{(t/\tau)^2}{2!} - \frac{(t/\tau)^3}{3!} + \dots$

$t \in [0, 300] \text{ s}$

$RC = \tau \gg 300$

$0.03 = \frac{300}{\tau}$

good for maximum 5 min


t/τ

$(t/\tau)^2$

$(t/\tau)^3$

9×10^{-4}

27×10^{-6}

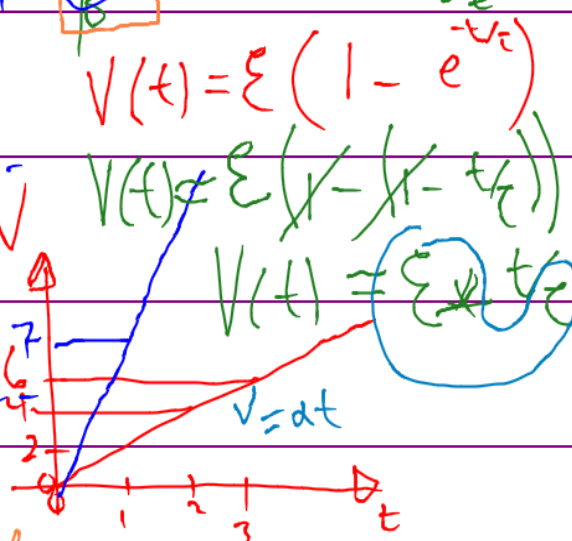

10090 >> 0.0009 >>>

$\epsilon = 10 \text{ volt}$ $\tau = 10^4 = R * C$

300

$10^4 = R * 10 * 10^{-6}$


$R = 10^9 = 1000 \text{ M}\Omega$

$V(t) = \frac{20}{10000} t$

$10^5 * 10^9$

$t = \frac{1000}{500} * V(R)$

$R = 5 \text{ M}\Omega = 5 * 10^6$

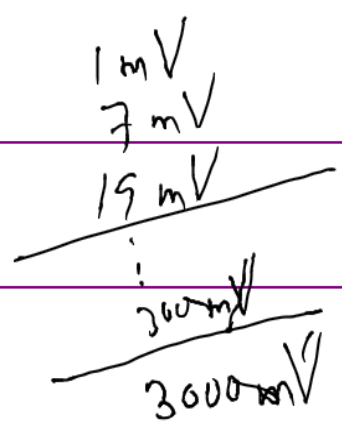

$RC = 10000$


$5 * 10^6 C = 10^4$

$\therefore C = \frac{1}{5} * 10^{-2} = 2 * 10^{-3}$
 $C = 2 \text{ mF}$

~~$t = 3000$~~

Digital Electronics

01234--9

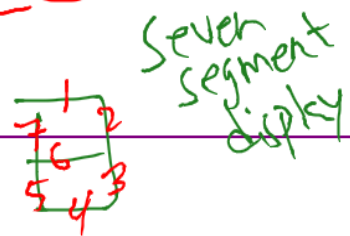

Seven segment display

$t = 1000 \text{ V}$

