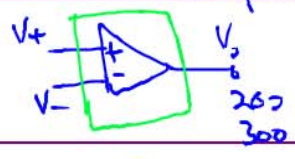


1.1.13

Amplifier


numerical computation
output

ideal amplifier





operational amplifier 741

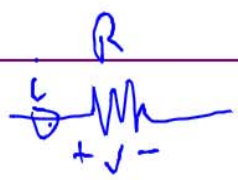2 rules operation +, -, *, $\frac{d}{dt}$




$$P(t) = i(t) * V(t)$$

$$\int \frac{d}{dt}$$

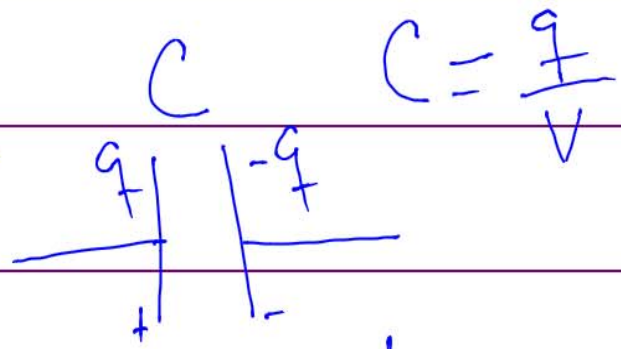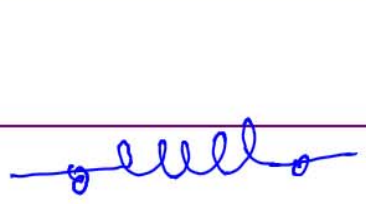


$$V = V_+ - V_-$$

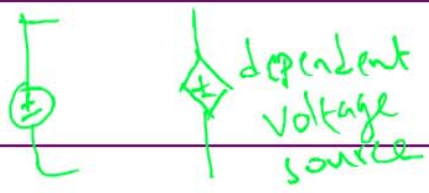

$$V = iR$$

$$5 - 7 = -2V$$

vert ground // 0 volt

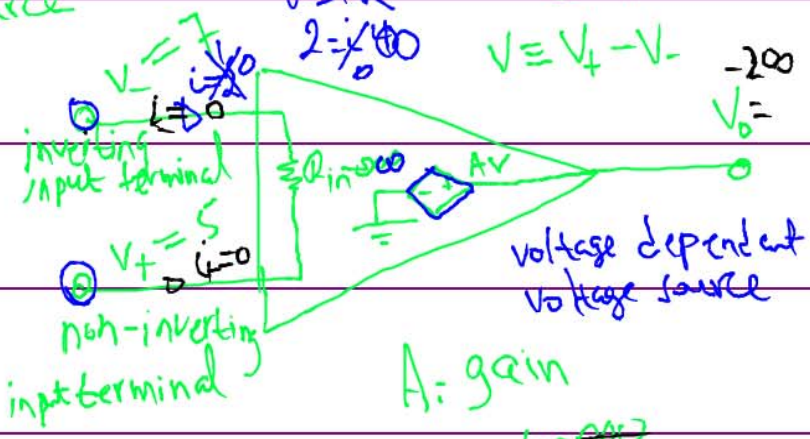

A: gain
~ 100000

Totally


$$V_0 = A V$$

$$\Rightarrow V_+ - V_- = 0$$

$V_+ = V_-$

① No current goes into the input terminals $A(V_+ - V_-) = V_o$

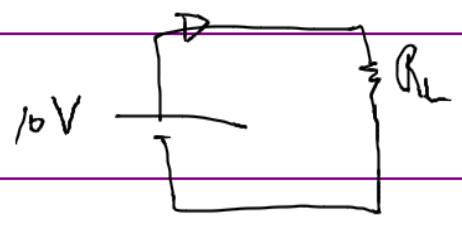② V_o is independent of what is connected to the amplifier



Load i
 \sum
 \checkmark
 \times
 \checkmark
 $\{$

good amplifier (eg. 741)
 $A \rightarrow \infty$

$A = 10$
 100
 600
 700000

Approximation

① $V_+ = V_-$

② $i_+ = i_- = 0$


Two simple rules for analyzing OPAMP Circuits

OPAMP Circuits $V_+ = 4$
 $V_- = 4$

$V \equiv V_+ - V_- = 0$

ideal

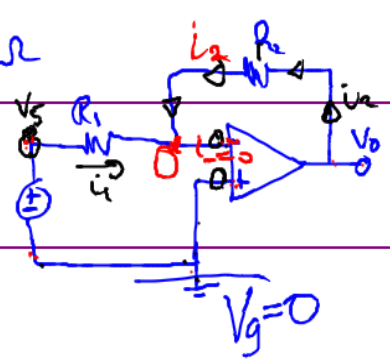
$R_1 = 400\Omega$
 $R_2 = 5000\Omega = 5k\Omega$
 $V_s = 0.005V = 5mV$



V_s : signal potential

$V_o(R_1, R_2, V_s)$

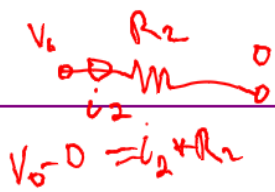KCL: $i_1 + i_2 = 0 \Rightarrow i_2 = -i_1$



$$V_o - 0 = i_2 R_2$$

$$V_s - 0 = i_1 R_1$$

$$V_o = -i_1 R_2$$

$$V_s = i_1 R_1$$

+ -

* $\int \frac{d}{dt}$

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1}$$

inverting amplifier

$$R_2 = R_1 = 4k\Omega$$

$$\frac{V_o}{V_s} = -\frac{4000}{4000} = -1$$

$$V_o = -V_s$$

$$\frac{V_o}{V_s} = -\frac{50\mu\text{V}}{4\mu\text{V}} = -12.5$$

$$V_s = 5\text{mV}$$


$$V_o = -5 * 12.5 = -62.5\text{mV}$$

$$-62.5\text{mV}$$

non-inverting amplifier

$$V_+ = V_-$$

$$i_+ = i_- = 0$$

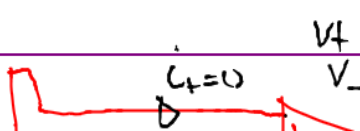


$$V_+ = V_s$$

$$V_- = V_o$$

$$V = 0 = V_+ - V_-$$

V_o

$$V_+ = V_-$$

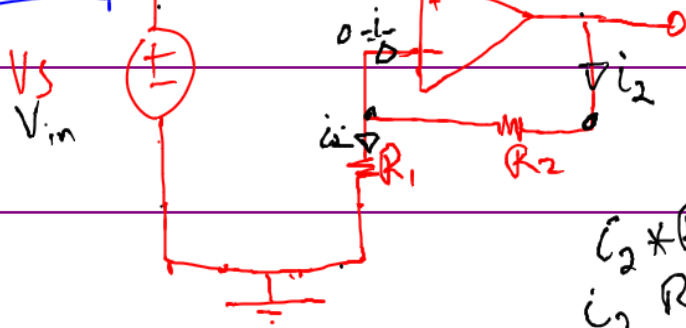

$$i_2 R_2 = V_o - V_s$$

$$i_2 R_1 = V_s - 0$$

$$V_o = i_2 R_2 + i_2 R_1 = i_2 (R_1 + R_2)$$

$$V_s = i_2 R_1$$

$$\frac{V_o}{V_s} = \frac{i_2 (R_1 + R_2)}{i_2 R_1} = \frac{R_1 + R_2}{R_1}$$

$$\frac{V_o}{V_s} = 1 + \frac{R_2}{R_1}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_s$$

$$R_2 = 5000 \Omega$$

$$R_1 = 400 \Omega$$

$$V_s = -5 \text{ mV}$$

$$V_o = 13.5 \times 5 \text{ mV}$$

$$= -67.5 \text{ mV}$$


$$V_o = 40V_a + 62V_b$$

Adding / Summing amplifier
 V_A, V_B

$$V_o \approx V_A + V_B$$


$$60000 (V_A + V_B)$$

Interaction:

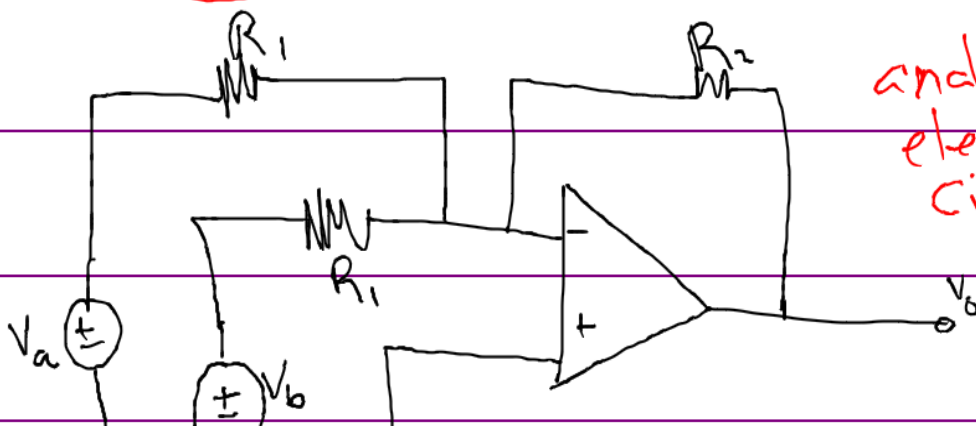

analysis of
 electronic
 circuits

$$V_a > 0$$

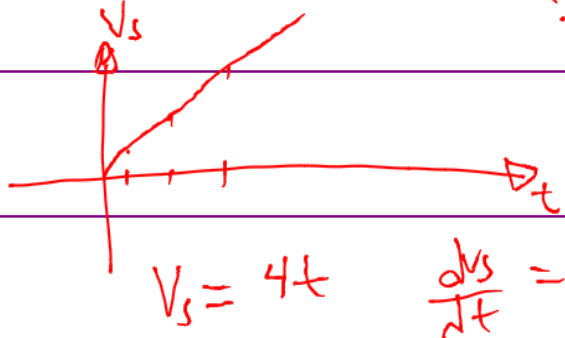

$$V_o = - \left(\frac{R_1}{R_1 + R_2} \right) (V_a + V_b)$$



$$V_o = -1 * 4 = -4$$

$$C \frac{dV_s}{dt} = i_1$$

$$V_o - 0 = i_2 R$$

$$-RC \frac{dV_s}{dt} = V_o$$

KCL

$$i_1 + i_2 = 0$$

$$i_2 = -i_1$$

$$i_1 = i_2 = 0$$

$$R = 100k\Omega$$

$$C = 10\mu F$$

$$40t = 2\pi 20t$$

$$V_s = 50 \sin\left(\frac{40t}{\pi}\right) \text{ mV}$$

$$V_s(t) = 50 \sin(2\pi 20t) \text{ mV}$$

$$f = 20 \text{ Hz}$$



$$RC = 1s$$

$$RC = 100 * 10^3 * 10 * 10^{-6} = 1s$$

$$\frac{dV_s}{dt} = 50 * 40\pi \cos(2\pi 20t) \text{ mV/s}$$

$$V_o = -1 / 2000\pi \cos(40\pi t) \text{ mV/s}$$

$$= -2000\pi \cos(40\pi t)$$

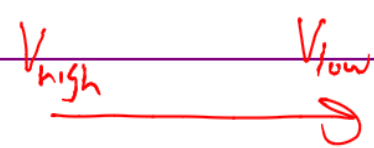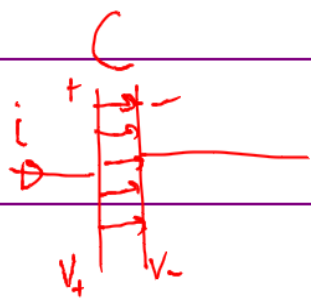

$$V \equiv V_+ - V_- > 0$$

$$C = \frac{q}{V}$$

$$\frac{d}{dt} CV = \frac{dq}{dt}$$

$$C \frac{dv}{dt} = i$$