

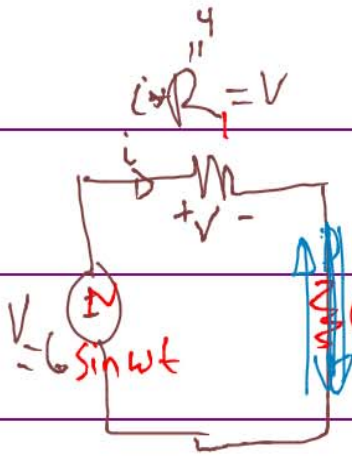


Time domain

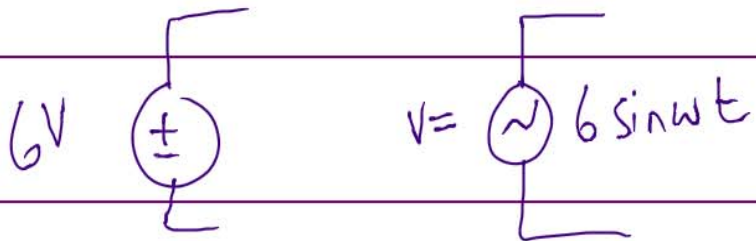

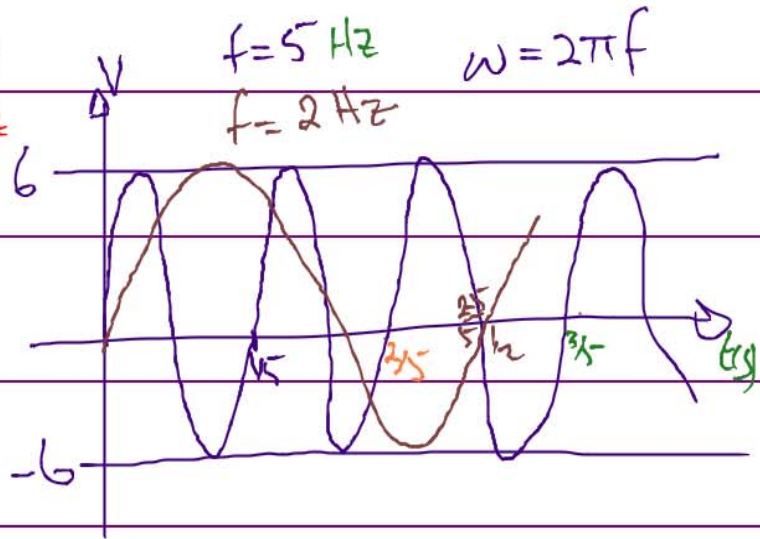$i \times R_1 = V$
 $\omega = 2\pi \times 40$
 $f = 40 \text{ Hz}$
 $Ht = 5'$
 $R_2 = 2 \Omega$




$i \times 4 = 6$
 $i = 6/4 = 1.5 \text{ A}$

$V = iR$
 $6 \sin 80\pi t = i \times 4 \Rightarrow i = 1.5 \sin 80\pi t$
 $= 1.5 \sin (2\pi \times 40 t)$


$i = 1 \sin (2\pi \times 40 t)$

$\epsilon_0 \approx 8.85 \times 10^{-12}$

$C = \epsilon_0 \frac{A}{d}$

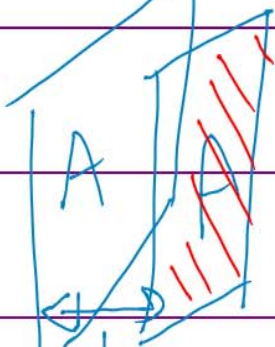

Capacitors:

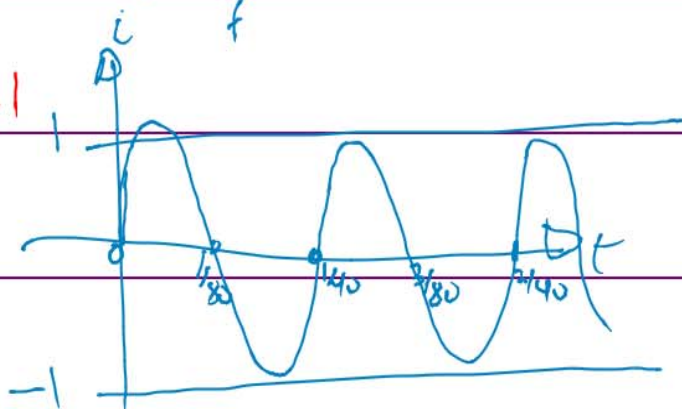


$5 \rightarrow 3, -5 \rightarrow -3$




$V = V_+ - V_-$

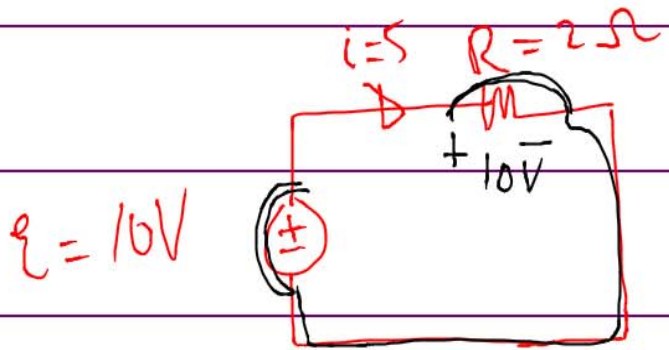
$C = \frac{9}{V}$
 $5 \rightarrow 3$
 $50 \rightarrow 30$



$$KVL = \sum V_j = 0$$

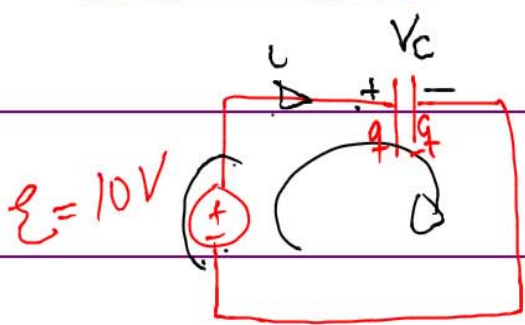

$$V_c = 10 \text{ Volt}$$

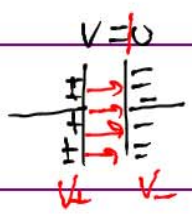

$$C = 2 \mu F$$

$Q = \mu \times 10^{-6}$

$$C = \frac{q}{V}$$


$$V = \frac{q}{C}$$

$$2 \mu F = \frac{q}{10V}$$

$$q = 20 \mu C$$



$t=0^+$ KVL: $\mathcal{E} + V_R + V_c = 0 \Rightarrow \mathcal{E} = iR$

$$C = \frac{q}{V} \text{ F}$$

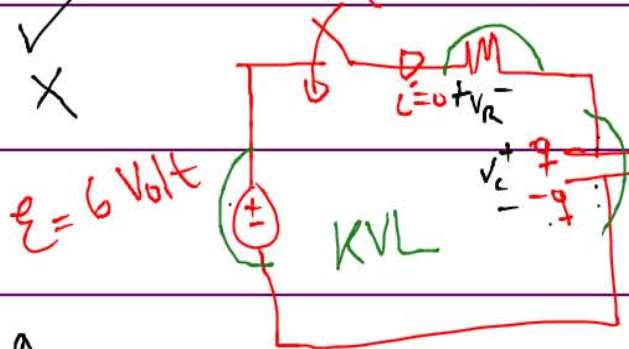

$t=0$ $R = 4000 \Omega$ $i = \frac{\mathcal{E}}{R}$

$$V_R = iR$$

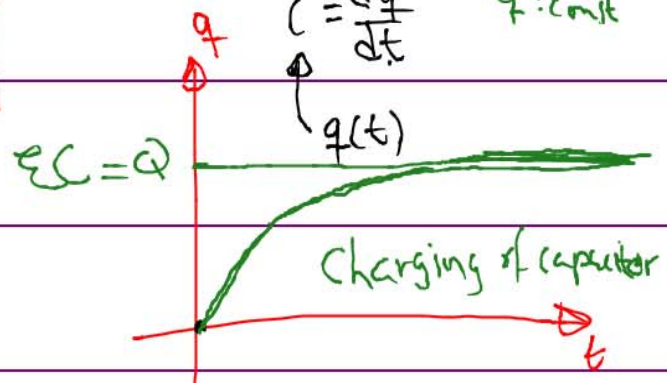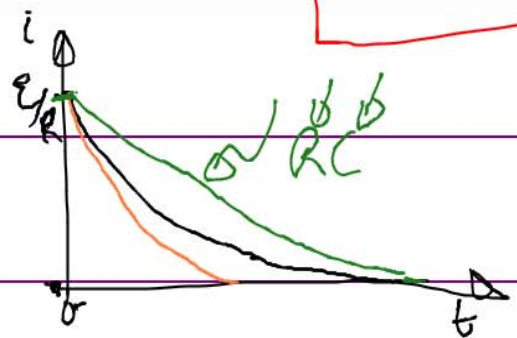

$t \rightarrow \infty$ $V_c = \frac{Q}{C} = \mathcal{E}$

$V_R = 0$

$$\mathcal{E} - V_R - V_c = 0 \Rightarrow \mathcal{E} = V_c = \frac{Q}{C}$$

$$\mathcal{E} - iR - q/C = 0 \Rightarrow \boxed{\frac{q}{C} + R \frac{dq}{dt} = \mathcal{E}}$$

$$Q = \mathcal{E}C$$

first order linear differential Eqn.

$$q(t) = Q \left(1 - e^{-t/RC} \right) \quad e^{-\infty} = 0$$

$$i(t) = \frac{dq}{dt} = \frac{Q}{RC} e^{-t/RC} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$i(0) = \mathcal{E}/R$$

$$i(t \rightarrow \infty) = 0$$




$$e^{-10} \approx 0$$

$$e^0 = 1$$

$$e^{-\infty} \rightarrow 0$$

$$t = 10\tau$$
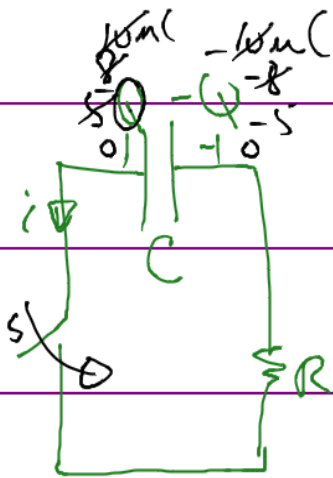
$$RC \equiv \tau \quad \text{time constant}$$




First order circuit

تفريغ
discharging $\tau = RC$

$$q(t) = Q e^{-t/\tau}$$
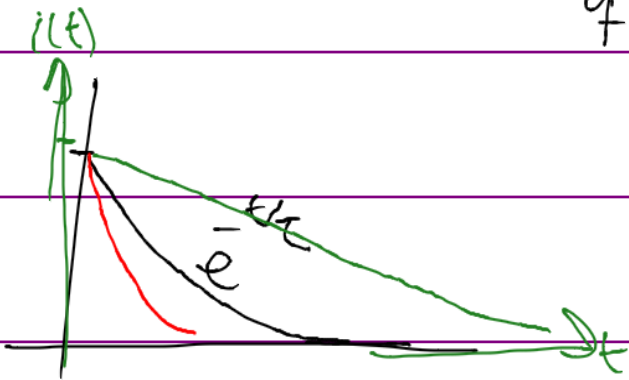
$$\approx 0 \quad t \rightarrow \infty \quad e^{-\infty} = 0$$



$$t = 10\tau = 10RC$$

$$e^{-10} \approx 0$$

$$i(t) = \frac{dq}{dt} = \frac{Q}{\tau} e^{-t/\tau}$$

$$i(0) = \frac{Q}{\tau} = 1$$

$$i(t \rightarrow \infty) = \frac{Q}{\tau} e^{-\infty} \rightarrow 0$$

~~882ktz~~
information

Filters:


Demodulation $R * F = S$
 $R = 1000 \Omega$

$\omega = 2\pi f = \frac{2\pi}{T}$

$C = 4 \mu F$
 $\tau = RC = 400 \mu s$

$V(t) = V_0 \sin \omega t$

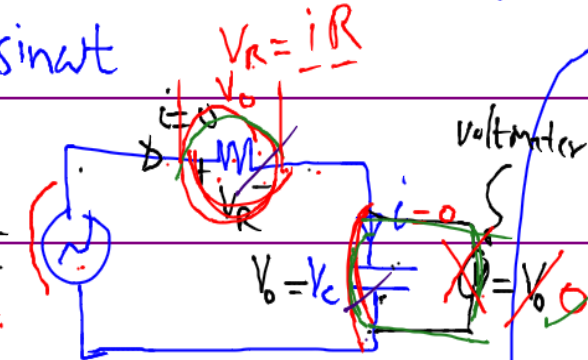$V(t) = V_1 \sin \omega_1 t + V_2 \sin \omega_2 t$




$C = \frac{q}{V}$
 $V = \frac{q}{C}$
 $\frac{dV}{dt} = \frac{1}{C} \frac{dq}{dt}$
 $C \frac{dV}{dt} = i$

$\approx 400 \mu s$
 $4ms = 4000 \mu s$
 $\tau \ll T$

$V_1 = 4mV$ $\omega_1 = 100$
 $V_2 = 5mV$ $\omega_2 = 600,000$

$\omega \rightarrow 2000000000 Hz$

~~low~~ pass filter ✓

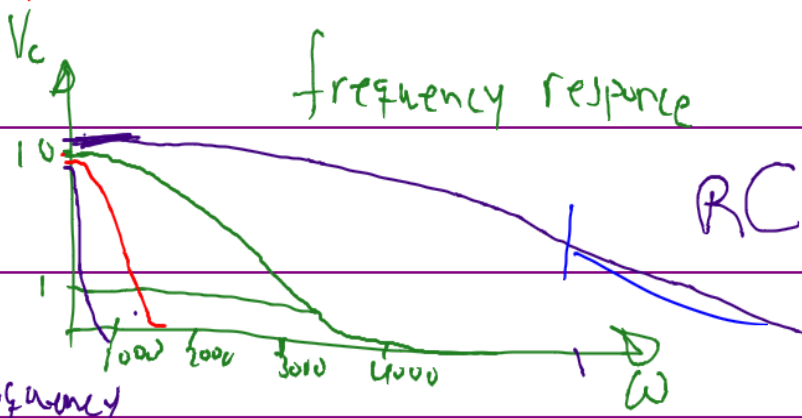

breaking frequency

$R = 1000 \Omega$ $C = 4 \mu F$
 $\omega_B = \frac{1}{RC} = \frac{1}{4 \times 10^{-3}} = \frac{1000}{4} = 250 Hz$
 $\frac{1}{RC} = 1000$

$\omega_B = 1000 Hz$

LPF

$\omega \ll \omega_B$

$\omega \gg \omega_B$

V_C big ✓
 $V_C \sim 0$ ✗

High pass filter

HPF

$$\omega \ll \omega_B$$

$$V \sim 0$$

$$\omega \gg \omega_B$$

$$V \text{ big}$$

200 - 2000 Hz

20 - 20,000

Voutput



$$f = 882 \text{ kHz}$$

