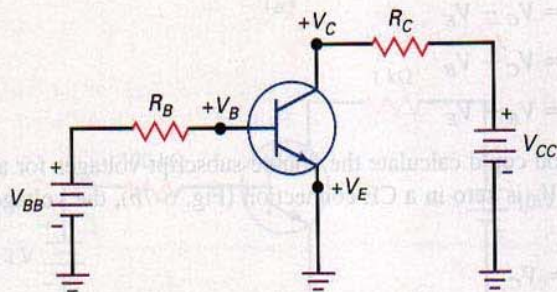


(a)



(b)

FIGURE 6-7 CE connection. (a) Basic circuit; (b) circuit with grounds.

Handwritten notes:
 $V_{BE} = 0.7V$
 $V_{CE} = V_{CC} - I_C R_C$

