

Name:

Id#



COE 301/ICS 233, Term 171

Computer Architecture & Assembly Language

Quiz# 5

Date: Tuesday, Nov. 28, 2017

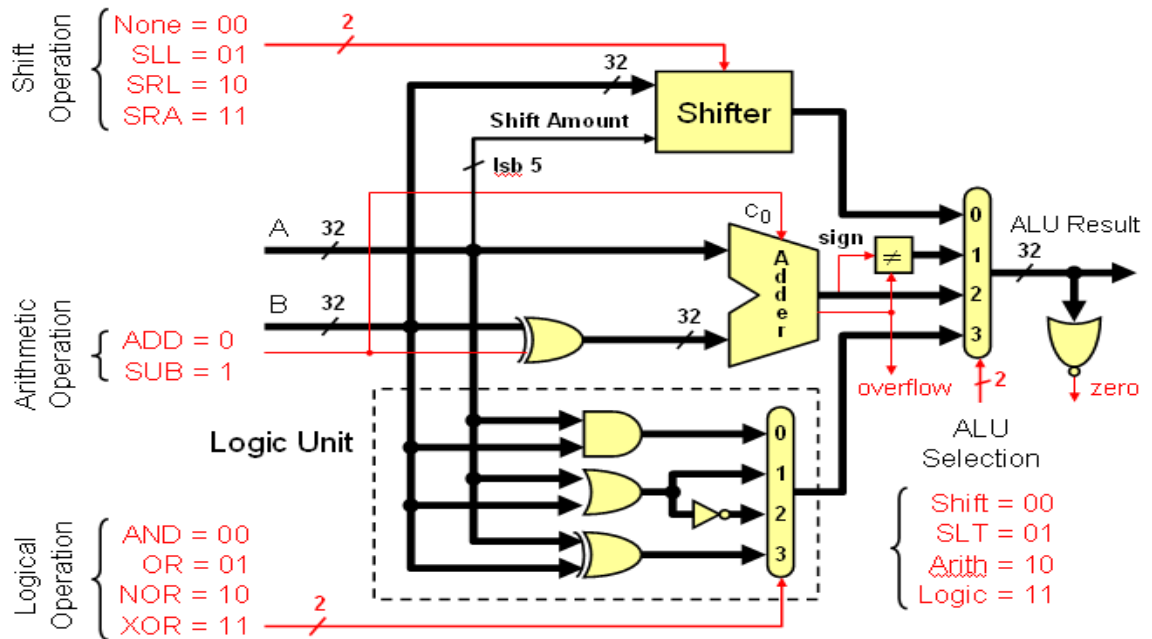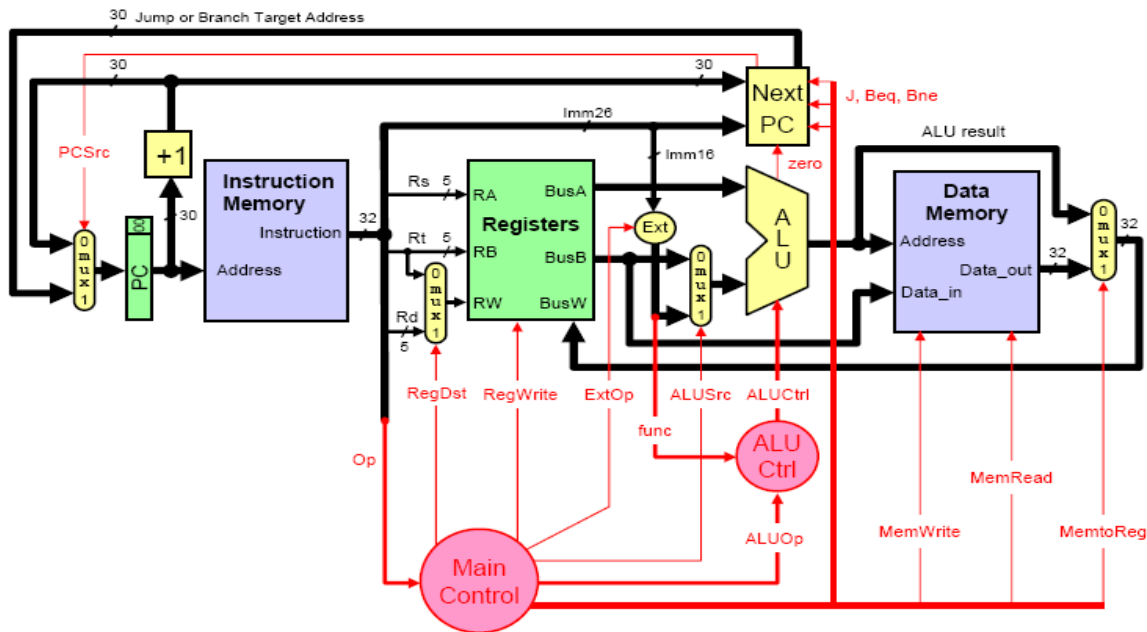Q1. Consider the single-cycle datapath and control given below along with ALU design for the MIPS processor implementing a subset of the instruction set:



- (i) Show the control signals generated for the execution of the following instructions by filling the table given below: **(5 points)**

Op	RegDst	RegWrite	ExtOp	ALUSrc	ALUOp	Beq	Bne	J	MemRead	MemWrite	MemtoReg
R-type											
slti											
sw											
beq											
j											

- (ii) Excluding the ALUOp, Beq, Bne and J signals, show the design of the control unit for the control signals given in the table above based on the given instructions. Assume that the opcode of these instructions is a 6-bit opcode such that the opcode for R-type instructions is 0, the opcode for slti is 1, the opcode for sw is 2, and so on for the rest of the instructions. **(5 points)**

(iii) Show the design of the Next PC block. (4 points)

(iv) We wish to add the following instructions to the MIPS single-cycle datapath. Add any necessary datapath modifications and control signals needed for the implementation of these instructions. Show only the **modified** and **added** components to the datapath.

a. sra (3 points)

Instruction		Meaning	Format					
sra	rd, rt, imm ⁵	rd = rt >> imm ¹⁶	Op ⁶ = 0	0	rt ⁵	rd ⁵	Imm ⁵	f ⁶ = 3

b. jr (3 points)

Instruction		Meaning	Format					
jr	rs	PC=rs	op ⁶ = 0	rs ⁵	0	0	0	8

(v) Assume that the propagation delays for the major components used in the datapath are as follows:

- Instruction and data memories: 120 ps
- ALU and adders: 30 ps
- Register file access (read or write): 14 ps
- Main control: 8 ps
- ALU control: 7 ps

Ignore the delays in the multiplexers, PC access, extension logic, and wires. What is the cycle time for the single-cycle datapath given above? **(3 points)**