

## COE 405, Term 162

### Design & Modeling of Digital Systems


#### Assignment# 1 Solution

Due date: Saturday, March 4

**Q.1.** Consider the two functions  $f=(a \oplus b) + (a \oplus c)$  and  $g=a b + a' c + b' c'$ .

 (i) Implement the function  $f$  using only 2x1 MUXs and inverters minimizing the number of MUXs used.

$$\begin{aligned} f &= a' (b + c) + a (b' + c') \\ &= a' (b' (c) + b (1)) + a (b' (1) + b (c')) \end{aligned}$$



(ii) Compute the function  $f \oplus g$  based on orthonormal basis expansion.

$$f = a' b' (c) + a' b (1) + a b' (1) + a b (c')$$


$$\begin{aligned} g &= a' (b' + c) + a (b + c') \\ &= a' (b' (1) + b (c)) + a (b' (c') + b (1)) \\ &= a' b' (1) + a' b (c) + a b' (c') + a b (1) \end{aligned}$$

$$\begin{aligned} f \oplus g &= a' b' (c \oplus 1) + a' b (1 \oplus c) + a b' (1 \oplus c') + a b (c' \oplus 1) \\ &= a' b' (c') + a' b (c') + a b' (c) + a b (c) \\ &= a' c' + a c \end{aligned}$$

**Q.2.** It is required to design an iterative combinational circuit that computes the equation  $Z=3*X-3$ , where  $X$  is an  $n$ -bit unsigned number.

 - (i) Determine the number of inputs and outputs needed for your 1-bit cell. Explain the meaning of values in the interface signals.

This circuit can be designed by assuming that we have a borrow of 3 feeding the first cell or by representing  $-3$  as  $-1+-1+-1$  where  $-1$  is represented in 2's complement as  $11\dots111$  and thus adding 3 to each cell. I will follow the second approach. We need to represent carry-out values in the range 0 to 5. Thus, we need three signals to represent Carry out values propagation across cells.



- (ii) Derive the truth table of your 1-bit cell.

$C_{i-2}$	$C_{i-1}$	$C_{0i-1}$	$X_i$	$C_{2i}$	$C_{1i}$	$C_{0i}$	$Z_i$
0	0	0	0	0	0	1	1
0	0	0	1	0	1	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	1
0	1	0	0	0	1	0	1
0	1	0	1	1	0	0	0
0	1	1	0	0	1	1	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	1	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	1	1
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

- (iii) Derive minimized equations for your 1-bit using K-Map method.

	00	01	11	10
00	1 0	0 1	1 3	0 2
01	1 4	0 5	1 7	0 6
11	?12	?13	?15	?14
10	1 8	0 9	1 11	0 10

$$Z_i = C_{0i-1}' X_i' + C_{0i-1} X_i = (C_{0i-1} \oplus X_i)'$$

	00	01	11	10
00	1 0	1 1	1 3	0 2
01	0 4	0 5	0 7	1 6
11	?12	?13	?15	?14
10	1 8	1 9	1 11	0 10

$$\begin{aligned}
C0i &= C1i-1' C0i-1' + C1i-1' Xi + C1i-1 C0i-1 Xi' \\
&= C1i-1' (C0i-1' + Xi) + C1i-1 C0i-1 Xi' \\
&= C1i-1 \oplus (C0i-1' + Xi)
\end{aligned}$$

	00	01	11	10
00	0 0	1 1	1 3	1 2
01	1 4	0 5	0 7	1 6
11	?12	?13	?15	?14
10	1 8	0 9	0 11	0 10

$$\begin{aligned}
C1i &= C1i-1 Xi' + C2i-1' C1i-1' Xi + C2i-1' C0i-1 Xi' + C2i-1 C0i-1' Xi' \\
&= C1i-1 Xi' + C2i-1' C1i-1' Xi + Xi' (C2i-1 \oplus C0i-1)
\end{aligned}$$

	00	01	11	10
00	0 0	0 1	0 3	0 2
01	0 4	1 5	1 7	0 6
11	?12	?13	?15	?14
10	0 8	1 9	1 11	1 10

$$C2i = C1i-1 Xi + C2i-1 Xi + C2i-1 C0i-1$$

- (iv) Write a Verilog model for modeling your 1-bit cell by using an assign statement for each output.

```

module OneCell (output C2i, C1i, C0i, Zi, input C2i_1, C1i_1, C0i_1, Xi);

assign Zi = C0i_1 ~^ Xi;

assign C0i = C1i_1 ^ (~C0i_1 | Xi);

assign C1i = C1i_1 & ~Xi | ~C2i_1 & ~C1i_1 & Xi | ~Xi & (C2i_1 ^ C0i_1);

assign C2i = C1i_1 & Xi | C2i_1 & Xi | C2i_1 & C0i_1;

endmodule

```

- (v) Write a Verilog model for modeling a 4-bit circuit based on the 1-bit model you have.

```

module D3XM3 (output C2, C1, C0, output [3:0] Z, input [3:0] X);

```

```

OneCell M1 (C2_0, C1_0, C0_0, Z[0],0, 0, 0, X[0]);
OneCell M2 (C2_1, C1_1, C0_1, Z[1],C2_0, C1_0, C0_0, X[1]);
OneCell M3 (C2_2, C1_2, C0_2, Z[2],C2_1, C1_1, C0_1, X[2]);
OneCell M4 (C2, C1, C0, Z[3],C2_2, C1_2, C0_2, X[3]);

```

```
endmodule
```

- (vi) Write a Verilog test bench to test the correctness of your design for the following input values: {X=1}, {X=3}, {X=5} and {X=4}.

```

module D3XM3_Test();

reg [3:0] X;
wire C2, C1, C0;
wire [3:0] Z;

D3XM3 M1 (C2, C1, C0, Z, X);

initial begin

X=4'b0001;

#100 X=4'b0011;

#100 X=4'b0101;

#100 X=4'b0100;

end

endmodule

```

The generated simulation waveform verifies the correct functionality of the designed circuit:

