

April 4, 2013

COMPUTER ENGINEERING DEPARTMENT

COE 405

DESIGN & MODELING OF DIGITAL SYSTEMS

Midterm Exam

Second Semester (122)

Time: 1:00-3:30 PM

OPEN BOOK EXAM

Student Name : __KEY_____

Student ID. : _____


Question	Max Points	Score
Q1	20	
Q2	15	
Q3	30	
Q4	25	
Q5	10	
Total	100	

Dr. Aiman El-Maleh

[20 Points]

(Q1) It is required to design an **iterative** combinational circuit that receives an **n-bit** number X and computes the result $Y=3*X$. The design should be based on a one-bit cell (i.e. processing one bit X_i) that can be copied n times to construct the n -bit design. (Hint: $3*X = X+X+X$. Note that the maximum carry from one cell to the next is 2.)

 - i) Determine the inputs and outputs for a one-bit cell.
- ii) Derive the truth table for a one-bit cell.
- iii) Derive minimized sum-of-product equations for a one-bit cell.
- iv) Show the block diagram for a 4-bit design.



ii) Truth Table:

x_i	CI_1	CI_0	CO_1	CO_0	y_i
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	x	x	x
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	x	x	x

iii)

		$C_1 C_0$			
x_i		00	01	11	10
0		0	0	X	0
1		0	1	X	1

$$C_01 = x_i C_1 + x_i C_0$$


		$C_1 C_0$			
x_i		00	01	11	10
0		0	0	X	1
1		1	0	X	0

$$C_00 = \bar{x}_i C_1 + x_i \bar{C}_1 \bar{C}_0$$

		$C_1 C_0$			
x_i		00	01	11	10
0		0	1	X	0
1		1	0	X	1

$$y_i = \bar{x}_i C_0 + x_i \bar{C}_0$$

iv)

 


[15 Points]

(Q2) It is required to design a synchronous sequential circuit that receives a serial input **X** and produces a serial output **Z**. The output **Z** will be 1 if the input has been **alternating for at least 3 clock periods**. Assume the existence of an asynchronous reset input to reset the machine to a reset state. Draw the state diagram of the circuit assuming a Mealy model. *You are not required to derive the equations and the circuit.* The following is an example of some input and output streams:

Example:


Input	X	1 0 1 0 1 0 1 1 1 0 1 0 1 0 0 1 0
Output	Z	0 0 0 1 1 1 1 0 0 0 1 1 1 0 0 0

 



[30 Points]

(Q3) The ASMD chart given below describes a state machine that counts 1's in a word and terminates activity as soon as possible. The machine remains in its reset state, S_idle , until an external agent asserts $start$. This action asserts the output, $load_temp$, which will cause $data$ to be loaded into register $temp$ when the state makes a transition to $S_counting$ at the next active edge of clk . The machine remains in $S_counting$ while $temp$ contains a 1. Two actions occur concurrently at each subsequent clock: (1) $temp$ is shifted towards its LSB and (2) $temp[0]$ is added to bit_count . When $temp$ finally has a 1 in only the LSB, the machine's state moves to $S_waiting$, where $done$ is asserted. The state remains in $S_waiting$ until $start$ is reasserted. Assume that when the synchronous $reset$ input is asserted the machine is reset to the state S_idle and bit_count and $temp$ are initialized to 0.

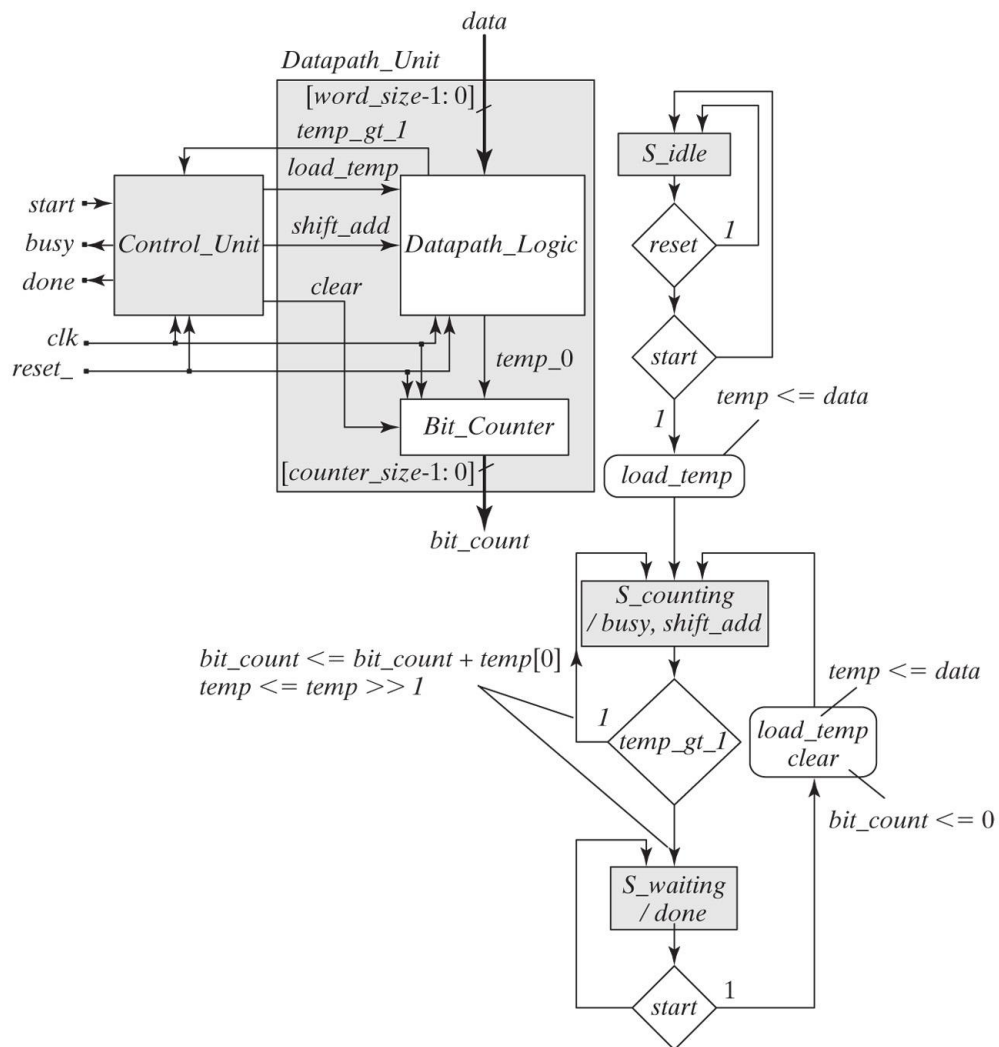- i) Show the design of the data-path unit.
- ii) Show the design of the control unit using the following state assignment: $S_idle=00$, $S_counting = 01$, and $S_waiting=10$.



i) DataPath Unit:

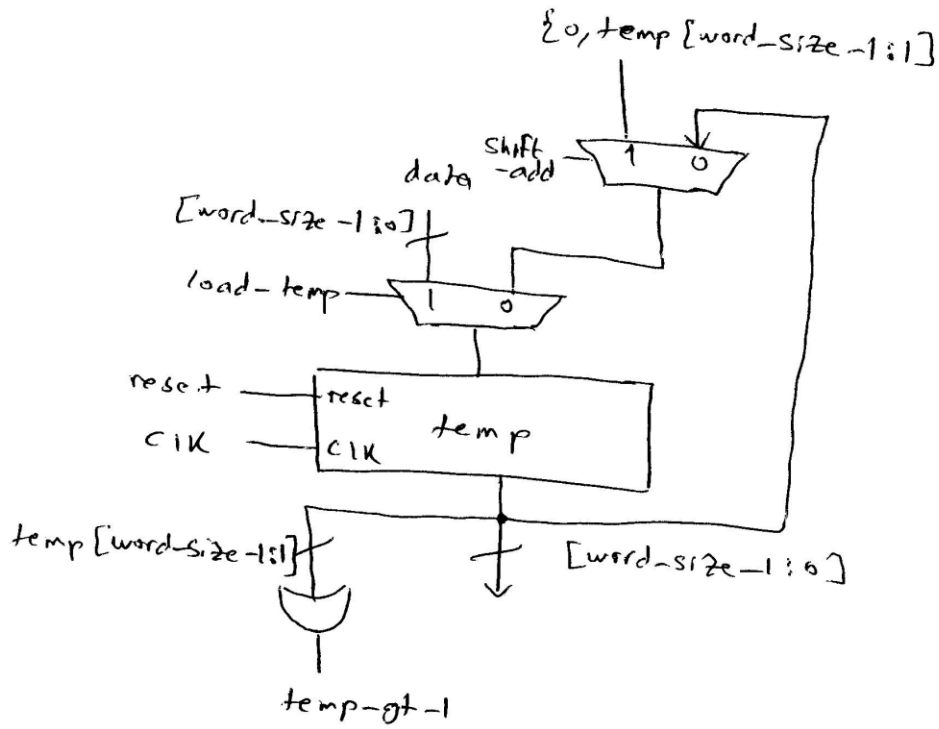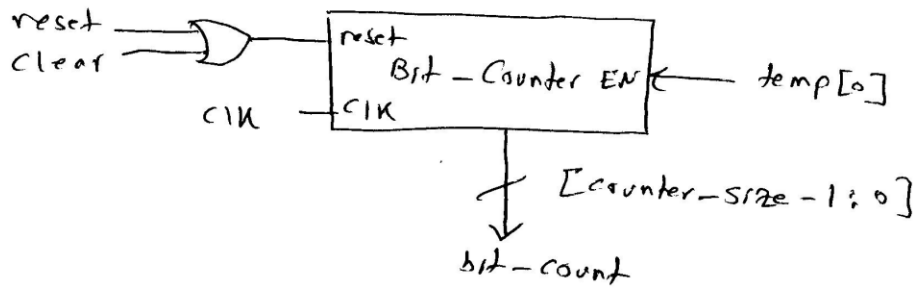

ii) Control Unit:

C.S.	Input		N.S.	Output				
	start	temp_gt_1		done	busy	load_temp	shift_add	clear
<i>S_idle</i>	0	x	<i>S_idle</i>	0	0	0	0	0
<i>S_idle</i>	1	x	<i>S_counting</i>	0	0	1	0	0
<i>S_counting</i>	x	1	<i>S_counting</i>	0	1	0	1	0
<i>S_counting</i>	x	0	<i>S_waiting</i>	0	1	0	1	0
<i>S_waiting</i>	1	x	<i>S_counting</i>	1	0	1	0	1
<i>S_waiting</i>	0	x	<i>S_waiting</i>	1	0	0	0	0

Assuming the two flip flops F1 and F2 for storing the machine state and the state assignment: $S_idle=00$, $S_counting = 01$, and $S_waiting=10$, the contrl signals will be as follows:

$$done = F1 F0'$$

$$busy = F1' F0$$

$$shift_add = F1' F0$$

$$load_temp = F0' start$$

$$clear = F1 F0' start$$


FiFo	start temp-st-1			
	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	x	x	x	x
10	1	1	0	0

FiFo	start temp-st-1			
	00	01	11	10
00	0	0	1	1
01	0	1	1	0
11	x	x	x	x
10	0	0	1	1

$$D1 = F1 \overline{start} + F0 \overline{temp-st-1}$$

$$D0 = \overline{F0} start + F0 temp-st-1$$

 (Q4) A JK flip-flop with the following interface is given below:




- i) Write a JKFF module with behavioral model for a rising-edge triggered JK flip-flop.

```

module JKFF (output reg Q, output QB, input J, K, CLK);
assign QB = ~Q;
always @( posedge CLK)
    case ({J,K})
        2'b00: Q <= Q;
        2'b01: Q <= 0;
        2'b10: Q <= 1;
        2'b11: Q <= ~Q;
    endcase
endmodule

```

 - ii) Using the JK flip-flop modeled in (i) model the 1-bit modular binary counter given below.




```

module OneBitCount (output Q, Cout, input Reset, Enable, CLK);
    and (J, ~Reset, Enable);
    or (K, Reset, Enable);
    and (Cout, Enable, Q);
    JKFF F (Q, , J, K, CLK);
endmodule

```

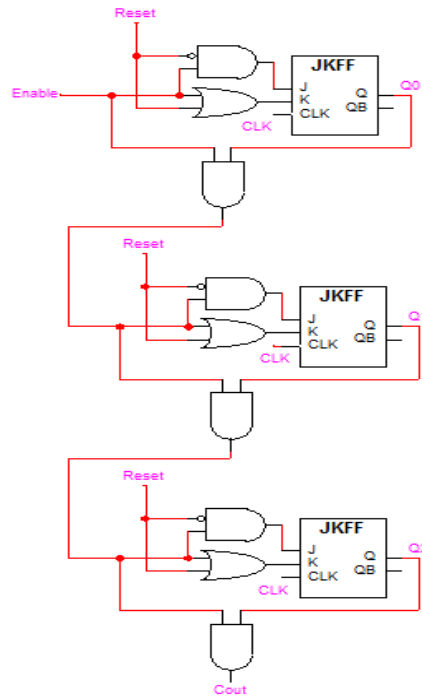- iii) Based on the 1-bit modular binary counter modeled in (ii), build a 3-bit binary up counter as shown below. The counter does not count when the count enable is 0. Otherwise, it counts on the rising-edge of the clock.



```

module ThreeBitCount (output Q2, Q1, Q0, Cout, input Reset, Enable, CLK);
    OneBitCount F0 (Q0, Cout0, Reset, Enable, CLK);
    OneBitCount F1 (Q1, Cout1, Reset, Cout0, CLK);
    OneBitCount F2 (Q2, Cout, Reset, Cout1, CLK);
endmodule

```

- iv) Write a test bench to test the 3-bit **counter** using the data given below. You need to generate the clock signal inside the test bench with a period of 10 and 50% duty cycle. The test bench should simulate the circuit for 300 delay units.

Time	Action
20	Reset=1
35	Reset=0
50	Enable=1
90	Enable=0
120	Enable=1

```


module t_ThreeBitCount ();
    wire Q2, Q1, Q0, Cout;
    reg CLK, Reset, Enable;
    ThreeBitCount C0 (Q2, Q1, Q0, Cout, Reset, Enable, CLK);
    initial #300 $finish;
    initial begin
        CLK = 0;
        forever #5 CLK = ~CLK;
    end
    initial fork
        #20 Reset = 1;

```

```


#35 Reset = 0;
#50 Enable = 1;
#90 Enable = 0;
#120 Enable = 1;
join
endmodule

```

 

[10 Points]

 (Q5) It is required to model a generic n-bit Ripple Carry Adder (RCA). A 4-bit RCA is shown below:



Model a behavioral n-bit RCA using repetitive constructs.

```

module RCA #(parameter n=4)
(output reg [n-1:0] Sum, output Cout, input [n-1:0] A, B, input Cin);

reg [n-1:0] Carry;
integer i;
assign Cout = Carry[n-1];
always @(A, B, Cin) begin
    Sum[0] = A[0] ^ B[0] ^ Cin;
    Carry[0] = A[0] & B[0] | Cin & (A[0] ^ B[0]);
    for (i=1; i < n; i=i+1) begin
        Sum[i] = A[i] ^ B[i] ^ Carry[i-1];
        Carry[i] = A[i] & B[i] | Carry[i-1] & (A[i] ^ B[i]);
    end
end
endmodule

```