


COE 405, Term 062

Design & Modeling of Digital Systems

HW# 1

Due date: Wednesday, March. 14

 Q.1. Consider the 4-bit carry-look-ahead adder (CLA) block shown below:



- (i) Describe an Entity **CLA4** in VHDL for this 4-bit CLA using exactly the same port names shown above.
- (ii) Write in VHDL an Architecture **Conc** for this 4-bit CLA using concurrent statements.
- (iii) Simulate the VHDL model **Conc** and verify that it is working properly. Include a snapshot of the simulated waveform.
- (iv) Model an 8-bit adder, **Adder8**, based on cascading two CLA4 components by connecting the carryout of the first component to the carry-in of the second component.
- (v) Simulate the VHDL model for the 8-bit adder and verify that it is working properly. Include a snapshot of the simulated waveform.

- Q.2.** It is required to model a 4-bit up-down counter with a synchronous rising-edge clock, and asynchronous reset. Assume that the counter has an input **DIR** when set to 0, it counts up otherwise it counts down.
- (i) Describe an Entity **UDC4** in VHDL for the 4-bit up-down counter.
 - (ii) Model Architecture **Behavior** for the 4-bit up-down counter using a process.
 - (iii) Simulate the VHDL model **Behavior** and verify that it is working properly. Include a snapshot of the simulated waveform.
- Q.3.** It is required to design a sequential circuit that receives a serial input **X**, and produces a serial output **Z**, equivalent to $3 \cdot X$, i.e., $Z = 3 \cdot X$. The input coming to the **X** input is transmitted from the least significant bit to the most significant bit. The number of bits transmitted will be equal to the number of bits needed in the output **Z**. For example, for sending the decimal value 3, the input sequence 0011 will be transmitted and the output sequence 1001 will be produced.
- (i) Show the state diagram of this circuit assuming **Mealy** model.
 - (ii) Model an Entity **Times3** and an Architecture **Behavior** for this circuit using a process. Assume that the circuit will have a synchronous reset and is rising-edge triggered.
 - (iii) Simulate the VHDL model **Behavior** and verify that it is working properly. Verify the correctness of your circuit by the following decimal numbers: 9, 10, and 15. Include a snapshot of the simulated waveform.