

COE 405, Term 122

Design & Modeling of Digital Systems

HW# 1

Due date: Monday, Feb. 18

- Q.1.** Consider the two functions $f=(a+bc)(a'+cd)$ and $g=(a+b)(c+d)$.
- (i) Implement the function f using a single 4×1 MUX.
 - (ii) Compute the complement of f .
 - (iii) Compute the function $f \oplus g$ based on orthonormal basis expansion.
- Q.2.** You are required to design a circuit that computes the remainder of dividing a 4-bit number by 3. For example, if the input is 1010 the circuit produces a remainder output of 01 and if the input is 1111 the circuit produces an output of 00.
- (i) Derive the truth table of your circuit.
 - (ii) Using k-map simplification, find the minimum sum-of-products expressions for each of the output signals.
 - (iii) Perform multilevel optimizations if possible.
 - (iv) Model your circuit using logic works and verify that it is working properly by simulation. Provide a snapshot of your simulation waveform.
- Q.3.** You are required to design a circuit that computes the remainder of dividing a N -bit number by 3, where N is a multiple of 4-bit numbers. The design needs to be modular in such a way that you design a cell that computes the remainder of dividing a 4-bit number by 3, and use this cell to construct the required circuit.
- (i) Derive the truth table of your basic cell.
 - (ii) Using k-map simplification, find the minimum sum-of-products expressions for each of the output signals.
 - (iii) Perform multilevel optimizations if possible.
 - (iv) Model your cell using logic works and verify that it is working properly by simulation. Provide a snapshot of your simulation waveform.
 - (v) Using your design cell, construct a circuit that computes the remainder of dividing an 8-bit number by 3. Verify the correct functionality of your circuit by simulation.