

## COE 405, Term 152

### Design & Modeling of Digital Systems

#### HW# 1

**Due date: Thursday, Feb. 11**

- Q.1.** Consider the two functions  $f = a \oplus b \oplus c$  and  $g = a b + a c + b c$ .
- (i) Implement the function  $g$  using only 2x1 MUXs.
  - (ii) Compute the function  $f \oplus g$  based on orthonormal basis expansion.
- Q.2.** It is required to design a combinational circuit that computes the equation  $Y = 3 * X - 1$ , where  $X$  is an  $n$ -bit signed 2's complement number.
- (i) Design the circuit as a modular circuit where each module receives a single bit of the input,  $X_i$ .
  - (ii) Derive the truth table of your 1-bit module in (i).
  - (iii) Derive minimized two-level sum-of-product equations for your 1-bit module circuit.
  - (iv) Verify the correctness of your design by modeling and simulating a circuit to compute the required equation assuming  $X$  is a 4-bit number using logicworks.

*This assignment can be solved based on a group of two students. The solution should be well organized. Submit a soft copy of your solution in a zip file including your logicworks files. Your solution should be submitted in a **word file** that contains the following items:*

- i. Your name and ID*
- ii. Assignment number*
- iii. Problem statement*
- iv. Your solution*
- v. Include snapshots of simulation output to illustrate the correctness of your solution.